

Power System Analysis

Chapter 8 Unbalanced network: component models

Outline

1. Overview
2. Mathematical properties
3. Three-phase device models
4. Three-phase line models
5. Three-phase transformer models

Outline

1. Overview

- Internal & terminal variables
- 3-phase device models
- 3-phase line & transformer models
- 3-phase network models


2. Mathematical properties

3. Three-phase device models

4. Three-phase line models


5. Three-phase transformer models

Overview

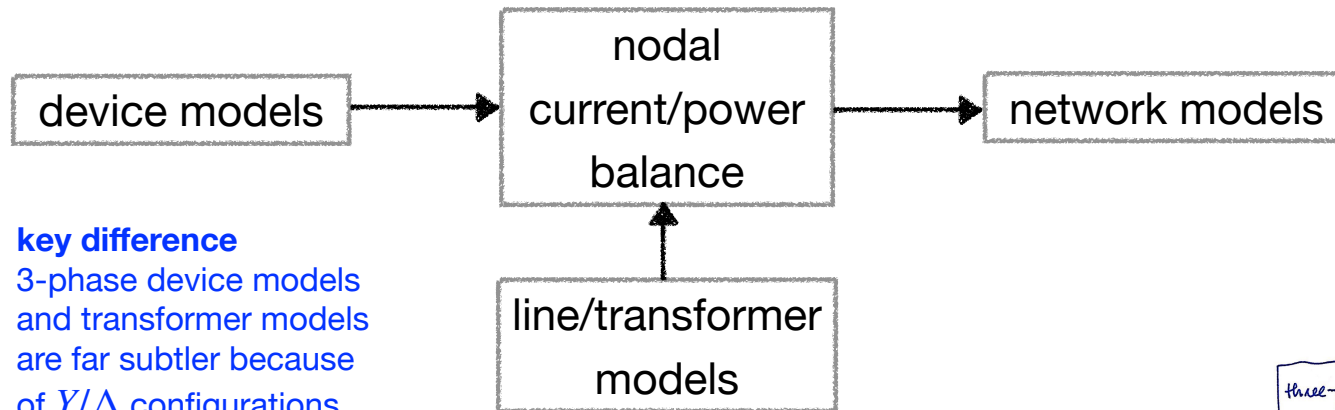

key difference

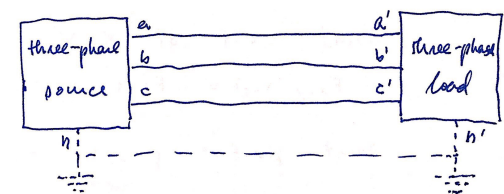3-phase device models and transformer models are far subtler because of Y/Δ configurations



single-phase or 3-phase

Example

Single-phase system

System model = device model + network model



1. Device model: $V_1 = \frac{V_{\text{gen}}}{\sqrt{3} e^{i\pi/6}}$, $V_{\text{load}} = Z_{\text{load}} I_{\text{load}}$

2. Transformer model: $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = Y_{\text{transformer}} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

3. Line model: $\begin{bmatrix} I_2 \\ I_{\text{load}} \end{bmatrix} = Y_{\text{line}} \begin{bmatrix} V_2 \\ V_{\text{load}} \end{bmatrix}$

4. Nodal (current) balance are implicitly taken into account

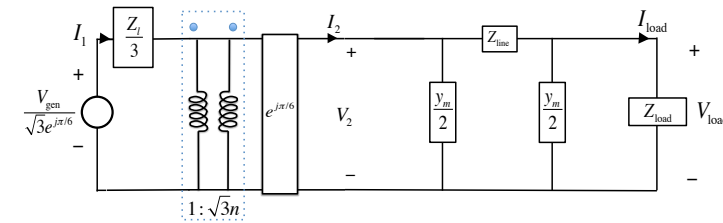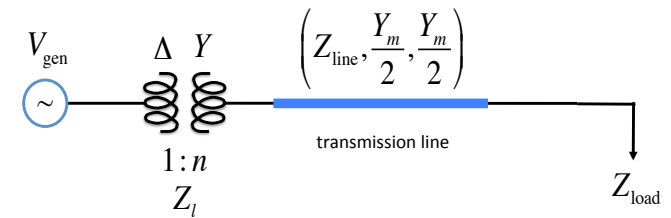5. 6 (linear) equations in 6 unknowns $(V_1, V_2, V_{\text{load}})$, $(I_1, I_2, I_{\text{load}})$ each in \mathbb{C}





Example


Three-phase **unbalanced** system

System model = device model + network model

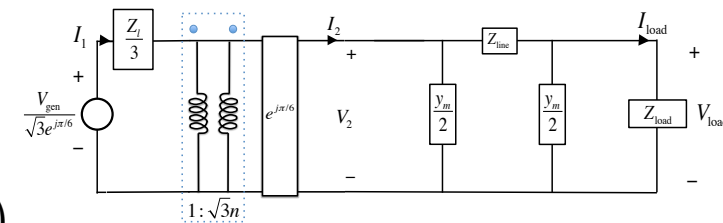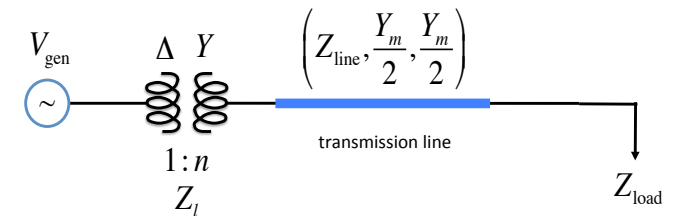
1. Device model: Y/Δ -configured devices are a key difference
2. Transformer model: Y/Δ -configured transformers are a key difference
3. Line model: 3-phase lines have straightforward extension
4. Nodal (current) balance are the same as for 1-phase network
5. 6 (linear) equations in 6 unknowns $(V_1, V_2, V_{\text{load}}), (I_1, I_2, I_{\text{load}})$ each in \mathbb{C}^3



Overview

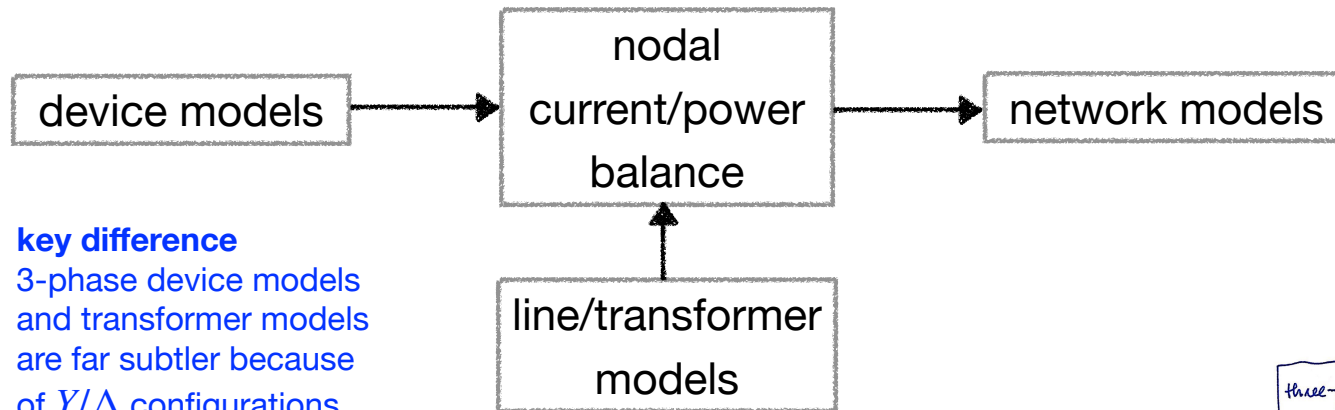

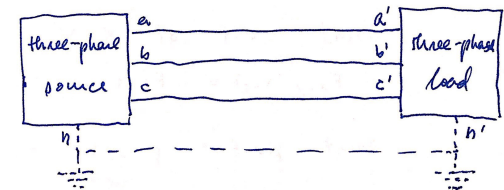key difference
3-phase device models and transformer models are far subtler because of Y/Δ configurations



single-phase or 3-phase

Key question

How to derive **external models** of 3-phase devices

1. Voltage/current/power sources, impedances (1-phase device: internal models)
2. ... in Y/Δ configurations (conversion rules: int \rightarrow ext)
3. ... with or without neutral lines, grounded or ungrounded, zero or nonzero grounding impedances


similar principle to derive external models of 3-phase transformers (but different details)

Internal variables

Y configuration

Internal voltage, current, power across **single-phase** devices:
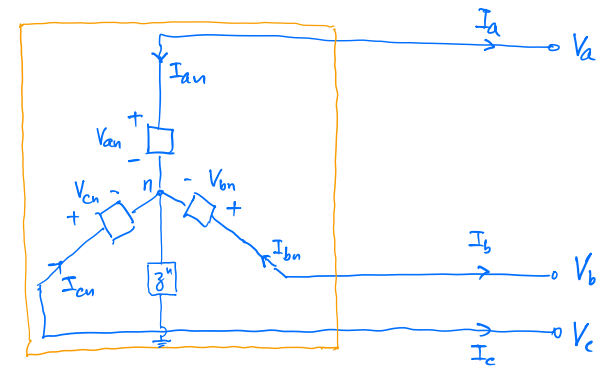
$$V^Y := \begin{bmatrix} V^{an} \\ V^{bn} \\ V^{cn} \end{bmatrix}, \quad I^Y := \begin{bmatrix} I^{an} \\ I^{bn} \\ I^{cn} \end{bmatrix}, \quad S^Y := \begin{bmatrix} S^{an} \\ S^{bn} \\ S^{cn} \end{bmatrix} := \begin{bmatrix} V^{an} \bar{I}^{an} \\ V^{bn} \bar{I}^{bn} \\ V^{cn} \bar{I}^{cn} \end{bmatrix}$$



neutral voltage (wrt common reference pt) $V^n \in \mathbb{C}$

neutral current (away from neutral) $I^n \in \mathbb{C}$


- Neutral line may or may not be present
- Device may or may not be grounded
- Neutral impedance z^n may or may not be zero

Internal variables

Δ configuration

Internal voltage, current, power across [single-phase](#) devices:
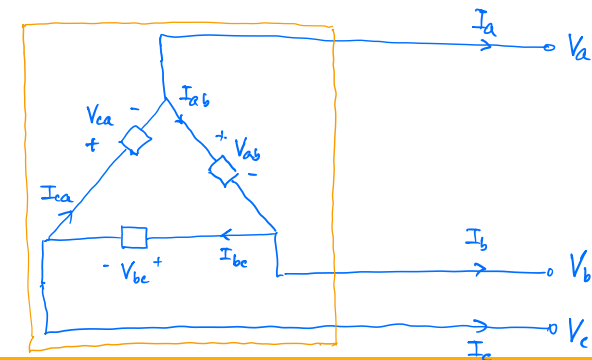
$$V^\Delta := \begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix}, \quad I^\Delta := \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}, \quad S^\Delta := \begin{bmatrix} S^{ab} \\ S^{bc} \\ S^{ca} \end{bmatrix} := \begin{bmatrix} V_{ab} \bar{I}_{ab} \\ V_{bc} \bar{I}_{bc} \\ V_{ca} \bar{I}_{ca} \end{bmatrix}$$





Terminal variables

Terminal voltage, current, power (for both Y and Δ) **to reference**:

$$V := \begin{bmatrix} V^a \\ V^b \\ V^c \end{bmatrix}, \quad I := \begin{bmatrix} I^a \\ I^b \\ I^c \end{bmatrix}, \quad s := \begin{bmatrix} s^a \\ s^b \\ s^c \end{bmatrix} := \begin{bmatrix} V^a \bar{I}^a \\ V^b \bar{I}^b \\ V^c \bar{I}^c \end{bmatrix}$$

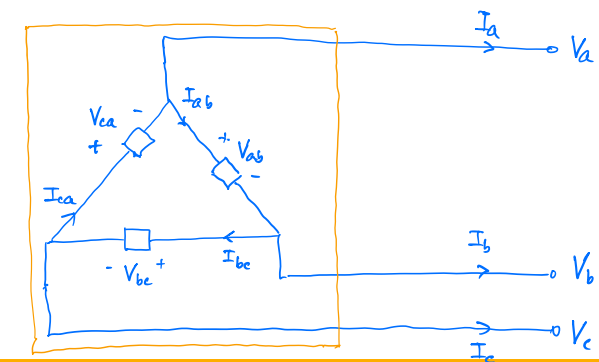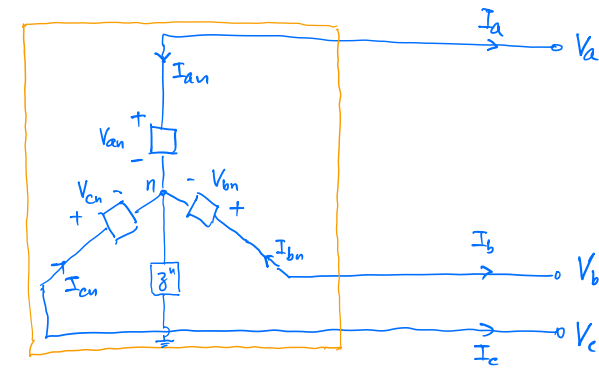
- V is with respect to an arbitrary common reference point, e.g. the ground
- I and s are in the direction **out** of the device



Internal vs terminal power

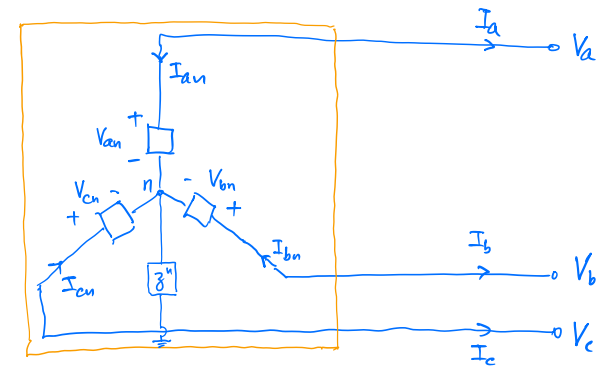
1. Internal power:

- Across each single-phase device: $s^{Y/\Delta} := \text{diag} (V^{Y/\Delta} I^{Y/\Delta H})$
- Across neutral conductor: $s^n := V^n \bar{I}^n$



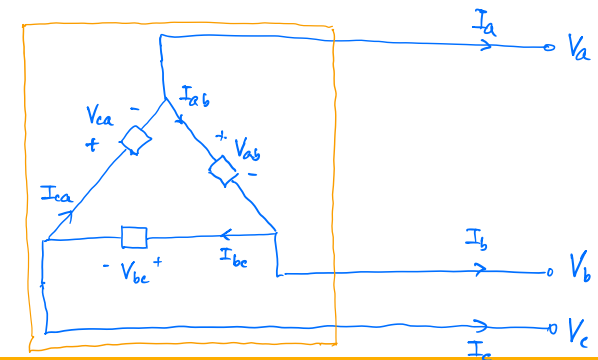2. Terminal power:



- Power injected from device to network: $s := \text{diag} (VI^H)$



Summary: variables

	Voltage	Current	Power	Neutral line
Internal variable	V^Y/Δ	I^Y/Δ	s^Y/Δ	(V^n, I^n, s^n)
External variable	V	I	s	$(V^{n'}, I^{n'}, s^{n'})$

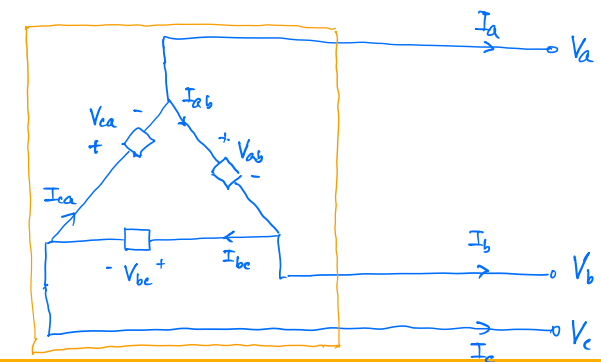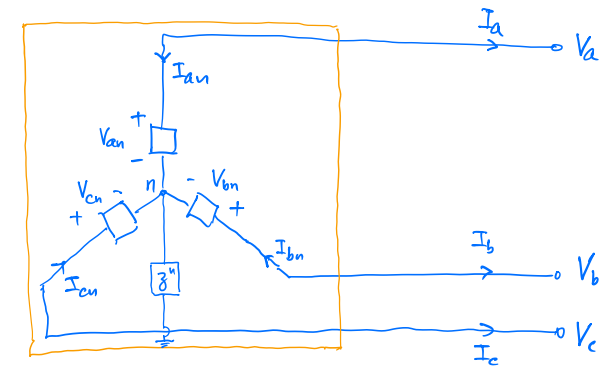- Neutral line may or may not be present
- Device may or may not be grounded
- Neutral impedance z^n may or may not be zero



Device models



Internal model

1. Relation between internal vars: $f^{\text{int}}(V^{Y/\Delta}, I^{Y/\Delta}) = 0, \quad \text{diag}(V^{Y/\Delta} I^{Y/\Delta H}) = s^{Y/\Delta}$

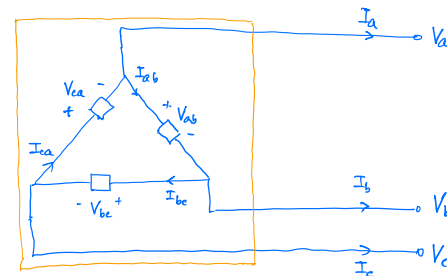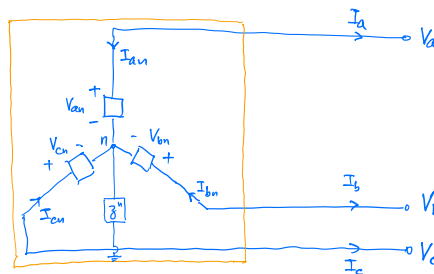2. Examples

ideal voltage source: $V^{Y/\Delta} = E^{Y/\Delta}, \quad s^{Y/\Delta} = \text{diag}(E^{Y/\Delta} (I^{Y/\Delta})^H)$

impedance: $V^{Y/\Delta} = z^{Y/\Delta} I^{Y/\Delta}, \quad s^{Y/\Delta} = \text{diag}(V^{Y/\Delta} (I^{Y/\Delta})^H)$



Device models

Internal model

1. Relation between internal vars: $f^{\text{int}}(V^{Y/\Delta}, I^{Y/\Delta}) = 0$, $\text{diag}(V^{Y/\Delta} I^{Y/\Delta H}) = s^{Y/\Delta}$

2. Examples

ideal voltage source: $V^{Y/\Delta} = E^{Y/\Delta}$, $s^{Y/\Delta} = \text{diag}(E^{Y/\Delta} (I^{Y/\Delta})^H)$

impedance: $V^{Y/\Delta} = z^{Y/\Delta} I^{Y/\Delta}$, $s^{Y/\Delta} = \text{diag}(V^{Y/\Delta} (I^{Y/\Delta})^H)$

3. Internal model

- Independent of Y or Δ configuration
- Depends only on behavior of single-phase devices
- Voltage/current/power source, impedance

Device model

External model

1. **External model** = Internal model + Conversion rule

- External model: relation between (V, I, s)

$$f^{\text{ext}}(V, I) = 0, \quad s = \text{diag}(VI^H)$$



- Devices interact over network **only** through their terminal vars

2. **Internal model** : relation between $(V^{Y/\Delta}, I^{Y/\Delta}, s^{Y/\Delta})$

- Independent of Y or Δ configuration
- Depends only on behavior of single-phase devices

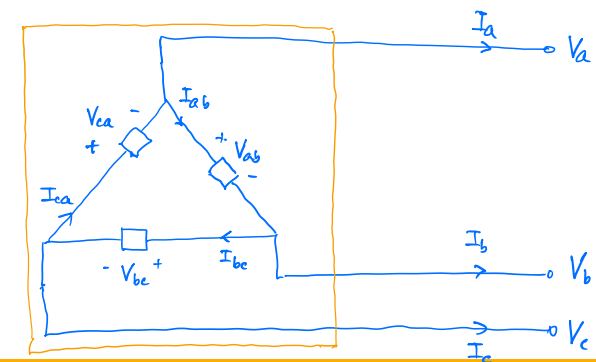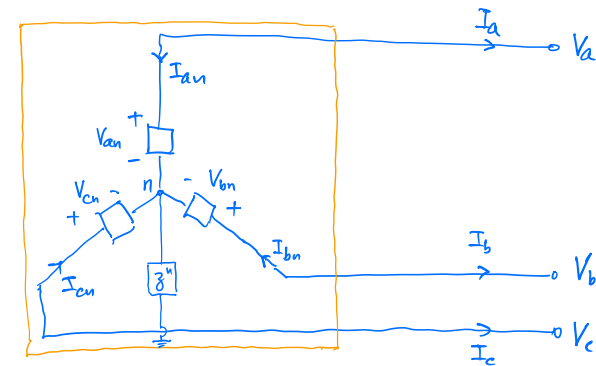3. **Conversion rule** : converts between internal and terminal vars

- Depends only on Y or Δ configuration
- Independent of type of single-phase devices



Line or transformer model


1. A line or transformer has two terminals j and k
 - Each terminal may have 3 wires (ports) or 4 wires (ports) if neutral line present

2. Terminal variables (3-wired)

- Terminal voltages: $V_j := (V_j^a, V_j^b, V_j^c) \in \mathbb{C}^3$, $V_k := (V_k^a, V_k^b, V_k^c) \in \mathbb{C}^3$
- Sending-end currents: $I_{jk} := (I_{jk}^a, I_{jk}^b, I_{jk}^c) \in \mathbb{C}^3$, $I_{kj} := (I_{kj}^a, I_{kj}^b, I_{kj}^c) \in \mathbb{C}^3$
- Sending-end powers: $S_{jk} := (S_{jk}^a, S_{jk}^b, S_{jk}^c) \in \mathbb{C}^3$, $S_{kj} := (S_{kj}^a, S_{kj}^b, S_{kj}^c) \in \mathbb{C}^3$

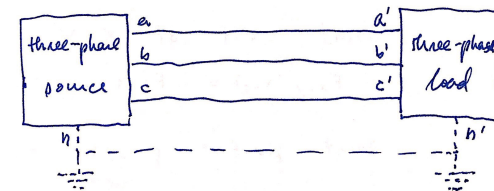3. Model in terms of 3×3 admittance matrices:

- IV relation: $g(V_j, V_k, I_{jk}, I_{kj}) = 0$
- sV relation: $S_{jk}^\phi := V_j^\phi (I_{jk}^\phi)^H$ or in vector form $S_{jk} := \text{diag}(V_j I_{jk}^H)$, $S_{kj} := \text{diag}(V_k I_{kj}^H)$




Network model

Network balance equations relate terminal vars

- Nodal current balance: $I_j = \sum_{k:j \sim k} I_{jk}$

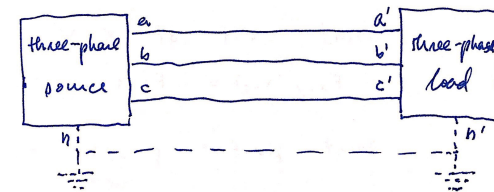- Nodal power balance: $s_j = \sum_{k:j \sim k} S_{jk}$



Overall model

Device + network

1. **Device model** for each 3-phase device
 - Internal model on $\left(V_j^{Y/\Delta}, I_j^{Y/\Delta}, S_j^{Y/\Delta} \right)$ + conversion rules
 - External model on $\left(V_j, I_j, S_j \right)$
 - Either can be used
 - Power source models are nonlinear; other devices are linear
2. **Network model** relates terminal vars (V, I, s)
 - Nodal current balance equation: linear
 - Nodal power balance equation: nonlinear
 - Either can be used

Overall model will be linear if and only if only voltage/current sources and impedances are present (but no power sources)



Outline

1. Overview
2. Mathematical properties
 - Conversion matrices Γ , Γ^T
 - Sequence variables
3. Three-phase device models
4. Three-phase line models
5. Three-phase transformer models

Conversion matrices

$$\Gamma := \begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix}, \quad \Gamma^T := \begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$

Incidence matrices for:

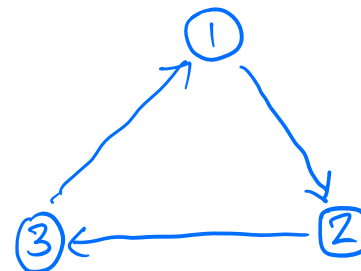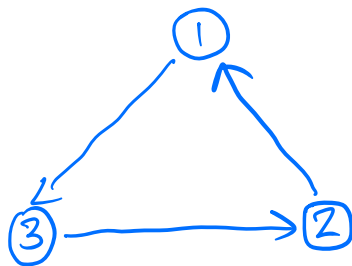

Conversion matrices

Convert between **internal** vars and **external** vars

$$\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix}}_{\Gamma} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}, \quad \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = - \underbrace{\begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}}_{\Gamma^T} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$

Conversion matrices

Convert between **internal** vars and **external** vars

$$\begin{bmatrix} V_{ab} \\ V_{bc} \\ V_{ca} \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 0 & 1 & -1 \\ -1 & 0 & 1 \end{bmatrix}}_{\Gamma} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}, \quad \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = - \underbrace{\begin{bmatrix} 1 & 0 & -1 \\ -1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}}_{\Gamma^T} \begin{bmatrix} I_{ab} \\ I_{bc} \\ I_{ca} \end{bmatrix}$$

In vector form

$$\begin{array}{ccc} V^\Delta = \Gamma V, & I = -\Gamma^T I^\Delta \\ \uparrow & \uparrow & \uparrow & \uparrow \\ \text{internal} & \text{terminal} & \text{terminal} & \text{internal} \\ \text{voltage} & \text{voltage} & \text{current} & \text{current} \end{array}$$

Conversion matrices

Lemma

Let $M \in \mathbb{C}^{n \times n}$ be a normal matrix, i.e., $MM^H = M^H M$.

1. *Decomposition*: $M = U\Lambda U^H$ where $\Lambda = \text{diag}(\lambda_1, \dots, \lambda_n)$ are eigenvalues and columns of U are eigenvectors of M .
2. *Pseudo-inverse*: $M^\dagger = U\Lambda^\dagger U^H$ where $\Lambda^\dagger := \text{diag}(\lambda_1^{-1}, \dots, \lambda_n^{-1})$ with $\lambda_j^{-1} := 0$ if $\lambda_j = 0$.
3. *Solution of $Mx = b$* : A solution x exists if and only if b is orthogonal to $\text{null}(M^H)$ in which case

$$x = M^\dagger b + w, \quad w \in \text{null}(M)$$

Conversion matrices

Spectral decomposition

Spectral decomposition:

$$\Gamma = F\Lambda\bar{F}, \quad \Gamma^\top = \bar{F}\Lambda F$$

where

$$\Lambda := \begin{bmatrix} 0 & & \\ & 1 - \alpha & \\ & & 1 - \alpha^2 \end{bmatrix},$$

and $\alpha := e^{-i2\pi/3}$

eigenvectors
of Γ, Γ^\top

$$F := \frac{1}{\sqrt{3}} \begin{bmatrix} 1 & 1 & 1 \\ 1 & \alpha & \alpha^2 \\ 1 & \alpha^2 & \alpha \end{bmatrix}$$

positive-seq
balanced
vector α_+

negative-seq
balanced
vector α_-

Conversion matrices

Theorem

1. The null spaces of Γ and Γ^\top are both $\text{span}(1)$.
2. Γ is normal. Moreover, $\Gamma\Gamma^\dagger = \Gamma^\dagger\Gamma = \frac{1}{3}\Gamma\Gamma^\top = \frac{1}{3}\Gamma^\top\Gamma = \mathbb{I} - \frac{1}{3}11^\top$
3. Their pseudo-inverses are: $\Gamma^\dagger = \frac{1}{3}\Gamma^\top$, $\Gamma^{\top\dagger} = \frac{1}{3}\Gamma$
4. Consider $\Gamma x = b$. Solutions x exist if and only if $1^\top b = 0$, in which case

$$x = \frac{1}{3}\Gamma^\top b + \gamma 1, \quad \gamma \in \mathbb{C}$$

5. Consider $\Gamma^\top x = b$. Solutions x exist if and only if $1^\top b = 0$, in which case

$$x = \frac{1}{3}\Gamma b + \beta 1, \quad \beta \in \mathbb{C}$$

Sequence variables

Fortescue matrix F

1. F is unitary and complex symmetric (recall $\Gamma = F\Lambda\bar{F}$)
2. Its inverse is:

$$F^{-1} = F^H = \bar{F} = \frac{1}{\sqrt{3}} \begin{bmatrix} 1 & \bar{\alpha}_+ & \bar{\alpha}_- \end{bmatrix}$$

3. F defines a similarity transformation:

$$x = F\tilde{x}, \quad \tilde{x} := F^{-1}x = \bar{F}x$$

4. \tilde{x} is called the **sequence variable** of x . Its components are

$$\tilde{x}_0 := \frac{1}{\sqrt{3}} 1^H x, \quad \tilde{x}_+ := \frac{1}{\sqrt{3}} \alpha_+^H x, \quad \tilde{x}_- := \frac{1}{\sqrt{3}} \alpha_-^H x$$

zero-sequence positive-sequence negative-sequence

Sequence variables

Sequence voltage, current, power

1. Sequence voltage and current:

$$\tilde{V} = \bar{F}V, \quad \tilde{I} = \bar{F}I$$

2. Powers in phase and sequence coordinates:

$$s := \text{diag}(VI^H), \quad \tilde{s} := \text{diag}(\tilde{V}\tilde{I}^H)$$

3. The total powers are equal $\mathbf{1}^T \tilde{s} = \mathbf{1}^T s$:

$$\mathbf{1}^T \tilde{s} = \tilde{I}^H \tilde{V} = (I^H \bar{F}^H) (\bar{F}V) = I^H V = \mathbf{1}^T s$$

since $\bar{F}^H \bar{F} = F \bar{F} = \mathbb{I}$



Outline

1. Overview
2. Mathematical properties
3. Three-phase device models
 - Conversion rules
 - Devices in Y configuration
 - Devices in Δ configuration
 - Y - Δ transformation (ideal devices)
4. Three-phase line models
5. Three-phase transformer models

How to derive external models

Recall

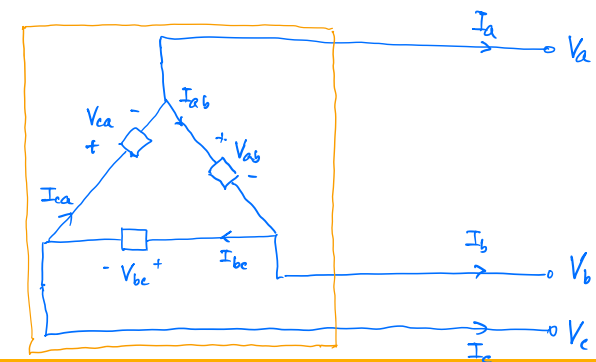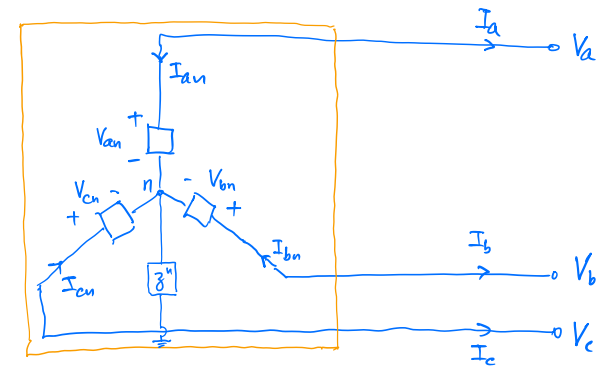1. **External model** = Internal model + Conversion rule
 - External model: relation between (V, I, s)
 - Devices interact over network **only** through their terminal vars
2. **Internal model** : relation between $(V^{Y/\Delta}, I^{Y/\Delta}, s^{Y/\Delta})$
 - Independent of Y or Δ configuration
 - Depends only on behavior of single-phase devices
 - Voltage/current/power source, impedance
3. **Conversion rule** : converts between internal and terminal vars
 - Depends only on Y or Δ configuration
 - Independent of type of single-phase devices



Conversion rule

Y configuration

1. Converts between internal and terminal variables

$$V = V^Y + V^n \mathbf{1}, \quad I = -I^Y, \quad s = - (s^Y + V^n \bar{I}^Y)$$


$$\mathbf{1}^T I = -\mathbf{1}^T I^Y = -I^n$$

2. Negative signs in I, s due to directions of currents and powers

- (I, s) : current & power injection from 3-phase device to rest of network
- (I^Y, s^Y) : current & power delivered to the single-phase devices

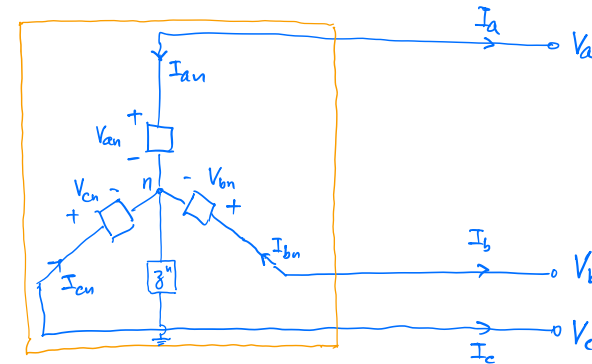3. If there is no neutral line, then $z^n := \infty, I^n := 0$

- $\mathbf{1}^T I = -\mathbf{1}^T I^Y = 0, V^n$ determined by network interaction



Conversion rule

Y configuration: assumption C8.1

1. Assumption C8.1


- All voltages are defined wrt the ground
- All neutrals are grounded through z^n (which may be zero)

2. If Assumption C8.1 holds

- $V^n = -z^n (1^T I)$
- $V^n = 0$ if $z^n = 0$

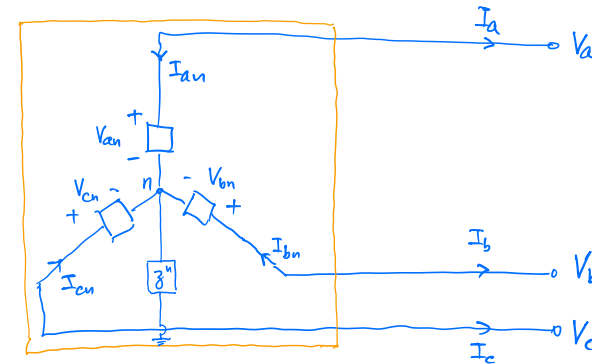3. If neutrals are ungrounded but connected to neutrals of other devices through 4-wire lines

- (V^n, I^n) determined by network interaction



C8.1 often assumed sometimes implicitly in literature

Conversion rule

Δ configuration: voltage conversion

1. Converts between internal and terminal voltages & currents

$$\boxed{V^\Delta = \Gamma V}, \quad I = -\Gamma^T I^\Delta$$


2. Given V^Δ , solution V exists iff $1^T V^\Delta = 0$, i.e.

- $V^{ab} + V^{bc} + V^{ca} = 0$ (Kirchhoff's Voltage Law)

3. Solution: terminal voltage $V = \frac{1}{3} \Gamma^T V^\Delta + \gamma 1, \quad \gamma \in \mathbb{C}$

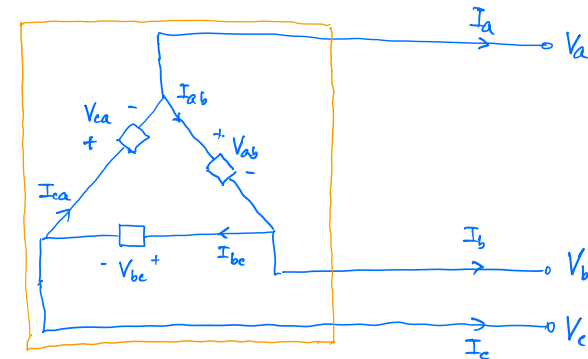4. $\gamma := \frac{1}{3} 1^T V$: (scaled) zero-sequence terminal voltage

- A given reference voltage, e.g., $V_0 := \alpha_+$, fixes γ for every Δ -configured device



Conversion rule

Δ configuration: current conversion

1. Converts between internal and terminal voltages & currents

$$V^\Delta = \Gamma V,$$

$$I = -\Gamma^T I^\Delta$$


2. Given I , solution I^Δ exists iff $1^T I = 0$, i.e.

- $I^a + I^b + I^c = 0$ (Kirchhoff's Current Law)

3. Solution: internal current $I^\Delta = -\frac{1}{3}\Gamma I + \beta 1, \quad \beta \in \mathbb{C}$

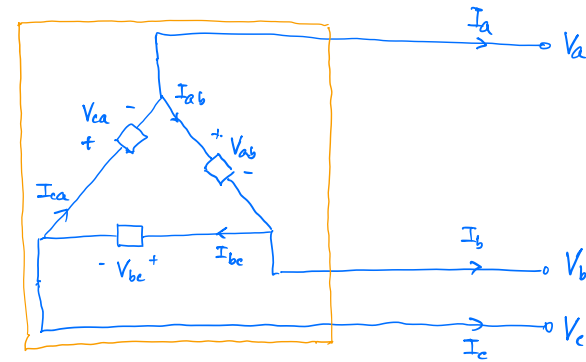4. $\beta := \frac{1}{3}1^T I^\Delta$: (scaled) zero-sequence internal current

- Zero-sequence internal current does not affect terminal current I



Conversion rule

Δ configuration: power conversion

1. Relation between s and s^Δ is **indirect**, through (V^Δ, I^Δ) , through (V, I) , or through (V, I^Δ)

- Follows from voltage and current conversions

2. Given (V^Δ, I^Δ) with $\mathbf{1}^\top V^\Delta = 0$, $s^\Delta := \text{diag}(V^\Delta I^{\Delta H})$ and terminal power is

$$s := \text{diag}(VI^H) = -\text{diag}\left(\Gamma^\dagger (V^\Delta I^{\Delta H}) \Gamma\right) + \gamma \bar{I}$$

3. Given (V, I) with $\mathbf{1}^\top I = 0$, $s := \text{diag}(VI^H)$ and internal power is

$$s^\Delta := \text{diag}(V^\Delta I^{\Delta H}) = -\text{diag}\left(\Gamma (VI^H) \Gamma^\dagger\right) + \bar{\beta} V^\Delta$$

4. Zero-sequence voltage γ and current β may be determined by spec or network interaction

5. Total powers $\mathbf{1}^\top s$ and $\mathbf{1}^\top s^\Delta$ are independent of (γ, β)

- Because $\mathbf{1}^\top I = 0$ and $\mathbf{1}^\top V^\Delta = 0$

Conversion rule

Δ configuration: power conversion

6. Relation between s and s^Δ through (V, I^Δ) :

$$s = -\text{diag}(VI^{\Delta H}\Gamma), \quad s^\Delta = \text{diag}(\Gamma VI^{\Delta H})$$

- no direct relation between s and s^Δ
- follows from voltage & current conversions

- The parameterization (V, I^Δ) implicitly contains $\gamma := \frac{1}{3}1^\top V$ and $\beta := \frac{1}{3}1^\top I^\Delta$ and is more convenient computationally

Three-phase devices

We next specify internal models and derive external models of 3-phase devices:



1. **External model** = Internal model + Conversion rule

- Internal model: relation between $(V^{Y/\Delta}, I^{Y/\Delta}, s^{Y/\Delta})$
- External model: relation between (V, I, s)

2. ... for devices

- Voltage source
- Current source
- Power source
- Impedance

3. ... in Y and Δ configurations

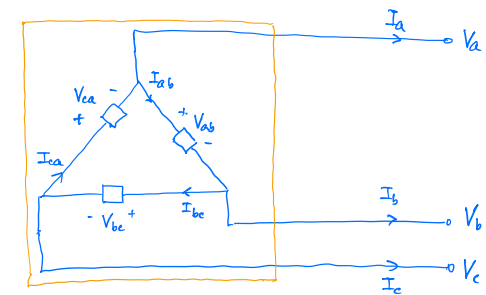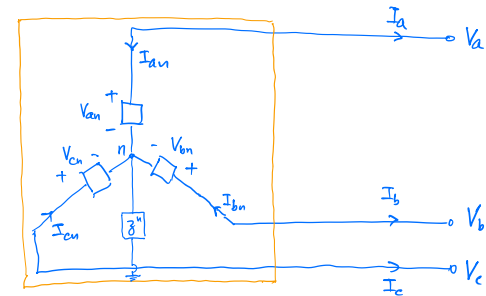

Voltage source (E^Y, z^Y, z^n) : Y configuration


Internal model

1. Internal voltages and currents

$$V^Y = E^Y + z^Y I^Y, \quad I^n = \mathbf{1}^T I^Y, \quad V^n = z^n (\mathbf{1}^T I^Y)$$

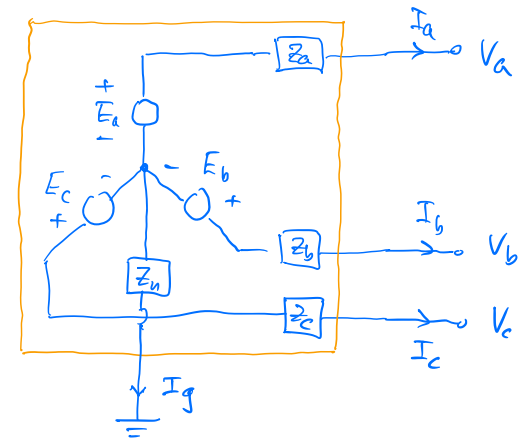2. Internal powers:

- Across each single-phase device: $s^Y := \text{diag}(V^Y I^{YH})$
- Across neutral conductor: $s^n := V^n \bar{I}^n$



$$s^Y = \text{diag}(E^Y I^{YH}) + \text{diag}(z^Y I^Y I^{YH}) = \underbrace{\begin{bmatrix} E^{an} I^{anH} \\ E^{bn} I^{bnH} \\ E^{cn} I^{cnH} \end{bmatrix}}_{s_{\text{ideal}}^Y} + \underbrace{\begin{bmatrix} z^{an} | I^{an} |^2 \\ z^{bn} | I^{bn} |^2 \\ z^{cn} | I^{cn} |^2 \end{bmatrix}}_{s_{\text{imp}}}, \quad s^n = z^n | \mathbf{1}^T I^Y |^2$$

Voltage source (E^Y, z^Y, z^n) : Y configuration

External model

1. Internal model

$$V^Y = E^Y + z^Y I^Y$$


2. Conversion rule for Y configuration

$$V = V^Y + V^{n1}, \quad I = -I^Y$$

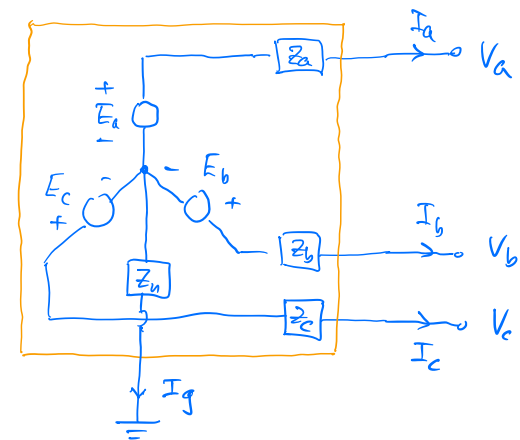3. \implies External model (under Assumption C8.1 $\implies V^n = -z^n (1^T I)$)

$$V = E^Y - \underbrace{(z^Y + z^n 11^T)}_{z^Y} I \quad \text{neutral conductor } z^n \text{ couples the phases}$$

$$s = \text{diag} \left(V (E^Y - V)^H ((Z^Y)^{-1})^H \right)$$



Voltage source (E^Y, z^Y, z^n) : Y configuration


External model

4. Comparison


Single-phase : $V = E - zI \in \mathbb{C}$

Three-phase : $V = E^Y - Z^Y I \in \mathbb{C}^3$
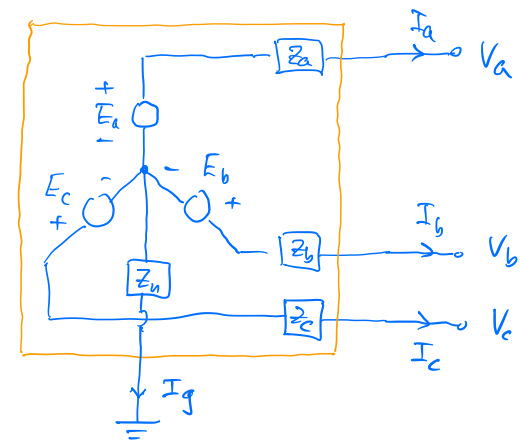
$$Z^Y := \begin{bmatrix} z^{an} + z^n & z^n & z^n \\ z^n & z^{bn} + z^n & z^n \\ z^n & z^n & z^{cn} + z^n \end{bmatrix}$$



1-phase device

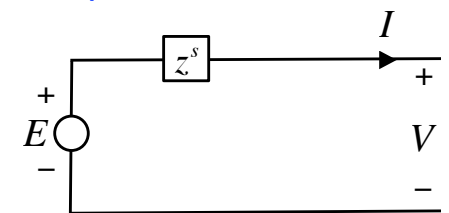

Voltage source (E^Y, z^Y, z^n) : Y configuration

Ideal source

1. Assumptions

- $z^Y = 0$
- Assumption C8.1 with $z^n = 0$: $V^n = 0$

2. Internal model

$$V^Y = E^Y$$


3. Conversion rule for Y configuration

$$V = V^Y, \quad I = -I^Y$$

4. \implies External model

$$V = E^Y$$

$$s = \text{diag}(E^Y I^H)$$

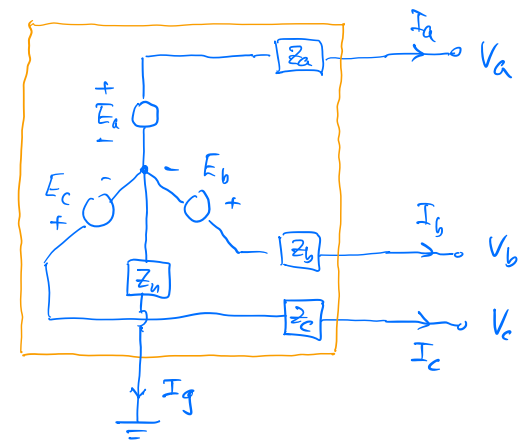

Current source (J^Y, y^Y, z^n) : Y configuration

Internal model

1. Internal voltages and currents


$$I^Y = J^Y + y^Y V^Y$$

2. Internal powers:

$$s^Y := \text{diag}(V^Y I^{YH}) = \text{diag}(V^Y J^{YH}) + \text{diag}(V^Y V^{YH} y^{YH})$$

$$= \underbrace{\begin{bmatrix} V^{an} J^{anH} \\ V^{bn} J^{bnH} \\ V^{cn} J^{cnH} \end{bmatrix}}_{s^Y_{\text{ideal}}} + \underbrace{\begin{bmatrix} y^{anH} | V^{an}|^2 \\ y^{bnH} | V^{bn}|^2 \\ y^{cnH} | V^{cn}|^2 \end{bmatrix}}_{s^Y_{\text{adm}}}$$

$$s^n := V^n I^{nH} = z^n \left| 1^T J^Y + \text{diag}(y^Y)^T V^Y \right|^2$$

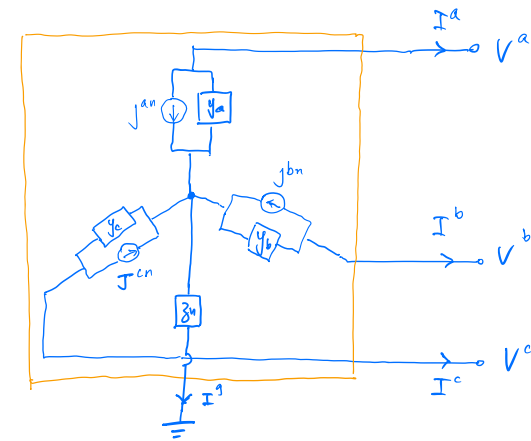

Current source (J^Y, y^Y, z^n) : Y configuration

External model

1. Internal model

$$I^Y = J^Y + y^Y V^Y$$


2. Conversion rule

$$V = V^Y + V^n \mathbf{1}, \quad I = -I^Y$$

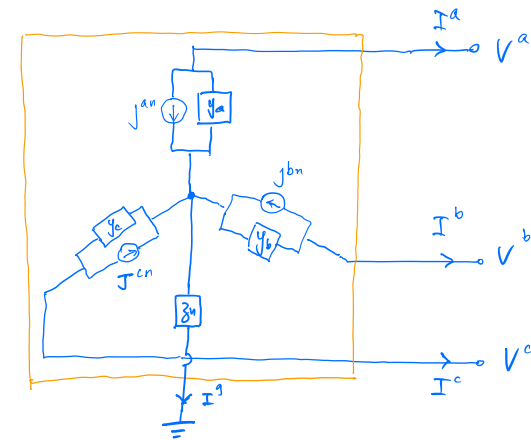3. \implies External model (under Assumption C8.1 $\implies V^n = -z^n (1^T I)$)

$$I = -A (J^Y + y^Y V) \quad \text{where } A := \mathbb{I} - \frac{z^n}{1 + z^n (1^T y^Y \mathbf{1})} y^Y \mathbf{1} \mathbf{1}^T$$

$$s = -\text{diag} \left(V (J^{YH} + V^H y^{YH}) A^H \right)$$



Current source (J^Y, y^Y, z^n) : Y configuration

External model


4. Comparison

Single-phase : $I = J - yV$


Three-phase : $I = A (-J^Y - y^Y V)$

$$A := \mathbb{1} - \frac{z^n}{1 + z^n (1^T y^Y 1)} y^Y 1 1^T$$

$A = \mathbb{1}$ if $z^n = 0$

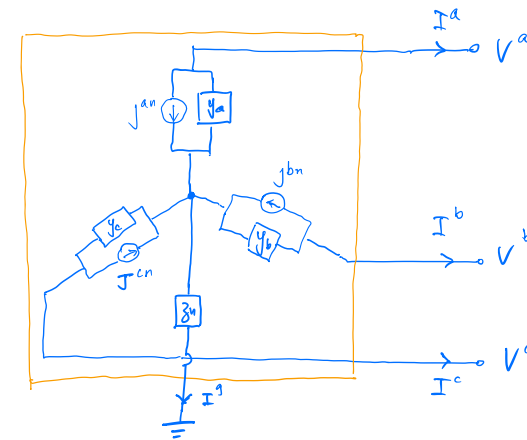

1-phase device

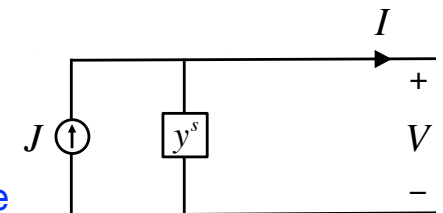

Note: directions of J are opposite

Current source (J^Y, y^Y, z^n) : Y configuration

Ideal source


1. Assumptions

- $y^Y = 0$
- Assumption C8.1 with $z^n = 0$: $V^n = 0$

2. \implies External model

$$I = -J^Y$$

$$s = -\text{diag}(VJ^{YH})$$

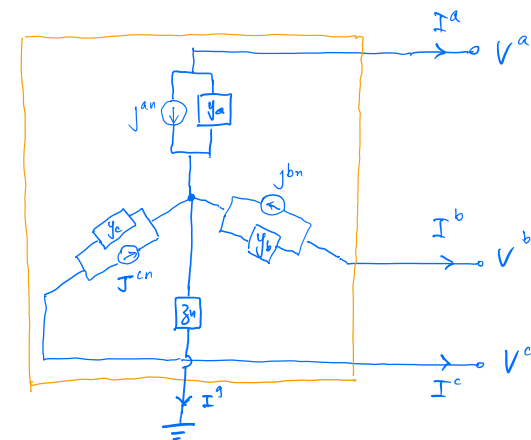


Power source (σ^Y, z^n) : Y configuration

Internal model

1. Internal powers

$$s^Y = \sigma^Y, \quad s^n := V^n I^{nH} = z^n \left| 1^T I^Y \right|^2$$

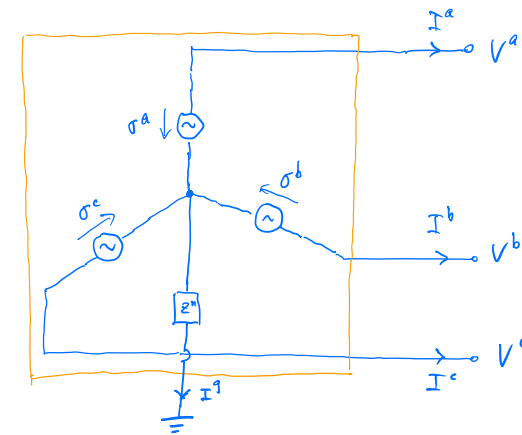

Power source (σ^Y, z^n) : Y configuration

External model

1. Internal model

$$s^Y = \sigma^Y$$


2. Conversion rule

$$V = V^Y + V^n \mathbf{1}, \quad I = -I^Y$$

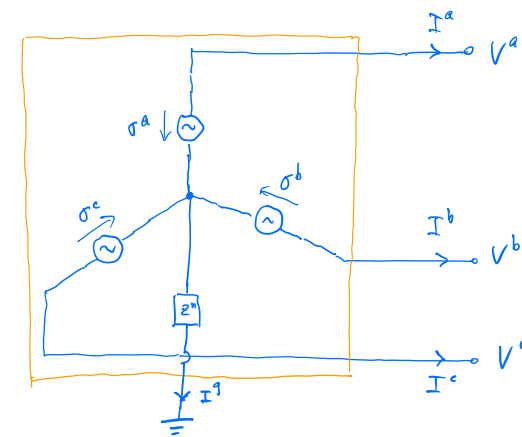3. \implies External model (under Assumption C8.1 $\implies V^n = -z^n (\mathbf{1}^\top I)$)

$$IV \text{ relation: } V = -\text{diag}(I^H)^{-1} \sigma^Y - z^n (\mathbf{1} \mathbf{1}^\top) I$$

$$Is \text{ relation: } s = -\left(\sigma^Y + z^n (\bar{H}^\top) \mathbf{1}\right)$$



Power source (σ^Y, z^n) : Y configuration

External model

4. Comparison


Single-phase : $s = \sigma$

Three-phase : $s = - \left(\sigma^Y + z^n (\bar{I} I^T) 1 \right)$

Total power (3-phase) :

$$-1^T \sigma^Y = 1^T s + \underbrace{z^n (1^T I^Y)}_{-V^n} \underbrace{(1^T \bar{I}^Y)}_{-I^{nH}} = 1^T s + s^n$$

power delivered to z^n

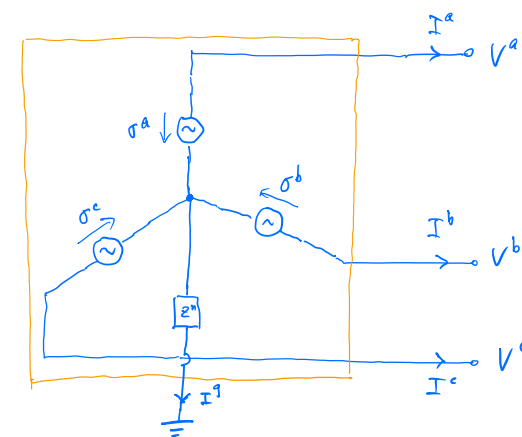

1-phase device



Note: directions of σ are opposite

Power source (σ^Y, z^n) : Y configuration


Ideal source

1. Assumption

- Assumption C8.1 with $z^n = 0$: $V^n = 0$

2. \implies External model

$$s = -\sigma^Y$$

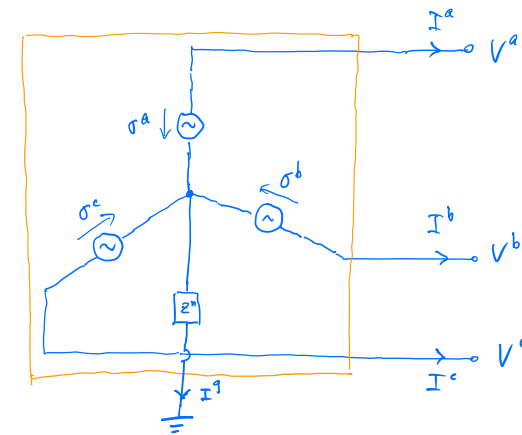

Impedance (z^Y, z^n) : Y configuration

Internal model


1. Internal voltage and current:

$$V^Y = z^Y I^Y$$

2. Internal power:

$$s^Y := \text{diag}(V^Y I^{YH}) = \text{diag}(V^Y V^{YH} (y^Y)^H)$$

$$s^n := V^n I^{nH} = z^n |1^T I^Y|^2$$

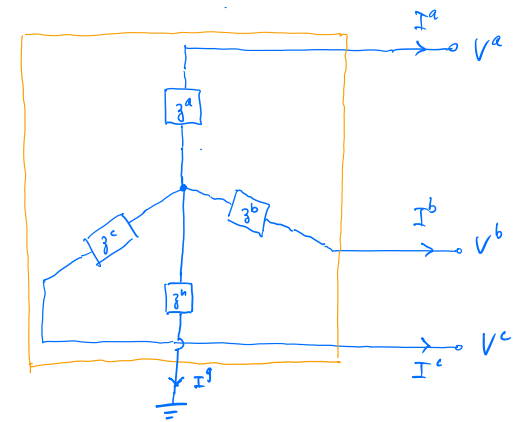

Impedance (z^Y, z^n) : Y configuration

External model

1. Internal model

$$V^Y = z^Y I^Y$$


2. Conversion rule for Y configuration

$$V = V^Y + V^{n1}, \quad I = -I^Y$$

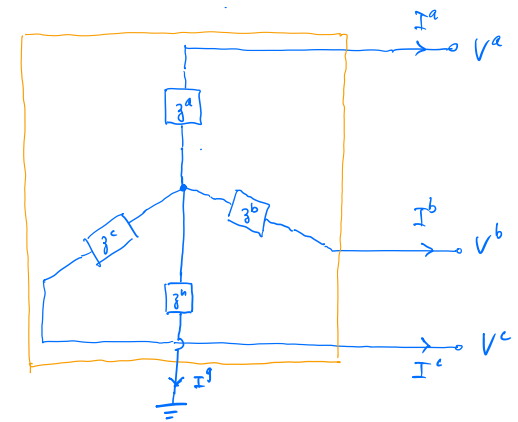3. \implies External model (under Assumption C8.1 $\implies V^n = -z^n (1^T I)$)

$$V = -Z^Y I = (z^Y + z^n 11^T) I$$

$$s = -\text{diag} \left(V V^H ((Z^Y)^{-1})^H \right)$$



neutral conductor z^n couples the phases

Impedance (z^Y, z^n) : Y configuration


External model

4. Comparison


Single-phase : $V = -zI \in \mathbb{C}$

Three-phase : $V = -Z^Y I \in \mathbb{C}^3$
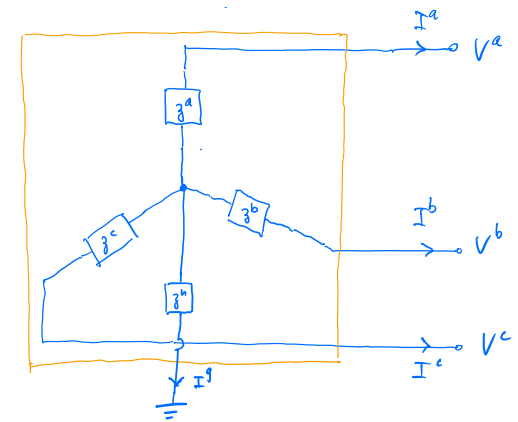
$$Z^Y := \begin{bmatrix} z^{an} + z^n & z^n & z^n \\ z^n & z^{bn} + z^n & z^n \\ z^n & z^n & z^{cn} + z^n \end{bmatrix}$$



1-phase device

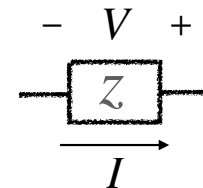

Impedance (z^Y, z^n) : Y configuration

Ideal impedance


1. Assumption

- Assumption C8.1 with $z^n = 0$: $V^n = 0$

2. \implies External model

$$Z^Y = z^Y, \quad V = z^Y I$$

phases are decoupled

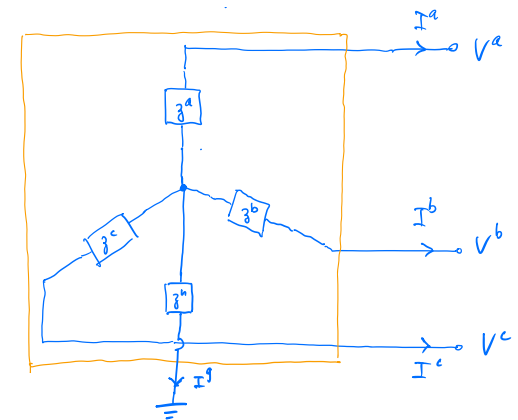

Balanced impedance

When $z^n \neq 0$ but z^Y is balanced, i.e., $z^{an} = z^{bn} = z^{cn}$, then similarity transformation using F produces a sequence impedance that is decoupled in the sequence coordinate

$$\tilde{Z}^Y = \begin{bmatrix} z^{an} + 3z^n & 0 & 0 \\ 0 & z^{an} & 0 \\ 0 & 0 & z^{an} \end{bmatrix}$$

Recap: external models

Y -configured devices (ideal)

Device	Y configuration	
Voltage source	$V = E^Y + \gamma \mathbf{1}$	$s = \text{diag} (E^Y I^H) + \gamma \bar{\mathbf{1}}$
Current source	$I = -J^Y$	$s = -\text{diag} (V J^{YH})$
Power source	$\text{diag} (I^H) (V - \gamma \mathbf{1}) = -\sigma$	$s = -\sigma^Y + \gamma \bar{\mathbf{1}}$
Impedance	$V = -z^Y I + \gamma \mathbf{1}$	$s = -\text{diag} (V (V - \gamma \mathbf{1})^H y^{YH})$

1. $\gamma := V^n$ is neutral voltage
2. Negative signs are only due to directions of I and s (out of device)
3. total terminal power $\mathbf{1}^T s =$ total internal power $\mathbf{1}^T s^Y +$ power delivered across neutral

Outline

1. Overview
2. Mathematical properties
3. Three-phase device models
 - Conversion rules
 - Devices in Y configuration
 - Devices in Δ configuration
 - Y - Δ transformation
4. Three-phase line models
5. Three-phase transformer models

Voltage source (E^Δ, z^Δ) : Δ configuration


Internal model

1. Internal voltages and currents

$$V^\Delta = E^\Delta + z^\Delta I^\Delta \quad \text{independent of } Y/\Delta \text{ config}$$

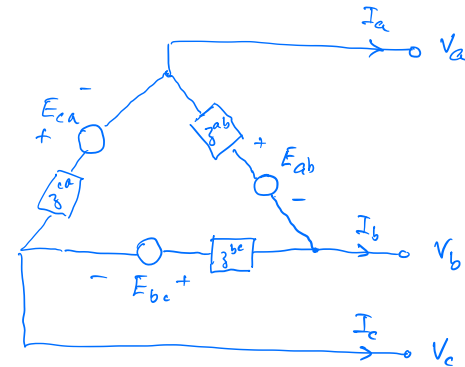2. Internal powers:

$$s^\Delta := \text{diag}(V^\Delta I^{\Delta H}) = \text{diag}(E^\Delta I^{\Delta H}) + \text{diag}(z^\Delta I^\Delta I^{\Delta H})$$



Voltage source (E^Δ, z^Δ) : Δ configuration


External model

1. Internal model

$$V^\Delta = E^\Delta + z^\Delta I^\Delta$$

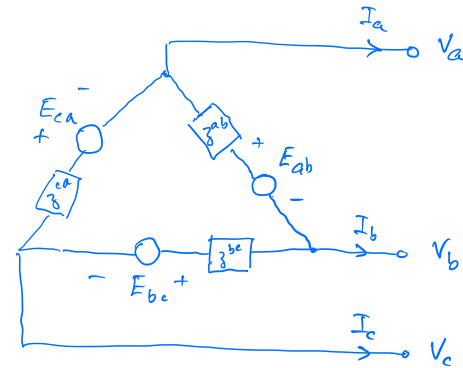2. Conversion rule for Δ configuration

$$V^\Delta = \Gamma V, \quad I = -\Gamma^\top I^\Delta$$



Voltage source (E^Δ, z^Δ) : Δ configuration

External model

1. Internal model

$$V^\Delta = E^\Delta + z^\Delta I^\Delta$$


2. Conversion rule for Δ configuration

$$V^\Delta = \Gamma V, \quad I = -\Gamma^\top I^\Delta$$

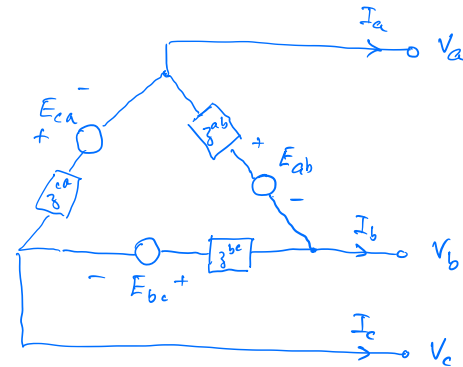3. Two (asymmetric) relations between terminal vars (V, I)

- Given V , 1st relation uniquely determines I (hence (V^Δ, I^Δ) as well)
- Given I , 2nd relation determines V up to zero-sequence voltage γ

Asymmetry is because V contains more info (γ) than I does (which contains no info about zero-sequence current $\beta := \frac{1}{3} \mathbf{1}^\top I^\Delta$)



Voltage source (E^Δ, z^Δ) : Δ configuration

External model

4. Given V ,

$$I = (\Gamma^\top y^\Delta) E^\Delta - Y^\Delta V$$

$$Y^\Delta := \Gamma^\top y^\Delta \Gamma = \begin{bmatrix} y^{ab} + y^{ca} & -y^{ab} & -y^{ca} \\ -y^{ab} & y^{ab} + y^{bc} & -y^{bc} \\ -y^{ca} & -y^{bc} & y^{ca} + y^{bc} \end{bmatrix}, \quad y^\Delta := (z^\Delta)^{-1}$$

Voltage source (E^Δ, z^Δ) : Δ configuration

External model

4. Given V ,

$$I = (\Gamma^\top y^\Delta) E^\Delta - Y^\Delta V$$

$$Y^\Delta := \Gamma^\top y^\Delta \Gamma = \begin{bmatrix} y^{ab} + y^{ca} & -y^{ab} & -y^{ca} \\ -y^{ab} & y^{ab} + y^{bc} & -y^{bc} \\ -y^{ca} & -y^{bc} & y^{ca} + y^{bc} \end{bmatrix}, \quad y^\Delta := (z^\Delta)^{-1}$$

5. Given I with $1^\top I = 0$,

$$V = \hat{\Gamma} E^\Delta - Z^\Delta I + \gamma 1, \quad 1^\top I = 0$$

$$\hat{\Gamma} := \frac{1}{3} \Gamma^\top \left(\mathbb{1} - \frac{1}{\zeta} \tilde{z}^\Delta 1^\top \right), \quad Z^\Delta := \frac{1}{9} \Gamma^\top z^\Delta \left(\mathbb{1} - \frac{1}{\zeta} 1 \tilde{z}^{\Delta\top} \right) \Gamma$$


Voltage source (E^Δ, z^Δ) : Δ configuration

External model

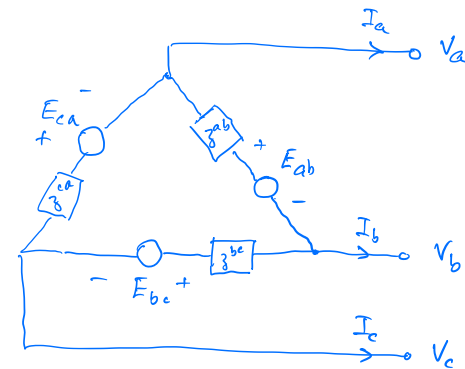6. Terminal power in terms of V or I :

$$s = \text{diag}(VI^H) = \text{diag}\left(V(\Gamma^T y^\Delta E^\Delta - Y^\Delta V)^H\right)$$

$$s = \text{diag}(VI^H) = \text{diag}\left(\left(\hat{\Gamma}E^\Delta - Z^\Delta I\right)I^H\right) + \gamma \bar{I}$$



Power due to zero-sequence voltage γ

Total power $1^T s$ is independent of γ because $\gamma 1^T \bar{I} = 0$


Voltage source (E^Δ, z^Δ) : Δ configuration

External model

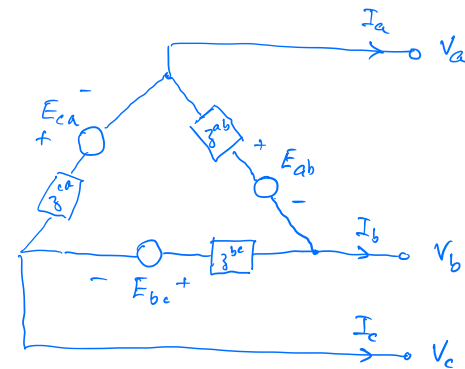
7. Comparison

Single-phase : $V = E - zI$

Three-phase : $V = \hat{\Gamma}E^\Delta - Z^\Delta I + \gamma 1, \quad 1^T I = 0$



1-phase device

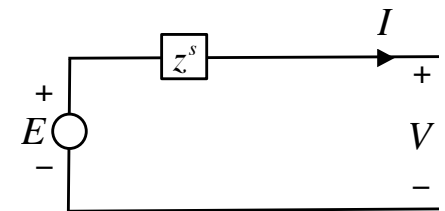

Voltage source (E^Δ, z^Δ) : Δ configuration

Ideal source

1. Assumption

- $z^\Delta = 0$


2. $\implies \hat{\Gamma} = \frac{1}{3}\Gamma^\top, \quad Z^\Delta = 0$

3. \implies External model

$$V = \frac{1}{3}\Gamma^\top E^\Delta + \gamma \mathbf{1}, \quad \mathbf{1}^\top I = 0$$

$$s = \frac{1}{3}\text{diag}(\Gamma^\top E^\Delta I^H) + \gamma \bar{I}$$


Zero-sequence voltage γ

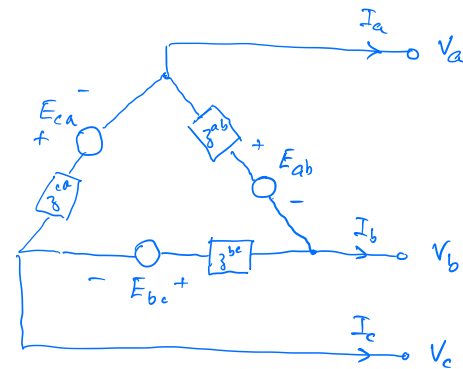

Voltage source (E^Δ, z^Δ) : Δ configuration

Voltage source specifies E^Δ which does not uniquely determine terminal voltage V

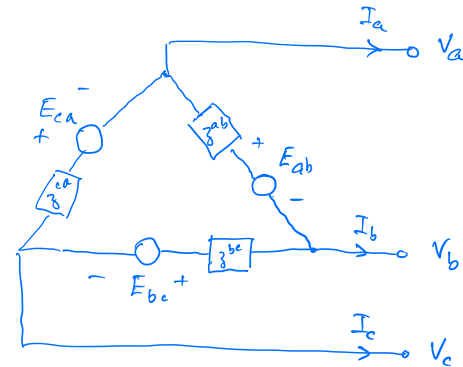- Because the zero-sequence voltage $\gamma := \frac{1}{3}1^T V$ is arbitrary
- γ needs to be specified, e.g., fixed by a reference voltage or grounding
- ... for both ideal or non-ideal voltage sources



Current source (J^Δ, y^Δ) : Δ configuration


Internal model

1. Internal voltages and currents

$$I^\Delta = J^\Delta + y^\Delta V^\Delta$$

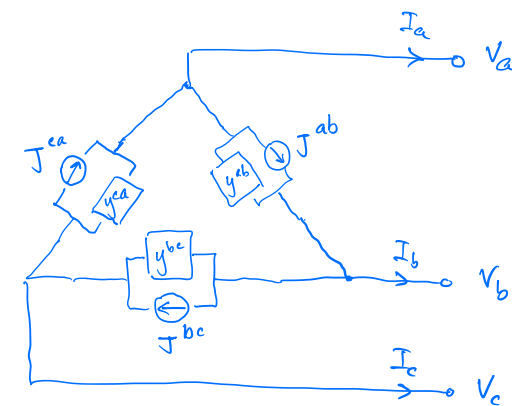2. Internal powers:

$$\begin{aligned} s^\Delta &:= \text{diag}(V^\Delta I^{\Delta H}) \\ &= \text{diag}(V^\Delta J^{\Delta H}) + \text{diag}(V^\Delta V^{\Delta H} y^{\Delta H}) \end{aligned}$$



Current source (J^Δ, y^Δ) : Δ configuration

External model

1. Internal model

$$I^\Delta = J^\Delta + y^\Delta V^\Delta$$

2. Conversion rule


$$V^\Delta = \Gamma V, \quad I = -\Gamma^\top I^\Delta$$

3. \implies External model

$$I = -(\Gamma^\top J^\Delta + Y^\Delta V)$$

where (as before): $Y^\Delta := \Gamma^\top y^\Delta \Gamma =$
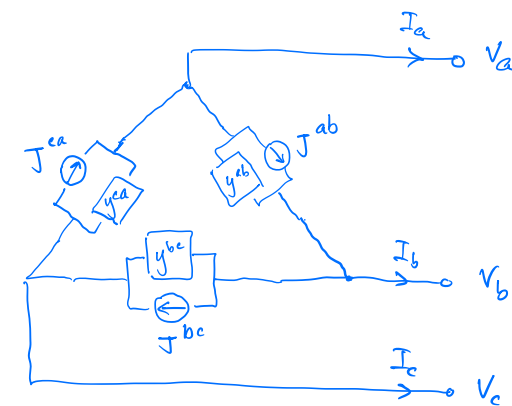
$$\begin{bmatrix} y^{ab} + y^{ca} & -y^{ab} & -y^{ca} \\ -y^{ab} & y^{ab} + y^{bc} & -y^{bc} \\ -y^{ca} & -y^{bc} & y^{ca} + y^{bc} \end{bmatrix}$$



Current source (J^Δ, y^Δ) : Δ configuration

External model

1. Internal model

$$I^\Delta = J^\Delta + y^\Delta V^\Delta$$


2. Conversion rule

$$V^\Delta = \Gamma V, \quad I = -\Gamma^\top I^\Delta$$

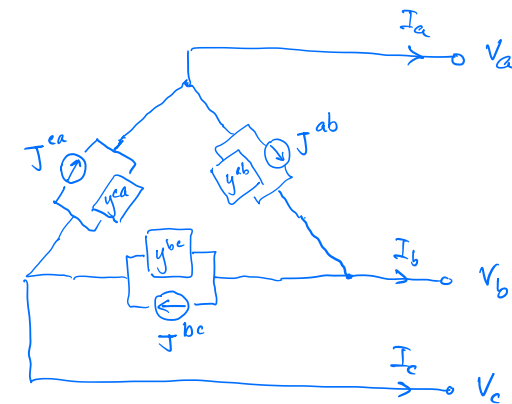3. \implies External model

$$I = -(\Gamma^\top J^\Delta + Y^\Delta V)$$

$$s = \text{diag}(VI^H) = -\text{diag}(VJ^{\Delta H}\Gamma + VV^H Y^{\Delta H})$$



Current source (J^Δ, y^Δ) : Δ configuration


External model

4. Comparison


Single-phase : $I = J - yV$

Three-phase : $I = -\Gamma^\top J^\Delta - Y^\Delta V$
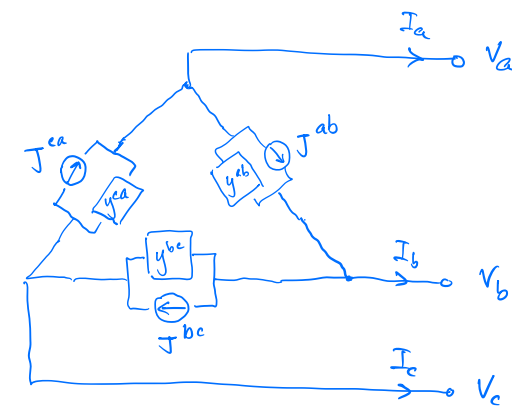
$$Y^\Delta := \Gamma^\top y^\Delta \Gamma$$



1-phase device

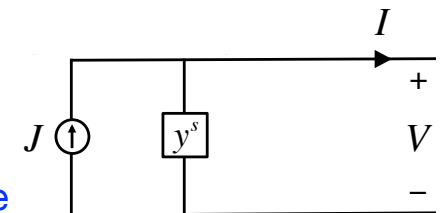

Note: directions of J are opposite

Current source (J^Δ, y^Δ) : Δ configuration

Ideal source


1. Assumption

- $y^\Delta = 0$

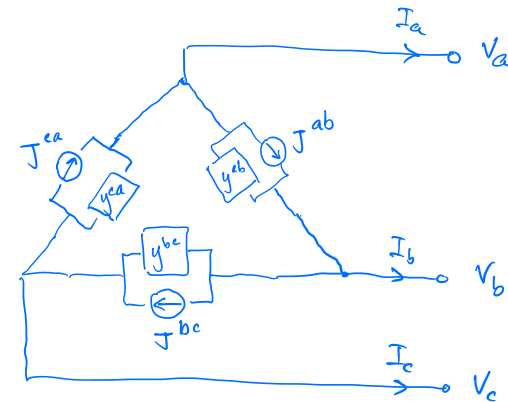2. \implies External model

$$I = -\Gamma^\top J^\Delta$$


$$s = -\text{diag}(VJ^{\Delta H}\Gamma)$$



Voltage & current sources: comparison

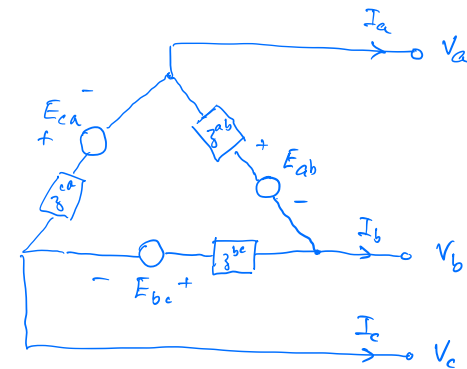
1. Voltage source specifies E^Δ which does not uniquely determine terminal voltage V

- $V = \hat{\Gamma}E^\Delta - Z^\Delta I + \gamma 1, \quad 1^\top I = 0$
- due to arbitrary zero-sequence voltage $\gamma := \frac{1}{3}1^\top V$



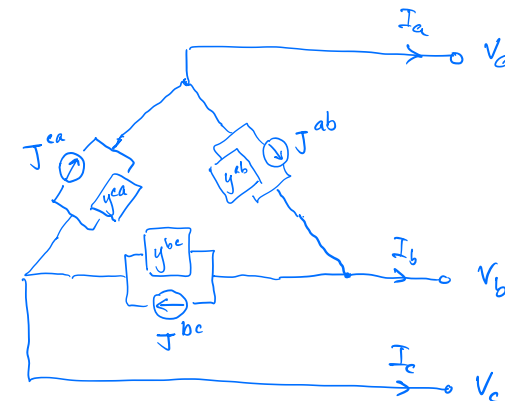2. Current source specifies J^Δ which uniquely determines terminal current I

- $I = -(\Gamma^\top J^\Delta + Y^\Delta V)$
- J^Δ contains its zero-sequence current $\beta := \frac{1}{3}1^\top J^\Delta$




Power source σ^Δ : Δ configuration

Internal model

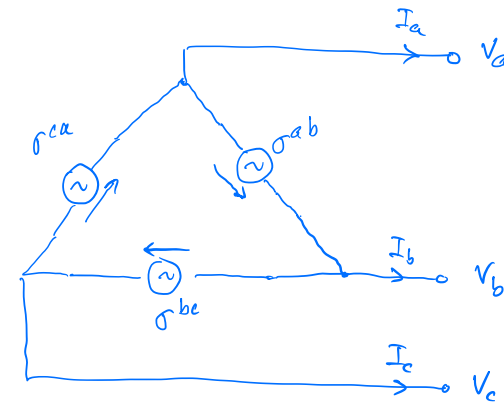1. Internal powers

$$s^\Delta := \text{diag}(V^\Delta I^{\Delta H}) = \sigma^\Delta$$



Power source σ^Δ : Δ configuration

External model

1. Internal model

$$s^\Delta = \sigma^\Delta$$


2. Conversion rule

$$V^\Delta = \Gamma V, \quad I = -\Gamma^\top I^\Delta$$

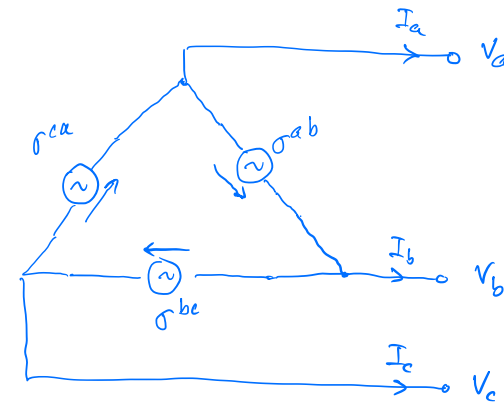3. \implies External model

$$IV \text{ relation: } \sigma^\Delta = -\frac{1}{3} \text{diag} \left(\Gamma (VI^H) \Gamma^\top \right) + \bar{\beta} \Gamma V, \quad \mathbf{1}^\top I = 0$$

7 complex vars (V, I, β) , 4 quadratic equations



Power source σ^Δ : Δ configuration

External model

1. Internal model

$$s^\Delta = \sigma^\Delta$$


2. Conversion rule

$$V^\Delta = \Gamma V, \quad I = -\Gamma^\top I^\Delta$$

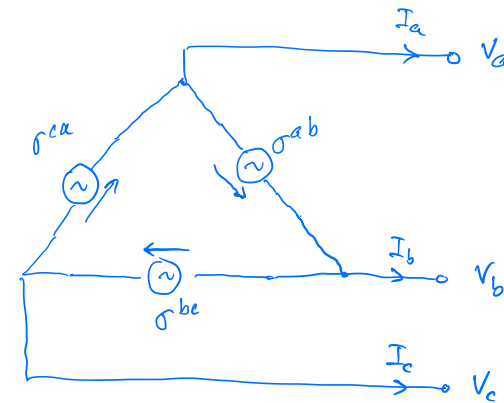3. \implies External model

$$IV \text{ relation: } \sigma^\Delta = -\frac{1}{3} \text{diag} \left(\Gamma (VI^H) \Gamma^\top \right) + \bar{\beta} \Gamma V, \quad \mathbf{1}^\top I = 0$$

$$\text{Equivalent model: } \sigma^\Delta = \text{diag} \left(\Gamma VI^{\Delta H} \right)$$



Power source σ^Δ : Δ configuration

External model

4. Comparison


Single-phase : $s = \sigma$

Three-phase : $s = -\text{diag}(\Gamma V I^{\Delta H} \Gamma)$

$$\sigma^\Delta = \text{diag}(\Gamma V I^{\Delta H} \Gamma) = \begin{bmatrix} (V_a - V_b) \bar{I}^{ab} \\ (V_b - V_c) \bar{I}^{bc} \\ (V_c - V_a) \bar{I}^{ca} \end{bmatrix}$$

Given V (and σ^Δ), I^Δ and hence s are uniquely determined

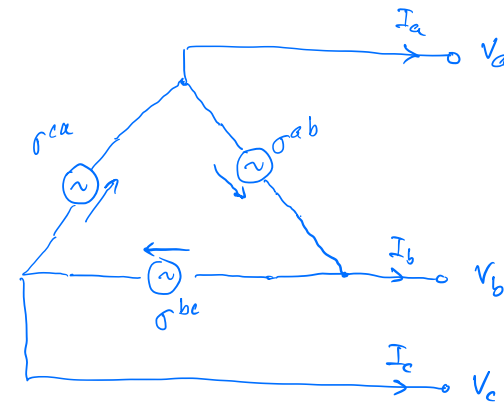Given I^Δ (and σ^Δ), only ΓV is uniquely determined, not V nor s



1-phase device



Power source σ^Δ : Δ configuration


Ideal source

1. Assumption

- Assumption C8.1 with $z^n = 0$: $V^n = 0$

2. \implies External model

$$s = -\sigma^Y$$

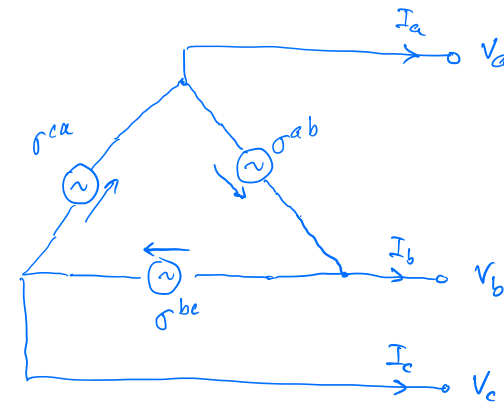

Impedance z^Δ : Δ configuration


Internal model

1. Internal voltage and current:

$$V^\Delta = z^\Delta I^\Delta$$

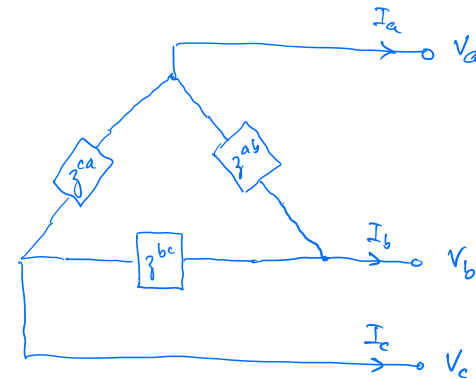2. Internal power:

$$s^\Delta = \text{diag}(V^\Delta I^{\Delta H}) := \text{diag}(z^\Delta I^\Delta I^{\Delta H})$$



Impedance z^Δ : Δ configuration

External model

1. Internal model

$$V^\Delta = z^\Delta I^\Delta$$

2. Conversion rule


$$V^\Delta = \Gamma V, \quad I = -\Gamma^\top I^\Delta$$

3. \implies External model

$$\text{Given } V, \quad I = -Y^\Delta V := -(\Gamma^\top y^\Delta \Gamma) V$$

$$\text{Given } I, \quad V = -Z^\Delta I + \gamma 1, \quad 1^\top I = 0$$
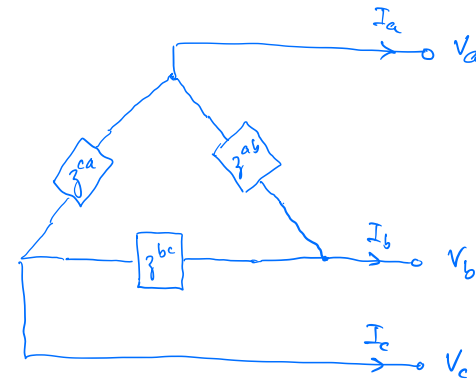
$$Z^\Delta := \frac{1}{9} \Gamma^\top z^\Delta \left(\mathbb{1} - \frac{1}{\zeta} 1 \tilde{z}^{\Delta \top} \right) \Gamma$$



As for voltage source, the asymmetry is because V contains more info (γ) than I does


Impedance z^Δ : Δ configuration

External model

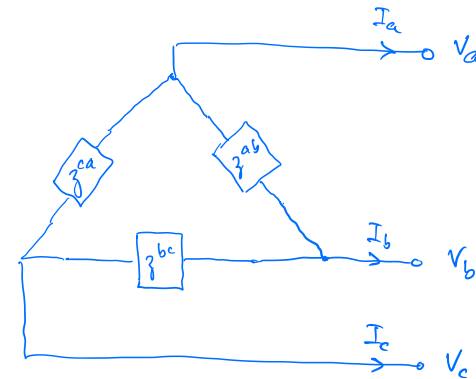4. Terminal power s can be related to V or to I :

$$\text{Given } V, s = \text{diag}(VI^H) = -\text{diag}(VV^HY^{\Delta H})$$

$$\text{Given } I, s = \text{diag}(VI^H) = -\text{diag}(Z^\Delta II^H) + \gamma \bar{I}$$



As for voltage source, the asymmetry is because V contains more info (γ) than I does

Impedance z^Δ : Δ configuration

External model


5. Comparison

Single-phase : $I = -yZ$ or $V = -zI \in \mathbb{C}$


Three-phase :

$$I = -Y^\Delta V \in \mathbb{C}^3$$
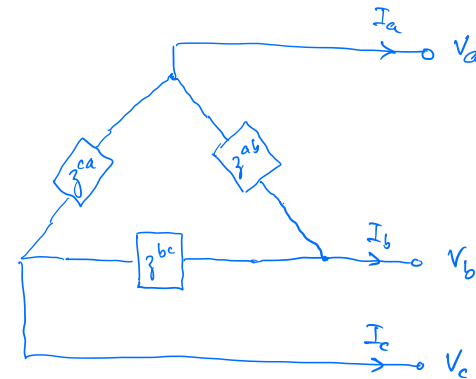
$$V = -Z^\Delta I + \gamma \mathbf{1}, \quad \mathbf{1}^T I = 0$$



1-phase device

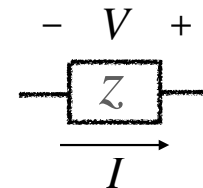

Impedance z^Δ : Δ configuration

Balanced impedance


1. Assumption

- $z^{ab} = z^{bc} = z^{ca}$

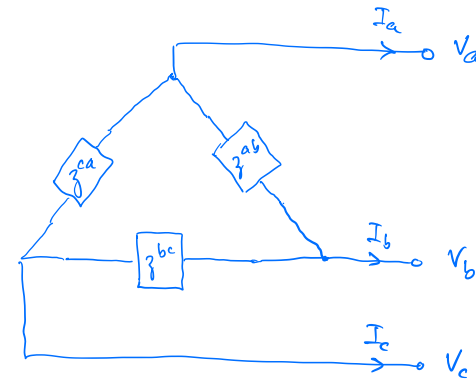2. External model

$$V = -Z^\Delta I + \gamma \mathbf{1}, \quad \mathbf{1}^\top I = 0$$

$$Z^\Delta = \frac{z^{ab}}{3} \left(\mathbb{I} - \frac{1}{3} \mathbf{1} \mathbf{1}^\top \right) \quad \text{phases are coupled } (Z^\Delta \text{ is not diagonal})$$



Impedance z^Δ : Δ configuration

Balanced impedance

1. Assumption

- $z^{ab} = z^{bc} = z^{ca}$


2. External model

$$V = -Z^\Delta I + \gamma \mathbf{1}, \quad \mathbf{1}^\top I = 0$$

$$Z^\Delta = \frac{z^{ab}}{3} \left(\mathbb{I} - \frac{1}{3} \mathbf{1} \mathbf{1}^\top \right) \quad \text{phases are coupled (} Z^\Delta \text{ is not diagonal)}$$

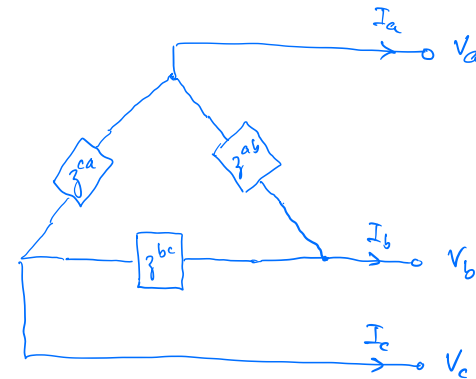3. Sequence impedance \tilde{Z}^Δ is decoupled in sequence coordinate

$$\tilde{Z}^\Delta = \frac{z^{ab}}{3} \begin{bmatrix} 0 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \quad \text{zero-sequence component (first row \& col) is zero because } I^a + I^b + I^c = 0$$



Recap: external models

Δ -configured devices (ideal)

Device	Δ configuration	
Voltage source	$V = \frac{1}{3}\Gamma^T E^\Delta + \gamma \mathbf{1}, \mathbf{1}^T I = 0$	$s = \frac{1}{3}\text{diag}(\Gamma^T E^\Delta I^H) + \gamma \bar{I}$
Current source	$I = -\Gamma^T J^\Delta$	$s = -\text{diag}(V J^{\Delta H} \Gamma)$
Power source	$\sigma^\Delta = \text{diag}(\Gamma V I^{\Delta H})$	
Impedance	$I = -Y^\Delta V$	$s = -\text{diag}(V V^H Y^{\Delta H})$

1. $\gamma := \frac{1}{3}\mathbf{1}^T V$ is zero-seq terminal voltage
2. total terminal power $\mathbf{1}^T s$ is independent of γ because $\mathbf{1}^T \bar{I} = 0$

Outline

1. Overview
2. Mathematical properties
3. Three-phase device models
 - Conversion rules
 - Devices in Y configuration
 - Devices in Δ configuration
 - Y - Δ transformation
4. Three-phase line models
5. Three-phase transformer models

Δ - Y transformation

Ideal voltage source (E^Δ, γ)

1. External model

$$V = \frac{1}{3} \Gamma^\top E^\Delta + \gamma \mathbf{1}, \quad \mathbf{1}^\top I = 0$$

2. Y equivalent

- Ideal voltage source $V = E^Y + V^n \mathbf{1}$, $\mathbf{1}^\top I = -I^n$ with

$$E^Y := \frac{1}{3} \Gamma^\top E^\Delta, \quad V^n := \gamma, \quad \text{no neutral line so that } I^n = 0$$

- **Not** necessarily balanced

Δ - Y transformation

Ideal voltage source (E^Δ, γ)

3. If E^Δ is balanced then

$$\Gamma^\top E^\Delta = (1 - \alpha^2)E^\Delta = \sqrt{3} e^{-i\pi/6} E^\Delta$$

$$V = \frac{1}{\sqrt{3}} e^{-i\pi/6} E^\Delta + \gamma \mathbf{1}, \quad \mathbf{1}^\top I = 0$$

Y equivalent:

$$E^Y = \frac{1}{\sqrt{3} e^{i\pi/6}} E^\Delta, \quad V^n := \gamma, \quad \text{no neutral line so that } I^n = 0$$

Δ - Y transformation

Non-ideal voltage source $(E^\Delta, z^\Delta, \gamma)$

1. External model

$$V = \hat{\Gamma}E^\Delta - Z^\Delta I + \gamma \mathbf{1}, \quad \mathbf{1}^\top I = 0$$

$$\text{where } \hat{\Gamma} := \frac{1}{3}\Gamma^\top \left(\mathbb{1} - \frac{1}{\zeta} \tilde{z}^\Delta \mathbf{1}^\top \right), \quad Z^\Delta := \frac{1}{9}\Gamma^\top z^\Delta \left(\mathbb{1} - \frac{1}{\zeta} \mathbf{1} \tilde{z}^{\Delta\top} \right) \Gamma$$

2. There is no Y equivalent

- Y equivalent has no neutral line so that $\mathbf{1}^\top I = 0$
- External model: $V = E^Y - z^Y I + V^n \mathbf{1}$
- Z^Δ is generally not diagonal (even if $z^\Delta = z^{ab\mathbb{1}}$), but z^Y is diagonal

Δ - Y transformation

Ideal current source J^Δ

1. External model

$$I = -\Gamma^\top J^\Delta$$

2. Y equivalent

- Ideal current source $I = -J^Y$, $\mathbf{1}^\top I = -I^n$ with

$$J^Y := \Gamma^\top J^\Delta, \quad \text{no neutral line } (\mathbf{1}^\top I = 0)$$

3. If J^Δ is balanced then

$$J^Y = (1 - \alpha^2)J^\Delta = \frac{\sqrt{3}}{e^{i\pi/6}} J^\Delta$$

Outline

1. Overview
2. Mathematical properties
3. Three-phase device models
4. Three-phase line models
 - 4-wire model
 - 3-wire model
5. Three-phase transformer models

4-wire line model

Series impedance matrix \hat{z}_{jk}^s

1. Single-phase line: $V_j - V_k = z_{jk}^s I_{jk}$
2. Three-phase line: $\hat{V}_j - \hat{V}_k = \hat{z}_{jk}^s I_{jk}$

$$\begin{bmatrix} V_j^a \\ V_j^b \\ V_j^c \\ V_j^n \end{bmatrix} - \begin{bmatrix} V_k^a \\ V_k^b \\ V_k^c \\ V_k^n \end{bmatrix} = \underbrace{\begin{bmatrix} \hat{z}_{jk}^{aa} & \hat{z}_{jk}^{ab} & \hat{z}_{jk}^{ac} & \hat{z}_{jk}^{an} \\ \hat{z}_{jk}^{ba} & \hat{z}_{jk}^{bb} & \hat{z}_{jk}^{bc} & \hat{z}_{jk}^{bn} \\ \hat{z}_{jk}^{ca} & \hat{z}_{jk}^{cb} & \hat{z}_{jk}^{cc} & \hat{z}_{jk}^{cn} \\ \hat{z}_{jk}^{na} & \hat{z}_{jk}^{nb} & \hat{z}_{jk}^{nc} & \hat{z}_{jk}^{nn} \end{bmatrix}}_{\text{impedance matrix } \hat{z}_{jk}^s} \begin{bmatrix} I_{jk}^a \\ I_{jk}^b \\ I_{jk}^c \\ I_{jk}^n \end{bmatrix}$$

3. Impedance matrix \hat{z}_{jk}^s depends on
 - wire materials, lengths, distances between wires, frequency, earth resistivity

4-wire line model

Interpretation

Complete circuit a only

$$\begin{bmatrix} V_j^a \\ V_j^b \\ V_j^c \\ V_j^n \end{bmatrix} - \begin{bmatrix} V_k^a \\ V_k^b \\ V_k^c \\ V_k^n \end{bmatrix} = \begin{bmatrix} \hat{z}_{jk}^{aa} & \hat{z}_{jk}^{ab} & \hat{z}_{jk}^{ac} & \hat{z}_{jk}^{an} \\ \hat{z}_{jk}^{ba} & \hat{z}_{jk}^{bb} & \hat{z}_{jk}^{bc} & \hat{z}_{jk}^{bn} \\ \hat{z}_{jk}^{ca} & \hat{z}_{jk}^{cb} & \hat{z}_{jk}^{cc} & \hat{z}_{jk}^{cn} \\ \hat{z}_{jk}^{na} & \hat{z}_{jk}^{nb} & \hat{z}_{jk}^{nc} & \hat{z}_{jk}^{nn} \end{bmatrix} \begin{bmatrix} I_{jk}^a \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

self impedance:

$$\hat{z}_{jk}^{aa} = \frac{V_j^a - V_k^a}{I_{jk}^a}$$

mutual impedance:

$$\hat{z}_{jk}^{ba} = \frac{V_j^b - V_k^b}{I_{jk}^a}$$

4-wire line model

With shunt admittances


Each line is characterized by

- Series admittance $\hat{y}_{jk}^s := \left(\hat{z}_{jk}^s\right)^{-1}$
- Shunt admittances $\left(\hat{y}_{jk}^m, \hat{y}_{kj}^m\right)$

Terminal voltages $\left(\hat{V}_j, \hat{V}_k\right)$ and terminal currents $\left(\hat{I}_{jk}, \hat{I}_{kj}\right)$ satisfy

$$\hat{I}_{jk} = \hat{y}_{jk}^s \left(\hat{V}_j - \hat{V}_k\right) + \hat{y}_{jk}^m \hat{V}_j$$
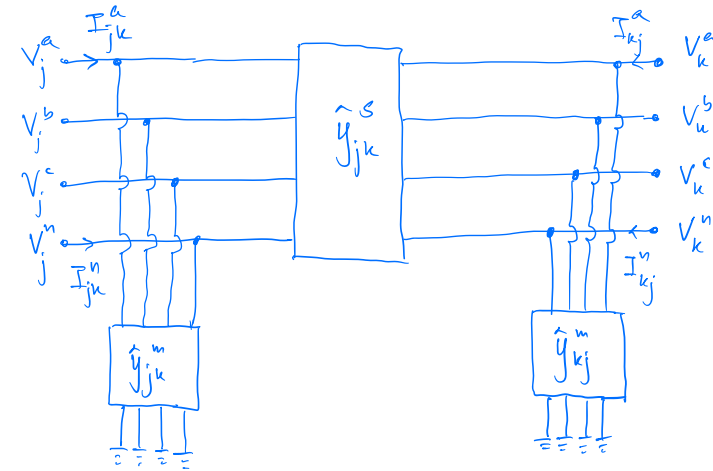
$$\hat{I}_{kj} = \hat{y}_{jk}^s \left(\hat{V}_k - \hat{V}_j\right) + \hat{y}_{kj}^m \hat{V}_k$$



3-wire line model

Series impedance matrix z_{jk}^s

$$\begin{bmatrix} V_j^a \\ V_j^b \\ V_j^c \\ V_j^n \end{bmatrix} - \begin{bmatrix} V_k^a \\ V_k^b \\ V_k^c \\ V_k^n \end{bmatrix} = \begin{bmatrix} \hat{z}_{jk}^{aa} & \hat{z}_{jk}^{ab} & \hat{z}_{jk}^{ac} & \hat{z}_{jk}^{an} \\ \hat{z}_{jk}^{ba} & \hat{z}_{jk}^{bb} & \hat{z}_{jk}^{bc} & \hat{z}_{jk}^{bn} \\ \hat{z}_{jk}^{ca} & \hat{z}_{jk}^{cb} & \hat{z}_{jk}^{cc} & \hat{z}_{jk}^{cn} \\ \hat{z}_{jk}^{na} & \hat{z}_{jk}^{nb} & \hat{z}_{jk}^{nc} & \hat{z}_{jk}^{nn} \end{bmatrix} \begin{bmatrix} I_{jk}^a \\ I_{jk}^b \\ I_{jk}^c \\ I_{jk}^n \end{bmatrix}$$

1. $I_{jk}^n = 0$: can eliminate last column and row of \hat{z}_{jk}^s
 - There is no neutral line, e.g., Δ -configured device
2. $V_j^n = V_k^n$: can eliminate $I_{jk}^n = -\frac{1}{\hat{z}_{jk}^{nn}} \left(\hat{z}_{jk}^{na} I_{jk}^a + \hat{z}_{jk}^{nb} I_{jk}^b + \hat{z}_{jk}^{nc} I_{jk}^c \right)$
 - Neutrals at both ends are grounded with $z_j^n = z_k^n = 0$

3-wire line model

Series impedance matrix z_{jk}^s

Both cases can be modeled by 3×3 impedance matrix

$$\begin{bmatrix} V_j^a \\ V_j^b \\ V_j^c \end{bmatrix} - \begin{bmatrix} V_k^a \\ V_k^b \\ V_k^c \end{bmatrix} = \underbrace{\begin{bmatrix} z_{jk}^{aa} & z_{jk}^{ab} & z_{jk}^{ac} \\ z_{jk}^{ba} & z_{jk}^{bb} & z_{jk}^{bc} \\ z_{jk}^{ca} & z_{jk}^{cb} & z_{jk}^{cc} \end{bmatrix}}_{z_{jk}^s} \begin{bmatrix} I_{jk}^a \\ I_{jk}^b \\ I_{jk}^c \end{bmatrix}$$


Three-phase line: $V_j - V_k = z_{jk}^s I_{jk}$

3-wire line model

With shunt admittances

Each line is characterized by

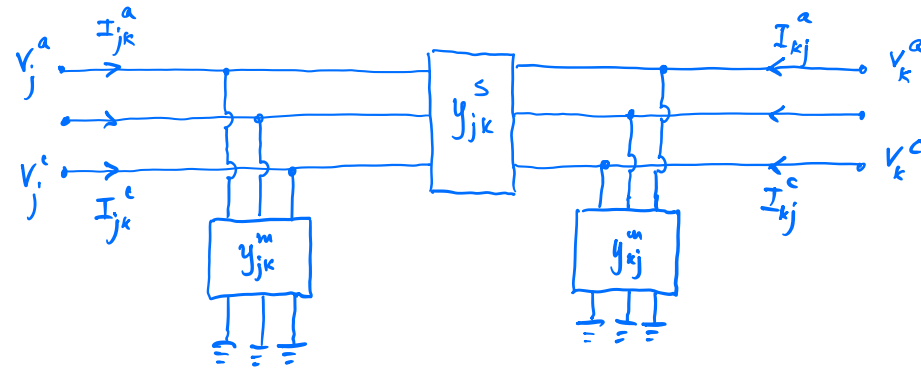- Series admittance $y_{jk}^s := (z_{jk}^s)^{-1}$
- Shunt admittances (y_{jk}^m, y_{kj}^m)



Terminal voltages (V_j, V_k) and terminal currents (I_{jk}, I_{kj}) satisfy

$$I_{jk} = y_{jk}^s (V_j - V_k) + y_{jk}^m V_j$$


$$I_{kj} = y_{jk}^s (V_k - V_j) + y_{kj}^m V_k$$

3-wire line model

With shunt admittances

Each line is characterized by

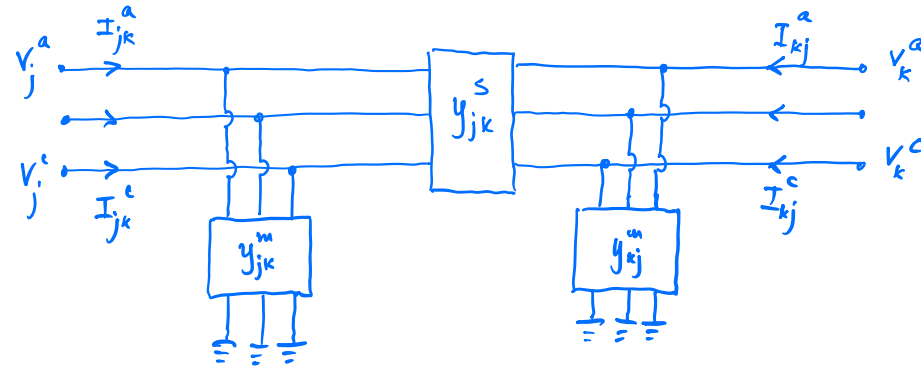- Series admittance $y_{jk}^s := (z_{jk}^s)^{-1}$
- Shunt admittances (y_{jk}^m, y_{kj}^m)



Terminal voltages (V_j, V_k) and line power matrices $(S_{jk}, S_{kj}) \in \mathbb{C}^{6 \times 6}$ satisfy

$$S_{jk} := V_j (I_{jk})^H = V_j (V_j - V_k)^H (y_{jk}^s)^H + V_j V_j^H (y_{jk}^m)^H$$

$$S_{kj} := V_k (I_{kj})^H = V_k (V_k - V_j)^H (y_{jk}^s)^H + V_k V_k^H (y_{kj}^m)^H$$

line flows are $\text{diag}(S_{jk}), \text{diag}(S_{kj})$

Comparison

IV relation

$$I_{jk}(V_j, V_k) = y_{jk}^s (V_j - V_k) + y_{jk}^m V_j$$

$$I_{kj}(V_j, V_k) = y_{jk}^s (V_k - V_j) + y_{kj}^m V_k$$

SV relation

$$S_{jk}(V_j, V_k) = V_j (V_j - V_k)^H (y_{jk}^s)^H + V_j V_j^H (y_{jk}^m)^H$$


$$S_{kj}(V_j, V_k) = V_k (V_k - V_j)^H (y_{jk}^s)^H + V_k V_k^H (y_{kj}^m)^H$$

same expressions for 1 or 3 phases !

	1-phase	3-phase (4-wire)	3-phase (3-wire)
admittances $y_{jk}^s, y_{jk}^m, y_{kj}^m$	\mathbb{C}	$\mathbb{C}^{4 \times 4}$	$\mathbb{C}^{3 \times 3}$
voltages V_j, V_k	\mathbb{C}	\mathbb{C}^4	\mathbb{C}^3
currents I_{jk}, I_{kj}	\mathbb{C}	\mathbb{C}^4	\mathbb{C}^3
line powers S_{jk}, S_{kj}	\mathbb{C}	$\mathbb{C}^{4 \times 4}$	$\mathbb{C}^{3 \times 3}$

3-wire line model


Example

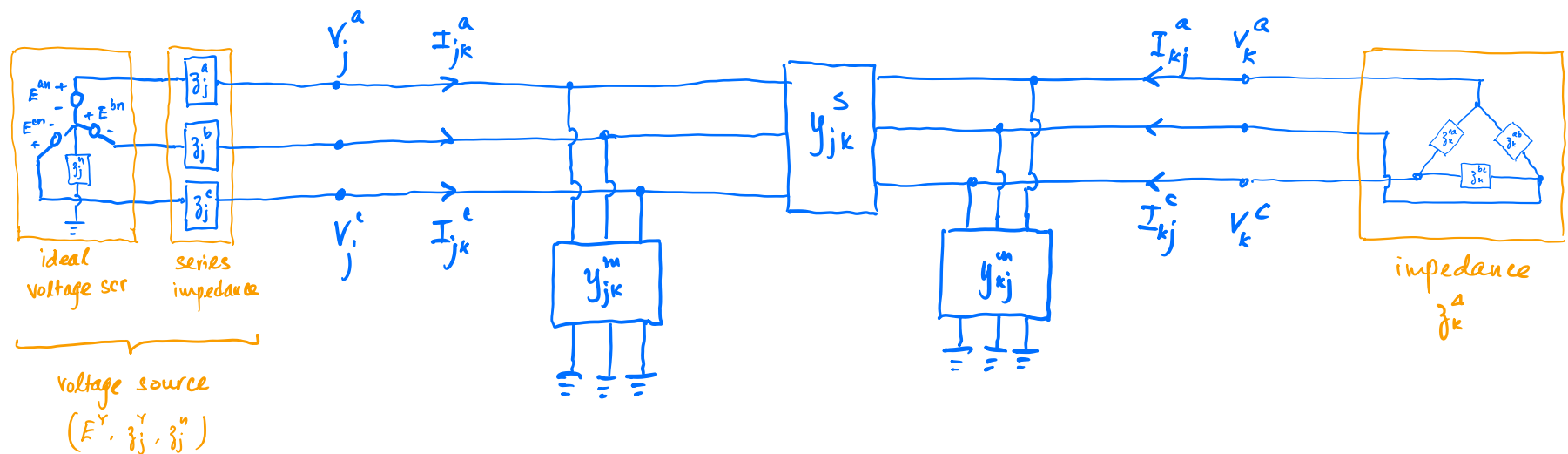

- Line model relates **terminal** voltages and currents at both ends of the line, regardless of device Y/Δ configuration

3-wire line model

Example

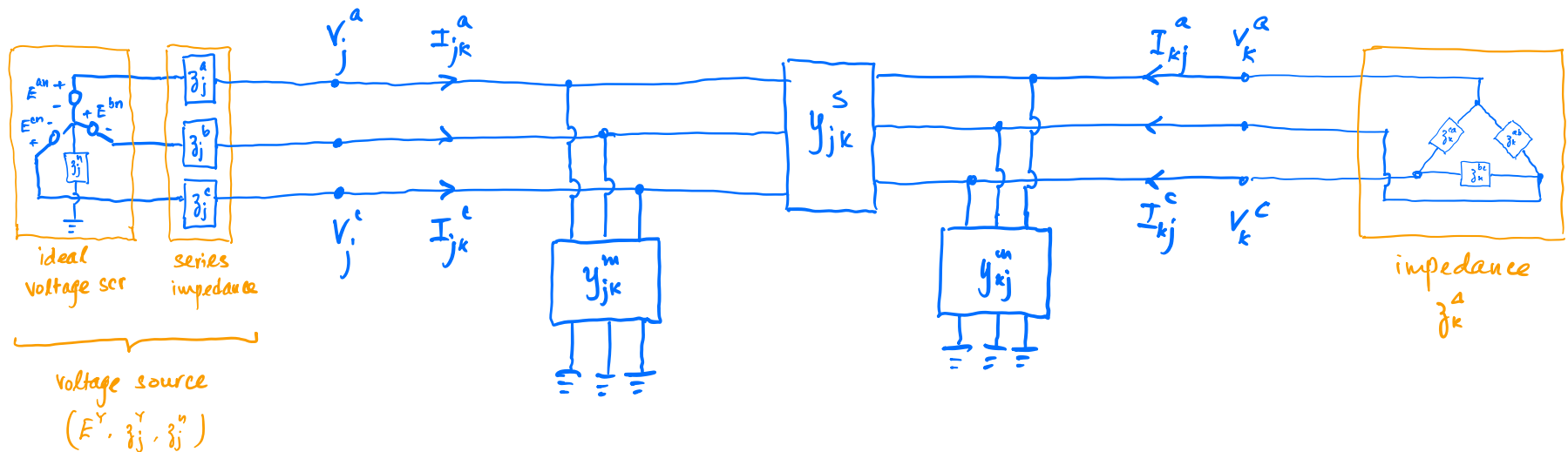


Terminal vars (V_j, I_j, s_j) at bus j satisfy external device model and line model (that relate (V_j, I_j, s_j) to V_k)

- Device j model: $0 = f_j^{\text{ext}}(V_j, I_j), \quad s_j = \text{diag}(V_j I_j^H)$
- Line (j, k) model: $I_j = I_{jk}(V_j, V_k), \quad s_j = \text{diag}(S_{jk}(V_j, V_k))$

3-wire line model

Properties

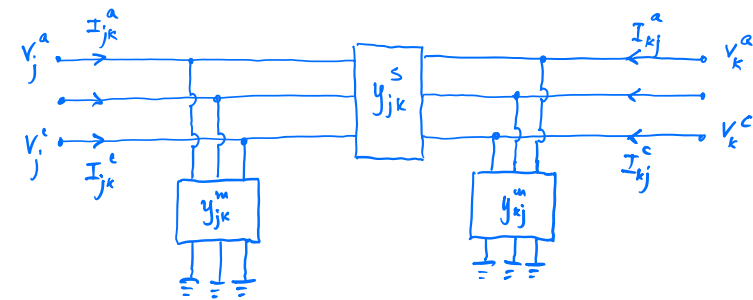1. Properties of admittance matrices $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$
 - They are typically complex symmetric (not Hermitian)
 - y_{jk}^s is typically invertible




Complex symmetry of y_{jk}^s leads to single-phase equivalent of 3-phase networks (see later)

3-wire line model

Properties

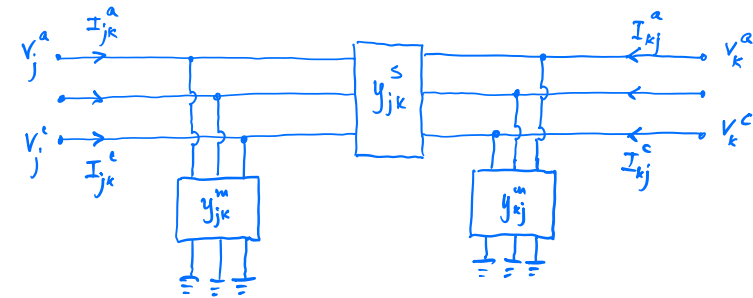1. Properties of admittance matrices $(y_{jk}^s, y_{jk}^m, y_{kj}^m)$
 - They are typically complex symmetric (not Hermitian)
 - y_{jk}^s is typically invertible
2. Symmetric line, e.g., through transpose and symmetric line geometry

$$z_{jk}^s = \begin{bmatrix} z_{jk}^1 & z_{jk}^2 & z_{jk}^2 \\ z_{jk}^2 & z_{jk}^1 & z_{jk}^2 \\ z_{jk}^2 & z_{jk}^2 & z_{jk}^1 \end{bmatrix}, \quad y_{jk}^s = \begin{bmatrix} y_{jk}^1 & y_{jk}^2 & y_{jk}^2 \\ y_{jk}^2 & y_{jk}^1 & y_{jk}^2 \\ y_{jk}^2 & y_{jk}^2 & y_{jk}^1 \end{bmatrix}$$



Outline

1. Overview
2. Mathematical properties
3. Three-phase device models
4. Three-phase line models
5. Three-phase transformer models
 - General derivation method
 - YY , $\Delta\Delta$, ΔY , $Y\Delta$ configurations
 - UVN-based model

Review: single-phase transformer

1. Internal and terminal vars


- Internal vars: (\hat{V}_j, \hat{I}_j) and (\hat{V}_k, \hat{I}_k)
- Terminal vars: (V_j, V_j^n, I_j) and (V_k, V_k^n, I_k)

2. Internal model on **internal** vars between primary & secondary sides

- (Ideal) transformer gains: $\hat{V}_k = n\hat{V}_j$, $\hat{I}_k = a\hat{I}_j$

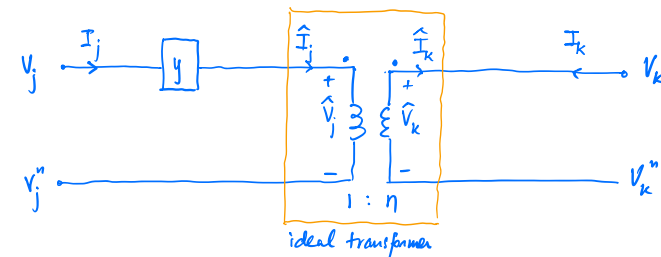3. Conversion between internal & terminal vars on **each** side

$$\begin{aligned} V_j &= y^{-1}\hat{I}_j + \hat{V}_j + V_j^n, & I_j &= \hat{I}_j \\ V_k &= \hat{V}_k + V_k^n, & I_k &= -\hat{I}_k \end{aligned}$$




Review: single-phase transformer

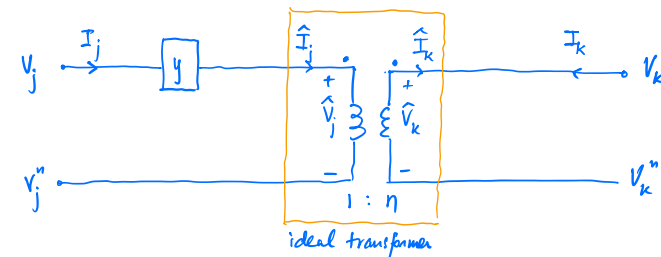4. External model on **external** vars across pri & sec sides

- Eliminate internal vars from internal model and conversion


$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix} \left(\begin{bmatrix} V_j \\ V_k \end{bmatrix} - \begin{bmatrix} V_j^n \\ V_k^n \end{bmatrix} \right)$$



5. If neutrals are grounded with zero grounding impedance so that $V_j^n = V_k^n = 0$ (often assumed)

$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$

- Reduces to a Π circuit

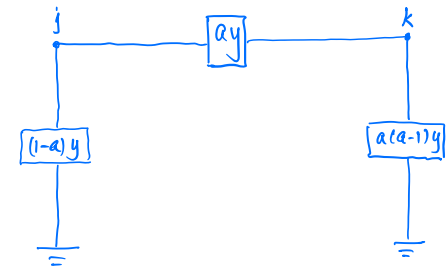

Three-phase transformers

1. Three-phase transformers consists of 3 single-phase transformers in Y/Δ configuration
2. External models can be derived following the [same](#) procedure

General method

Primary side



1. Internal vars (defined across individual windings)

$$\hat{V}_j^Y := \begin{bmatrix} \hat{V}_j^{an} \\ \hat{V}_j^{bn} \\ \hat{V}_j^{cn} \end{bmatrix}, \quad \hat{I}_j^Y := \begin{bmatrix} \hat{I}_j^{an} \\ \hat{I}_j^{bn} \\ \hat{I}_j^{cn} \end{bmatrix}, \quad \hat{V}_j^\Delta := \begin{bmatrix} \hat{V}_j^{ab} \\ \hat{V}_j^{bc} \\ \hat{V}_j^{ca} \end{bmatrix}, \quad \hat{I}_j^\Delta := \begin{bmatrix} \hat{I}_j^{ab} \\ \hat{I}_j^{bc} \\ \hat{I}_j^{ca} \end{bmatrix}$$

2. Terminal vars (voltages wrt common reference, e.g., ground)

$$V_j := \begin{bmatrix} V_j^a \\ V_j^b \\ V_j^c \end{bmatrix}, \quad I_j := \begin{bmatrix} I_j^a \\ I_j^b \\ I_j^c \end{bmatrix}, \quad \text{for } Y \text{ configuration: } (V_j^n, I_j^n)$$

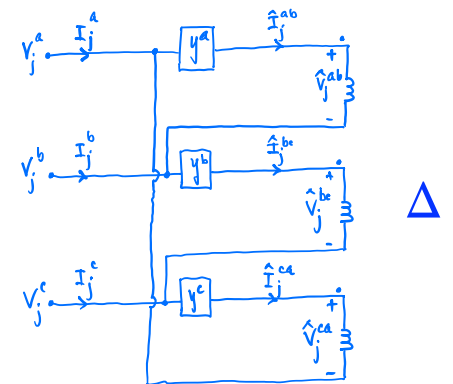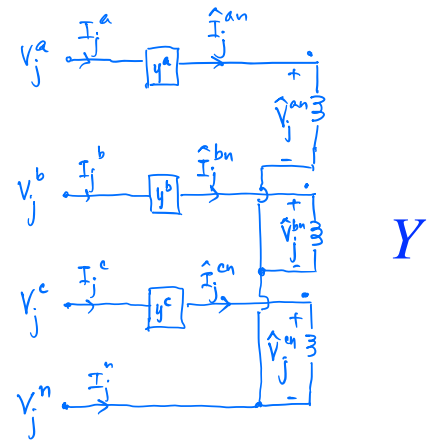3. Leakage admittance matrix $y := \text{diag}(y^a, y^b, y^c)$



General method

Primary side


4. Conversion between internal and terminal vars

- Y configuration


$$I_j = y \left(V_j - V_j^n - \hat{V}_j^Y \right), \quad I_j = \hat{I}_j^Y, \quad I_j^n = -1^T \hat{I}_j^Y$$

- Δ configuration
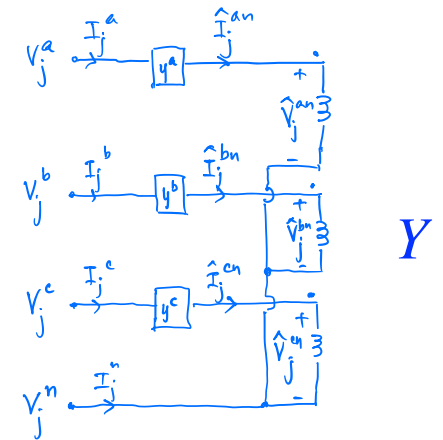
$$\hat{I}_j^\Delta = y \left(\Gamma V_j - \hat{V}_j^\Delta \right), \quad I_j = \Gamma^T \hat{I}_j^\Delta$$



Y

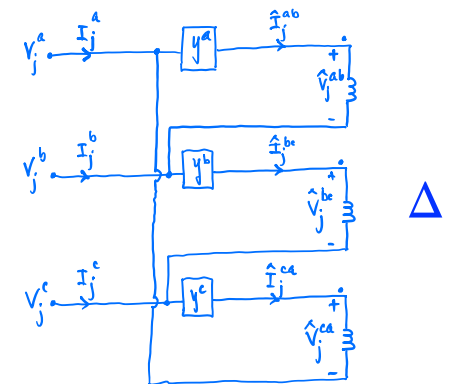

Δ

General method

Secondary side


1. Internal vars (defined across individual windings)

$$\hat{V}_k^Y := \begin{bmatrix} \hat{V}_k^{an} \\ \hat{V}_k^{bn} \\ \hat{V}_k^{cn} \end{bmatrix}, \quad \hat{I}_k^Y := - \begin{bmatrix} \hat{I}_k^{an} \\ \hat{I}_k^{bn} \\ \hat{I}_k^{cn} \end{bmatrix}, \quad \hat{V}_k^\Delta := \begin{bmatrix} \hat{V}_k^{ab} \\ \hat{V}_k^{bc} \\ \hat{V}_k^{ca} \end{bmatrix}, \quad \hat{I}_k^\Delta := - \begin{bmatrix} \hat{I}_k^{ab} \\ \hat{I}_k^{bc} \\ \hat{I}_k^{ca} \end{bmatrix}$$


2. Terminal vars (voltages defined wrt common reference, e.g., ground)

$$V_k := \begin{bmatrix} V_k^a \\ V_k^b \\ V_k^c \end{bmatrix}, \quad I_k := \begin{bmatrix} I_k^a \\ I_k^b \\ I_k^c \end{bmatrix}, \quad \text{for } Y \text{ configuration: } (V_k^n, I_k^n)$$

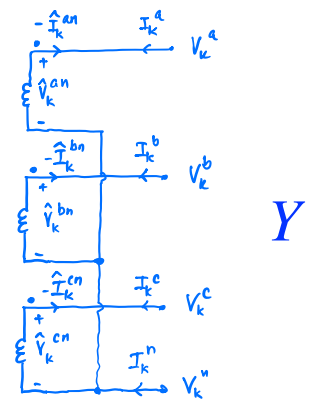3. Admittances in secondary side assumed to have been referred to primary



Y

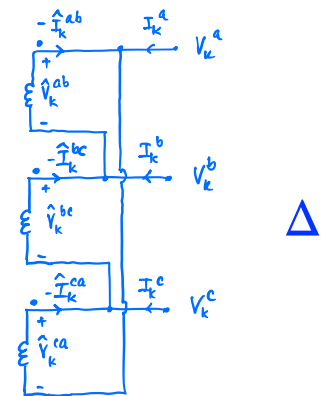

Δ

General method

Secondary side



4. Conversion between internal and terminal vars

- Y configuration

$$V_k = \hat{V}_k^Y + V_k^n \mathbf{1}, \quad I_k = -\hat{I}_k^Y, \quad I_k^n = \mathbf{1}^T \hat{I}_k^Y$$

- Δ configuration
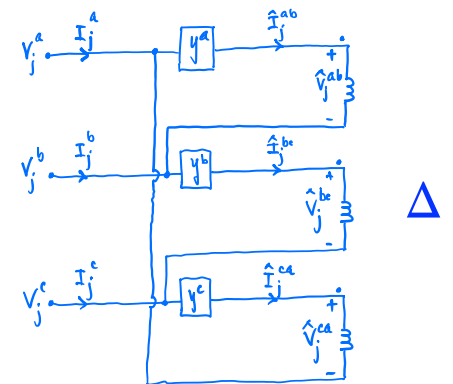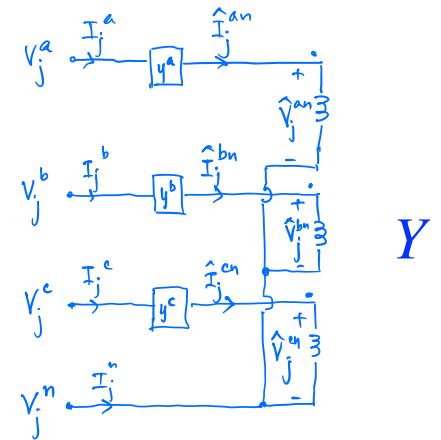
$$\hat{V}_k^\Delta = \Gamma V_k, \quad I_k = -\Gamma^T \hat{I}_k^\Delta$$



General method

Internal model

1. Voltage gain (real) $n := \text{diag}(n^a, n^b, n^c) \in \mathbb{R}^{3 \times 3}$, turns ratio $a := n^{-1} \in \mathbb{R}^{3 \times 3}$

- Voltage gains (or turns ratios) may be different across phases a, b, c

2. Transformer gains on **internal** vars across primary and secondary sides

$$YY \text{ configuration: } \hat{V}_k^Y = n \hat{V}_j^Y, \quad \hat{I}_k^Y = a \hat{I}_j^Y$$

$$\Delta\Delta \text{ configuration: } \hat{V}_k^\Delta = n \hat{V}_j^\Delta, \quad \hat{I}_k^\Delta = a \hat{I}_j^\Delta$$

$$\Delta Y \text{ configuration: } \hat{V}_k^Y = n \hat{V}_j^\Delta, \quad \hat{I}_k^Y = a \hat{I}_j^\Delta$$

$$Y\Delta \text{ configuration: } \hat{V}_k^\Delta = n \hat{V}_j^Y, \quad \hat{I}_k^\Delta = a \hat{I}_j^Y$$

Voltage and current gains follow the same gains as those for single-phase transformers, regardless of 3-phase configuration

General method

External model: summary

1. Couple internal vars $\left(\hat{V}_j^{Y/\Delta}, \hat{I}_j^{Y/\Delta}\right), \left(\hat{V}_k^{Y/\Delta}, \hat{I}_k^{Y/\Delta}\right)$ across pri and sec sides through transformer gains, the same way as in single-phase transformers
2. Relate terminal vars $\left(V_j, V_j^n, I_j\right), \left(V_k, V_k^n, I_k\right)$ to internal vars $\left(\hat{V}_j^{Y/\Delta}, \hat{I}_j^{Y/\Delta}\right), \left(\hat{V}_k^{Y/\Delta}, \hat{I}_k^{Y/\Delta}\right)$ on **each** of primary and secondary sides
3. Eliminate internal vars from equations in Steps 1 and 2 (in previous slides) to obtain an external model relating only terminal vars $\left(V_j, V_j^n, I_j\right), \left(V_k, V_k^n, I_k\right)$

The method is modular with respect to $YY, \Delta\Delta, \Delta Y, Y\Delta$ configurations, as we will see

3-phase transformers

Overview

- Let $V := (V_j, V_k) \in \mathbb{C}^6$ and $I := (I_j, I_k) \in \mathbb{C}^6$
- Define 6×6 admittance matrix Y_{YY} and column vector

$$Y_{YY} := \begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}, \quad \gamma := (V_j^{n1}, V_k^{n1})$$

$$\text{where } a := \text{diag}(a^a, a^b, a^c), \quad y := \text{diag}(y^a, y^b, y^c)$$

External models: $I = D^\top Y_{YY} D (V - \gamma)$ where

$$YY: D := \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \mathbb{1} \end{bmatrix}, \quad \Delta\Delta: D := \begin{bmatrix} \Gamma & 0 \\ 0 & \Gamma \end{bmatrix}, \quad \Delta Y: D := \begin{bmatrix} \Gamma & 0 \\ 0 & \mathbb{1} \end{bmatrix}, \quad Y\Delta: D := \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \Gamma \end{bmatrix}$$

3-phase transformers

Overview

External models: $I = D^T Y_{YY} D (V - \gamma)$ where

$$YY: D := \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \mathbb{1} \end{bmatrix}, \quad \Delta\Delta: D := \begin{bmatrix} \Gamma & 0 \\ 0 & \Gamma \end{bmatrix}, \quad \Delta Y: D := \begin{bmatrix} \Gamma & 0 \\ 0 & \mathbb{1} \end{bmatrix}, \quad Y\Delta: D := \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \Gamma \end{bmatrix}$$

- $YY, \Delta\Delta$: $D^T Y_{YY} D$ is block symmetric and has 3-phase Π circuit representation
- $\Delta Y, Y\Delta$: Not

Next: derive external models for each configuration in detail

YY configuration

Internal and terminal vars


1. Internal vars (defined across individual windings)

$$\hat{V}_j^Y := \begin{bmatrix} \hat{V}_j^{an} \\ \hat{V}_j^{bn} \\ \hat{V}_j^{cn} \end{bmatrix}, \quad \hat{I}_j^Y := \begin{bmatrix} \hat{I}_j^{an} \\ \hat{I}_j^{bn} \\ \hat{I}_j^{cn} \end{bmatrix}, \quad \hat{V}_k^Y := \begin{bmatrix} \hat{V}_k^{an} \\ \hat{V}_k^{bn} \\ \hat{V}_k^{cn} \end{bmatrix}, \quad \hat{I}_k^Y := - \begin{bmatrix} \hat{I}_k^{an} \\ \hat{I}_k^{bn} \\ \hat{I}_k^{cn} \end{bmatrix},$$

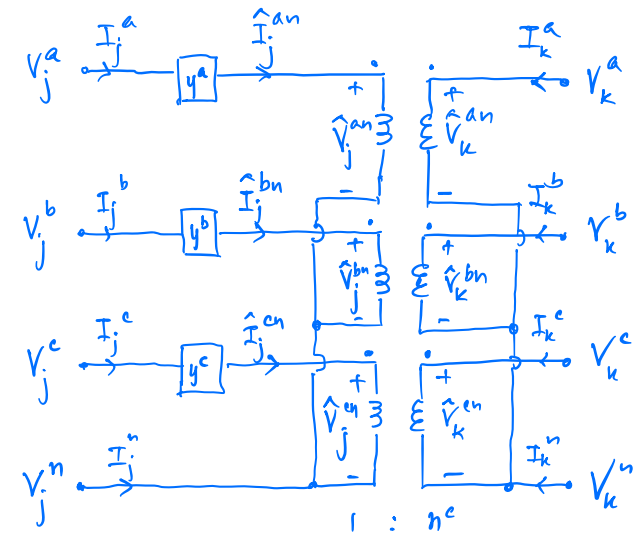2. Terminal vars (voltages wrt common reference, e.g., ground)

$$V_j := \begin{bmatrix} V_j^a \\ V_j^b \\ V_j^c \end{bmatrix}, \quad I_j := \begin{bmatrix} I_j^a \\ I_j^b \\ I_j^c \end{bmatrix}, \quad V_k := \begin{bmatrix} V_k^a \\ V_k^b \\ V_k^c \end{bmatrix}, \quad I_k := \begin{bmatrix} I_k^a \\ I_k^b \\ I_k^c \end{bmatrix}$$

$$\left(V_j^n, I_j^n \right), \quad \left(V_k^n, I_k^n \right)$$



YY configuration

External model

1. External model


$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \underbrace{\begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}}_{Y_{YY}} \left(\begin{bmatrix} V_j \\ V_k \end{bmatrix} - \begin{bmatrix} V_j^{n1} \\ V_k^{n1} \end{bmatrix} \right)$$

$$I_j^n = -1^\top I_j, \quad I_k^n = -1^\top I_k$$

2. If both neutrals are grounded with zero impedance and voltages are defined wrt ground

$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$

which can be represented as a Π circuit

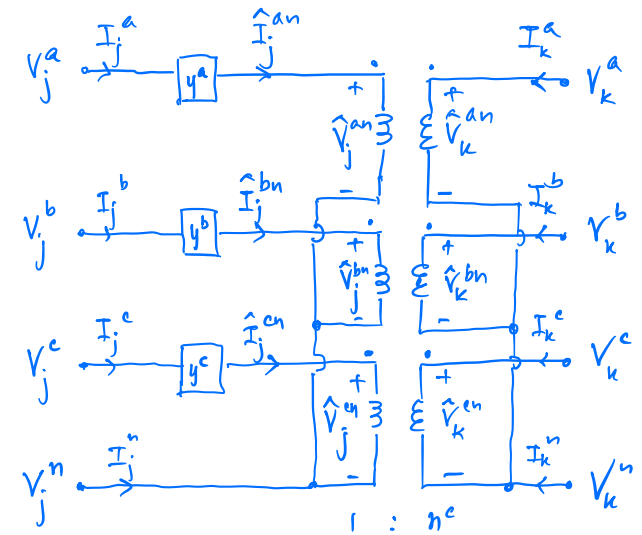


Comparison

With single-phase transformer

External models: **exactly the same** expression

$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \underbrace{\begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}}_{Y_{YY}} \left(\begin{bmatrix} V_j \\ V_k \end{bmatrix} - \begin{bmatrix} V_j^{n1} \\ V_k^{n1} \end{bmatrix} \right)$$

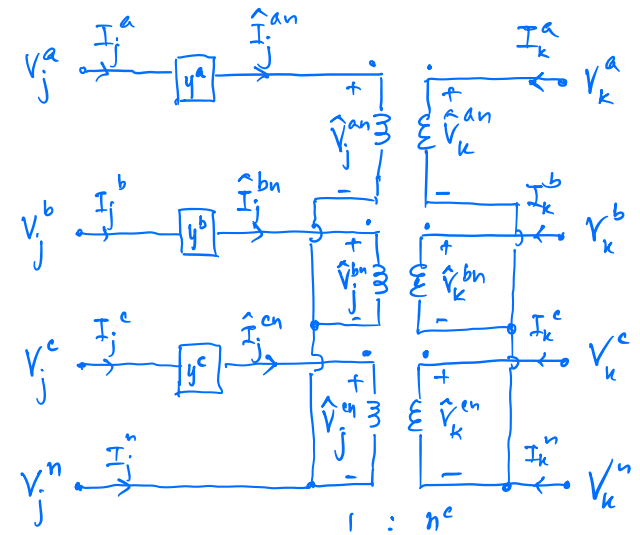- Single-phase: $Y_{YY} \in \mathbb{C}^{2 \times 2}$
- Three-phase: $Y_{YY} \in \mathbb{C}^{6 \times 6}$



$\Delta\Delta$ configuration


Internal and terminal vars

1. Internal vars (defined across individual windings)

$$\hat{V}_j^\Delta := \begin{bmatrix} \hat{V}_j^{ab} \\ \hat{V}_j^{bc} \\ \hat{V}_j^{ca} \end{bmatrix}, \quad \hat{I}_j^\Delta := \begin{bmatrix} \hat{I}_j^{ab} \\ \hat{I}_j^{bc} \\ \hat{I}_j^{ca} \end{bmatrix}, \quad \hat{V}_k^\Delta := \begin{bmatrix} \hat{V}_k^{ab} \\ \hat{V}_k^{bc} \\ \hat{V}_k^{ca} \end{bmatrix}, \quad \hat{I}_k^\Delta := - \begin{bmatrix} \hat{I}_k^{ab} \\ \hat{I}_k^{bc} \\ \hat{I}_k^{ca} \end{bmatrix}$$

2. Terminal vars (V_j, I_j) , (V_k, I_k) same as for YY config

- without neutral vars

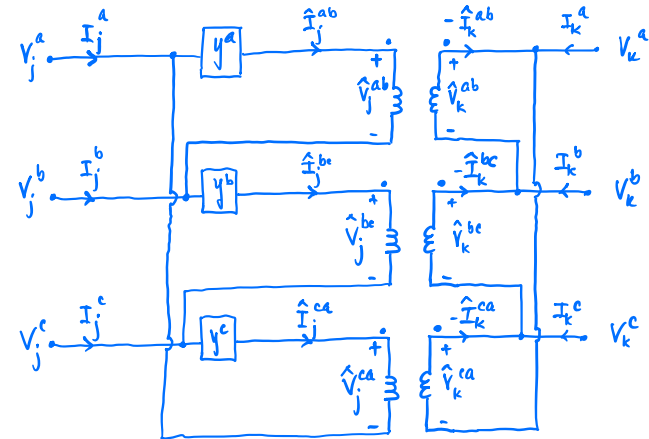


ΔΔ configuration

External model

External model

$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \begin{bmatrix} \Gamma^T & 0 \\ 0 & \Gamma^T \end{bmatrix} \underbrace{\begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}}_{Y_{YY}} \begin{bmatrix} \Gamma & 0 \\ 0 & \Gamma \end{bmatrix} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$

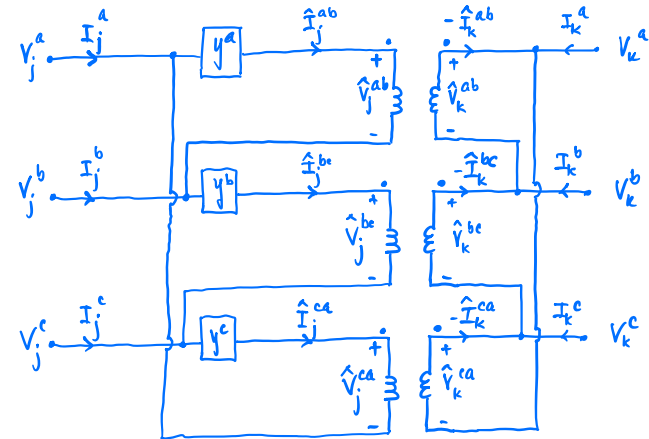- Can be represented as Π circuit
- Conversion matrices due to Δ configurations



Comparison

With single-phase transformer

Single-phase: $Y_{YY} \in \mathbb{C}^{2 \times 2}$


$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \underbrace{\begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}}_{Y_{YY}} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$

- No neutral lines

Three-phase: $Y_{YY} \in \mathbb{C}^{6 \times 6}$

$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \begin{bmatrix} \Gamma^T & 0 \\ 0 & \Gamma^T \end{bmatrix} \underbrace{\begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}}_{Y_{YY}} \begin{bmatrix} \Gamma & 0 \\ 0 & \Gamma \end{bmatrix} \begin{bmatrix} V_j \\ V_k \end{bmatrix}$$

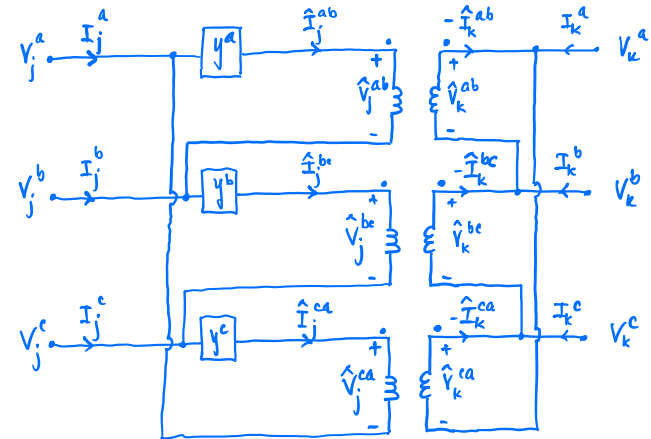- Conversion matrices due to Δ configurations




ΔY configuration

Internal and terminal vars

1. Internal vars (defined across individual windings)

$$\hat{V}_j^\Delta := \begin{bmatrix} \hat{V}_j^{ab} \\ \hat{V}_j^{bc} \\ \hat{V}_j^{ca} \end{bmatrix}, \quad \hat{I}_j^\Delta := \begin{bmatrix} \hat{I}_j^{ab} \\ \hat{I}_j^{bc} \\ \hat{I}_j^{ca} \end{bmatrix}, \quad \hat{V}_k^Y := \begin{bmatrix} \hat{V}_k^{an} \\ \hat{V}_k^{bn} \\ \hat{V}_k^{cn} \end{bmatrix}, \quad \hat{I}_k^Y := - \begin{bmatrix} \hat{I}_k^{an} \\ \hat{I}_k^{bn} \\ \hat{I}_k^{cn} \end{bmatrix},$$

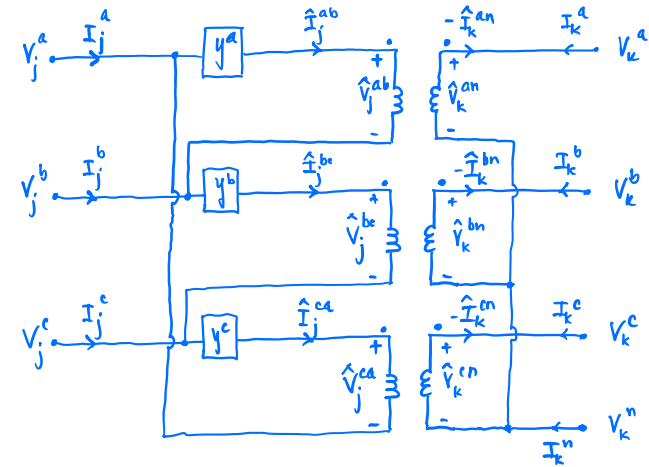2. Terminal vars (V_j, I_j) , (V_k, I_k) same as before



ΔY configuration


External model

1. External model

$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \begin{bmatrix} \Gamma^T & 0 \\ 0 & \mathbb{1} \end{bmatrix} \underbrace{\begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}}_{Y_{YY}} \begin{bmatrix} \Gamma & 0 \\ 0 & \mathbb{1} \end{bmatrix} \begin{bmatrix} V_j \\ V_k \end{bmatrix} - \begin{bmatrix} -\Gamma^T ay \\ a^2y \end{bmatrix} V_k^n$$

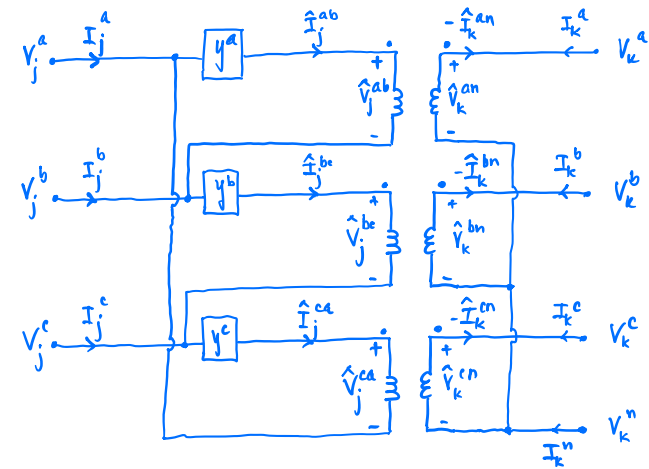2. Comparison with YY and $\Delta\Delta$ configurations (modular)

- I_j depends on (V_j, V_k) similarly to $\Delta\Delta$ config
- I_k depends on (V_j, V_k) similarly to YY config
- Even though there is no neutral line on primary side, I_j depends on V_k^n on secondary side
- If $a = a^a\mathbb{1}$, $y = y^a\mathbb{1}$, i.e., identical single-phase transformers, then I_j becomes independent of V_k^n (because $\Gamma^T \mathbf{1} = 0$)



YΔ configuration


External model

1. External model

$$\begin{bmatrix} I_j \\ I_k \end{bmatrix} = \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \Gamma^T \end{bmatrix} \underbrace{\begin{bmatrix} y & -ay \\ -ay & a^2y \end{bmatrix}}_{Y_{YY}} \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \Gamma \end{bmatrix} \begin{bmatrix} V_j \\ V_k \end{bmatrix} - \begin{bmatrix} y \\ -\Gamma^T ay \end{bmatrix} V_j^{n1}$$

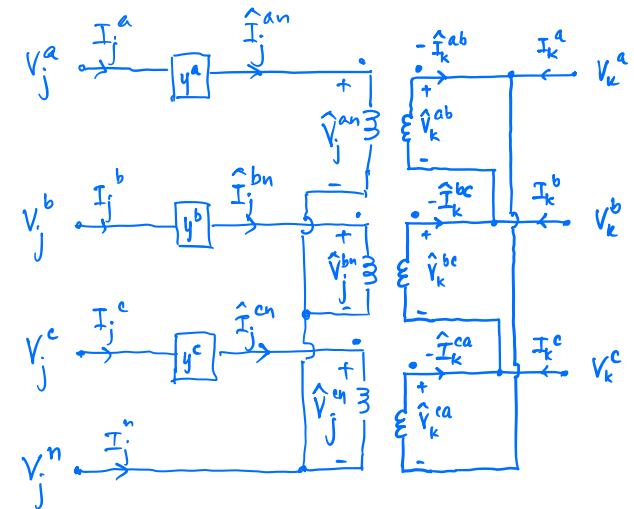2. Same modular structure as for ΔY configuration


- I_j depends on (V_j, V_k) similarly to YY config
- I_k depends on (V_j, V_k) similarly to ΔΔ config
- Even though there is no neutral line on secondary side, I_k depends on V_j^n on primary side
- If $a = a^a \mathbb{1}$, $y = y^a \mathbb{1}$, i.e., identical single-phase transformers, then I_k becomes independent of V_j^n (because $\Gamma^T \mathbf{1} = 0$)




Other transformers

Same method can be applied to derive external models for other transformers

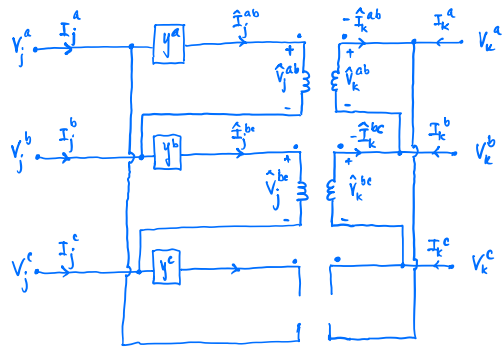- Open transformer
- Split-phase transformer
- See textbook



Open $\Delta\Delta$ transformer

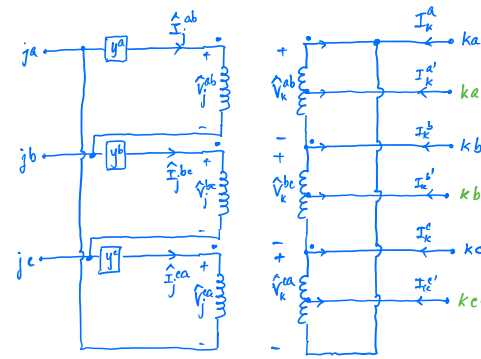


Split-phase transformer

Outline

1. Overview
2. Mathematical properties
3. Three-phase device models
4. Three-phase line models
5. Three-phase transformer models
 - General derivation method
 - $YY, \Delta\Delta, \Delta Y, Y\Delta$ configurations
 - UVN-based model

Three-phase transformers

Example: *YY* configuration

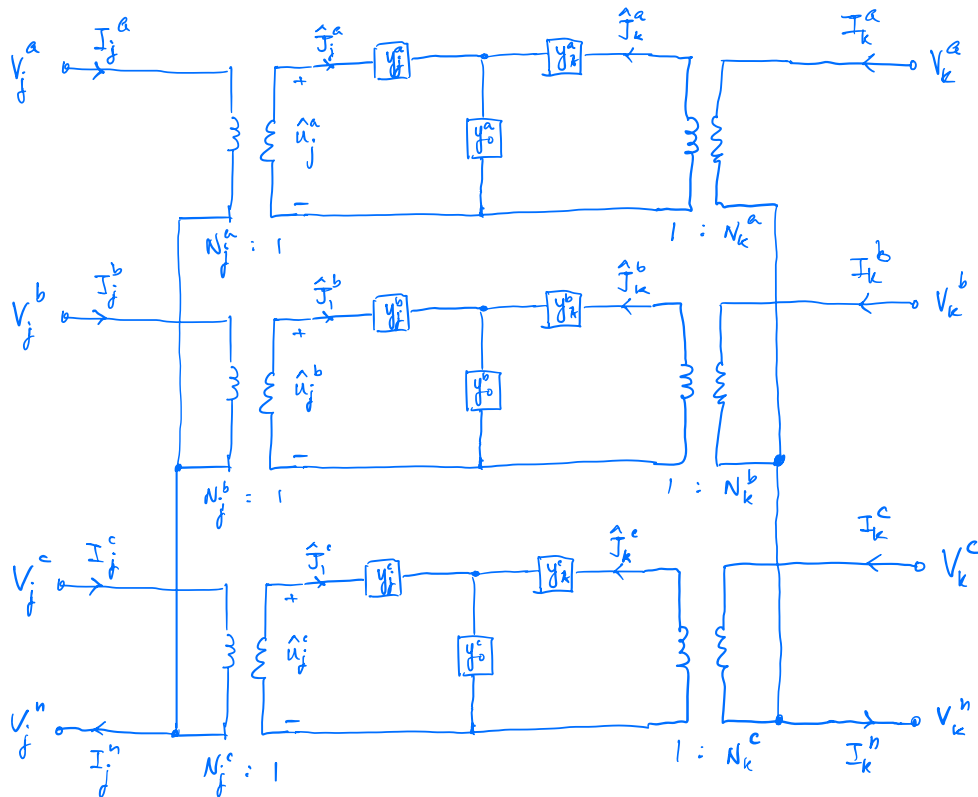

External vars:

$$I := \begin{bmatrix} I_j \\ I_k \end{bmatrix} \in \mathbb{C}^6, \quad V := \begin{bmatrix} V_j \\ V_k \end{bmatrix} \in \mathbb{C}^6$$

Transformer parameters:


$$M := \begin{bmatrix} \text{diag}(1/N_j^{abc}) & 0 \\ 0 & \text{diag}(1/N_k^{abc}) \end{bmatrix} \in \mathbb{C}^{6 \times 6}$$

$$y_i := \text{diag}(y_i^a, y_i^b, y_i^c) \in \mathbb{C}^{3 \times 3}, \quad i = 0, j, k$$

Unitary voltage network **per phase**

Three-phase transformers

Example: $\Delta\Delta$ configuration

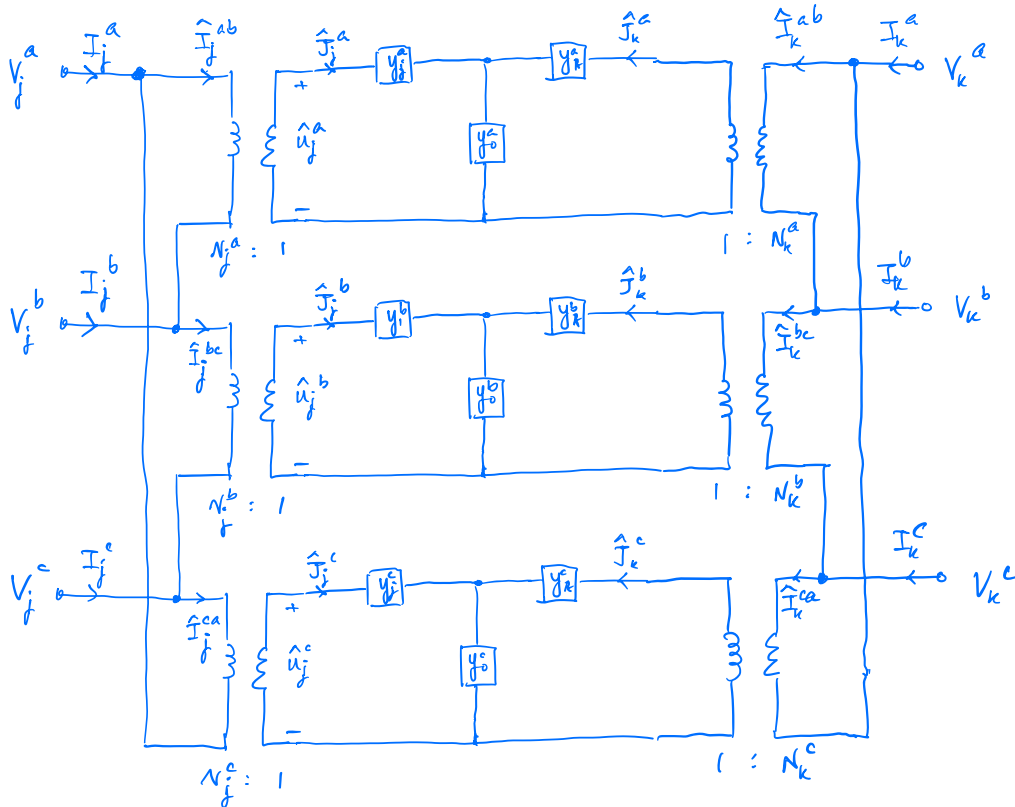

External vars:

$$I := \begin{bmatrix} I_j \\ I_k \end{bmatrix} \in \mathbb{C}^6, \quad V := \begin{bmatrix} V_j \\ V_k \end{bmatrix} \in \mathbb{C}^6$$

Transformer parameters:


$$M := \begin{bmatrix} \text{diag}(1/N_j^{abc}) & 0 \\ 0 & \text{diag}(1/N_k^{abc}) \end{bmatrix} \in \mathbb{C}^{6 \times 6}$$

$$y_i := \text{diag}(y_i^a, y_i^b, y_i^c) \in \mathbb{C}^{3 \times 3}, \quad i = 0, j, k$$

Unitary voltage network **per phase**

Three-phase transformers

Unitary voltage network per phase

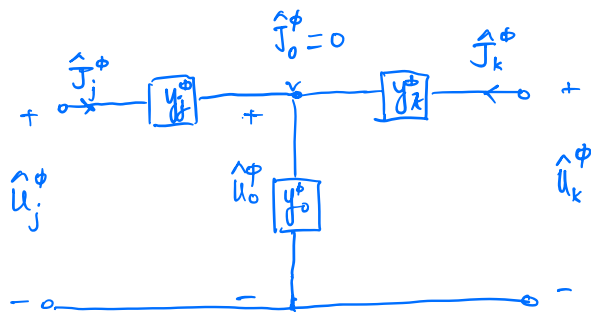

$$\hat{J}_j = y_k(\hat{U}_j - \hat{U}_0), \quad \hat{J}_k = y_k(\hat{U}_k - \hat{U}_0)$$

$$y_0\hat{U}_0 = \hat{J}_0 + \hat{J}_j + \hat{J}_k$$

Admittance matrix in $\mathbb{C}^{9 \times 9}$

$$\begin{bmatrix} \hat{J}_0 \\ \hat{J}_j \\ \hat{J}_k \end{bmatrix} = \begin{bmatrix} \sum_i y_i & -y_j & -y_k \\ -y_j & y_j & 0 \\ -y_k & 0 & y_k \end{bmatrix} \begin{bmatrix} \hat{U}_0 \\ \hat{U}_j \\ \hat{U}_k \end{bmatrix}$$

Since $\hat{J}_0 = 0$, can eliminate \hat{U}_0 to obtain Kron reduced admittance matrix


$$\hat{J} = Y_{\text{uvn}} \hat{U}$$

where

$$Y_{\text{uvn}} := \left(\mathbb{I}_2 \otimes \left(\sum_i y_i \right)^{-1} \right) \begin{bmatrix} y_j(y_0 + y_k) & -y_j y_k \\ -y_j y_k & y_k(y_0 + y_j) \end{bmatrix}$$

Three-phase transformers

External model: primary circuit

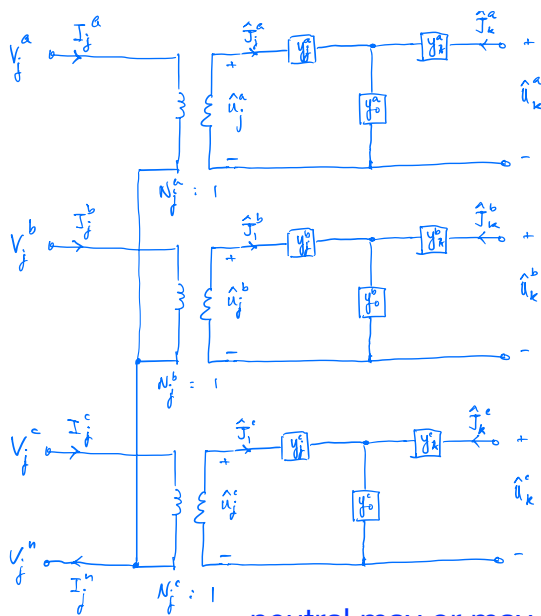

neutral may or may not be grounded!

Y config:

$$\hat{U}_j = M_j (V_j - V_j^n), \quad \hat{J}_j = M_j^{-1} I_j$$

Δ config:

$$\hat{U}_j = M_j \Gamma V_j, \quad \hat{J}_j = M_j^{-1} I_j^\Delta, \quad I_j = \Gamma^T I_j^\Delta$$

Three-phase transformers

External model: conversion rule

Primary circuit

$$Y \text{ configuration: } \hat{U}_j = M_j (V_j - V_j^{n_1}), \quad \hat{J}_j = M_j^{-1} I_j$$

$$\Delta \text{ configuration: } \hat{U}_j = M_j \Gamma V_j, \quad \hat{J}_j = M_j^{-1} I_j^\Delta, \quad I_j = \Gamma^\top I_j^\Delta$$

Secondary circuit

$$Y \text{ configuration: } \hat{U}_k = M_k (V_k - V_k^{n_1}), \quad \hat{J}_k = M_k^{-1} I_k$$

$$\Delta \text{ configuration: } \hat{U}_k = M_k \Gamma V_k, \quad \hat{J}_k = M_k^{-1} I_k^\Delta, \quad I_k = \Gamma^\top I_k^\Delta$$

Three-phase transformers

External model: admittance matrix

Eliminate internal vars (\hat{U}, \hat{J}):

$$I = D^T (MY_{uvn}M)D (V - \gamma)$$

where

$\gamma := (V_j^{n1}, V_k^{n1})$: neutral voltages in YY configuration

$D \in \mathbb{C}^{6 \times 6}$: configuration dependent

$$YY \text{ config: } D := \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \mathbb{1} \end{bmatrix}$$

$$\Delta\Delta \text{ config: } D := \begin{bmatrix} \Gamma & 0 \\ 0 & \Gamma \end{bmatrix}$$

$$\Delta Y \text{ config: } D := \begin{bmatrix} \Gamma & 0 \\ 0 & \mathbb{1} \end{bmatrix}$$

$$Y\Delta \text{ config: } D := \begin{bmatrix} \mathbb{1} & 0 \\ 0 & \Gamma \end{bmatrix}$$

For both single-phase & three-phase transformers:

- This model is equivalent to T equivalent circuit
- Different from simplified circuit (approximation)
- If shunt adm = 0, then all 3 models are equivalent