

# Power System Analysis

## Chapter 2 Transmission line models

# Outline

1. Line characteristics
2. Line models

# Outline

## 1. Line characteristics

- Resistance  $r$  and conductance  $g$
- Series inductance  $l$
- Shunt capacitance  $c$
- Balanced  $3\phi$  lines

## 2. Line models

# Three-phase line

Alternating currents in conductors line interact electromagnetically

Interactions couple voltages & currents across phases

In **balanced** operation, phases behave **as if** they are decoupled

In **each phase**, line is characterized by

- series impedance / meter  $z := r + i\omega l \quad \Omega/\text{m} \quad r > 0, l > 0$
- shunt admittance / meter to neutral  $y := g + i\omega c \quad \Omega^{-1}/\text{m} \quad g \geq 0, c > 0$

## Assumptions

$$i_1(t) + \cdots + i_n(t) = 0 \quad \text{for all } t$$

$$q_1(t) + \cdots + q_n(t) = 0 \quad \text{for all } t$$

# Line characteristics

## Series resistance $r$ and shunt conductance $g$

Series resistance  $r$  depends on

- Temperature and cross-sectional area of the conductor (this is called the dc resistance)
- AC frequency (this is called the ac resistance and defined to be  $P_{\text{loss}}/|I|^2$ )

Shunt conductance  $g$  accounts for real power loss between conductors or conductors and ground


- Due to leakage currents at insulators, depending on environment such as moisture level
- Due to corona when a strong electric field at conductor surface ionizes the air, causing it to conduct, depending on meteorological conditions such as rain
- Power loss due to shunt conductance  $g$  is typically much smaller than  $r|I|^2$ ; hence  $g$  is often assumed zero in transmission line models

# Line characteristics
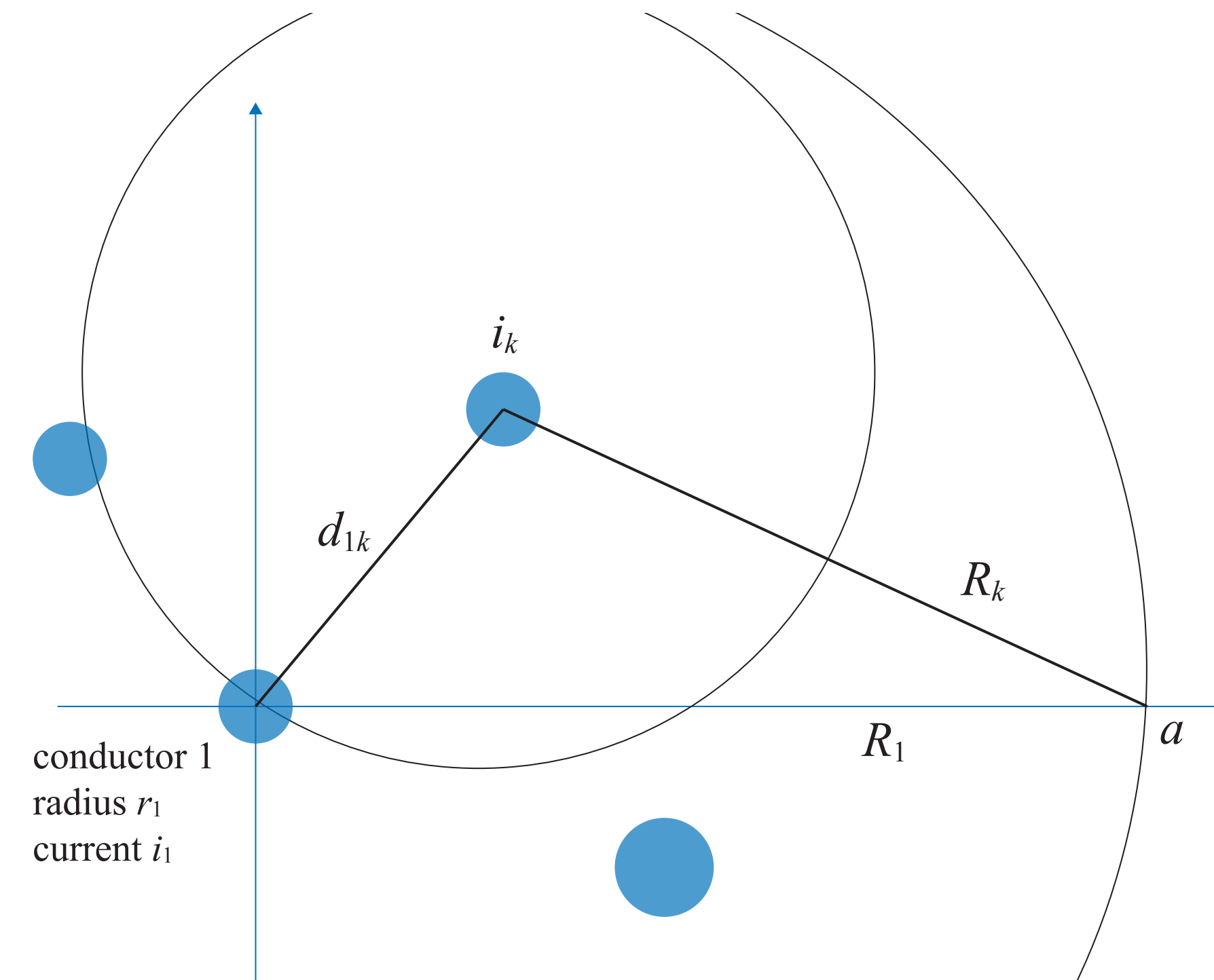
## Series inductance $L$

Total flux linkages  $\lambda_k$  of conductor  $k$  depends on currents  $i_k$  in all conductors  $k'$

$$\lambda_k = \underbrace{\left( \frac{\mu_0}{2\pi} \ln \frac{1}{r'_k} \right) i_k}_{\text{self inductance } L_{kk} \text{ henrys/m}} + \sum_{k' \neq k} \underbrace{\left( \frac{\mu_0}{2\pi} \ln \frac{1}{d_{kk'}} \right) i_{k'}}_{\text{mutual inductances } L_{kk'} \text{ henrys/m}}$$



# Line characteristics

## Series inductance $l$


Total flux linkages  $\lambda_k$  of conductor  $k$  depends on currents  $i_{k'}$  in all conductors  $k'$

$$\lambda_k = \left( \frac{\mu_0}{2\pi} \ln \frac{1}{r'_k} \right) i_k + \sum_{k' \neq k} \left( \frac{\mu_0}{2\pi} \ln \frac{1}{d_{kk'}} \right) i_{k'}$$

In vector form:  $\lambda = Li$

Faraday's law:  $v(t) = \frac{d}{dt} \lambda(t) = L \frac{d}{dt} i(t)$

voltage drop along conductor

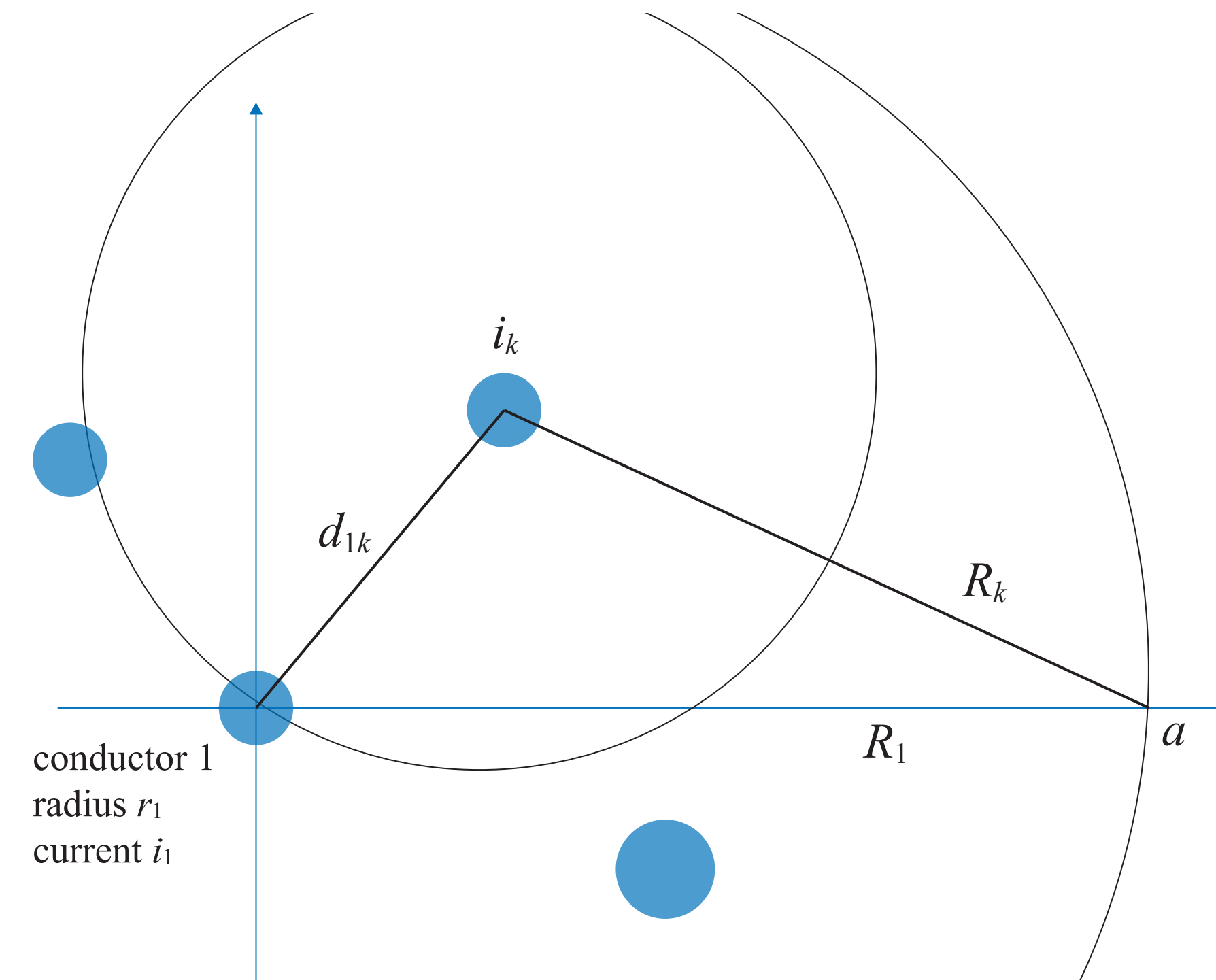


# Line characteristics
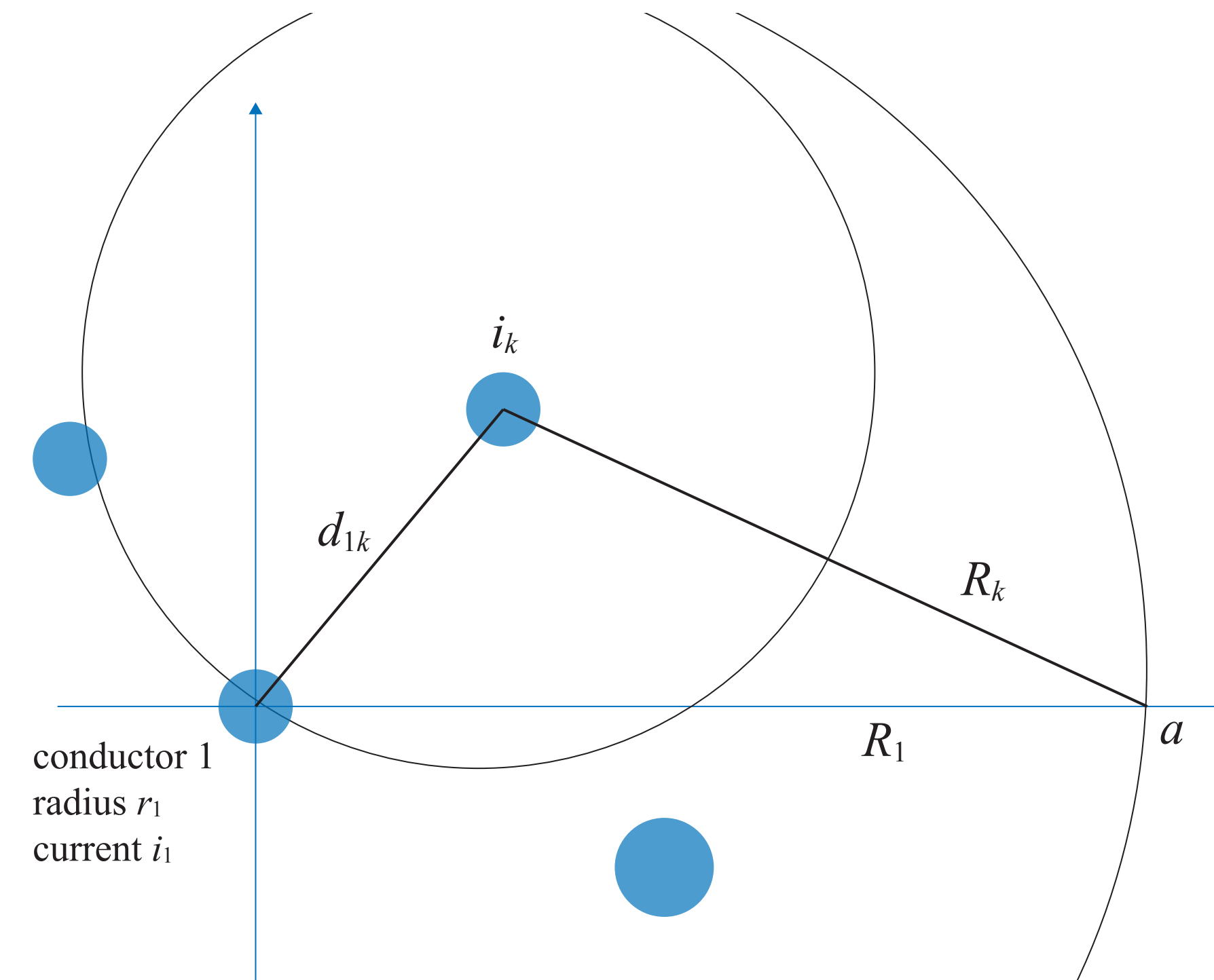
## Shunt capacitance $c$

Voltage on surface of conductor  $k$  relative to reference:

$$v_k = \left( \frac{1}{2\pi\epsilon} \ln \frac{1}{r_k} \right) q_k + \sum_{k' \neq k} \left( \frac{1}{2\pi\epsilon} \ln \frac{1}{d_{kk'}} \right) q_{k'}$$





# Line characteristics

## Shunt capacitance $c$


Voltage on surface of conductor  $k$  relative to reference:

$$v_k = \left( \frac{1}{2\pi\epsilon} \ln \frac{1}{r_k} \right) q_k + \sum_{k' \neq k} \left( \frac{1}{2\pi\epsilon} \ln \frac{1}{d_{kk'}} \right) q_{k'}$$

In vector form:  $v = F q$

Let  $C := F^{-1}$ .  $C_{kk}$  : self capacitance/m,  $C_{kk'}$  : mutual capacitance/m

Therefore:  $i(t) = C \frac{d}{dt} v(t)$

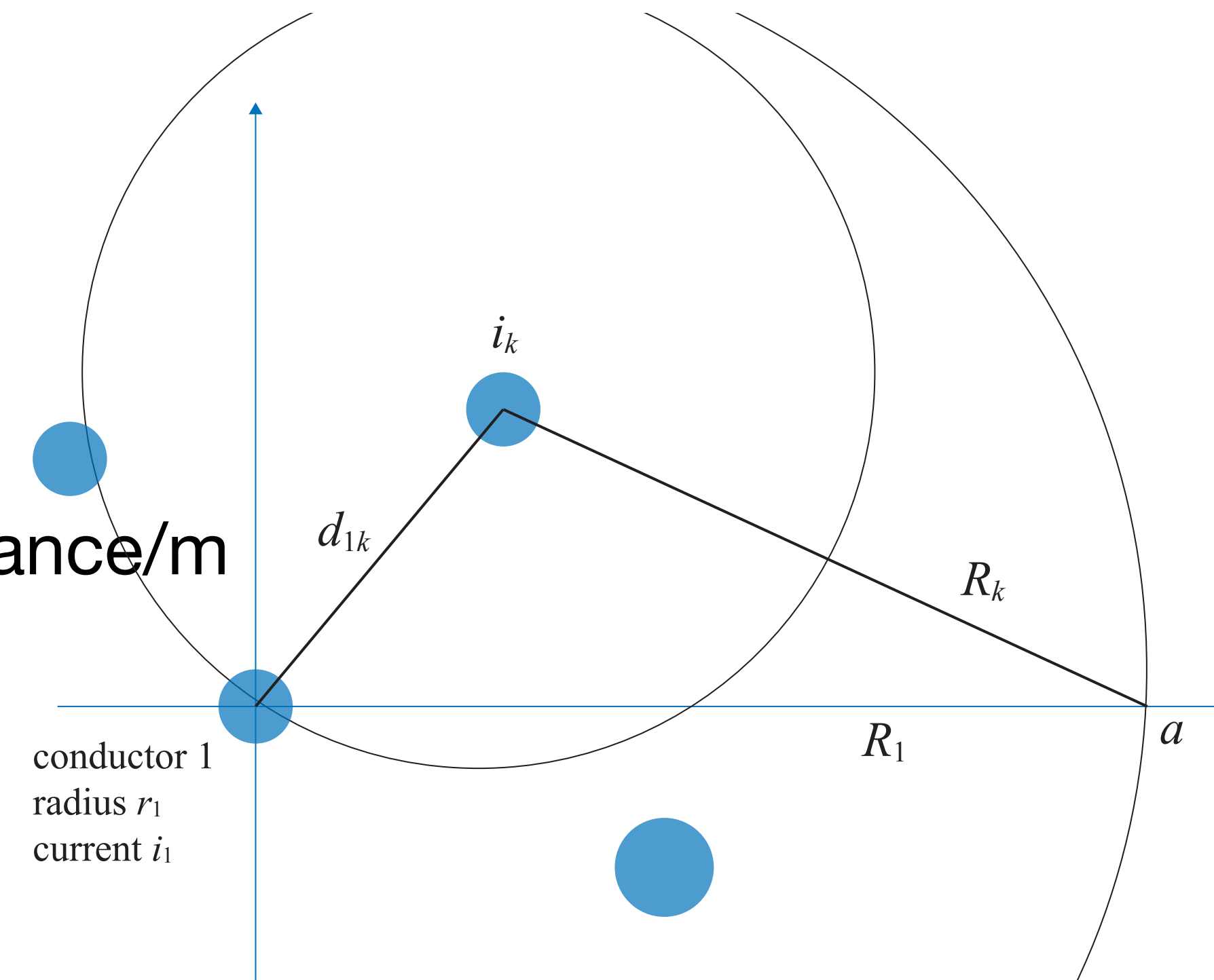


# Line characteristics

## Balanced three-phase line

### Assumptions:

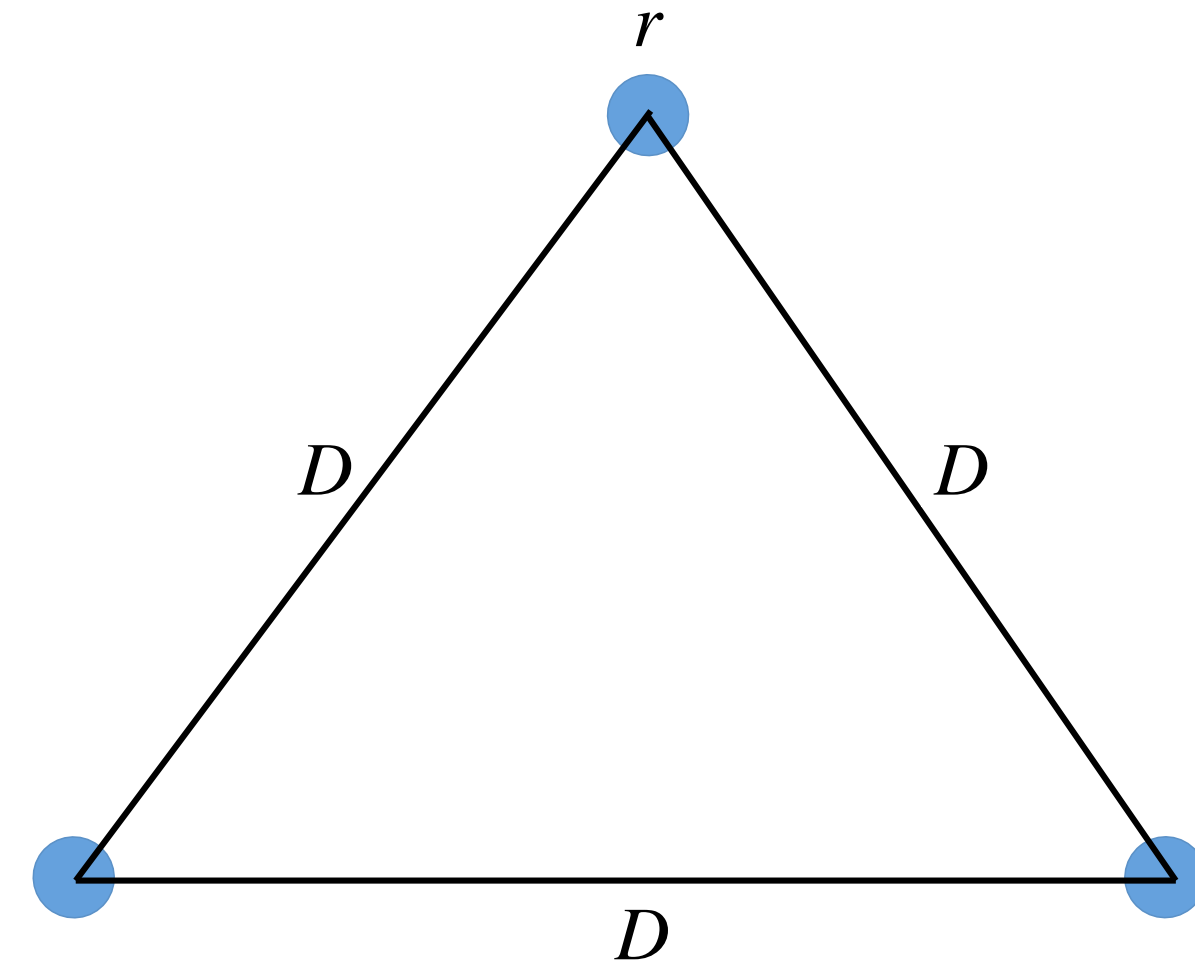1. Conductors equally spaced at  $D$  with equal radii  $r$
2.  $i_1(t) + \dots + i_n(t) = 0$  for all  $t$
3.  $q_1(t) + \dots + q_n(t) = 0$  for all  $t$




# Line characteristics

## Balanced three-phase line

### Assumptions:

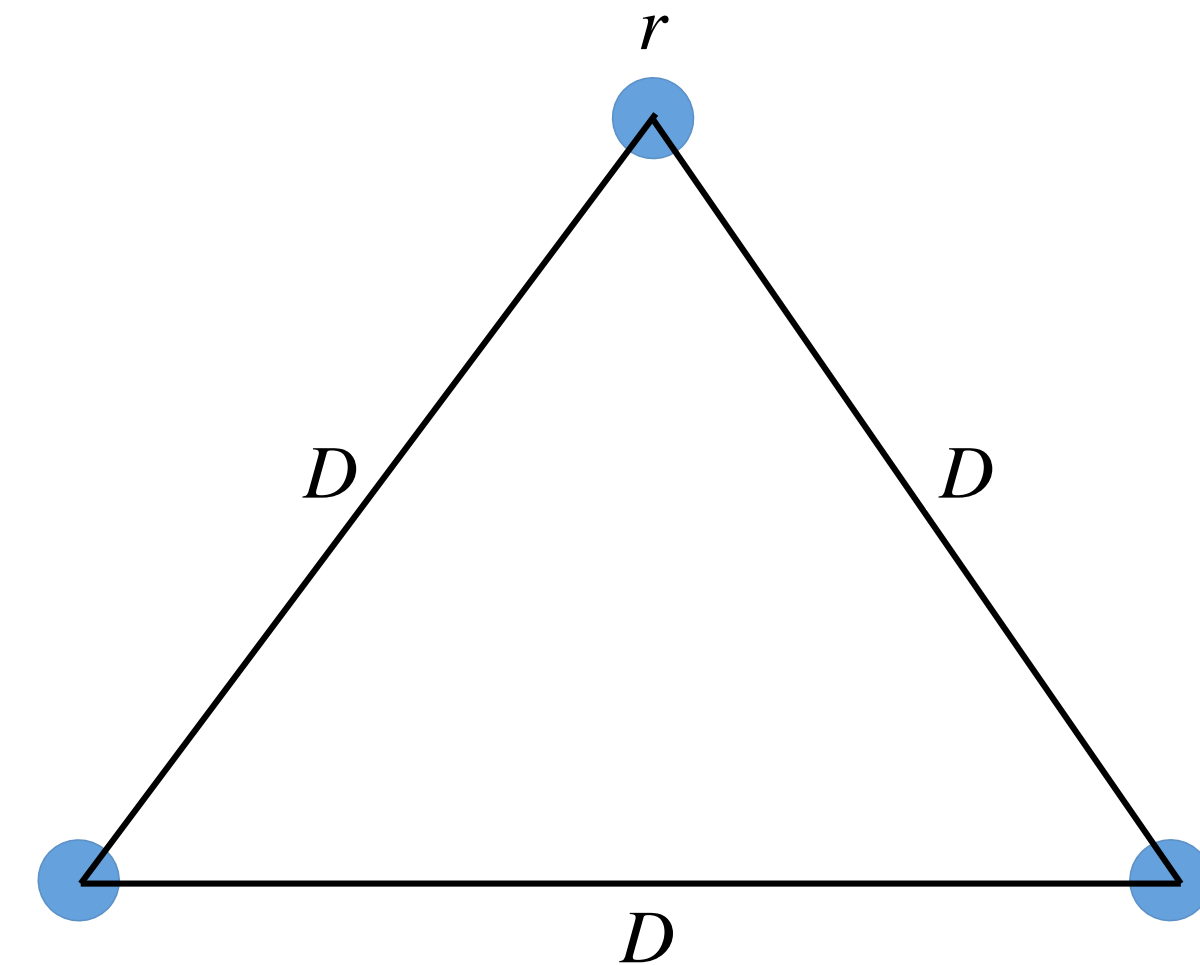1. Conductors equally spaced at  $D$  with equal radii  $r$
2.  $i_1(t) + \dots + i_n(t) = 0$  for all  $t$
3.  $q_1(t) + \dots + q_n(t) = 0$  for all  $t$

Phases are **decoupled** (vars of conductor  $k$  independent of vars of  $k' \neq k$ )



$$\lambda_k = \underbrace{\left( \frac{\mu_0}{2\pi} \ln \frac{D}{r} \right)}_{\text{inductance } l \text{ (H/m)}} i_k \qquad v_k = \underbrace{\left( \frac{1}{2\pi\epsilon} \ln \frac{D}{r} \right)}_{(\cdot)^{-1}: \text{capacitance } c \text{ (F/m)}} q_k$$

Per-phase line characteristics (balanced)

$$z := r + i\omega l, \quad r > 0, l > 0$$

$$y := g + i\omega c, \quad g \geq 0, c > 0$$


# Outline

1. Line characteristics
2. Line models
  - Transmission matrix
  - $\Pi$  circuit model
  - Real and reactive line losses
  - Special cases: lossless line, short line

# Balanced three-phase line

## Assumptions:

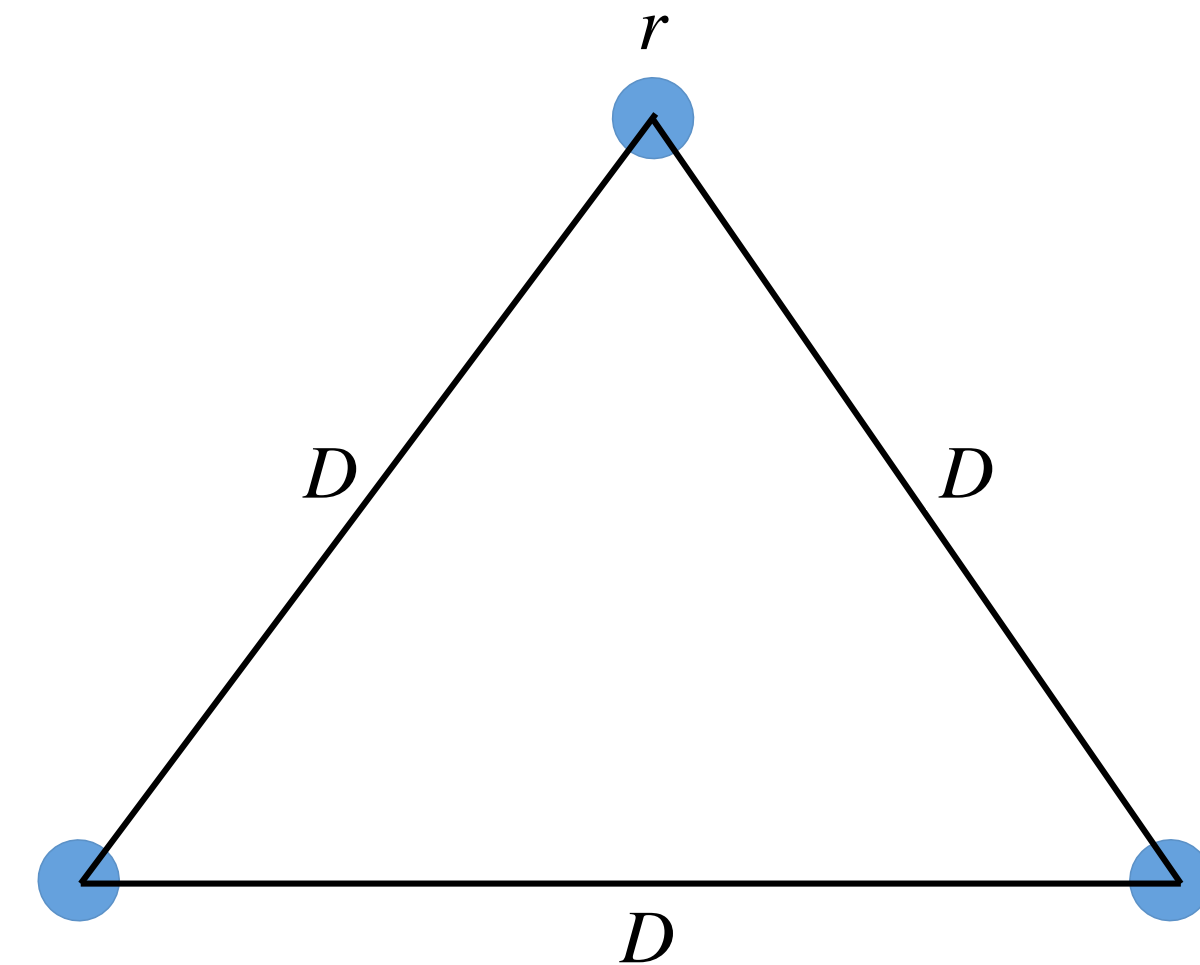1. Conductors equally spaced at  $D$  with equal radii  $r$
2.  $i_1(t) + \dots + i_n(t) = 0$  for all  $t$
3.  $q_1(t) + \dots + q_n(t) = 0$  for all  $t$




## Per-phase line characteristics

- series impedance / meter  $z := r + i\omega l$   $\Omega/\text{m}$   $r > 0, l > 0$
- shunt admittance / meter to neutral  $y := g + i\omega c$   $\Omega^{-1}/\text{m}$   $g \geq 0, c > 0$

Next: use line parameter  $(z, y)$  to model **end-to-end behavior** of per-phase line (transmission matrix)

# Transmission matrix

## Distributed element model

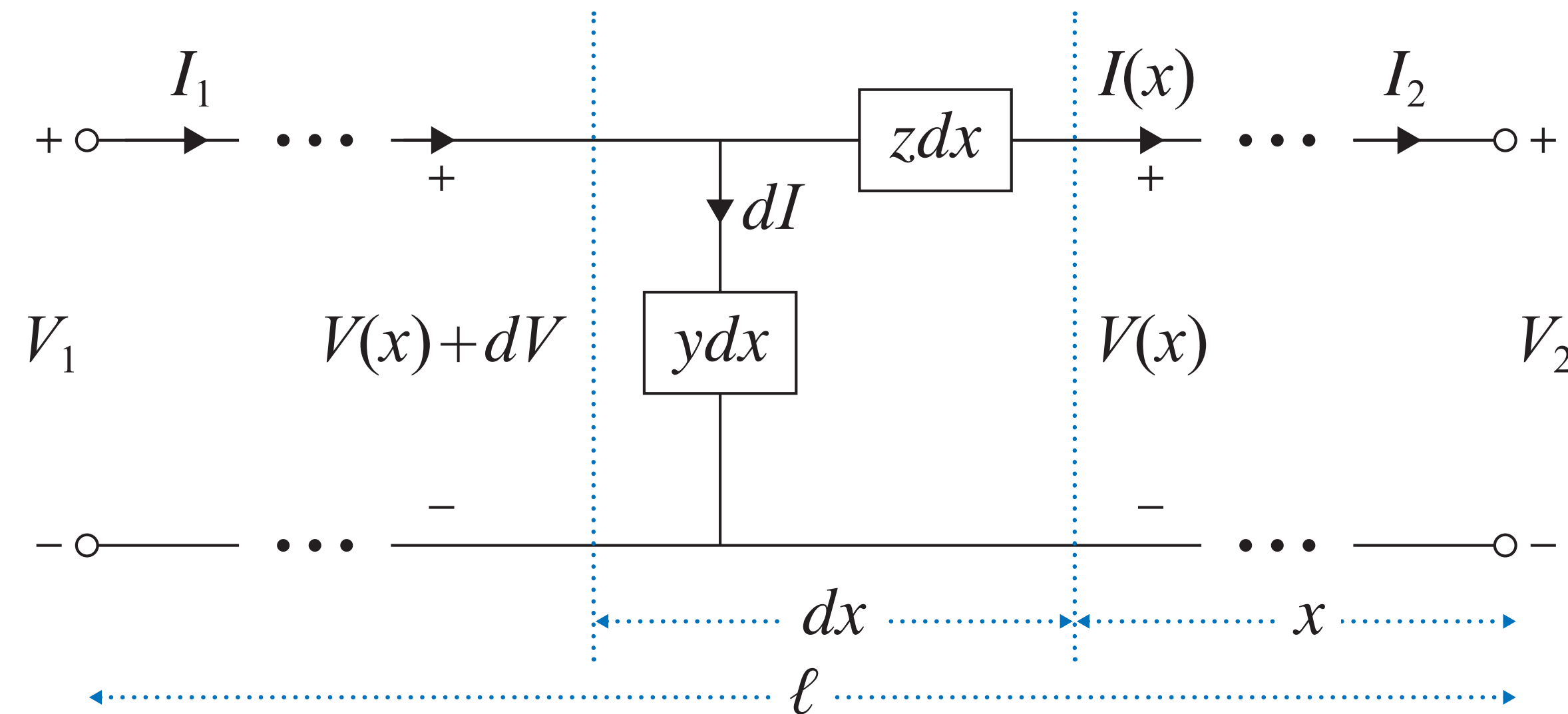

$$dV = zI(x) dx$$

$$dI = (V(x) + dV)y dx \approx yV(x) dx$$

ODE:


$$\frac{d}{dx} \begin{bmatrix} V \\ I \end{bmatrix} = \begin{bmatrix} 0 & z \\ y & 0 \end{bmatrix} \begin{bmatrix} V \\ I \end{bmatrix}$$

boundary cond:

$$V(0) = V_2, I(0) = I_2$$

# Transmission matrix

## Distributed element model

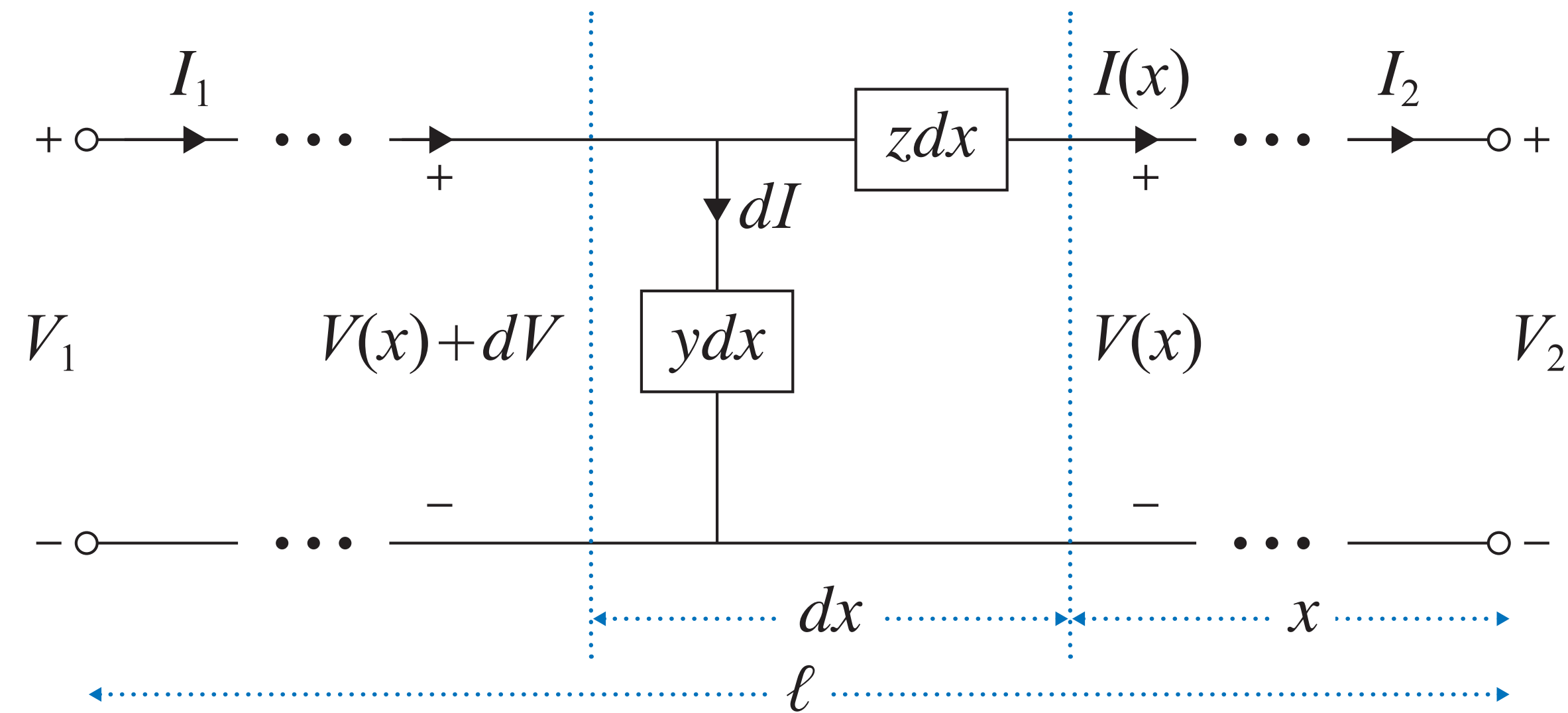

$$\begin{bmatrix} V(x) \\ I(x) \end{bmatrix} = U \begin{bmatrix} e^{\gamma x} & 0 \\ 0 & e^{-\gamma x} \end{bmatrix} U^{-1} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$U := \begin{bmatrix} Z_c & -Z_c \\ 1 & 1 \end{bmatrix}, \quad U^{-1} := \frac{1}{2Z_c} \begin{bmatrix} 1 & Z_c \\ -1 & Z_c \end{bmatrix}$$

characteristic impedance  $Z_c := \sqrt{\frac{z}{y}} \quad \Omega/m$

propagation constant  $\gamma := \sqrt{zy} \quad m^{-1}$

# Transmission matrix

## Distributed element model

Transmission matrix maps receiving-end  $(V_2, I_2)$  to sending-end  $(V_1, I_1)$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \cosh(\gamma \ell) & Z_c \sinh(\gamma \ell) \\ Z_c^{-1} \sinh(\gamma \ell) & \cosh(\gamma \ell) \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$


characteristic impedance  $Z_c := \sqrt{\frac{z}{y}} \quad \Omega/m$

propagation constant  $\gamma := \sqrt{zy} \quad m^{-1}$



# $\Pi$ circuit model

## Lumped element model

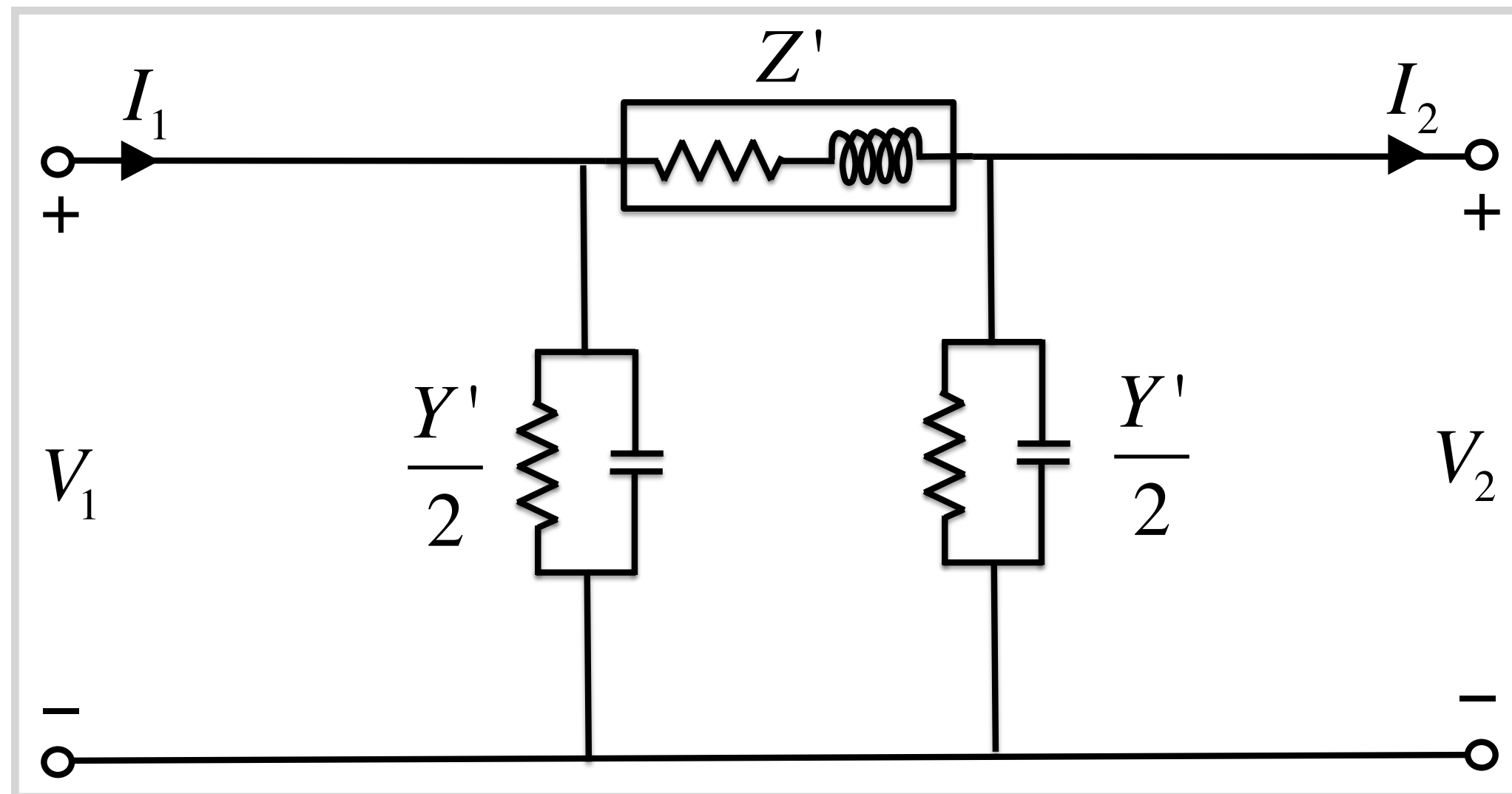

**Transmission matrix**

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 + Z'Y'/2 & Z' \\ Y'(1 + Z'Y'/4) & 1 + Z'Y'/2 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

**Admittance matrix**

$$\begin{bmatrix} I_1 \\ -I_2 \end{bmatrix} = \begin{bmatrix} Z'^{-1} + Y'/2 & -Z'^{-1} \\ -Z'^{-1} & Z'^{-1} + Y'/2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

*Long line* ( $\ell > 150$  miles) : use  $Z'$  and  $Y'$

*Medium line* ( $50 < \ell < 150$  miles) : use  $Z = z\ell$  and  $Y = i\omega C$

*Short line* ( $\ell < 50$  miles) : use  $Z = z\ell$  and  $Y = 0$

# Line current loss

Sending-end current

$$I_{12} = \frac{1}{Z'}(V_1 - V_2) + \frac{Y'}{2} V_1$$

$$I_{21} = \frac{1}{Z'}(V_2 - V_1) + \frac{Y'}{2} V_2$$

$$(I_{12} = I_1, I_{21} = -I_2)$$

# Line current loss

Sending-end current

$$I_{12} = \frac{1}{Z'}(V_1 - V_2) + \frac{Y'}{2} V_1$$

$$I_{21} = \frac{1}{Z'}(V_2 - V_1) + \frac{Y'}{2} V_2$$

$$(I_{12} = I_1, I_{21} = -I_2)$$

Line current loss

$$I_{12} + I_{21} = \frac{Y'}{2} (V_1 + V_2)$$

If  $Y' = 0$  then  $I_{12} = -I_{21}$  sending current = receiving current

# Line power loss

Sending-end power

$$S_{12} := V_1 \bar{I}_{12} = \frac{1}{\bar{Z}'} \left( |V_1|^2 - V_1 \bar{V}_2 \right) + \frac{\bar{Y}'}{2} |V_1|^2$$

$$S_{21} := V_2 \bar{I}_{21} = \frac{1}{\bar{Z}'} \left( |V_2|^2 - V_2 \bar{V}_1 \right) + \frac{\bar{Y}'}{2} |V_2|^2$$

Real and reactive power losses

$$S_{12} + S_{21} = Z' |I_{12}^s|^2 + \frac{\bar{Y}'}{2} \left( |V_1|^2 + |V_2|^2 \right)$$

# Outline

1. Line characteristics
2. Line models
  - Transmission matrix
  - $\Pi$  circuit model
  - Real and reactive line losses
  - Special cases: lossless line, short lossless line

# Special cases

## Per-phase transmission line

general per-phase line

$$z := r + i\omega l, \quad r > 0, l > 0$$

$$y := g + i\omega c, \quad g \geq 0, c > 0$$

lossless line

$$r = g := 0$$

short lossless line

$$r := 0, y := 0$$

# Lossless line: $r = g := 0$

Characteristic impedance is real


$$Z_c = \sqrt{\frac{\bar{z}}{y}} = \sqrt{\frac{i\omega l}{i\omega c}} = \sqrt{\frac{l}{c}} \quad \Omega$$

Propagation constant is imaginary

$$\gamma = \sqrt{zy} = \sqrt{(i\omega l)(i\omega c)} = i\omega\sqrt{lc} \quad m^{-1} \quad \beta := \omega\sqrt{lc}$$

**$\Pi$  circuit model:** both series impedance and shunt admittance are reactive:
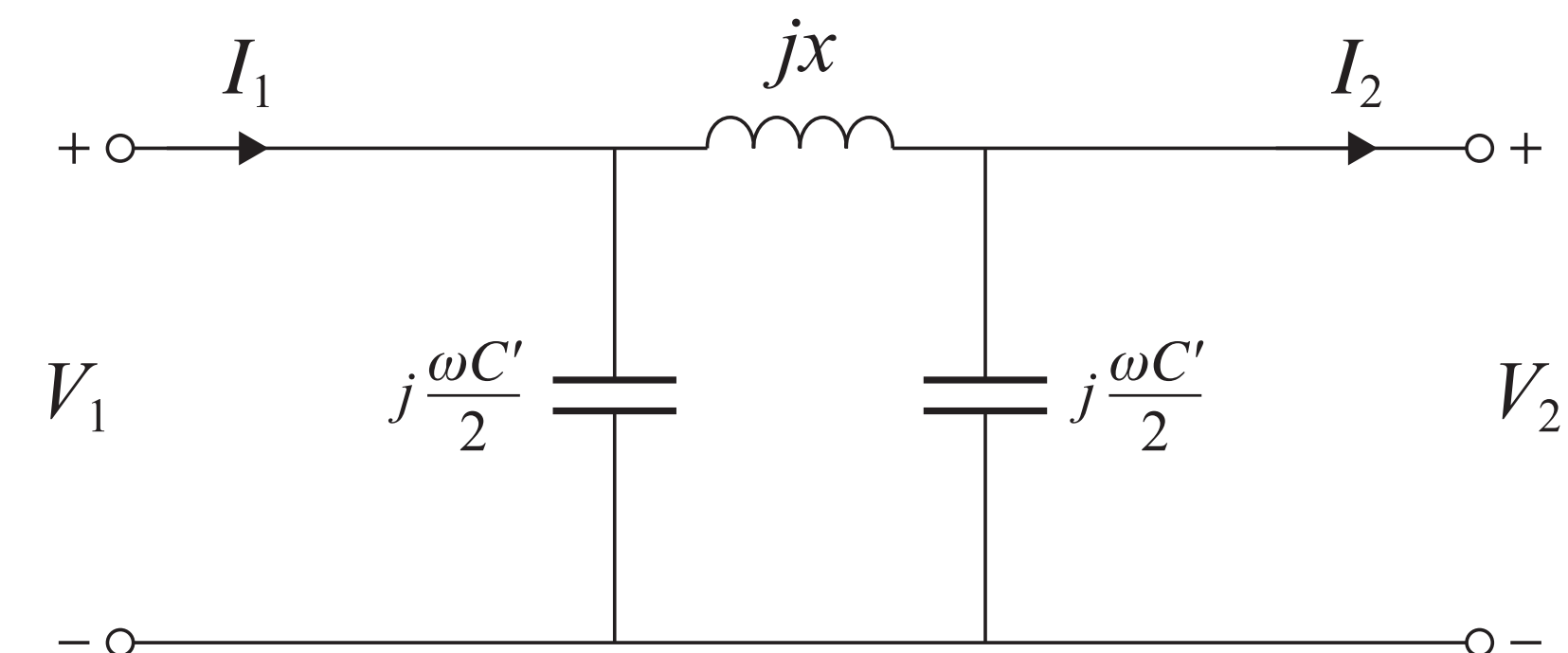
$$Z' = iZ_c \sin(\beta\ell) \quad \Omega, \quad \frac{Y'}{2} = i\frac{\omega c\ell}{2} \frac{\tan(\beta\ell/2)}{\beta\ell/2} \quad \Omega^{-1}$$




# Lossless line: $r = g := 0$

Voltage along the line

$$V(x) = V_2 \cos(\beta x) + i Z_c I_2 \sin(\beta x)$$

$$\beta := \omega \sqrt{lc}$$

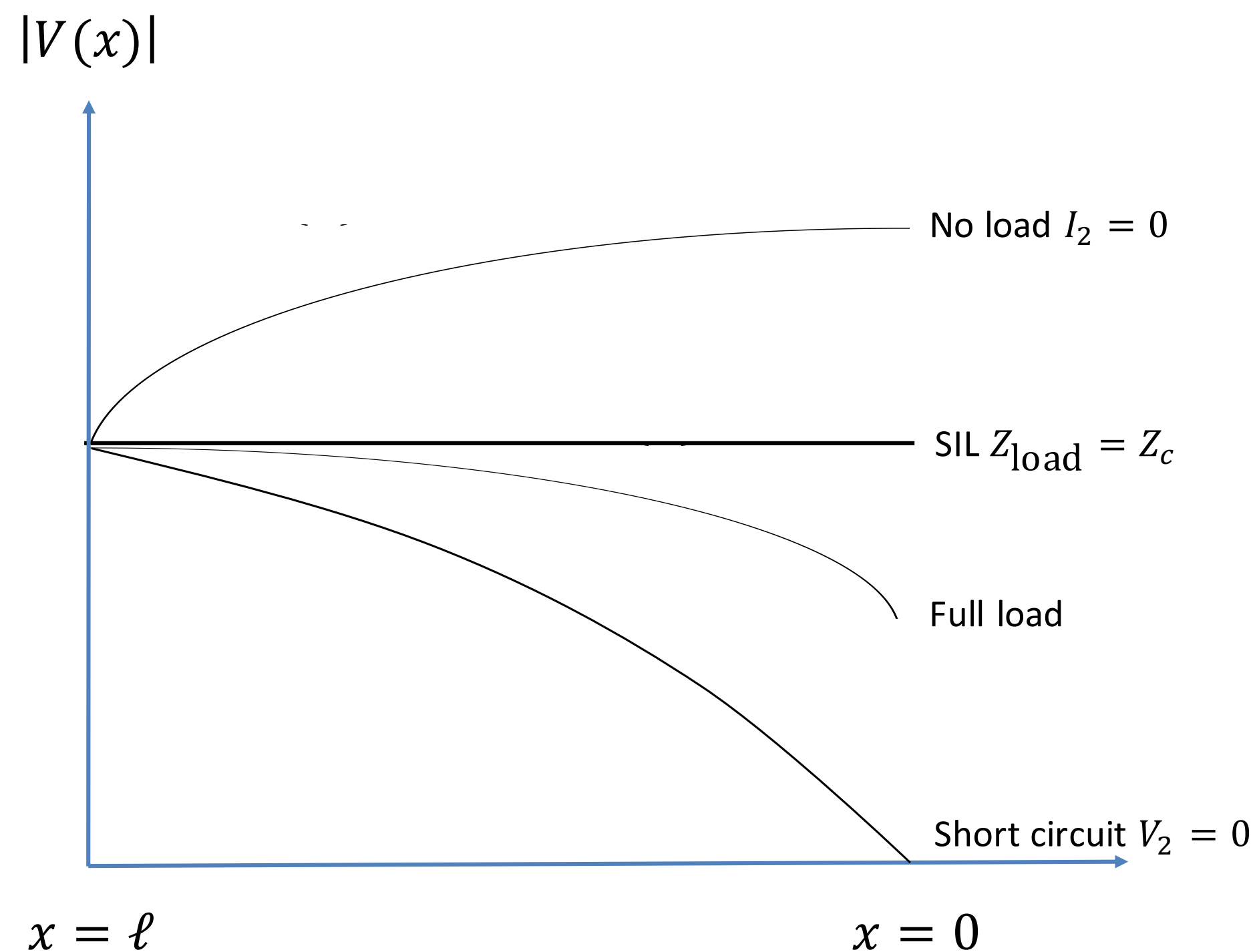

Generally voltage drops along the line towards load



# Short lossless line: $r := 0, y := 0$

Sending-end power from  $i$  to  $j$ :

$$S_{ij} = V_i \bar{I}_{ij} = V_i \frac{\bar{V}_i - \bar{V}_j}{iX} = i \frac{1}{X} \left( |V_i|^2 - V_i \bar{V}_j \right)$$

Explore 3 implications

- How does load voltage magnitude  $|V_2|$  depend on active load power  $P_{\text{load}}$  ?
- Decoupling:  $P$  mainly depends on  $\theta$ ,  $|V|$  on  $Q$
- Linear model: DC power flow

# Short lossless line: $r := 0, y := 0$

Sending-end power from  $i$  to  $j$ :

$$S_{ij} = V_i \bar{I}_{ij} = V_i \frac{\bar{V}_i - \bar{V}_j}{iX} = i \frac{1}{X} \left( |V_i|^2 - V_i \bar{V}_j \right)$$

Receiving-end load power at bus 2:

$$-S_{21} = -V_2 \bar{I}_{21} = -i \frac{1}{X} \left( |V_2|^2 - V_2 \bar{V}_1 \right)$$

**Suppose:**  $-S_{21}$  supplies a load with load power  $P_{\text{load}} + iQ_{\text{load}}$ , i.e.,

$$-S_{21} = P_{\text{load}}(1 + i \tan \phi)$$

$\phi := \theta_{V_2} - \theta_{-I_{21}}$ : load power factor angle

# Short lossless line: $r := 0, y := 0$

## Load voltage solution and collapse

How does load voltage  $|V_2|$  depend on active load power  $P_{\text{load}}$  ?

$$-i \frac{1}{X} \left( |V_2|^2 - V_2 \bar{V}_1 \right) = P_{\text{load}} (1 + i \tan \phi)$$

Assume:  $V_1 := 1 \angle 0^\circ \Rightarrow \theta_{21} := \theta_2 - \theta_1 = \theta_2$

Then

- 2 real equations in  $(|V_2|, \theta_2)$  with  $P_{\text{load}}$  as parameter
- Solve for load voltage  $|V_2|$  given any  $P_{\text{load}}$
- As load power  $P_{\text{load}}$  increases, solutions  $|V_2|$  trace out a **nose curve**
- If  $P_{\text{load}}$  increases further, no real solutions for  $|V_2|$  exists - **voltage collapse**

# Short lossless line: $r := 0, y := 0$

Sending-end power from  $i$  to  $j$ :

$$S_{ij} = V_i \bar{I}_{ij} = V_i \frac{\bar{V}_i - \bar{V}_j}{iX} = i \frac{1}{X} \left( |V_i|^2 - V_i \bar{V}_j \right)$$

Hence

$$P_{12} = \frac{|V_1| |V_2|}{X} \sin \theta_{12}$$

$$Q_{12} = \frac{1}{X} \left( |V_1|^2 - |V_1| |V_2| \cos \theta_{12} \right)$$

$$Q_{21} = \frac{1}{X} \left( |V_2|^2 - |V_1| |V_2| \cos \theta_{12} \right)$$

# Short lossless line: $r := 0, y := 0$

## Decoupling

1.  $P_{12}$  and  $|V_i|$  are roughly decoupled,  $Q_{ij}$  and  $\theta_{12}$  are roughly decoupled

$$\frac{\partial P_{12}}{\partial |V_i|} = \frac{|V_j|}{X} \sin \theta_{12} \approx 0 \quad \frac{\partial Q_{ij}}{\partial \theta_{12}} = \frac{|V_1||V_2|}{X} \sin \theta_{12} \approx 0$$

2.  $P_{12}$  mainly depends on  $\theta_{12}$  with rate

$$\frac{\partial P_{12}}{\partial \theta_{12}} = \frac{|V_1||V_2|}{X} \cos \theta_{12} \approx \frac{|V_1||V_2|}{X}$$

3. Voltage regulation

$$\frac{\partial Q_{12}}{\partial |V_2|} = -\frac{|V_1|}{X} \cos \theta_{12} < 0 \quad \frac{\partial Q_{21}}{\partial |V_2|} = \frac{1}{X} (2|V_2| - |V_1| \cos \theta_{12}) > 0$$

To maintain high load voltage  $|V_2|$ :

decrease sending-end  $Q_{12}$ , increase load injection  $Q_{21}$

# Short lossless line: $r := 0, y := 0$

## Linear model

DC power flow model:  $R = 0$ , fixed  $|V_i|$ ,  $\sin \theta_{12} \approx \theta_{12}$ , ignore  $Q_{ij}$

$$P_{ij} = \frac{|V_1||V_2|}{X} \theta_{12} =: b_{12}(\theta_1 - \theta_2)$$

- Widely used for electricity market and long-time planning applications
- Reasonable model for transmission system apps, not for distribution system apps where  $r$  is high