# Power System Analysis


**Chapter 3** Transformer models

## Outline

- 1. Single-phase transformer
- 2. Balanced three-phase transformers
- 3. Equivalent impedance
- 4. Per-phase analysis
- 5. Per-unit normalization

## Outline

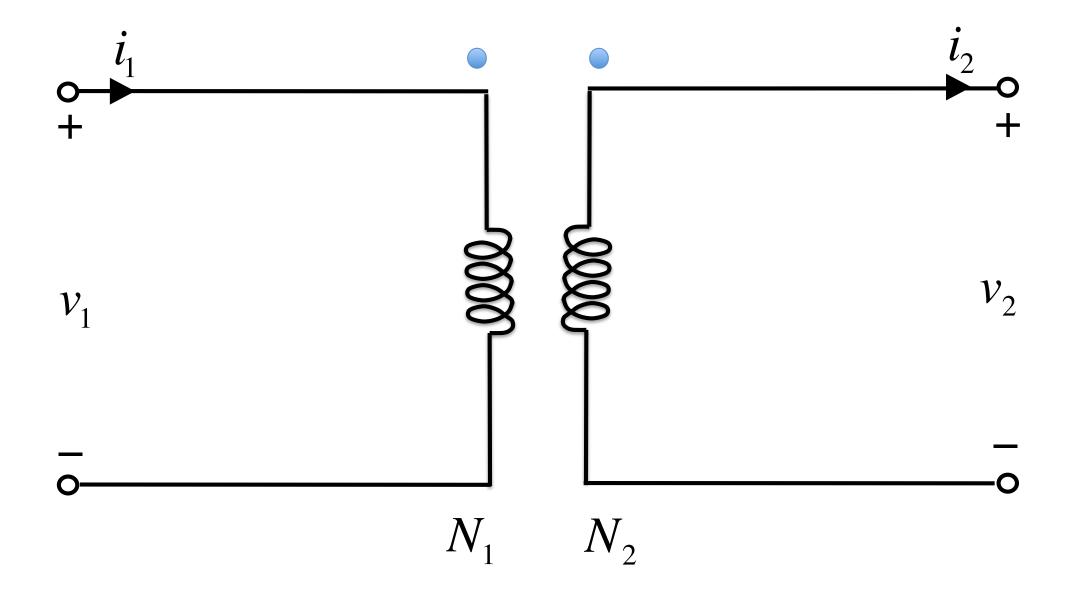
- 1. Single-phase transformer
  - Ideal transformer
  - Nonideal transformer
  - ullet Circuit models: T eq circuit, simplified circuit, UVN, split-phase
- 2. Balanced three-phase transformers
- 3. Equivalent impedance
- 4. Per-phase analysis
- 5. Per-unit normalization



voltage gain 
$$n:=\frac{N_2}{N_1}$$
 turns ratio  $a:=\frac{N_1}{N_2}$ 

Voltage & current gains
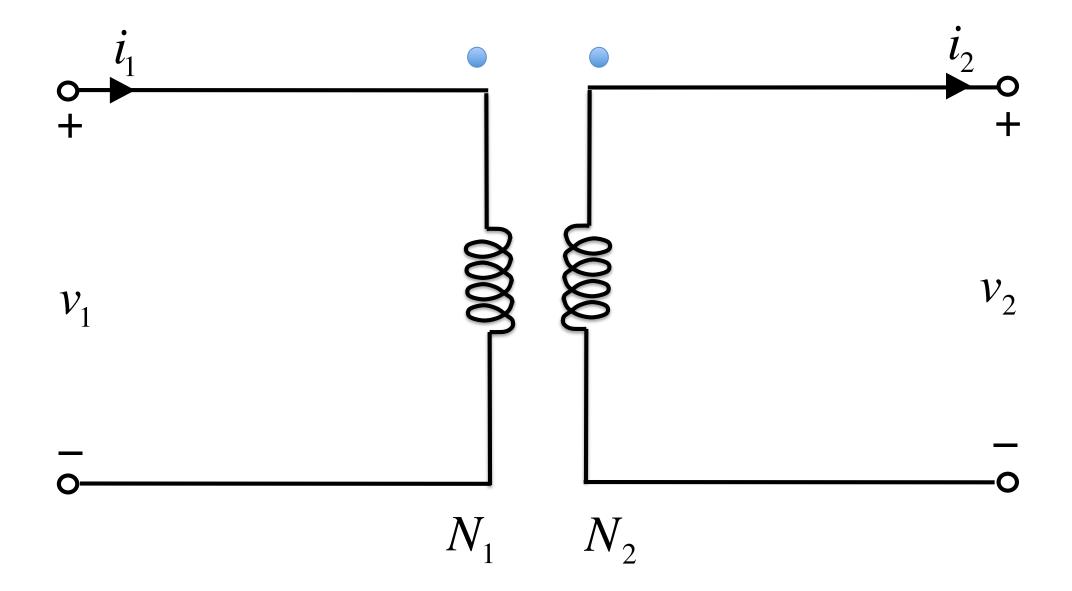
$$\frac{v_2(t)}{v_1(t)} = n \qquad \frac{i_2(t)}{i_1(t)} = a$$




voltage gain 
$$n:=\frac{N_2}{N_1}$$
 turns ratio  $a:=\frac{N_2}{N_2}$ 

Voltage & current gains

$$\frac{V_2}{V_1} = n \qquad \frac{I_2}{I_1} = a$$

Transmission matrix
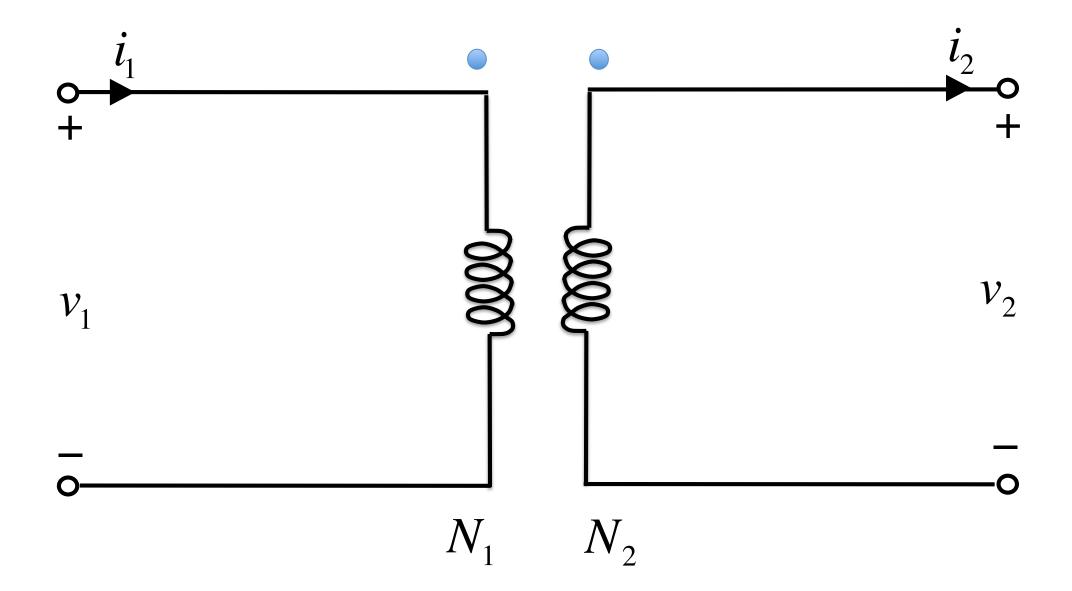
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a & 0 \\ 0 & n \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$




voltage gain 
$$n:=rac{N_2}{N_1}$$
 turns ratio  $a:=rac{N_2}{N_2}$ 

Power transfer


$$\frac{-S_{21}}{S_{12}} := \frac{V_2 \bar{I}_2}{V_1 \bar{I}_1} = n \cdot a = 1$$

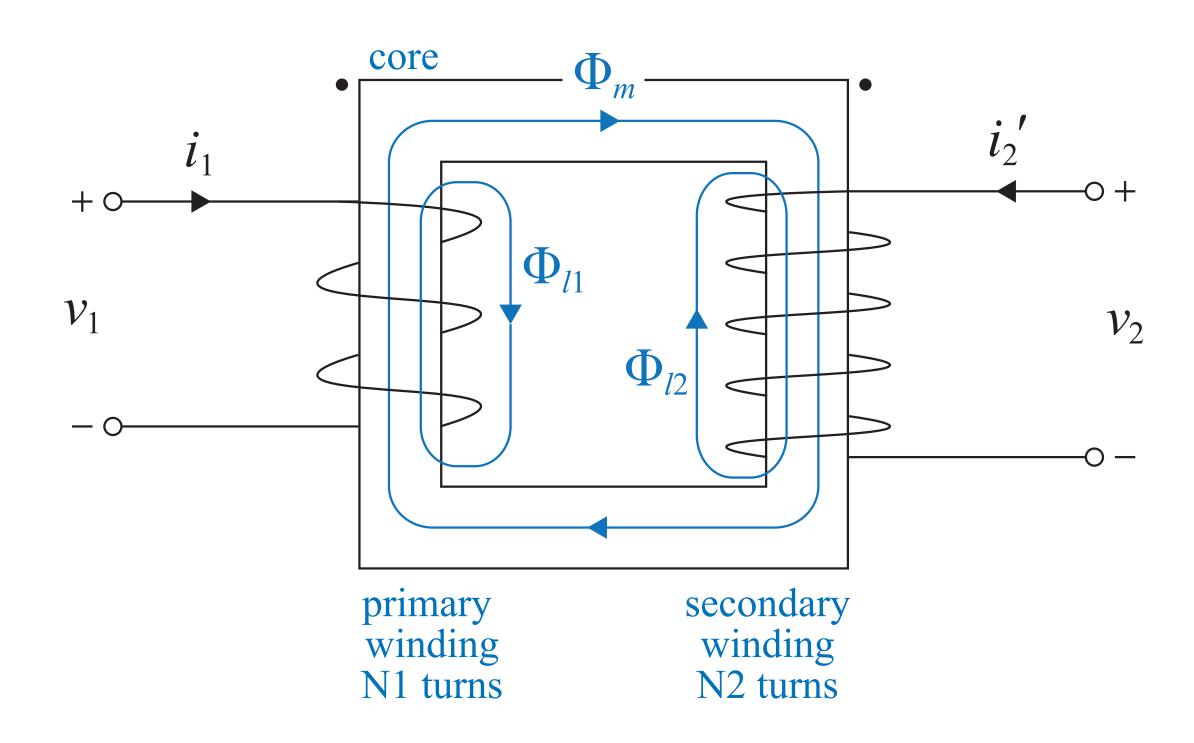i.e., deal transformer incurs no power loss


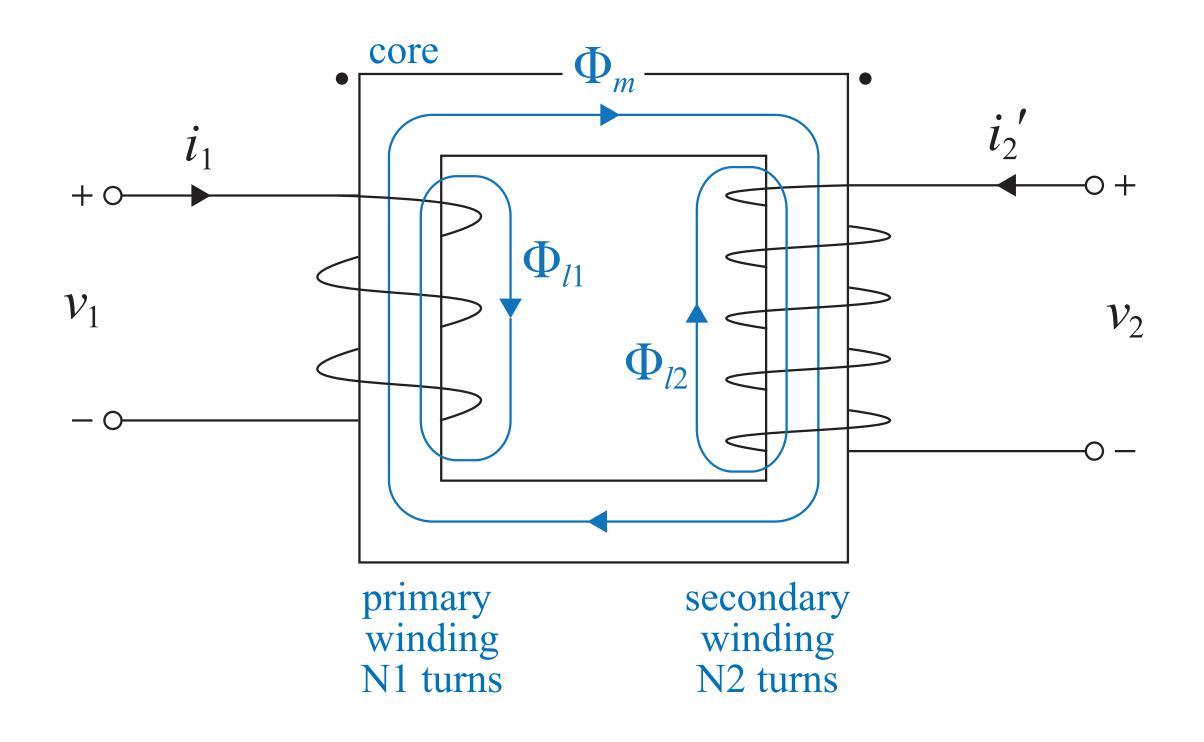
#### Nonideal behavior

- Power losses (coil resistances, eddy currents, hysteresis losses)
- . Leakage magnetic fluxes  $\left(\Phi_{l_1},\Phi_{l_2}\right)$
- Finite permeability of magnetic cores



Voltages

$$v_1 = r_1 i_1 + \frac{d\lambda_1}{dt}, \qquad v_2 = r_2 i_2' + \frac{d\lambda_2}{dt}$$


Total flux linkages

$$\lambda_1 = N_1 \Phi_m + \lambda_{l1}, \qquad \lambda_2 = N_2 \Phi_m + \lambda_{21}$$
 $\lambda_{l1} = L_{l1} i_1, \qquad \lambda_{l2} = L_{l2} i_2'$ 

Total magnetomotive force

$$F = N_1 i_1 + N_2 i_2' = R\Phi_m$$

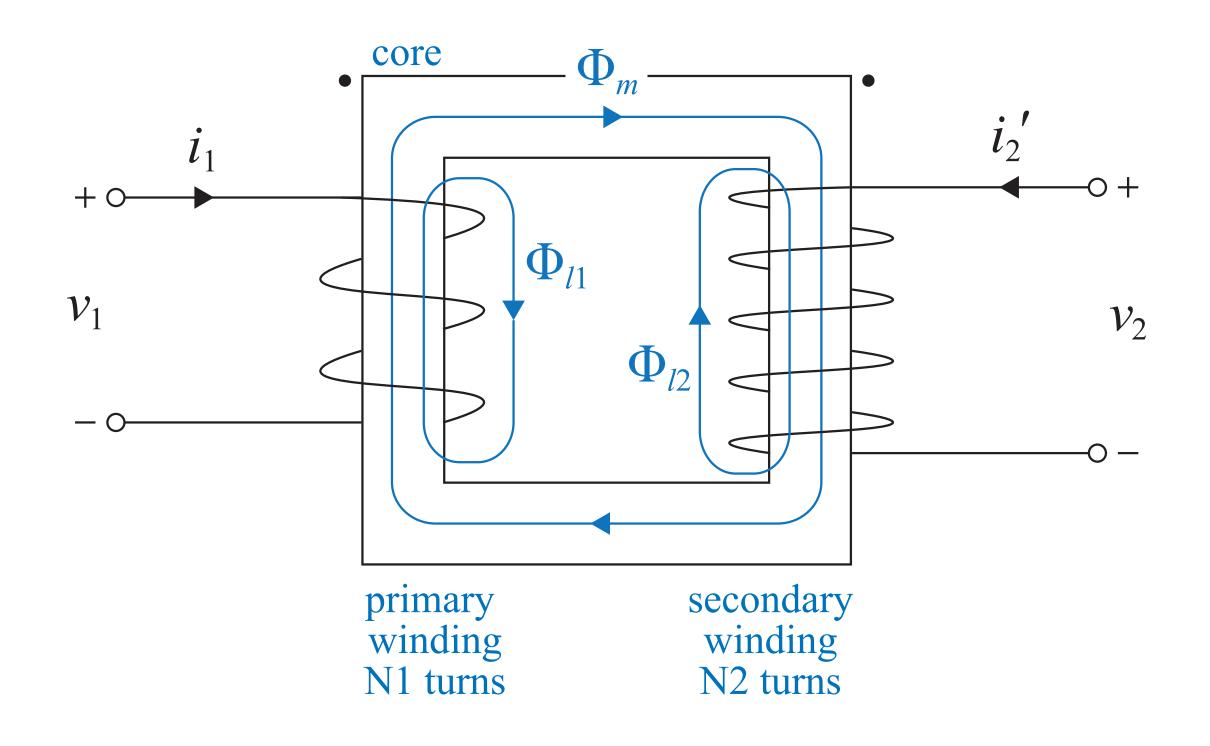Mutual flux linkages due to mutual flex  $\Phi_m$ :  $\left(N_1\Phi_m,N_2\Phi_m\right)$  Leakage flux linkages due to leakage fluxes  $\left(\Phi_{l_1},\Phi_{l_2}\right)$ :  $\left(\lambda_{l1},\ \lambda_{l2}\right)$ 



Voltages

$$v_1 = r_1 i_1 + \frac{d\lambda_1}{dt}, \qquad v_2 = r_2 i_2' + \frac{d\lambda_2}{dt}$$

Total flux linkages

$$\lambda_1 = N_1 \Phi_m + \lambda_{l1}, \qquad \lambda_2 = N_2 \Phi_m + \lambda_{21}$$
 $\lambda_{l1} = L_{l1} i_1, \qquad \lambda_{l2} = L_{l2} i_2'$ 

Total magnetomotive force


$$F = N_1 i_1 + N_2 i_2' = R\Phi_m$$

#### Ideal transformer

- Zero power losses:  $r_1 = r_2 = 0$
- Zero leakage flux linkages:  $L_{l1} = L_{l2} = 0$   $\Longrightarrow$

 $v_1 = N_1 \frac{d\Phi_m}{dt}, \quad v_2 = N_2 \frac{d\Phi_m}{dt}, \quad 0 = N_1 i_1 + N_2 i_2'$ 

Infinite permeability: R=0

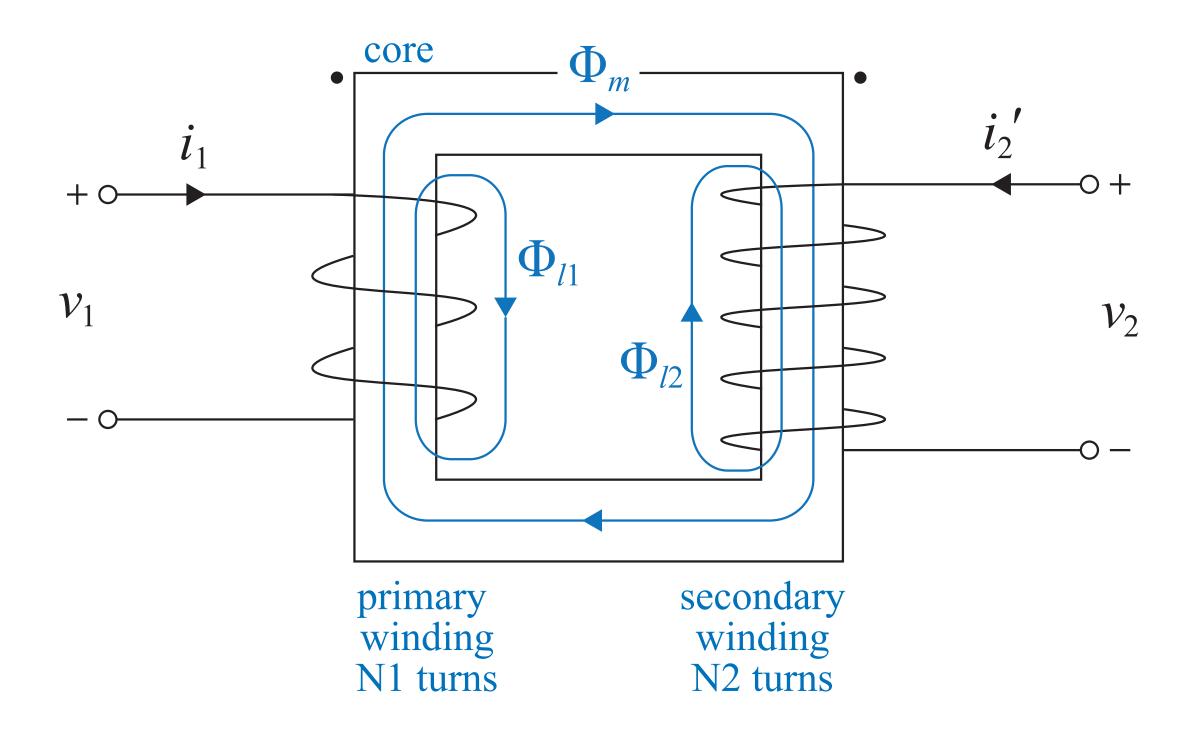

Voltages


$$v_{1} = r_{1}i_{1} + L_{l1}\frac{di_{1}}{dt} + N_{1}\frac{d\Phi_{m}}{dt}$$

$$v_{2} = r_{2}i'_{2} + L_{l2}\frac{di'_{2}}{dt} + N_{2}\frac{d\Phi_{m}}{dt}$$

Primary magnetizing current  $\hat{i}_m$ 

• primary current when secondary circuit is open  $i_2' := 0$ 

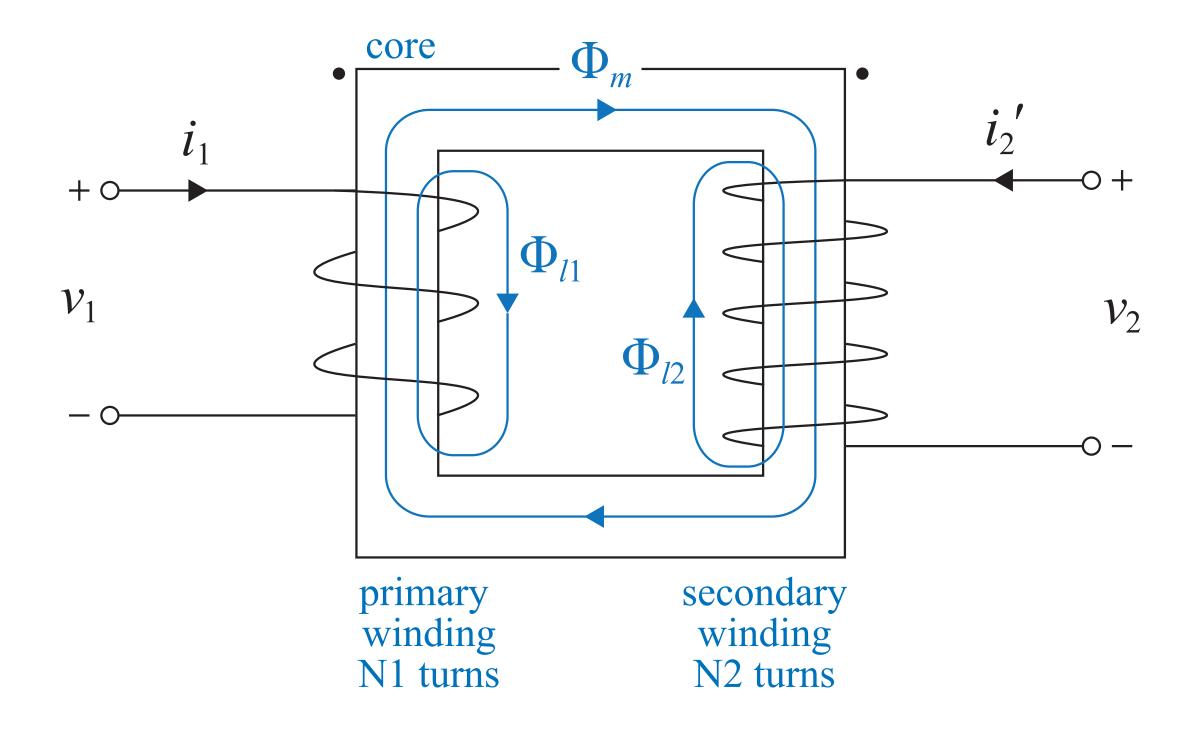• 
$$N_1\hat{i}_m=R\Phi_m$$
: let  $L_m:=N_1^2/R$  and 
$$\hat{u}_1:=N_1\frac{d\Phi_m}{dt}=L_m\frac{d\hat{i}_m}{dt}$$
 
$$\hat{u}_2:=N_2\frac{d\Phi_m}{dt}=\frac{N_2}{N_1}\hat{u}_1$$
 ideal transformer



Nonideal elements


$$v_{1} = r_{1}i_{1} + L_{l1}\frac{di_{1}}{dt} + \hat{u}_{1}, \quad \hat{u}_{1} = L_{m}\frac{d\hat{i}_{m}}{dt}$$

$$v_{2} = -r_{2}i_{2} - L_{l2}\frac{di_{2}}{dt} + \hat{u}_{2}$$

Ideal transformer

$$\hat{u}_2 = \frac{N_2}{N_1} \hat{u}_1, \qquad i_2 = \frac{N_1}{N_2} \left( i_1 - \hat{i}_m \right)$$

#### Circuit model

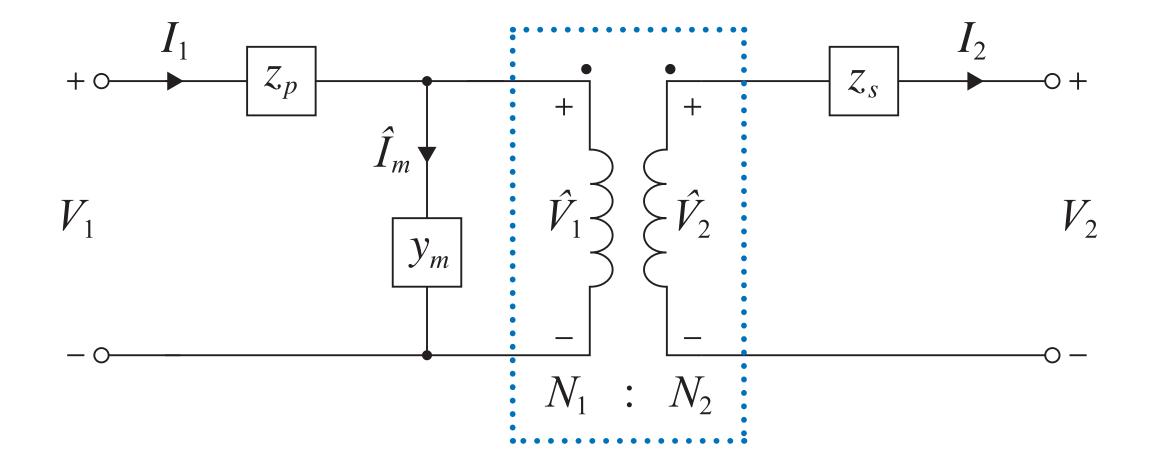


Nonideal elements (phasor domain)

$$V_1 = z_p I_1 + \hat{U}_1, \qquad \hat{I}_m = y_m \hat{U}_1$$
  
 $\hat{U}_2 = z_s I_2 + V_2$ 


Ideal transformer (phasor domain)

$$\hat{U}_2 = \frac{N_2}{N_1} \hat{U}_1, \qquad I_2 = \frac{N_1}{N_2} \left( I_1 - \hat{I}_m \right)$$

#### Circuit models

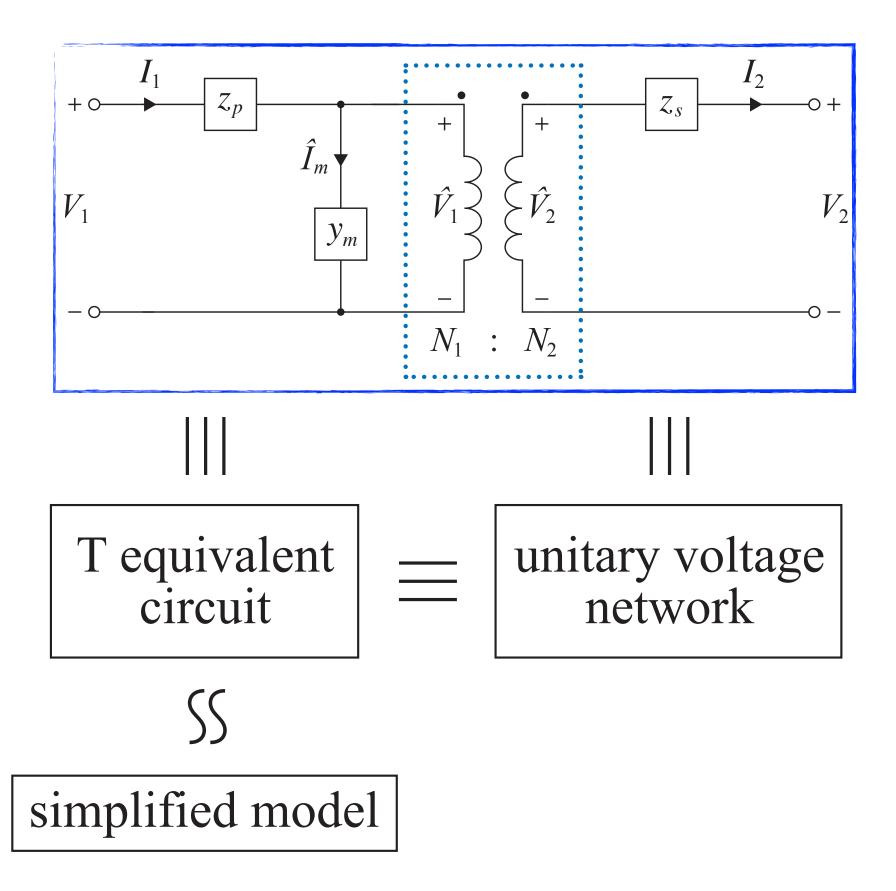

# T equivalent circuit

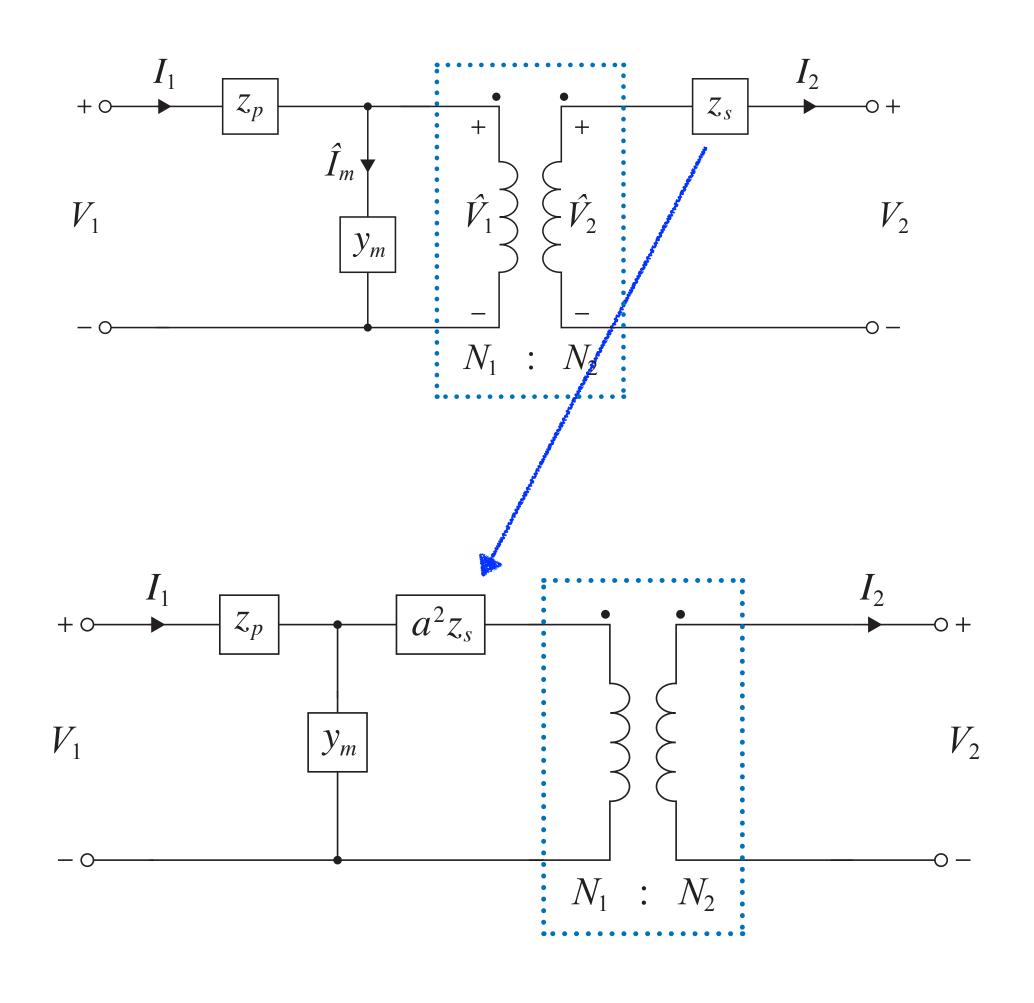

Refer series impedance  $z_s$  to the primary side  $\longrightarrow T$  equivalent circuit


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a \left( 1 + z_p y_m \right) & a z_s (1 + z_p y_m) + n z_p \\ a y_m & n + a z_s y_m \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

where  $n := N_2/N_1$ , a := 1/n

#### "Equivalent model" means

- Same end-to-end behavior, e.g., transmission matrix, or admittance matrix;
- Internal variables may be different

# T equivalent circuit

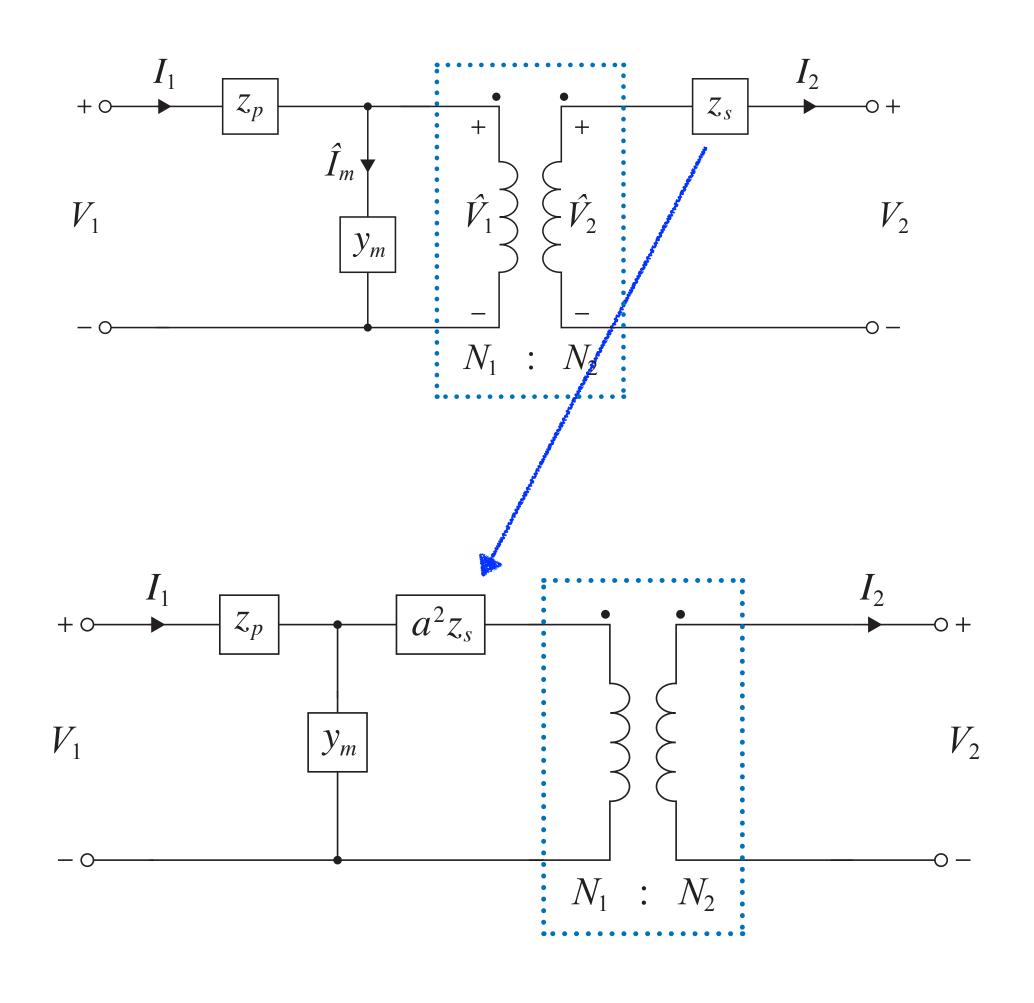

Refer series impedance  $z_s$  to the primary side  $\longrightarrow T$  equivalent circuit


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a \left( 1 + z_p y_m \right) & a z_s (1 + z_p y_m) + n z_p \\ a y_m & n + a z_s y_m \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

where  $n := N_2/N_1$ , a := 1/n


Model parameters  $(z_p, z_s, y_m)$  cannot be uniquely determined from just short-circuit & open-circuit tests

Additional tests are needed

#### Circuit models

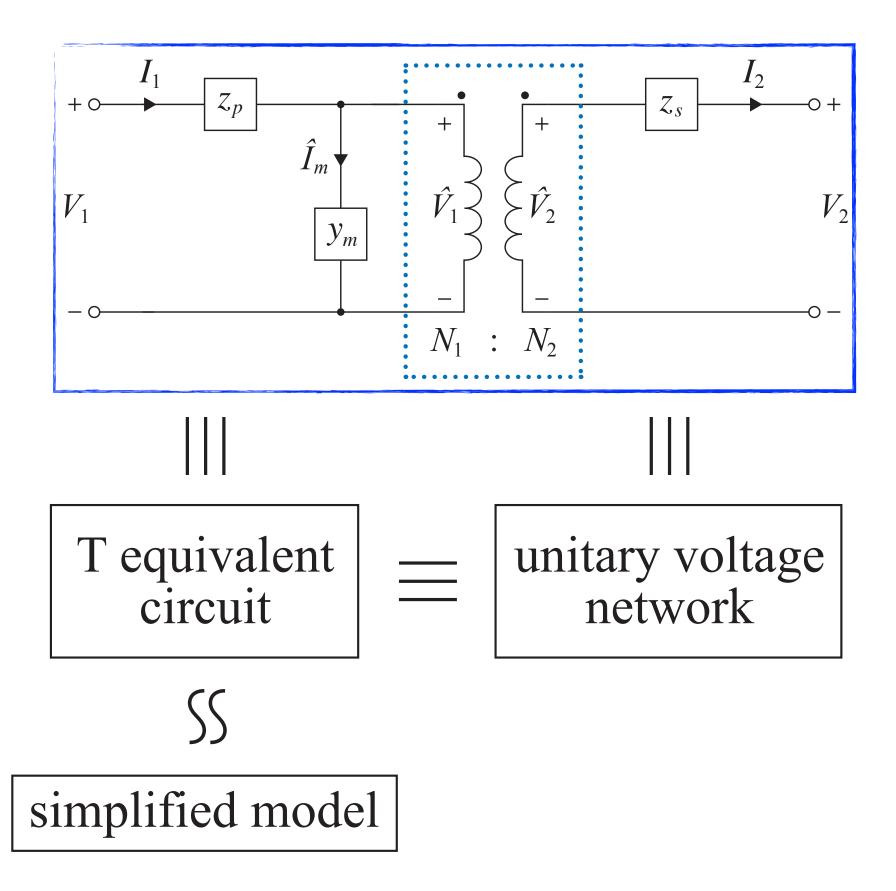

# Simplified circuit

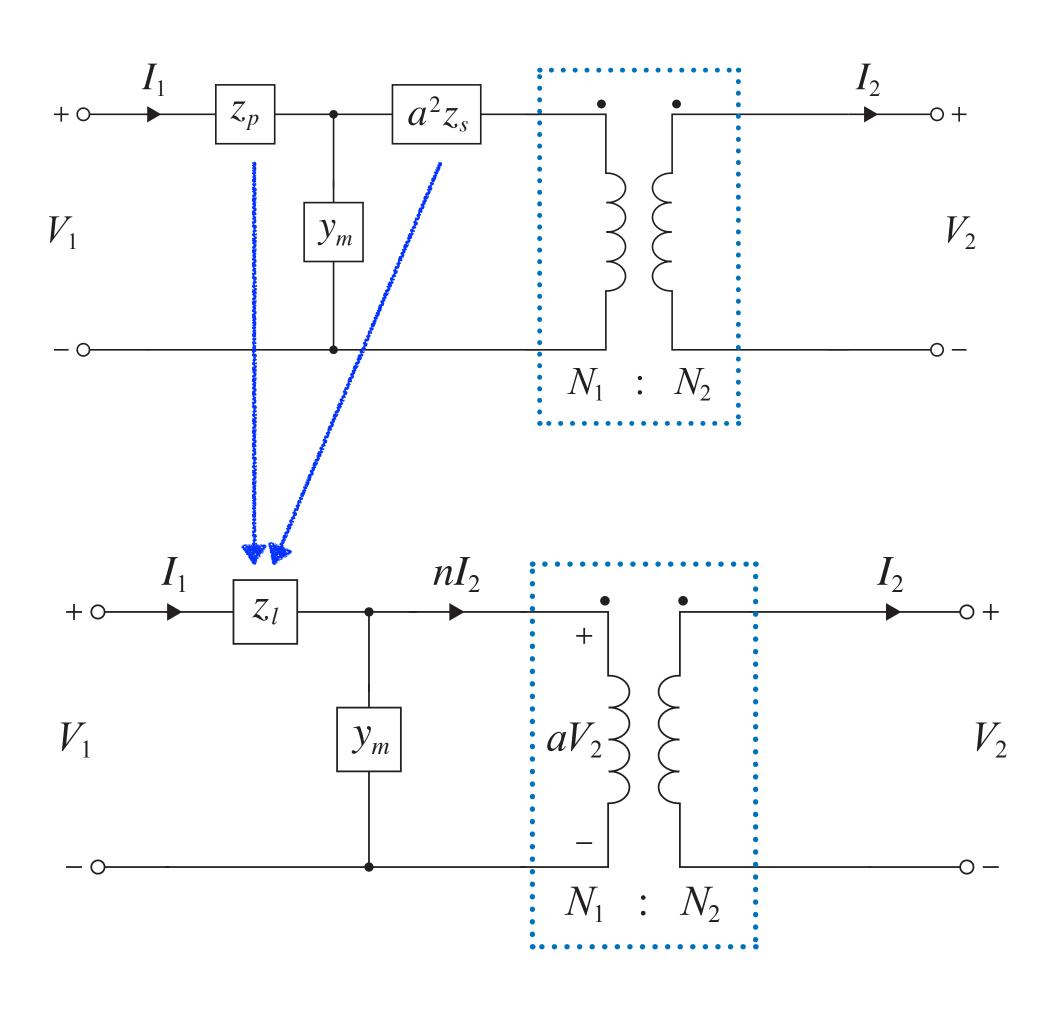


Interchange  $a^2z_s$  and  $y_m$  and combine with  $z_p$ :  $z_l := z_p + a^2z_s$ 

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a (1 + z_l y_m) & n z_l \\ a y_m & n \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

where  $n := N_2/N_1$ , a := 1/n

# Simplified circuit

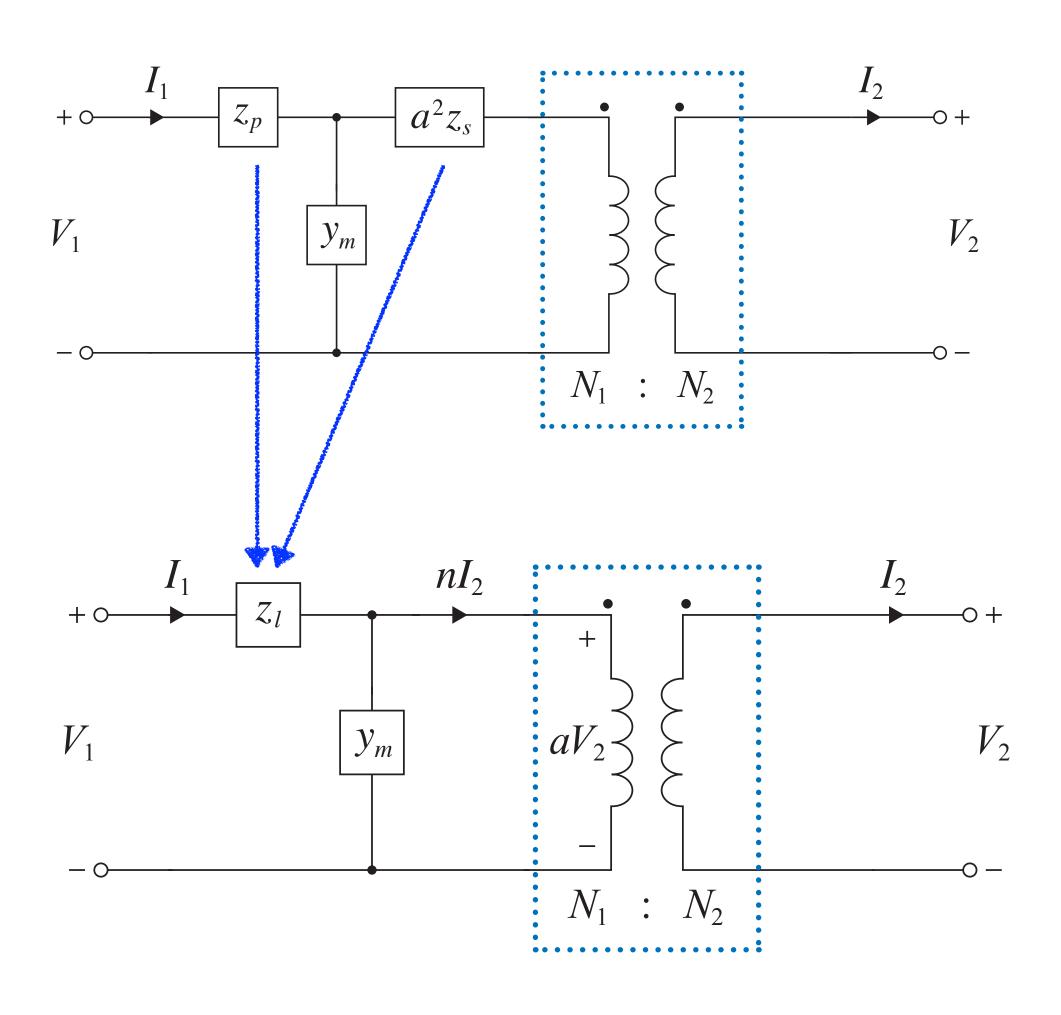

Interchange  $a^2z_s$  and  $y_m$  and combine with  $z_p$ :  $z_l := z_p + a^2z_s$ 

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a (1 + z_l y_m) & n z_l \\ a y_m & n \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

where  $n := N_2/N_1$ , a := 1/n

Good approximation of T equivalent circuit when  $|y_m| \ll 1/|a^2z_s|$ 


$$\frac{||M-T||}{||T||} < |\epsilon| \ll 1$$

M: transmission matrix of simplified model

T: transmission matrix of simplified model

$$\epsilon := a^2 z_s y_m$$

# Simplified circuit

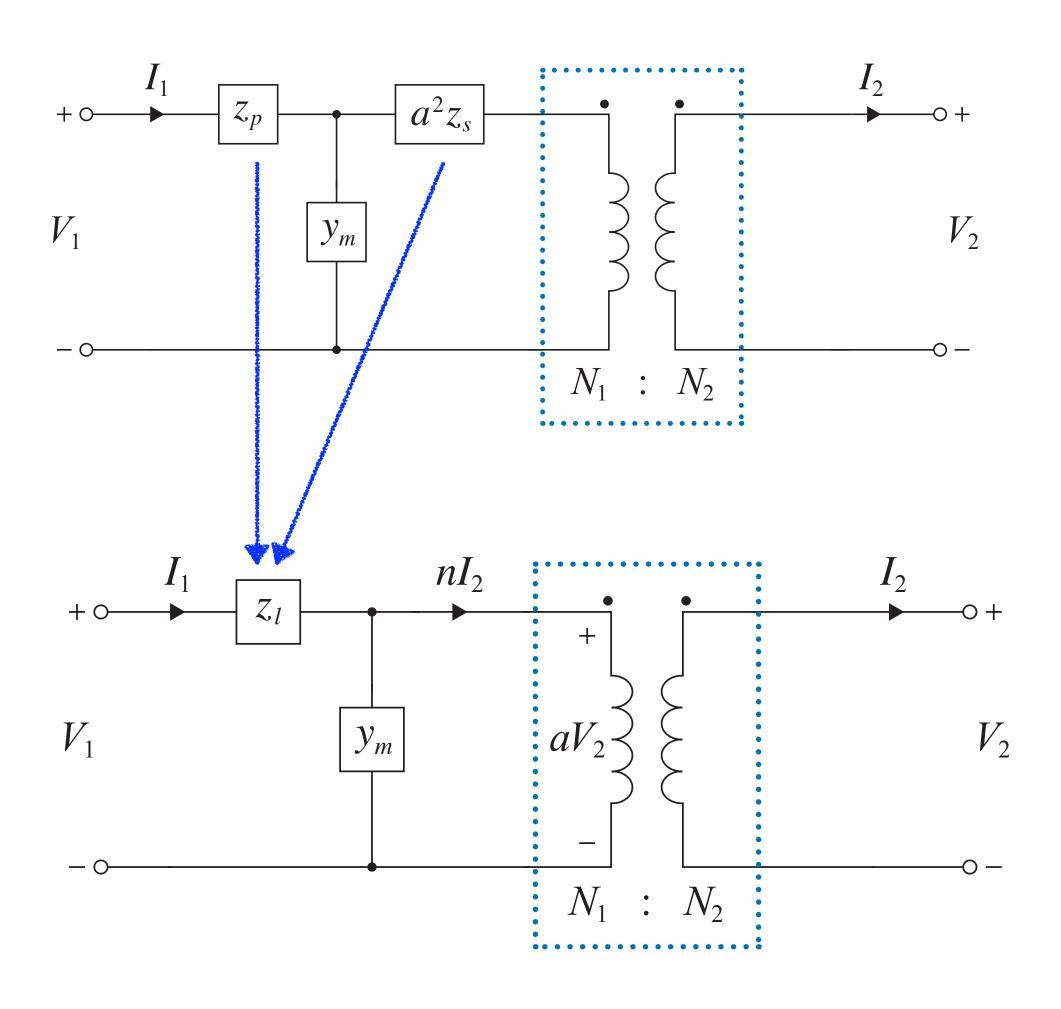

Interchange  $a^2z_s$  and  $y_m$  and combine with  $z_p$ :  $z_l := z_p + a^2z_s$ 

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a (1 + z_l y_m) & n z_l \\ a y_m & n \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

where  $n := N_2/N_1$ , a := 1/n


Good approximation when  $|y_m| \ll 1/|a^2z_s|$ 

$$\frac{\|M - T\|}{\|T\|} < |\epsilon| \ll 1$$

If  $y_m = 0$ : T equivalent circuit and simplified model are equivalent, M = T

## Parameter determination

### Short & open-circuit tests

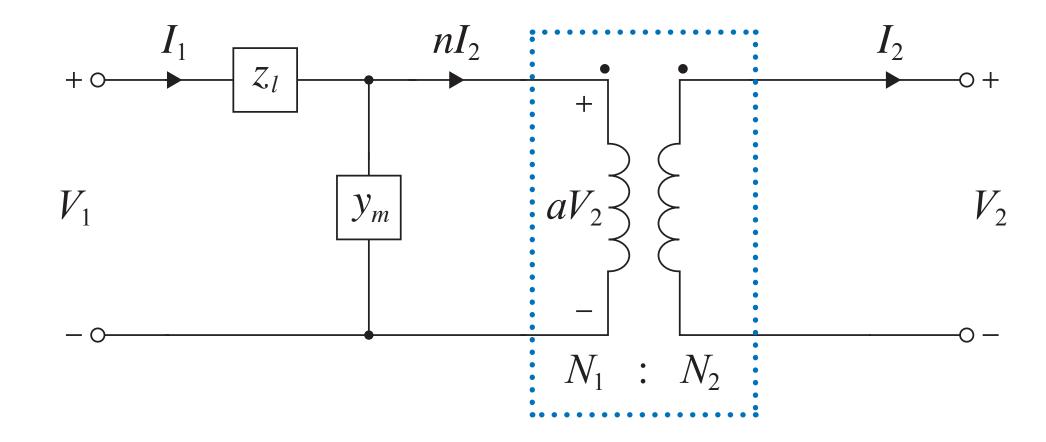

Most popular model (at least for transmission systems)

Parameters  $(z_l, y_m)$  can be determined from open and short-circuit tests

• Short-circuit test  $(V_2 := 0)$ :


$$z_l = \frac{V_{so}}{I_{sc}}$$

• Open-circuit test  $(I_2 := 0)$ :

$$\frac{1}{y_m} = \frac{V_{oc}}{I_{oc}} - \frac{V_{sc}}{I_{sc}}$$

## Parameter determination

### Short & open-circuit tests

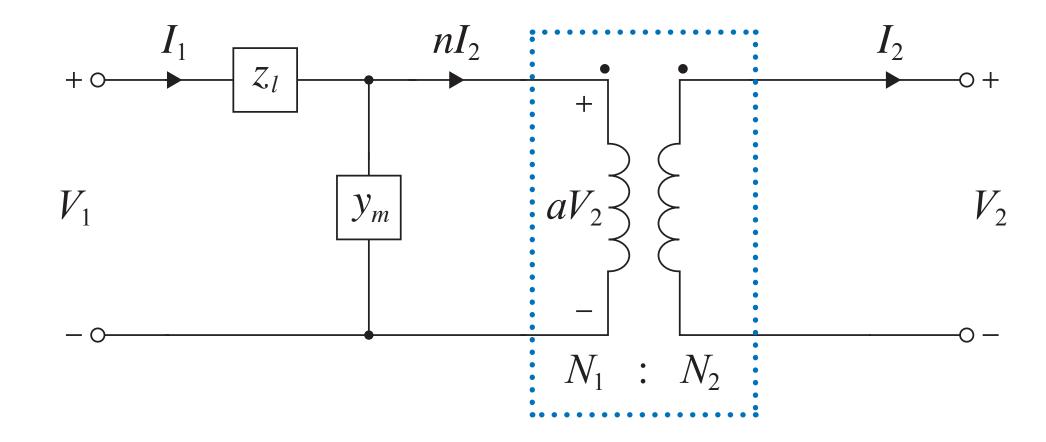

Most popular model (at least for transmission systems)

Parameters  $(z_l, y_m)$  can be determined from open and short-circuit tests

• Short-circuit test  $(V_2 := 0)$ :


$$z_l = \frac{V_{so}}{I_{sc}}$$


• Open-circuit test  $(I_2 := 0)$ :

$$\frac{1}{y_m} = \frac{V_{oc}}{I_{oc}} - \frac{V_{sc}}{I_{sc}}$$

## Parameter determination

### Zero shunt admittance $y_m = 0$

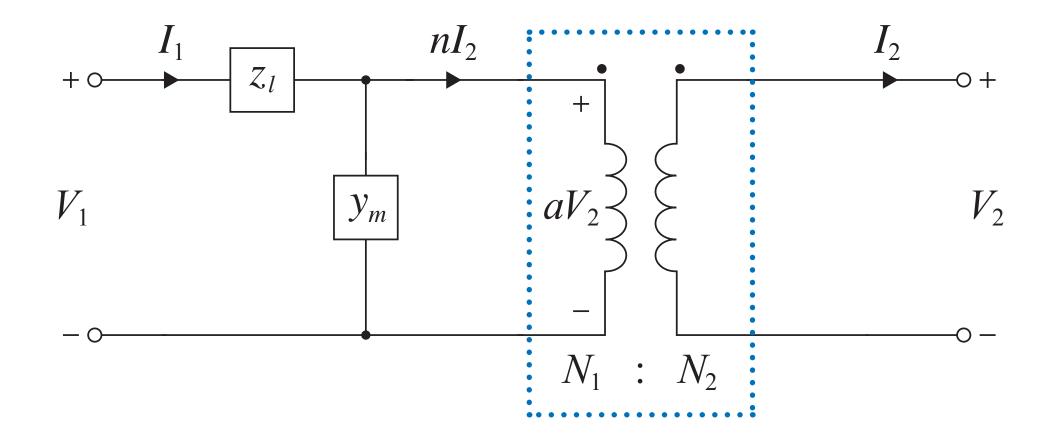

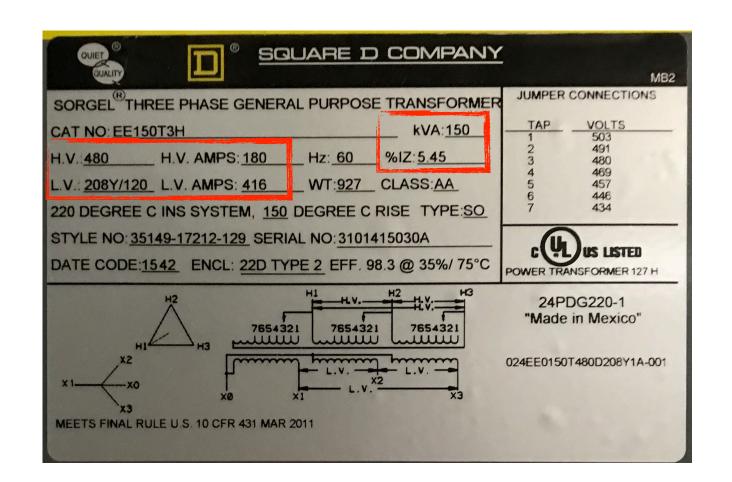


When  $y_m = 0$ , parameter  $z_l$  can be determined from standard 3-phase transformer ratings:

- . Rated primary line-to-line voltage  $\left|V_{\mathsf{pri}}\right|$
- . Rated primary line current  $\left|I_{\mathsf{pri}}\right|$
- Impedance voltage  $\beta$  on the primary side, per phase, as % of rated primary voltage


 $\beta$  : voltage needed on the primary side to produce rated primary current across each single-phase transformer is  $\beta\times$  rated primary voltage

#### Circuit models

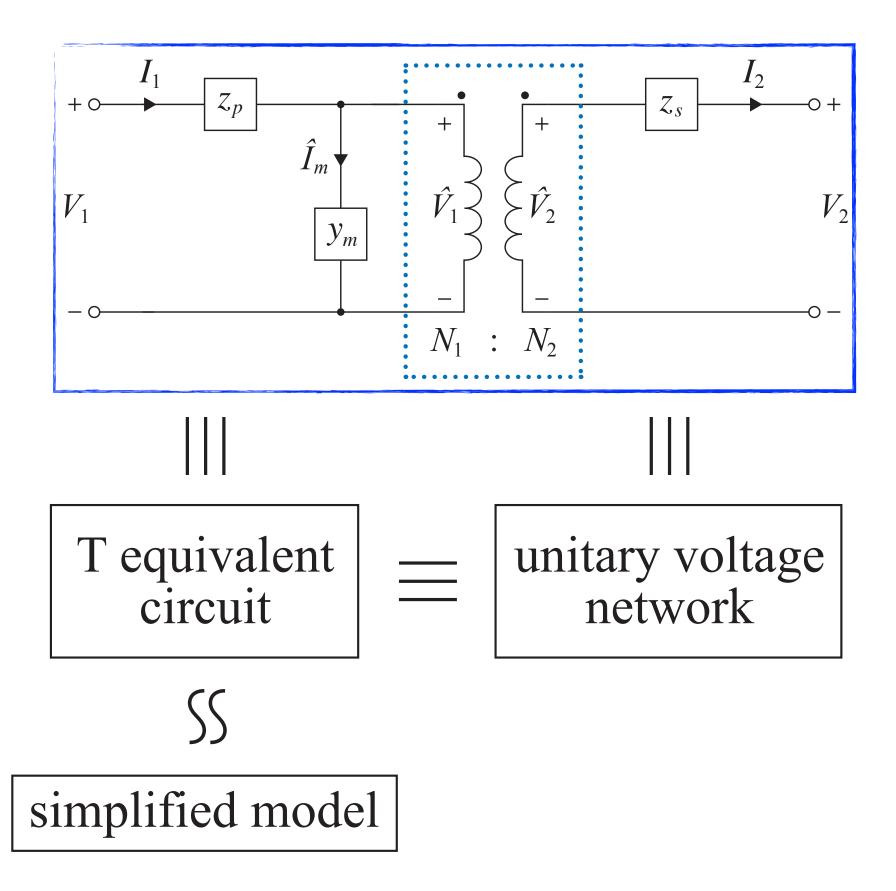

# Unitary voltage network

### Single-phase 2-winding transformer

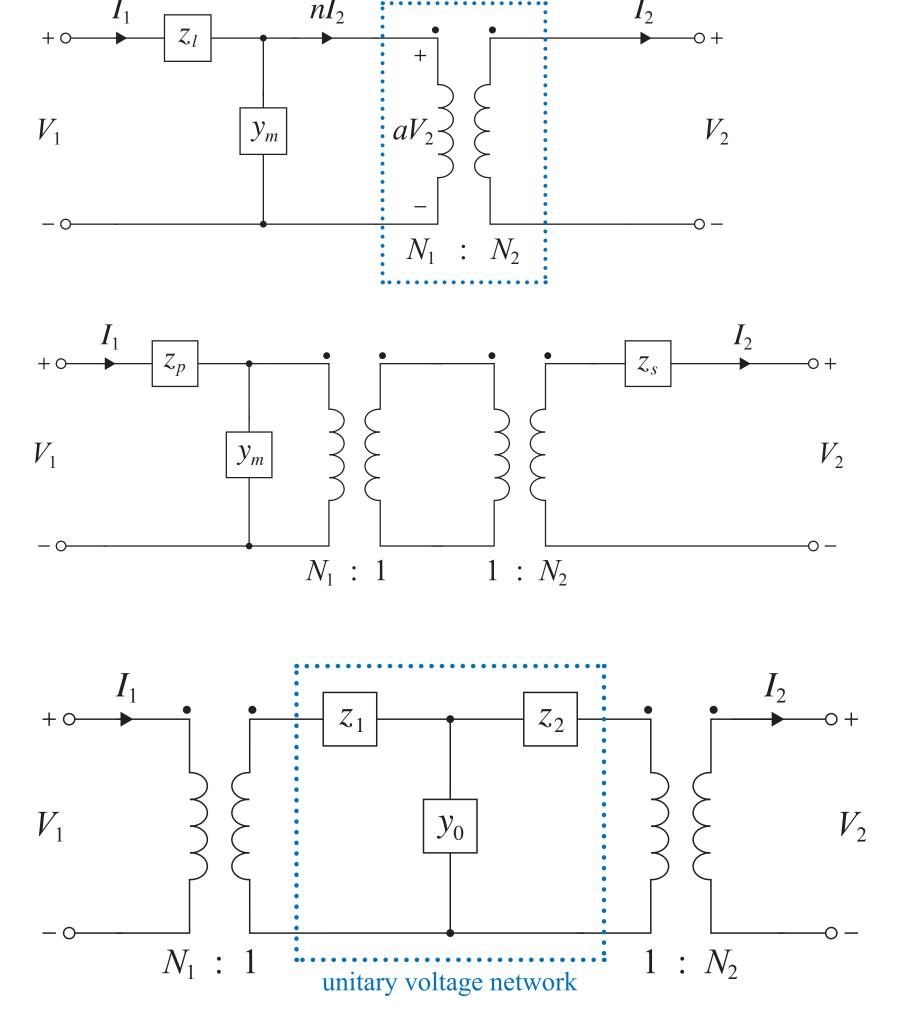



ref imp & adm across ideal transformers

#### UVN-based model


- Unitary voltage network (UVN) connecting 2 ideal transformers
- Equivalent to T equivalent circuit
- Simplified model is an approximation

#### Advantages

- UVN can be generalized to incorporate multiple windings, e.g., split-phase transformers
- Ideal transformers on both ends can be connected in various ways, e.g., 3-phase transformers in  $Y/\Delta$  configurations, non-standard transformers

# Single-phase transformer

### Unitary voltage network

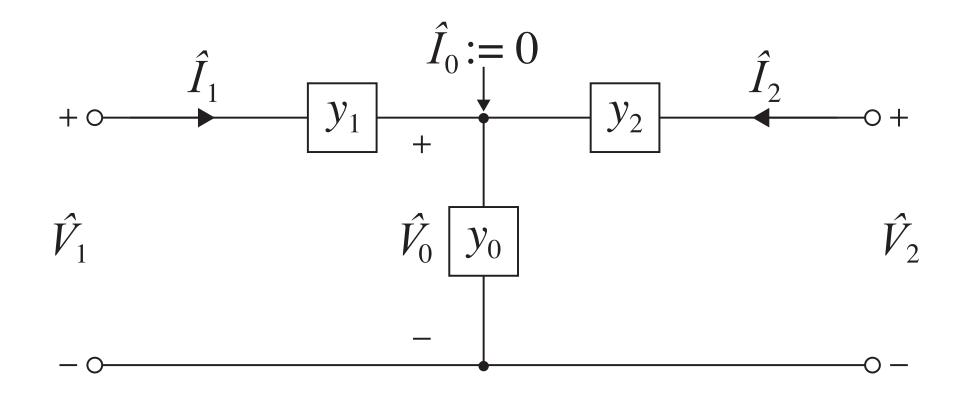

$$\hat{I}_1 = y_1(\hat{V}_1 - \hat{V}_0), \qquad \hat{I}_2 = y_2(\hat{V}_2 - \hat{V}_0)$$

$$y_0\hat{V}_0 = \hat{I}_0 + \hat{I}_1 + \hat{I}_2$$

Admittance matrix


$$\begin{bmatrix} \hat{I}_0 \\ \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \begin{bmatrix} y_0 + y_1 + y_2 & -y_1 & -y_2 \\ -y_1 & y_1 & 0 \\ -y_2 & 0 & y_2 \end{bmatrix} \begin{bmatrix} \hat{V}_0 \\ \hat{V}_1 \\ \hat{V}_2 \end{bmatrix}$$

Since  $\hat{I}_0 = 0$ , can eliminate  $\hat{U}_0$  to obtain Kron reduced admittance matrix

$$\begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \end{bmatrix} = \underbrace{\frac{1}{\sum_i y_i} \begin{bmatrix} y_1(y_0 + y_2) & -y_1 y_2 \\ -y_1 y_2 & y_2(y_0 + y_1) \end{bmatrix}}_{Y_{\text{uvn}}} \begin{bmatrix} \hat{V}_1 \\ \hat{V}_2 \end{bmatrix}$$

# Single-phase transformer

#### External model: admittance matrix

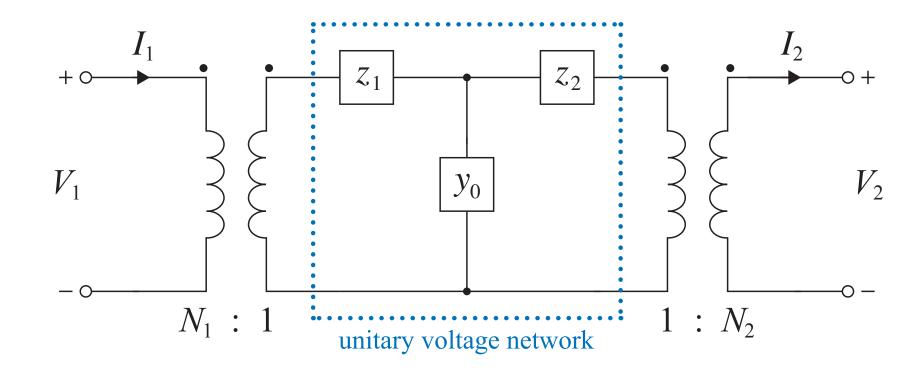

$$\begin{bmatrix} \hat{I}_{1} \\ \hat{I}_{2} \end{bmatrix} = \underbrace{\frac{1}{\sum_{i} y_{i}} \begin{bmatrix} y_{1}(y_{0} + y_{2}) & -y_{1}y_{2} \\ -y_{1}y_{2} & y_{2}(y_{0} + y_{1}) \end{bmatrix}}_{Y_{uvn}} \begin{bmatrix} \hat{V}_{1} \\ \hat{V}_{2} \end{bmatrix}$$

Let

$$I := \begin{bmatrix} I_1 \\ -I_2 \end{bmatrix}, \quad V := \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$
 $M := \begin{bmatrix} 1/N_1 & 0 \\ 0 & 1/N_2 \end{bmatrix}$ 

Conversion between internal vars & terminal vars across ideal transformers

$$\hat{U} = MV$$
,  $\hat{J} = M^{-1}I$ 

Hence, external model:

$$I = (MY_{\mathsf{uvn}}M) V$$


# Application of UVN model

### **Common distribution transformers**

line-to-line voltage (kV)	phase voltage (kV)	total power (MVA)
$\ V_{ab}\ $	$ V_{an} $	$ S_{3\phi} $
4.8	2.8	3.3
12.47	7.2	8.6
22.9	13.2	15.9
34.5	19.9	23.9

## Distribution transformer

### **Example: split-phase**

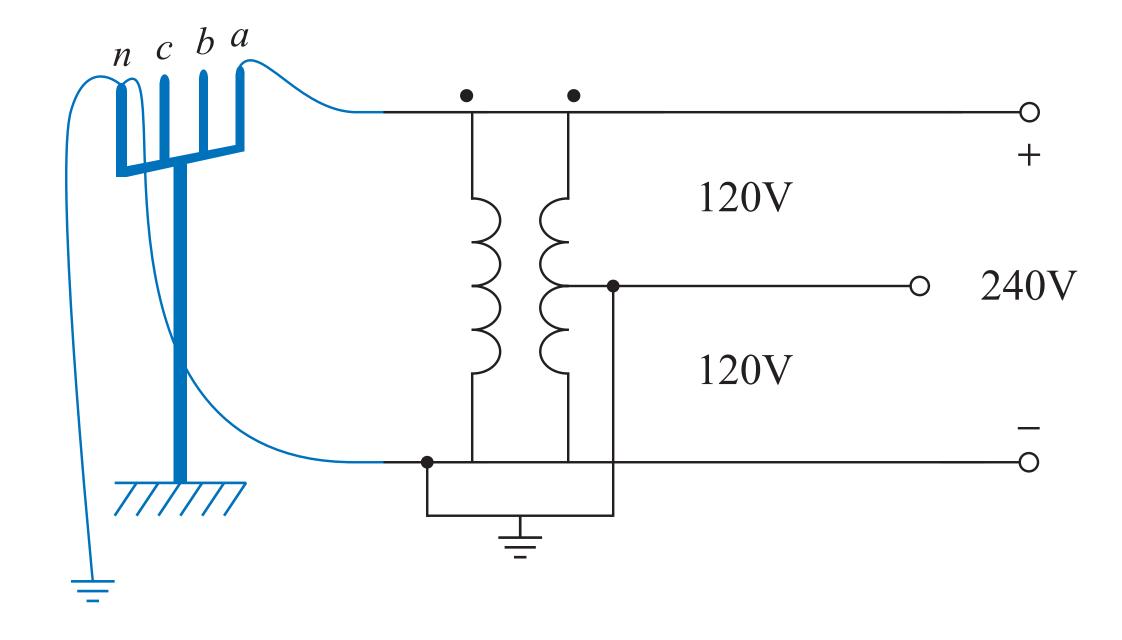


#### Common deployment in US


- Single phase
- Split-phase 120/240 V

# Multi-winding transformers

### **Example: split-phase**

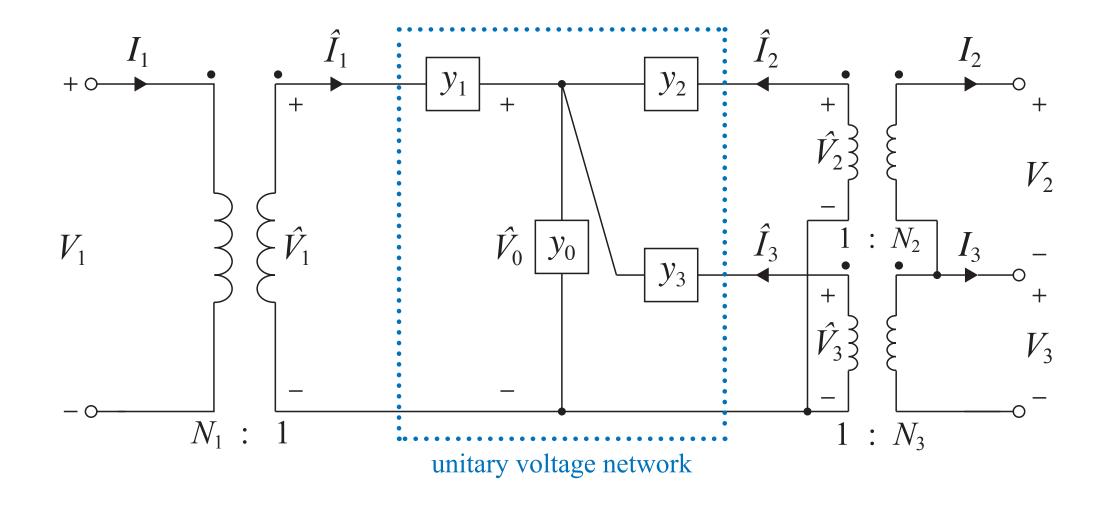
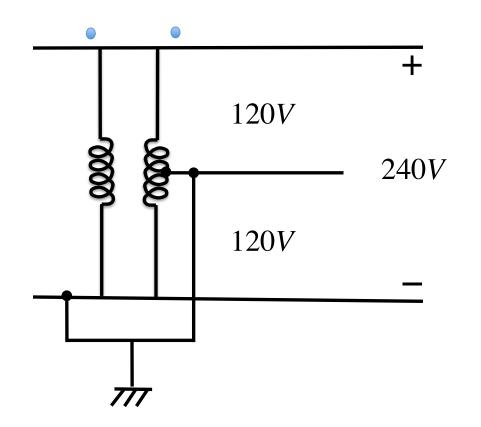
$$\begin{bmatrix} \hat{I}_0 \\ \hat{I}_1 \\ \hat{I}_2 \\ \hat{I}_3 \end{bmatrix} = \begin{bmatrix} \sum_{i=0}^3 & -y_1 & -y_2 & -y_3 \\ -y_1 & y_1 & 0 & 0 \\ -y_2 & 0 & y_2 & 0 \\ -y_3 & 0 & 0 & y_3 \end{bmatrix} \begin{bmatrix} \hat{V}_0 \\ \hat{V}_1 \\ \hat{V}_2 \\ \hat{V}_3 \end{bmatrix}$$




UVN: Kron-reduced admittance matrix

$$\begin{bmatrix} \hat{I}_1 \\ \hat{I}_2 \\ \hat{I}_3 \end{bmatrix} = \underbrace{\frac{1}{\sum_i y_i}}_{i} \begin{bmatrix} y_1(y_0 + y_2 + y_3) & -y_1y_2 & -y_1y_3 \\ -y_2y_1 & y_2(y_0 + y_1 + y_3) & -y_2y_3 \\ -y_3y_1 & -y_3y_2 & y_3(y_0 + y_1 + y_2) \end{bmatrix} \begin{bmatrix} \hat{V}_1 \\ \hat{V}_2 \\ \hat{V}_3 \end{bmatrix}$$

# Multi-winding transformers

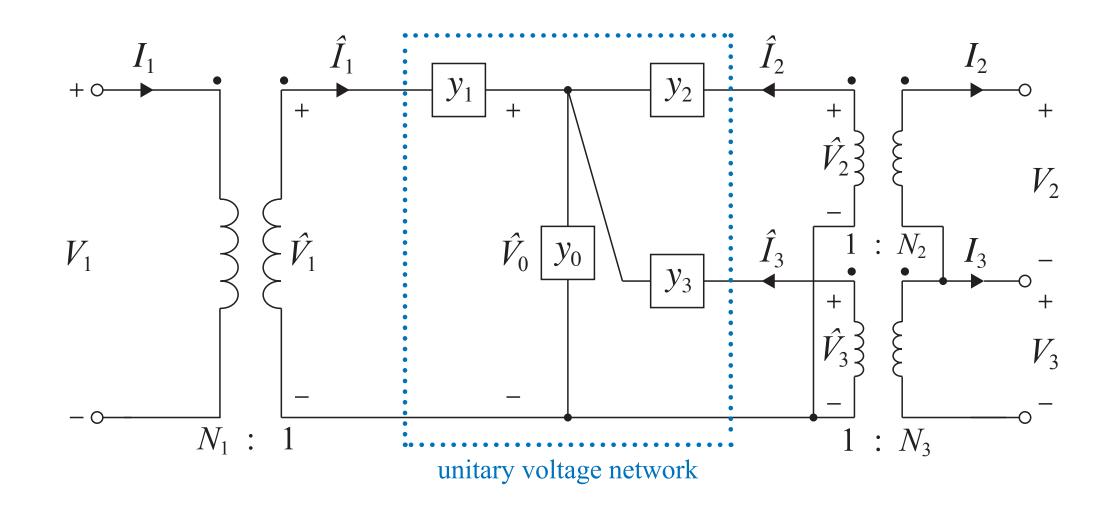
#### **Example: split-phase transformer**



Let

$$I := egin{bmatrix} I_1 \ -I_2 \ -I_3 \end{bmatrix}, \quad V := egin{bmatrix} V_1 \ V_2 \ V_3 \end{bmatrix}$$
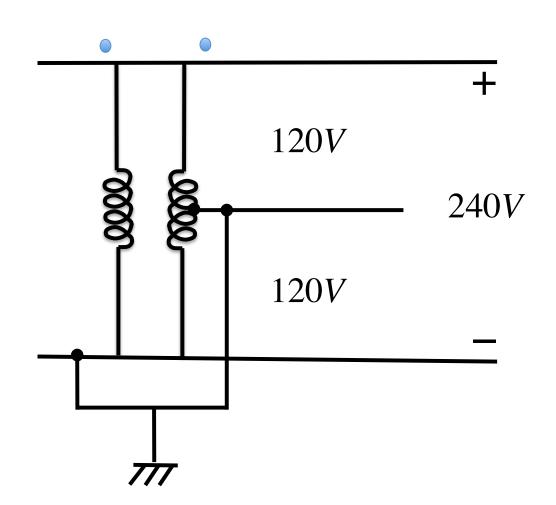
$$M := \begin{bmatrix} 1/N_1 & 0 & 0 \\ 0 & 1/N_2 & 0 \\ 0 & 0 & 1/N_3 \end{bmatrix}$$




Conversion between internal vars & terminal vars across ideal transformers:  $\hat{V} = MV$  and

$$\hat{I} = M^{-1} \begin{bmatrix} I_1 \\ -I_2 \\ -I_2 - I_3 \end{bmatrix} =: M^{-1}AI \text{ where } A := \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \end{bmatrix}$$

# Multi-winding transformers


### **Example: split-phase transformer**

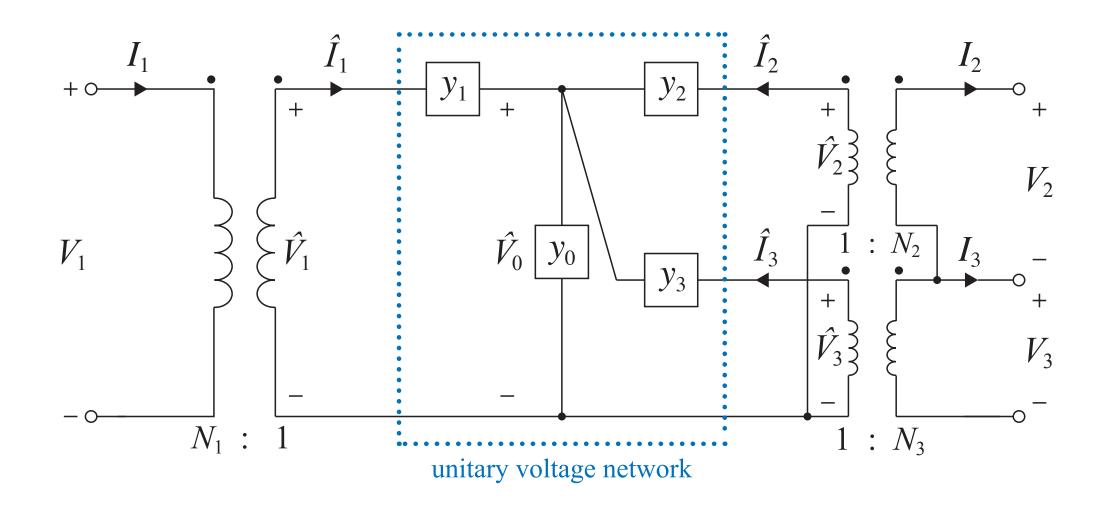

Let

$$I := \begin{bmatrix} I_1 \\ -I_2 \\ -I_3 \end{bmatrix}, \quad V := \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$
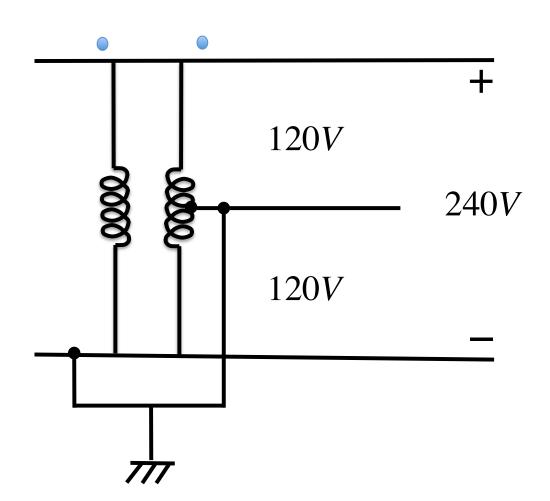
$$M := \begin{bmatrix} 1/N_1 & 0 & 0 \\ 0 & 1/N_2 & 0 \\ 0 & 0 & 1/N_3 \end{bmatrix}$$



Eliminate internal vars  $(\hat{I}, \hat{V})$  from

$$\hat{V} = Y_{\text{UVN}}\hat{I}, \quad \hat{V} = MV, \quad \hat{I} = M^{-1}AI$$


External model:

$$I = A^{-1} (MY_{\mathsf{uvn}} M) V$$

## Outline


- 1. Single-phase transformer
- 2. Balanced three-phase transformers
  - Ideal transformers
  - Nonideal transformers
- 3. Equivalent impedance
- 4. Per-phase analysis
- 5. Per-unit normalization

### Connectivity

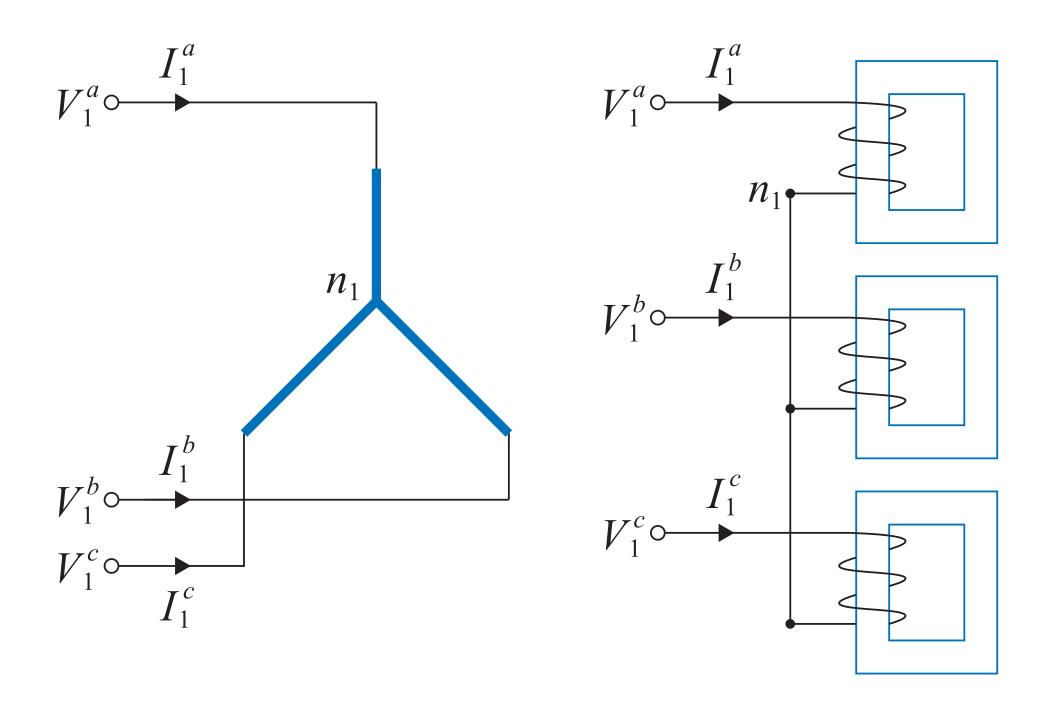

(a) Primary winding in Y configuration


### Connectivity

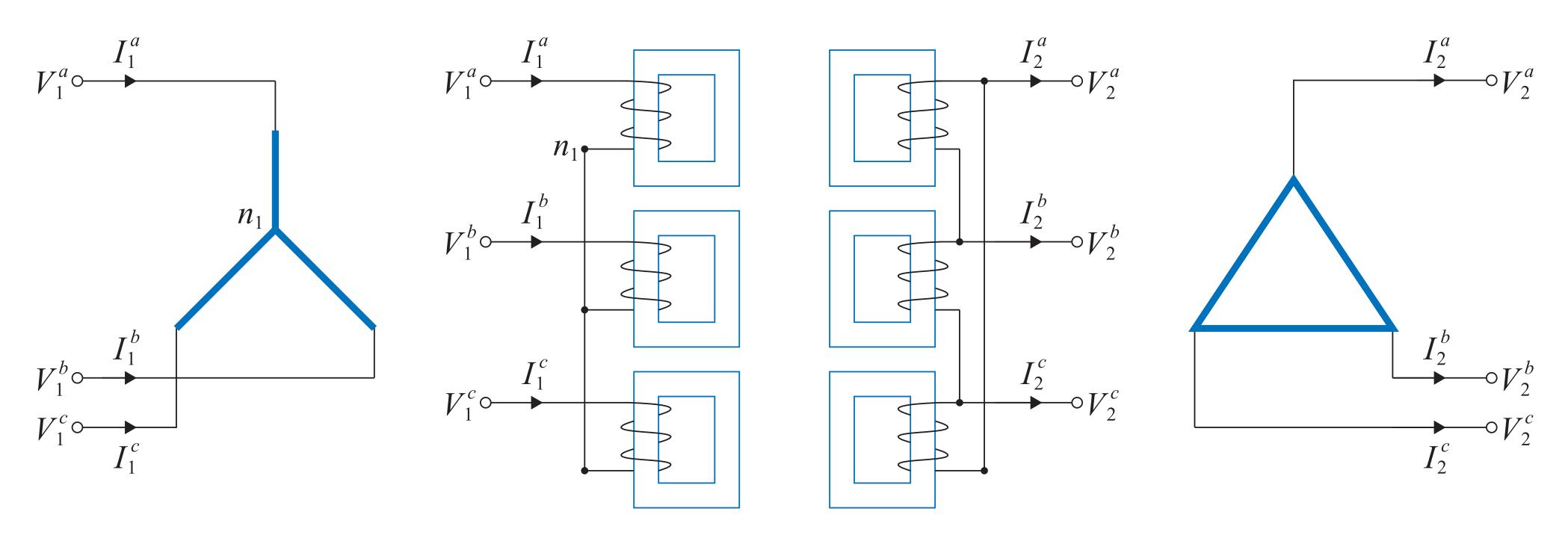



(a) Primary winding in Y configuration


(b) Secondary winding in  $\Delta$  configuration

## Configurations

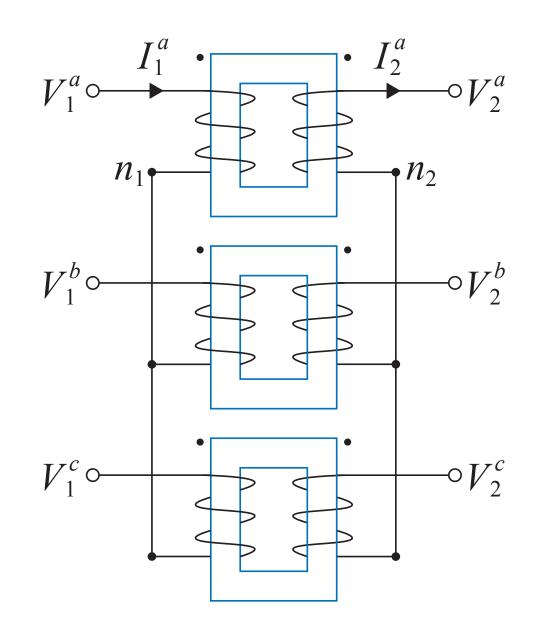

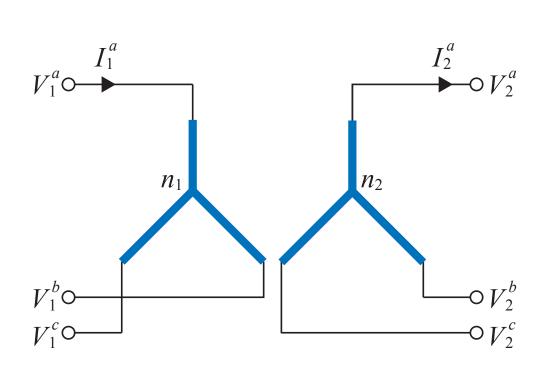

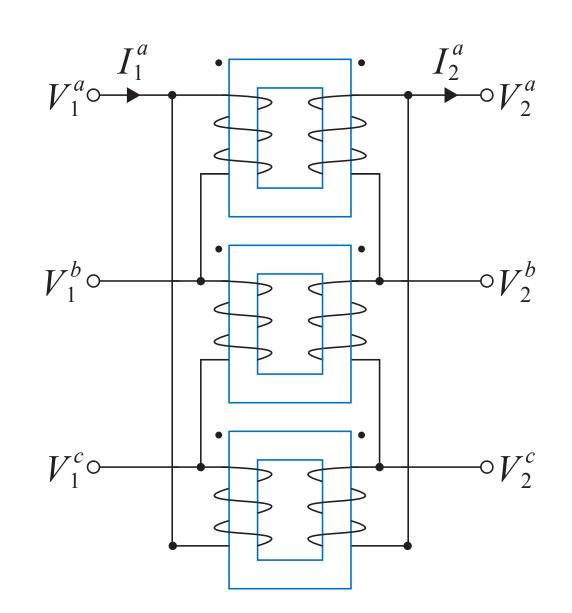


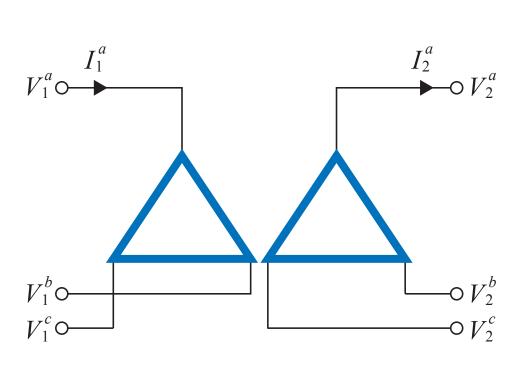



YY


 $\Delta \Delta$ 

### Configurations

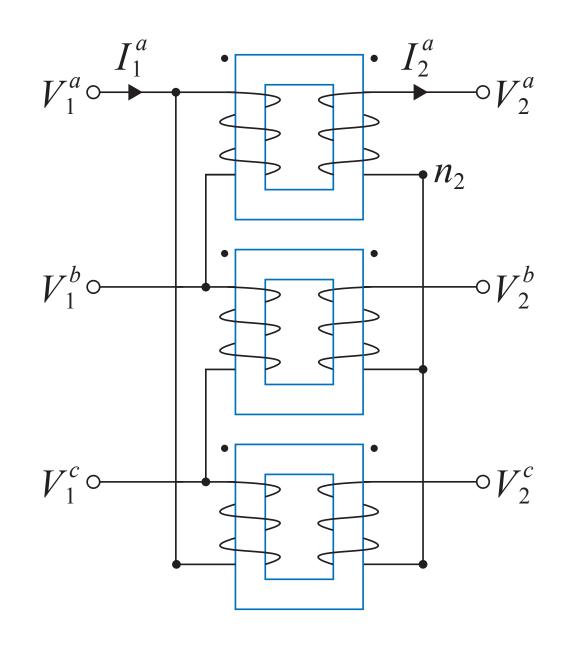

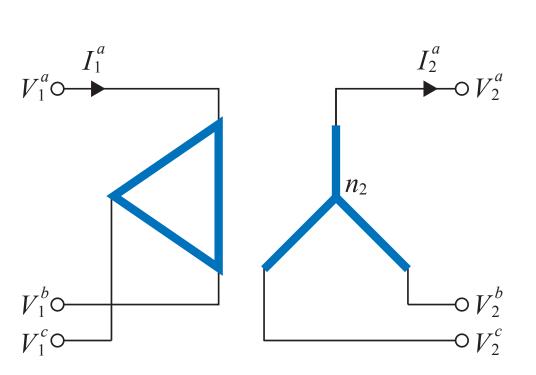

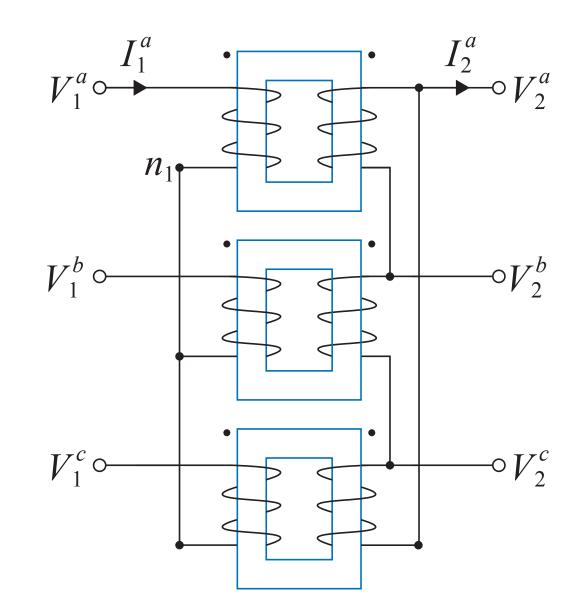

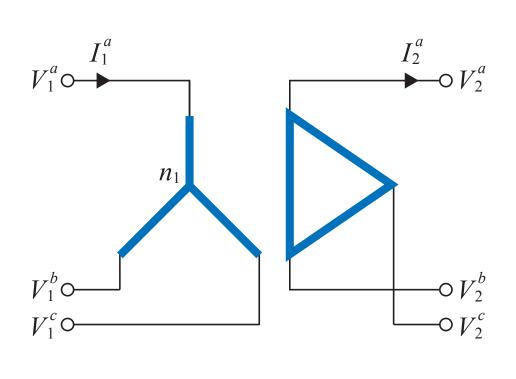

 $\Delta Y$ 

 $Y\Delta$ 

# Ideal transformers Summary

Property	Gain
Voltage gain Current gain Power gain Sec z <sub>l</sub> referred to pri	$\frac{K(n)}{\frac{1}{\bar{K}(n)}}$ $\frac{1}{z_{l}}$ $\frac{z_{l}}{ K(n) ^{2}}$

Configuration	Gain
YY	$K_{YY}(n) := n$
$\Delta\Delta$	$K_{\Delta\Delta}(n) := n$
$\Delta Y$	$K_{\Delta Y}(n) := \sqrt{3}n \ e^{\mathbf{i}\pi/6}$
$Y\Delta$	$K_{Y\Delta}(n) := \frac{n}{\sqrt{3}} e^{-\mathbf{i}\pi/6}$

# Per-phase equivalent

YY-equivalent of a balanced 3-phase transformer: balanced YY transformer with same external model, i.e., same voltage gain K(n)

• Single-phase equivalent: phase a model of YY-equivalent


$$YY: \quad V_{2}^{\text{line}} = (1-\alpha)V_{2}^{Y} = nV_{1}^{\text{line}}, \quad I_{2} = aI_{1}^{Y} \quad \Rightarrow \quad K_{YY}(n) := n$$

$$\Delta\Delta: \quad V_{2}^{\text{line}} = V_{2}^{\Delta} = nV_{1}^{\text{line}}, \quad I_{2} = aI_{1}^{Y} \quad \Rightarrow \quad K_{\Delta\Delta}(n) := n$$

$$\Delta Y: \quad V_{2}^{\text{line}} = (1-\alpha)V_{2}^{Y} = (1-\alpha)nV_{1}^{\text{line}}, \quad I_{2} = \frac{a}{1-\bar{\alpha}}I_{1} \quad \Rightarrow \quad K_{\Delta Y}(n) := (1-\alpha)n$$


$$\Delta\Delta: \quad V_{2}^{\text{line}} = V_{2}^{\Delta} = \frac{n}{1-\alpha}V_{1}^{\text{line}}, \quad I_{2} = -(1-\alpha^{2})I_{2}^{\Delta} = (1-\bar{\alpha})aI_{1} \quad \Rightarrow \quad K_{Y\Delta}(n) := n/(1-\alpha)$$

### YY configuration

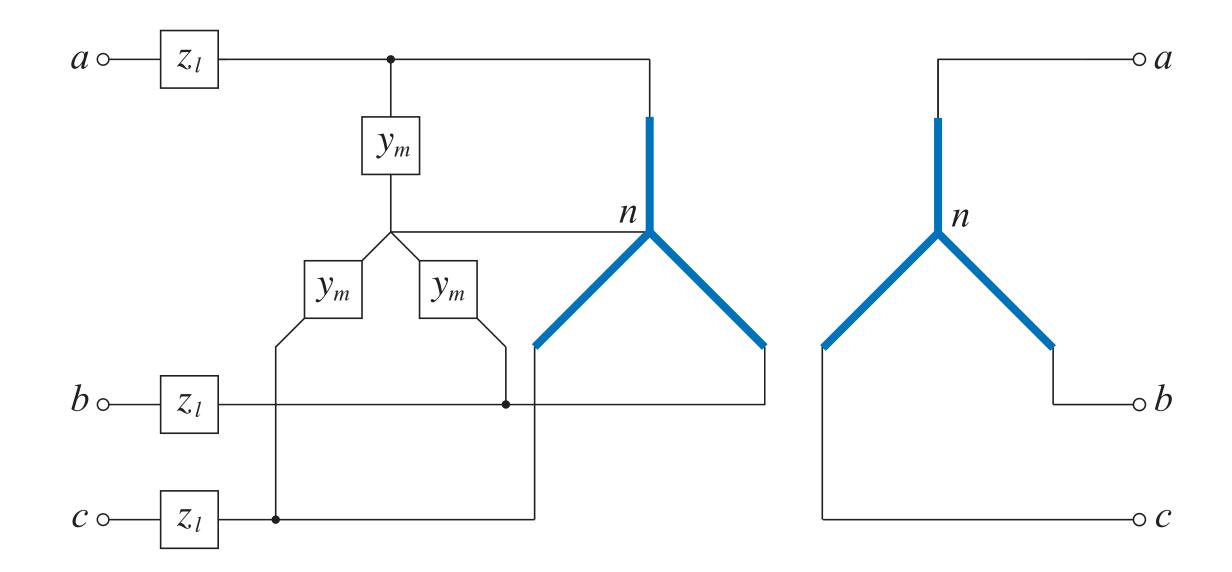


(a) YY configuration

#### YY configuration

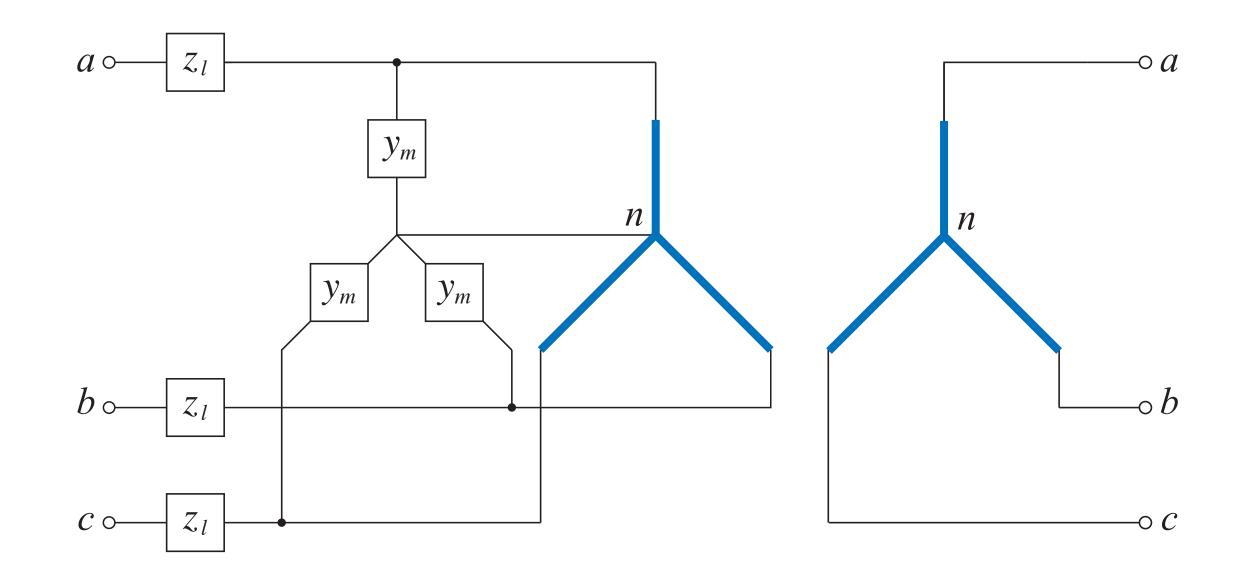


(a) YY configuration

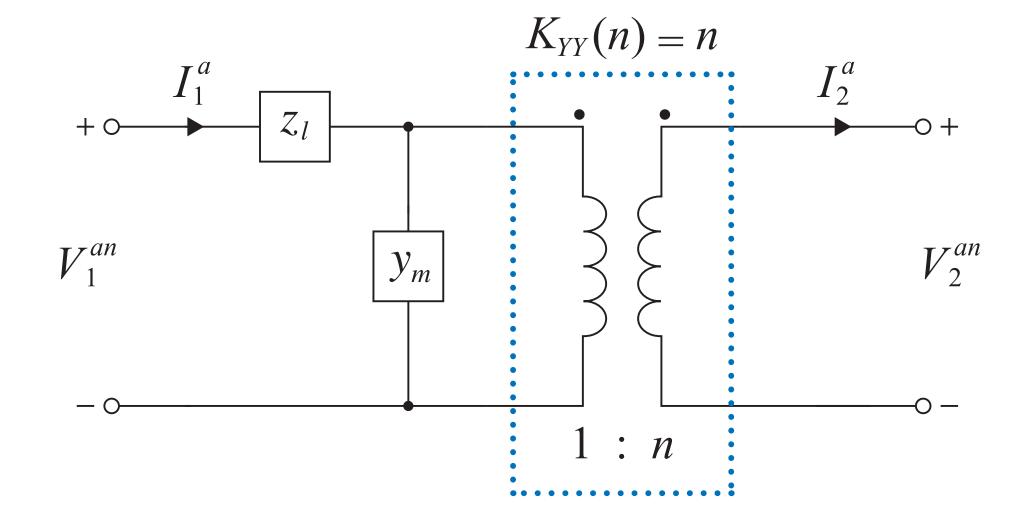


(b) Per-phase circuit

### $\Delta\Delta$ configuration

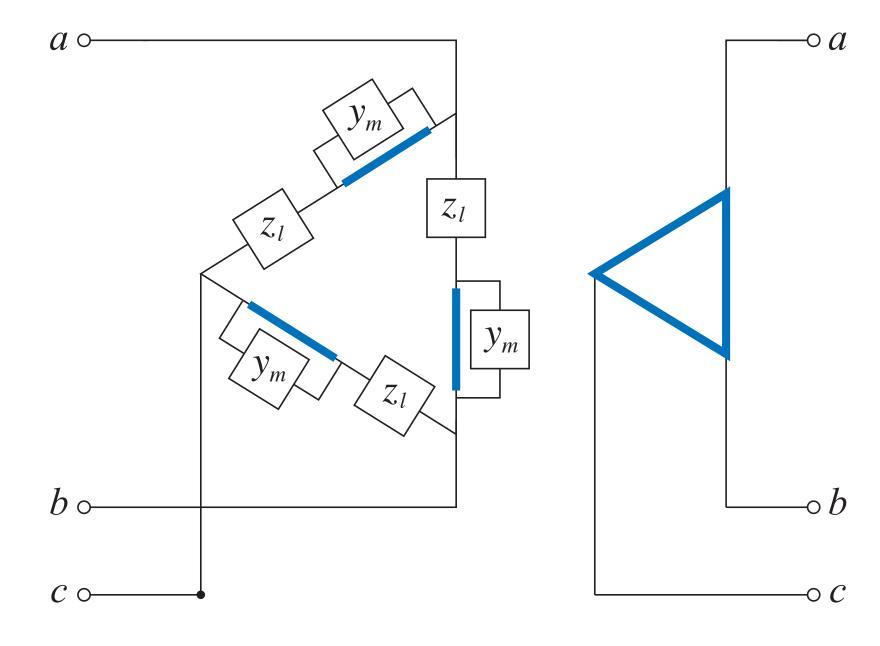


(a)  $\Delta\Delta$  configuration

#### $\Delta\Delta$ configuration

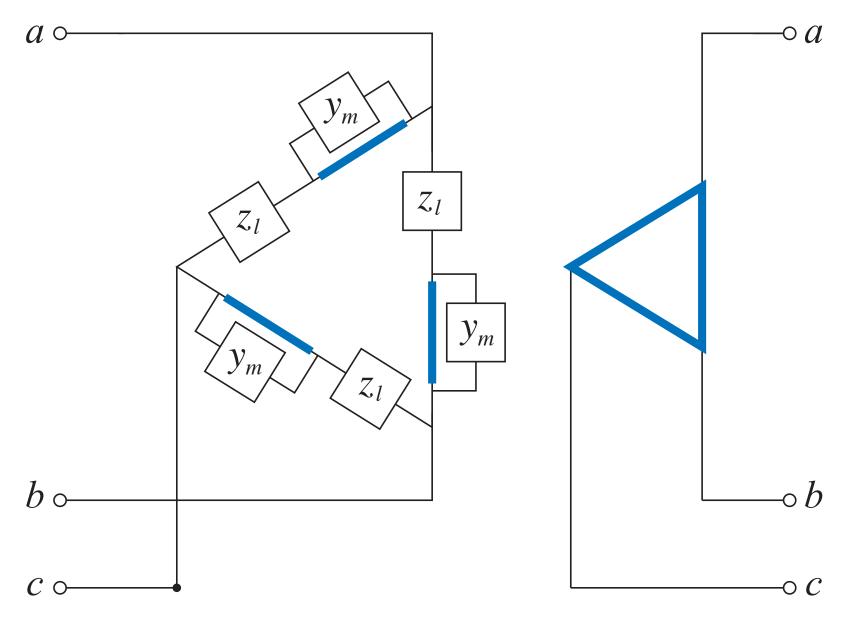


(a)  $\Delta\Delta$  configuration

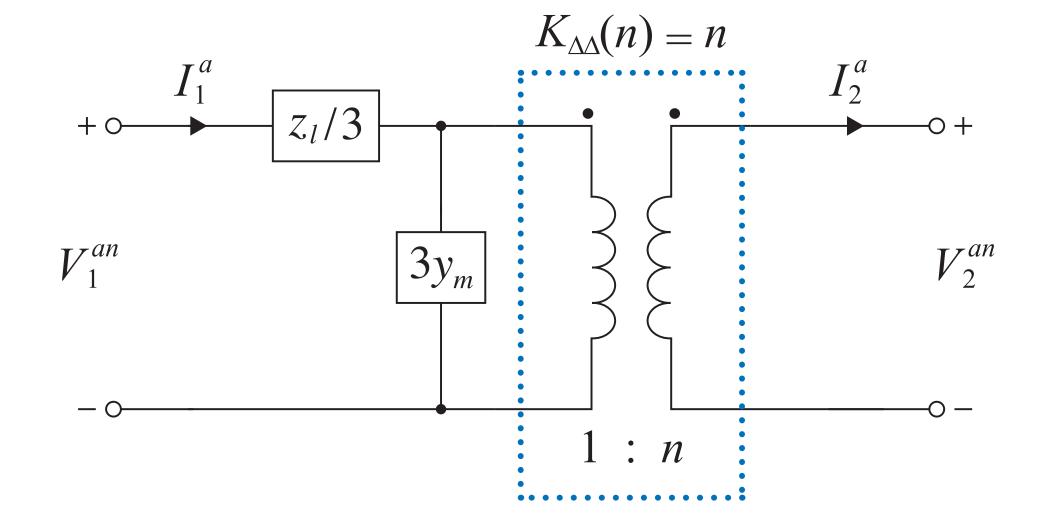


(b) Per-phase circuit

### $\Delta Y$ configuration

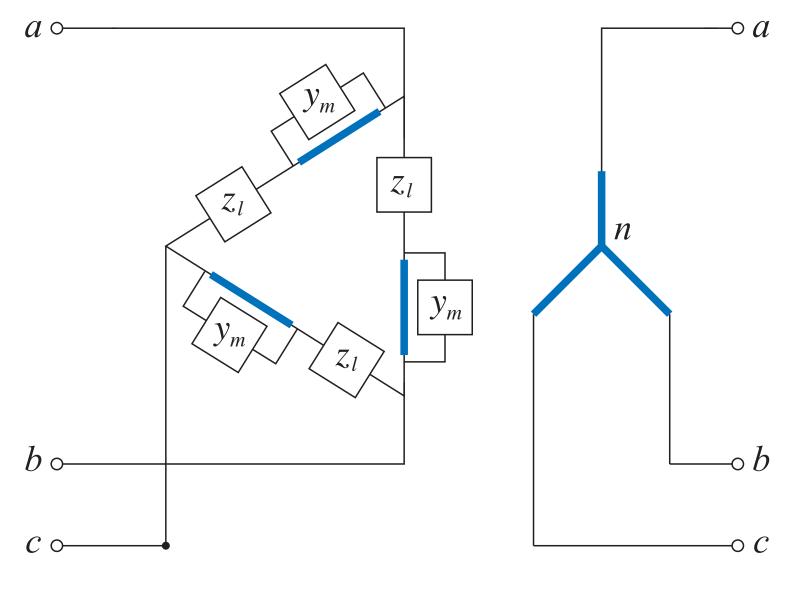


(a)  $\Delta Y$  configuration

#### $\Delta Y$ configuration

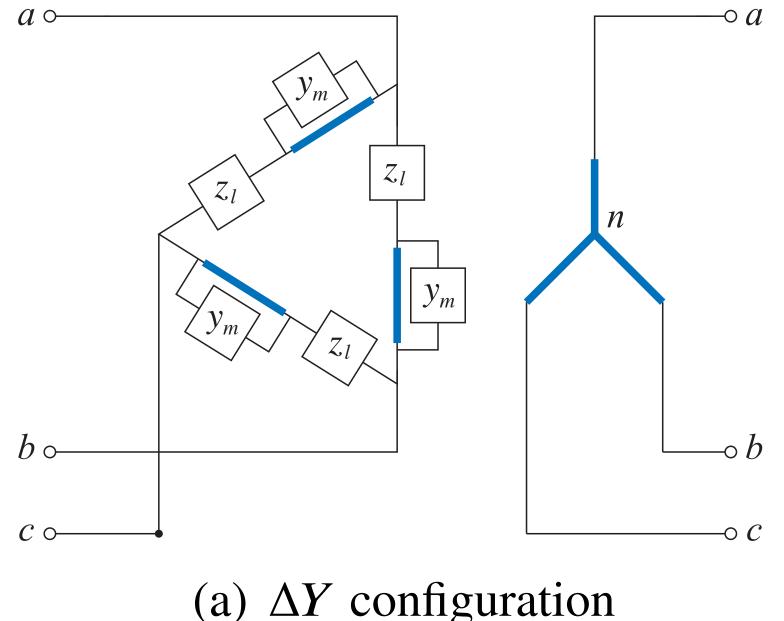


(a)  $\Delta Y$  configuration

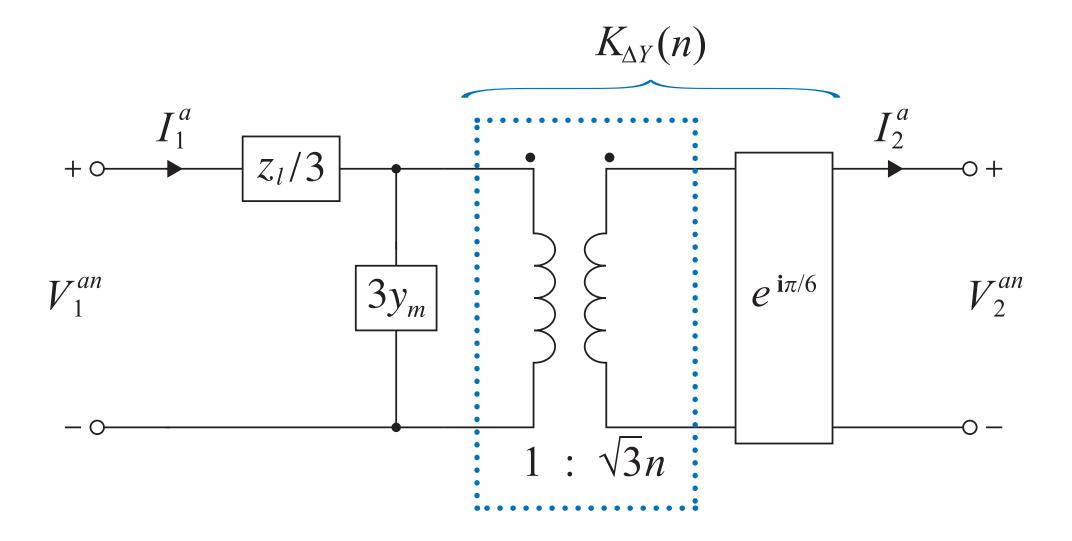


(b) Per-phase circuit

### $Y\Delta$ configuration

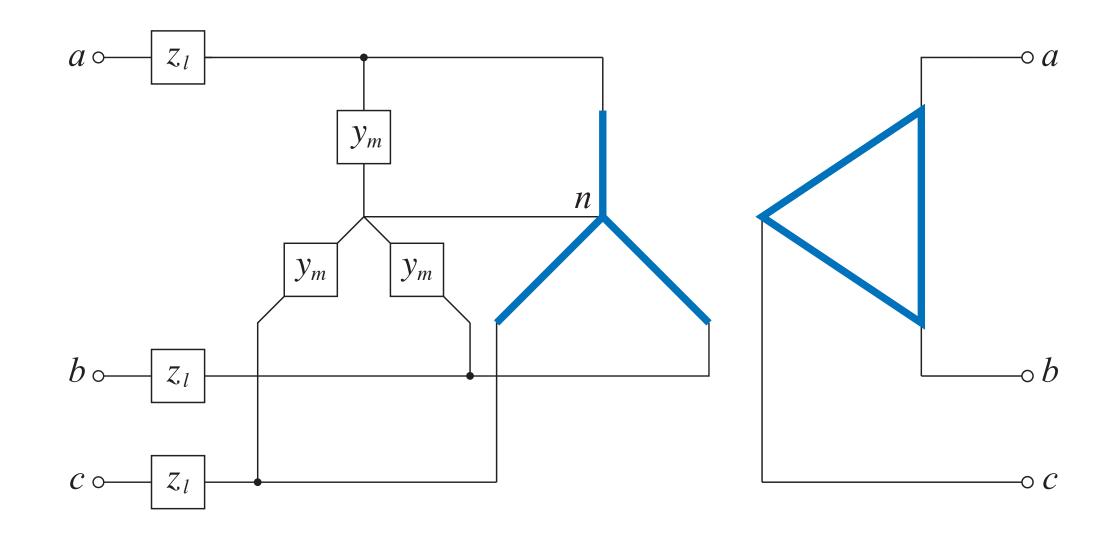

(a)  $Y\Delta$  configuration

#### $Y\Delta$ configuration

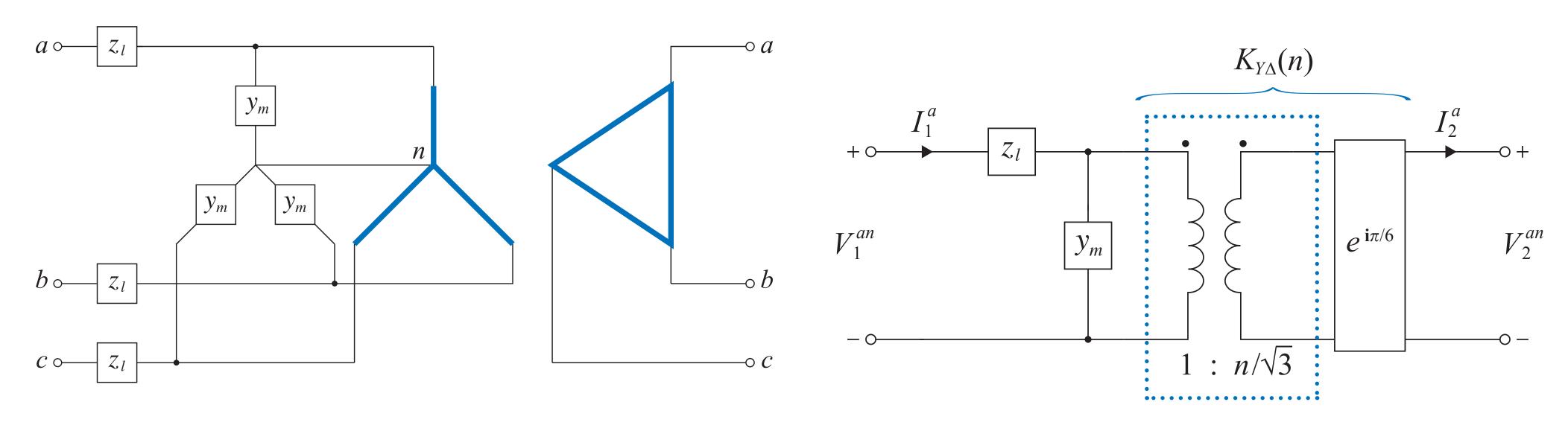

(a)  $Y\Delta$  configuration

(b) Per-phase circuit


## Outline

- 1. Single-phase transformer
- 2. Balanced three-phase transformers
- 3. Equivalent impedance
  - Transmission matrix
  - Driving-point impedance
- 4. Per-phase analysis
- 5. Per-unit normalization
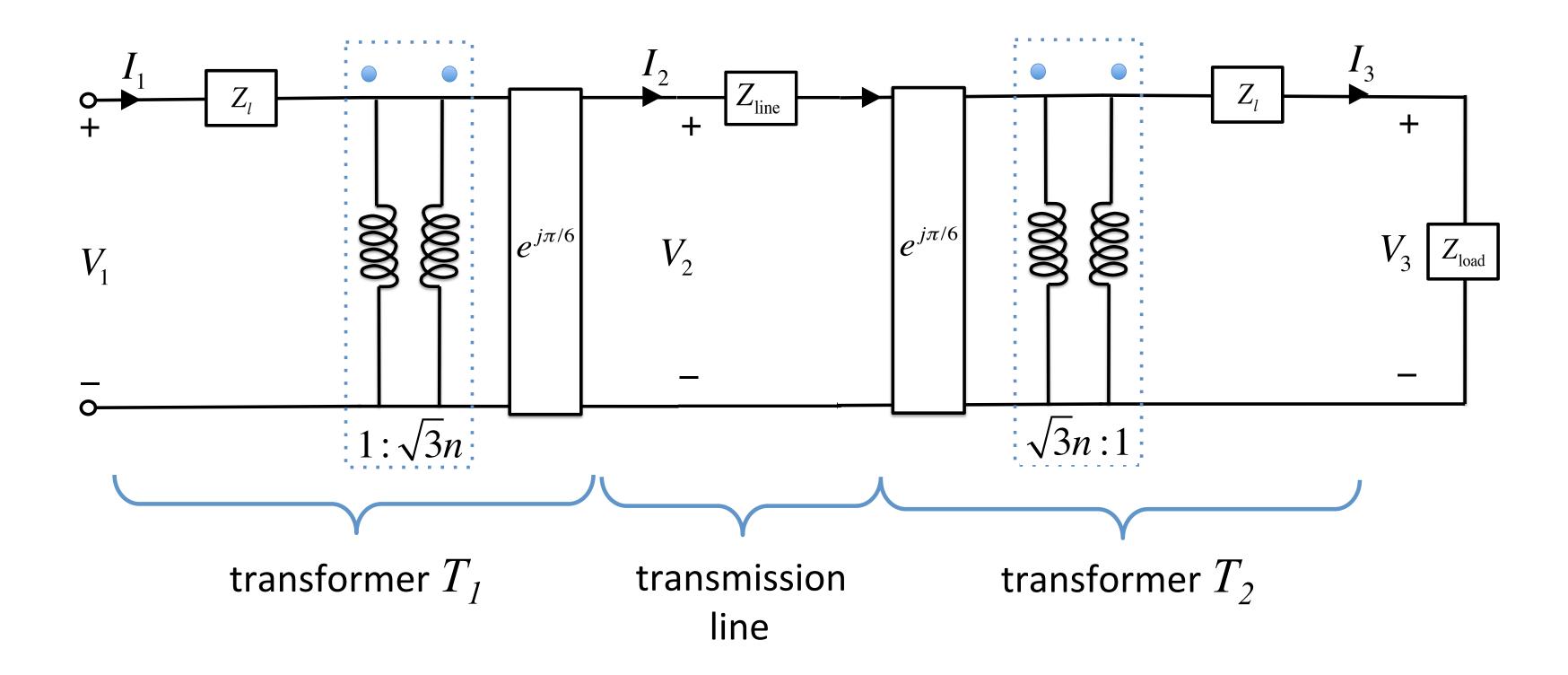
## Motivation

Short cut in analyzing circuits containing transformers

- Thevenin equivalent of impedances in series and in parallel
- Equivalent impedances in primary or secondary circuits



# Equivalent impedances

• referring  $Z_s$  in secondary to primary

$$Z_p = \frac{Z_s}{|K(n)|^2}$$

"It is equivalent to replace  $Z_{\!\scriptscriptstyle S}$  in the secondary circuit by  $Z_{\!\scriptscriptstyle p}$  in the primary circuit"

• referring  $Z_p$  in primary to secondary

$$Z_s = |K(n)|^2 Z_p$$

"It is equivalent to replace  $Z_p$  in the primary circuit by  $Z_{\!\scriptscriptstyle S}$  in the secondary circuit"

# Equivalent admittances

• referring  $Y_s$  in secondary to primary

$$Y_p = |K(n)|^2 Y_s$$

"It is equivalent to replace  $Y_{\scriptscriptstyle S}$  in the secondary circuit by  $Y_p$  in the primary circuit"

ullet referring  $Y_p$  in primary to secondary

$$Y_{s} = \frac{Y_{p}}{|K(n)|^{2}}$$


"It is equivalent to replace  $Y_p$  in the primary circuit by  $Y_{\scriptscriptstyle S}$  in the secondary circuit"

# Equivalent impedances

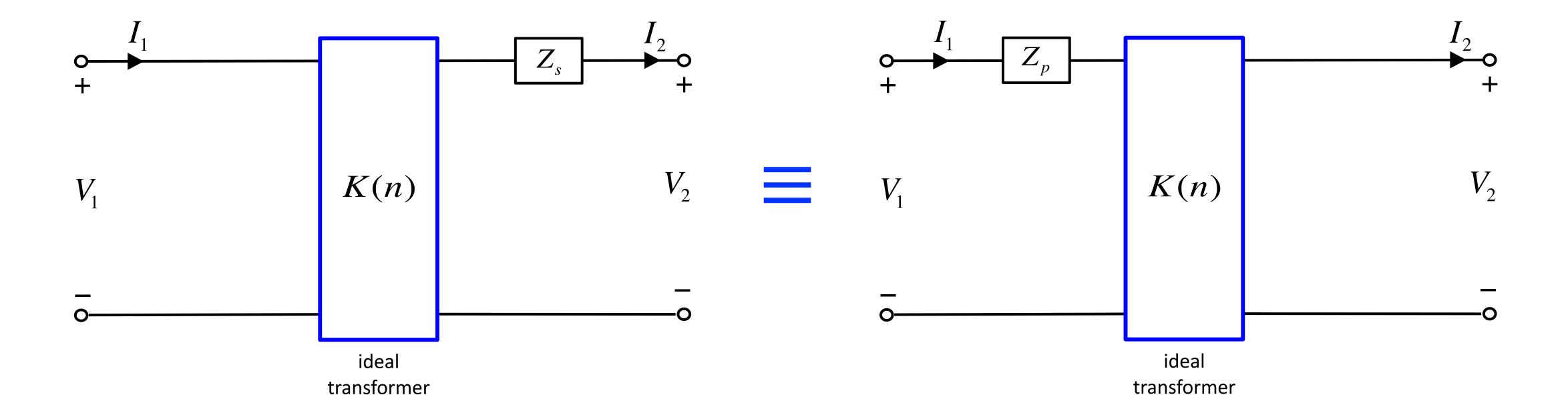
#### What is equivalence?

- Same transmission matrices
- Same driving-point impedance

This is a simple consequence of Kirchhoff's and Ohm's laws




External models (transmission matrices) of 2 circuits are equal if and only if  $Z_p = \frac{Z_s}{|K(n)|^2}$ 

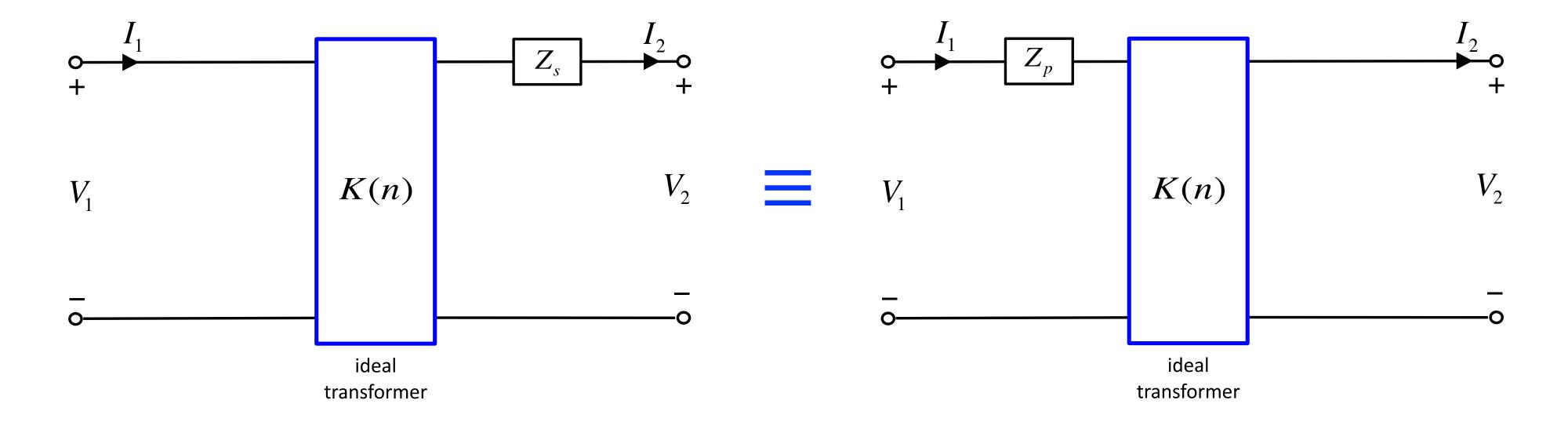


$$\begin{bmatrix} V \\ I \end{bmatrix} = \begin{bmatrix} 1 & Z_s \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$
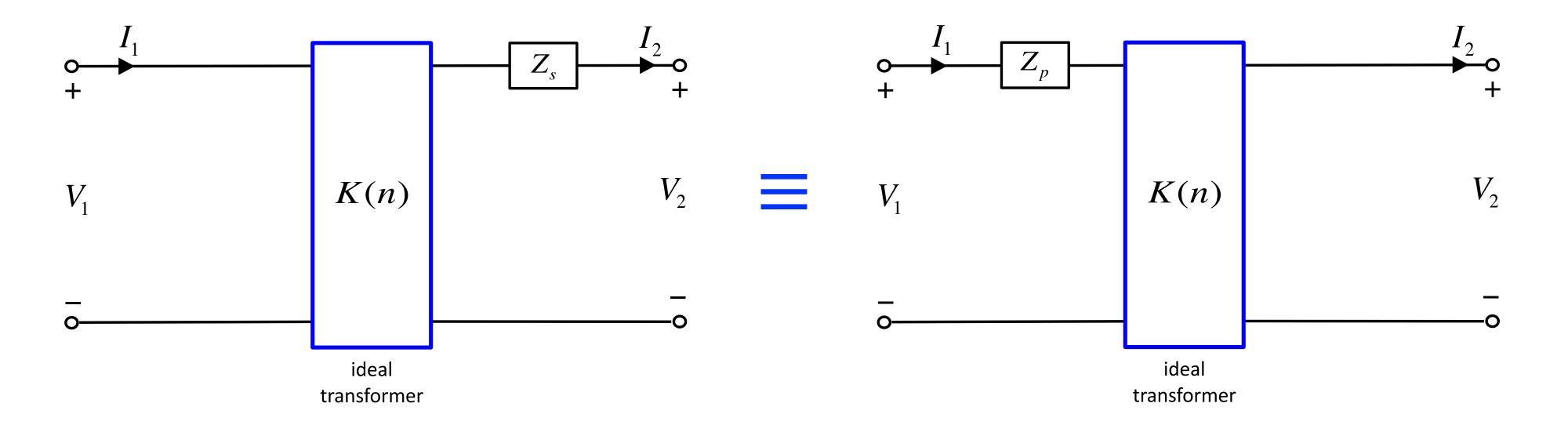
$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} K^{-1}(n) & 0 \\ 0 & K^*(n) \end{bmatrix} \begin{bmatrix} V \\ I \end{bmatrix}$$




$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} K^{-1}(n) & K^{-1}(n)Z_s \\ 0 & K^*(n) \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \qquad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} K^{-1}(n) & K^*(n)Z_p \\ 0 & K^*(n) \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

External models (transmission matrices) of 2 circuits are equal if and only if  $Z_p = \frac{Z_s}{|K(n)|^2}$ 

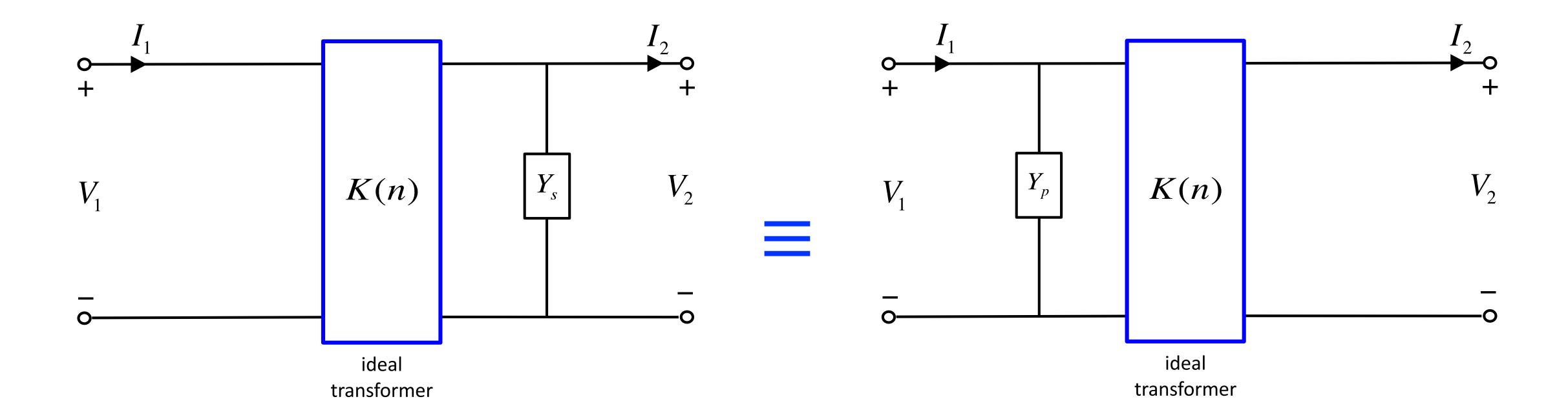

External models (transmission matrices) of 2 circuits are equal if and only if  $Y_p = |K(n)|^2 Y_s$ 

## Example

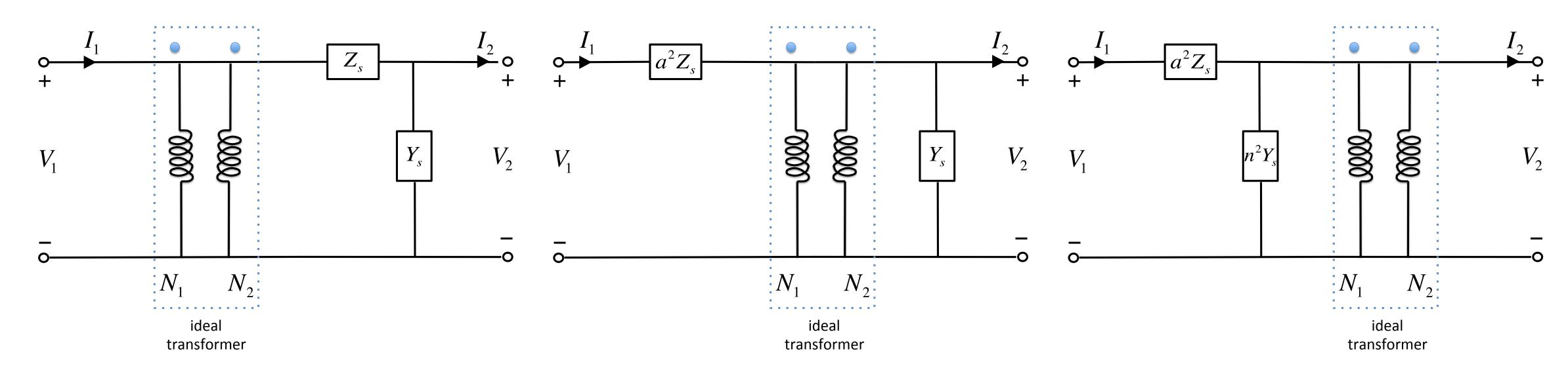


(a)  $(Z_s, Y_s)$  in the secondary circuit.

(b) Refer  $Z_s$  to the primary.


(c) Refer  $Y_s$  to the primary.

## Thevenin equivalent

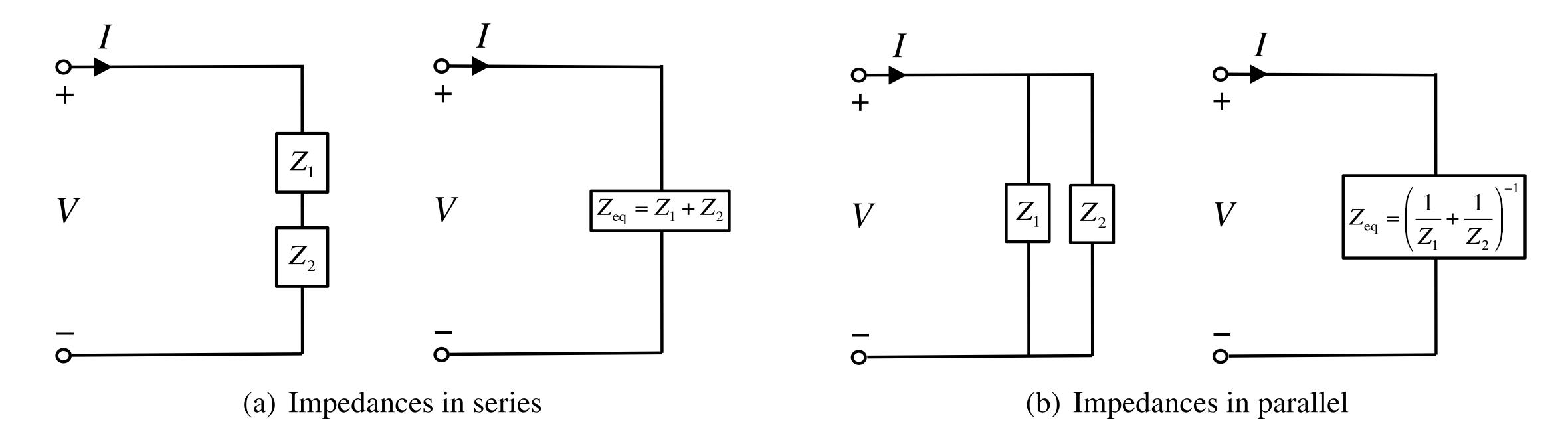


Thevenin equivalent is a short cut in analyzing circuits with impedances only

## Thevenin equivalent

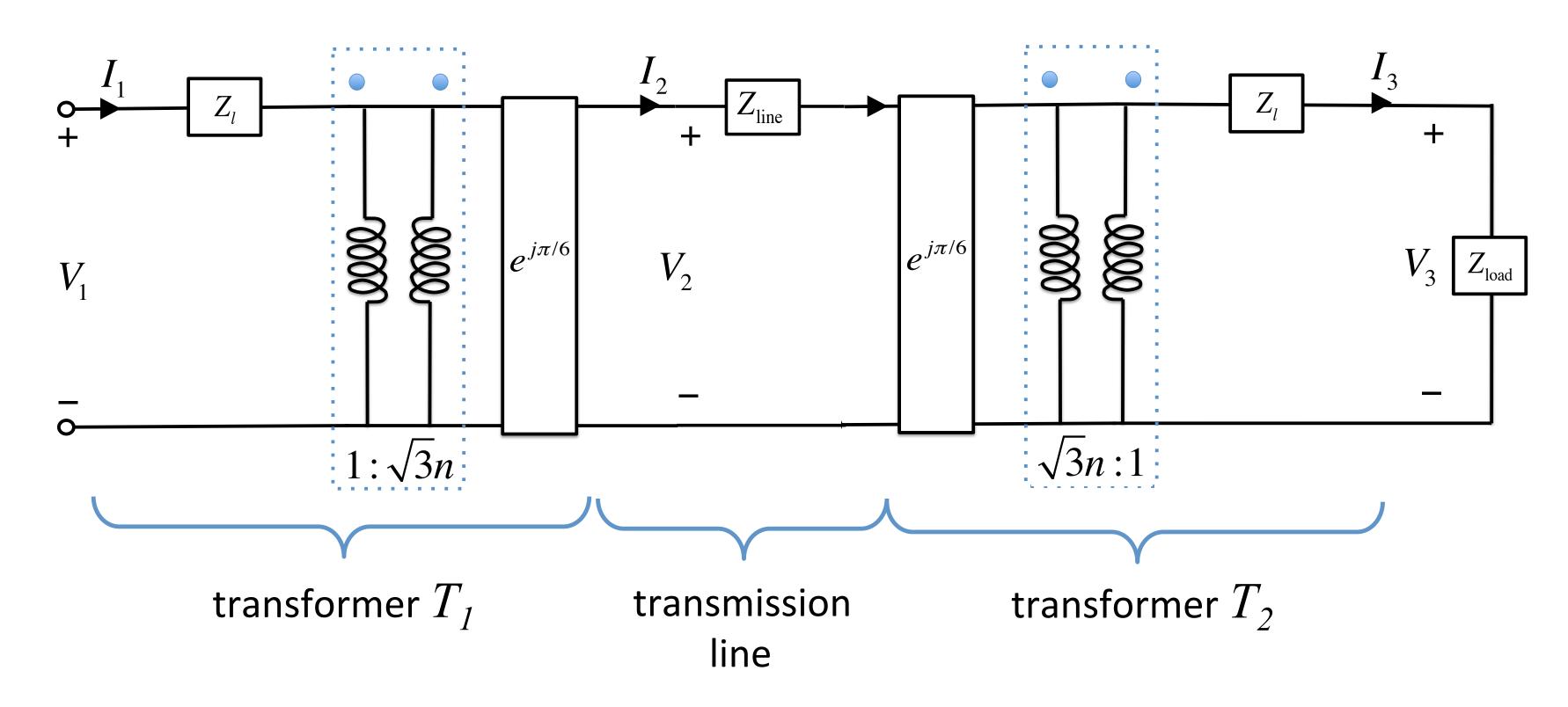

What if circuits contain both impedance and transformers?

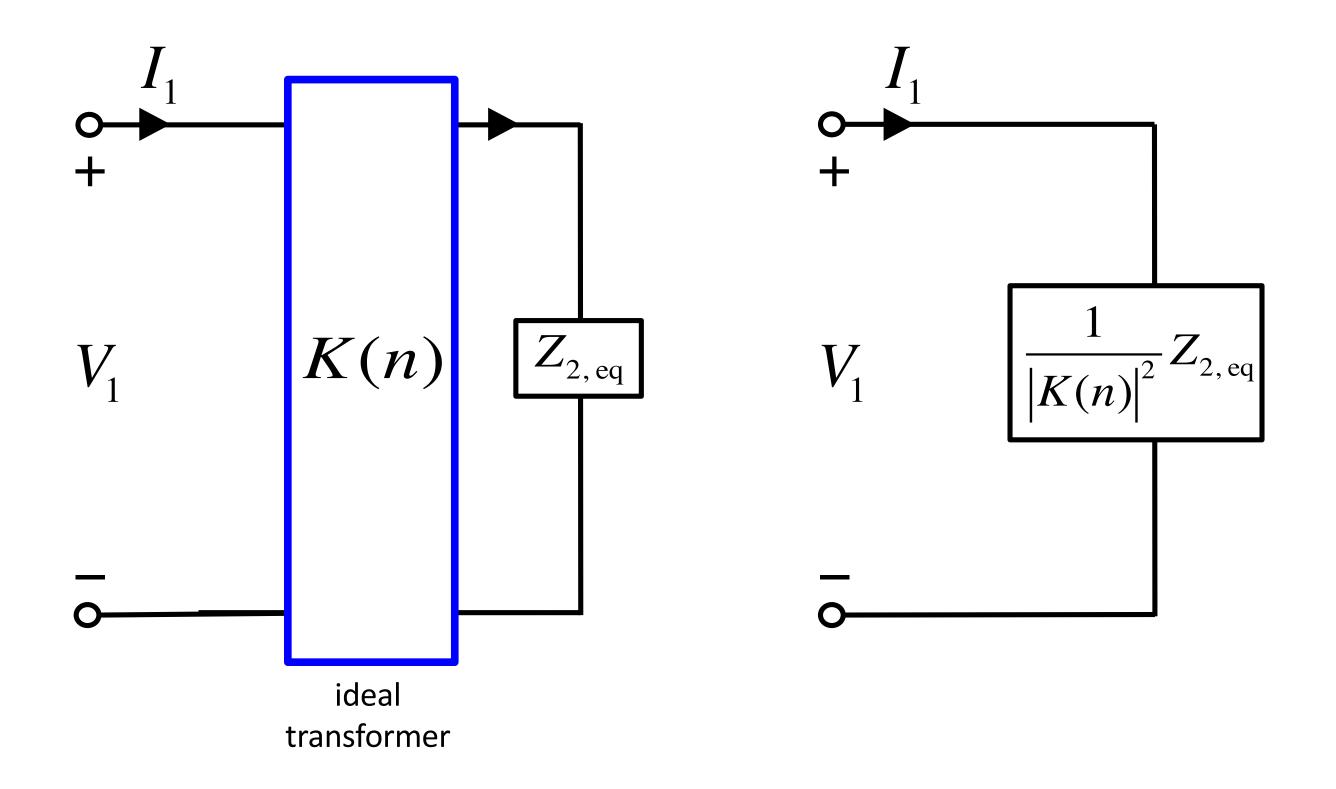
Referring impedance from secondary to primary



Both circuits have same driving-point impedance  $V_1/I_1$  on primary side

Can verify using Kirchhoff's and Ohm's laws

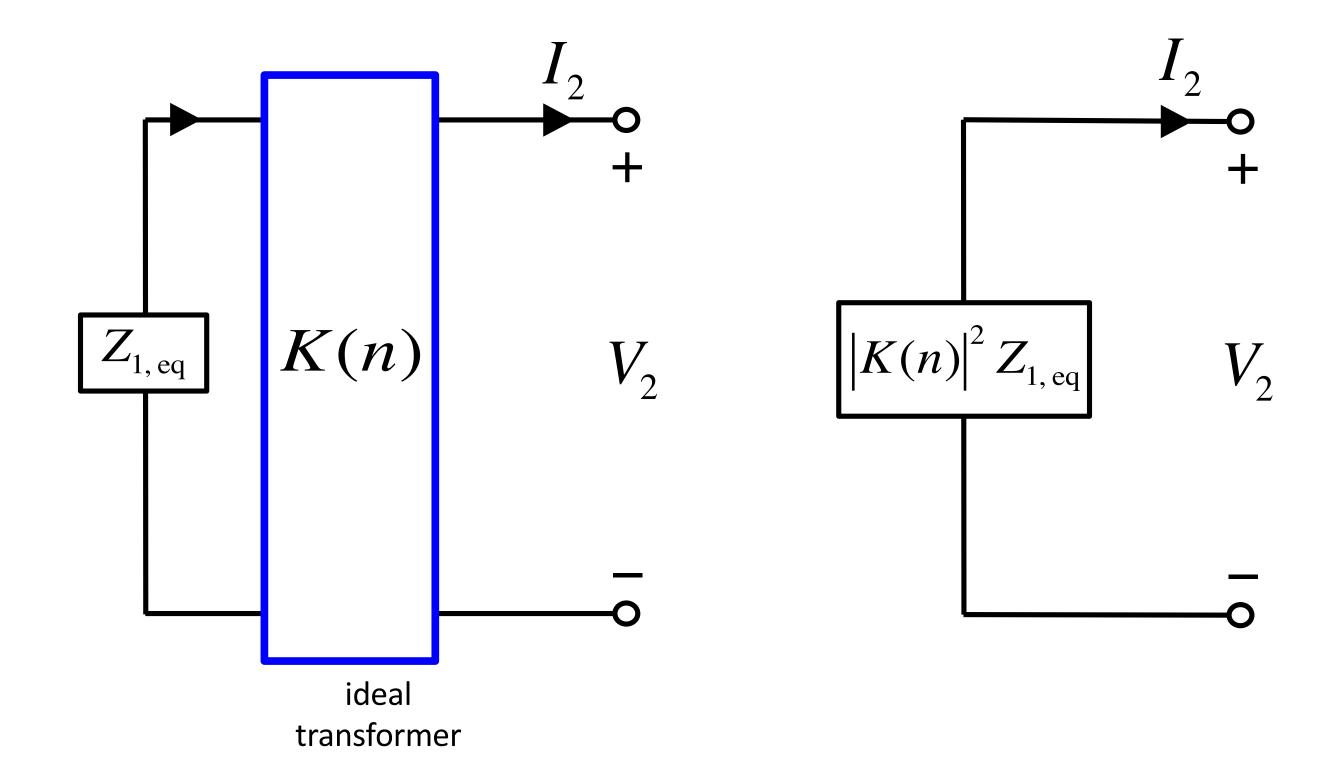
Referring impedance from primary to secondary



Both circuits have same driving-point impedance  $V_2/I_2$  on secondary side


Can verify using Kirchhoff's and Ohm's laws


#### Example

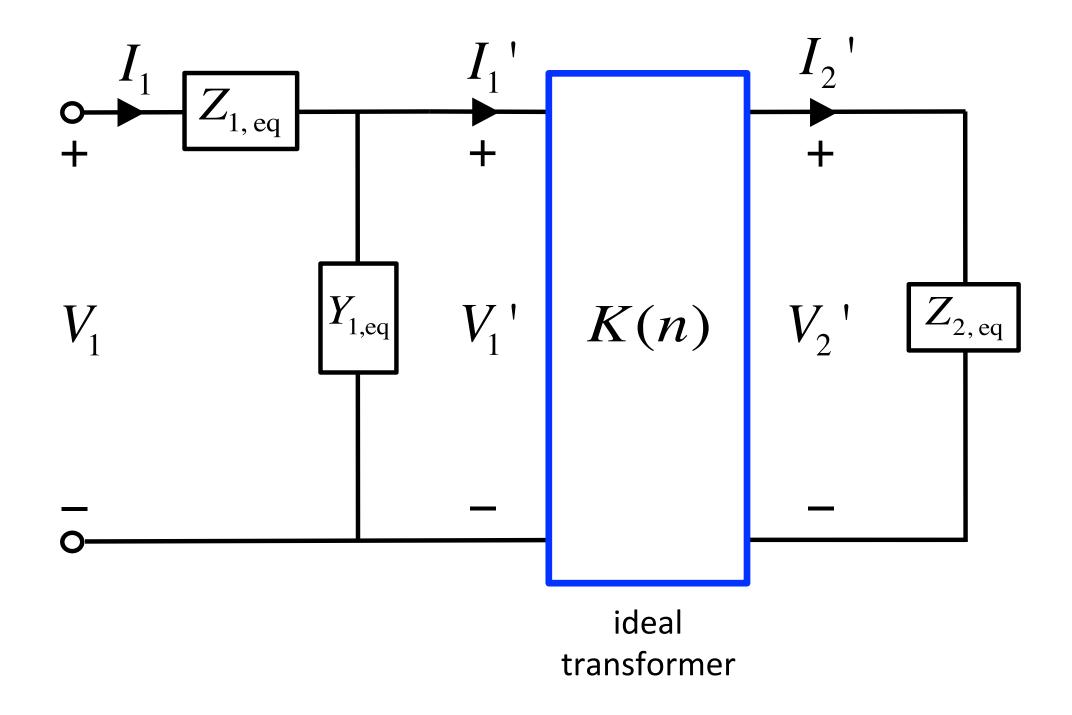

To find  $V_1/I_1$ , can analyze using Kirchhoff's and Ohm's laws


#### Example

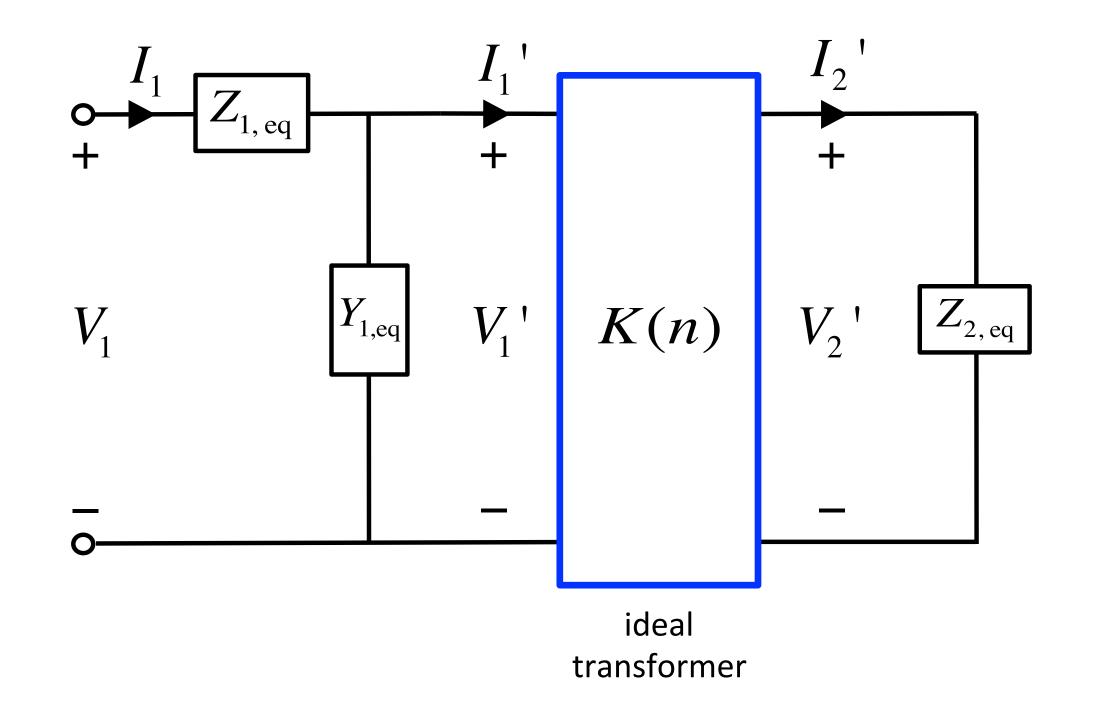

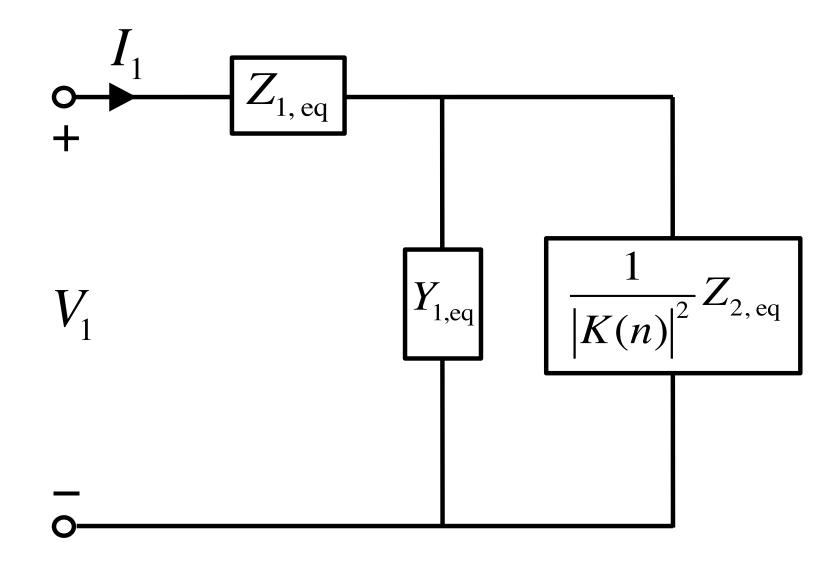


$$\frac{V_1}{I_1} = Z_{1,eq} + \left(Y_{1,eq} + \frac{1}{Z_{2,eq}/|K(n)|^2}\right)^{-1}$$


### **Example**

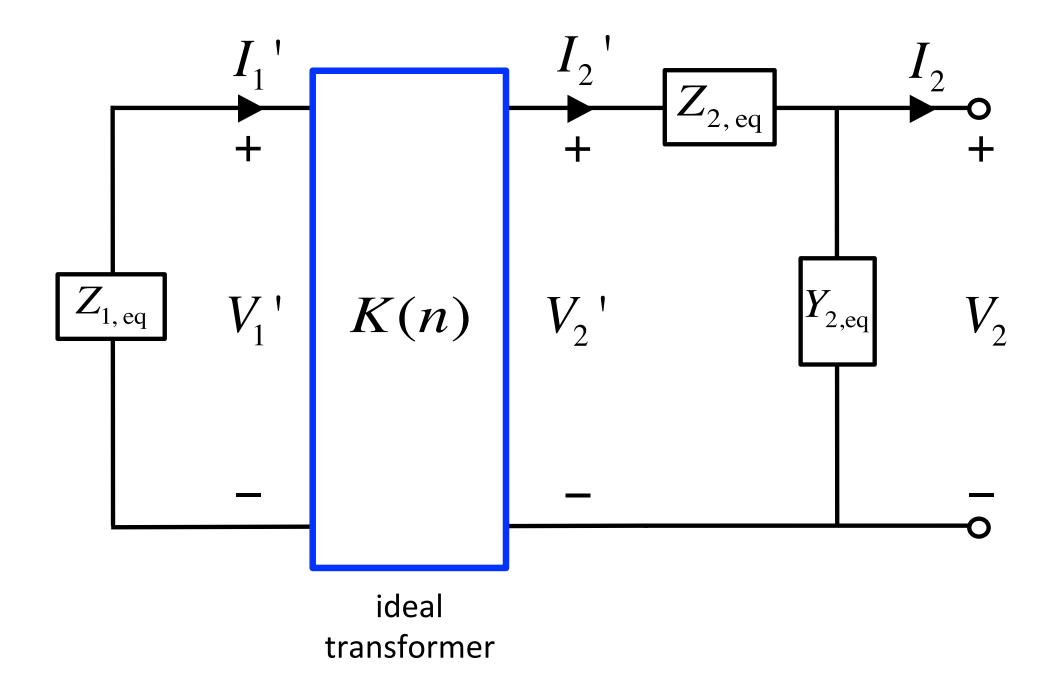

To find  $V_2/I_2$ , can analyze using Kirchhoff's and Ohm's laws

#### Example

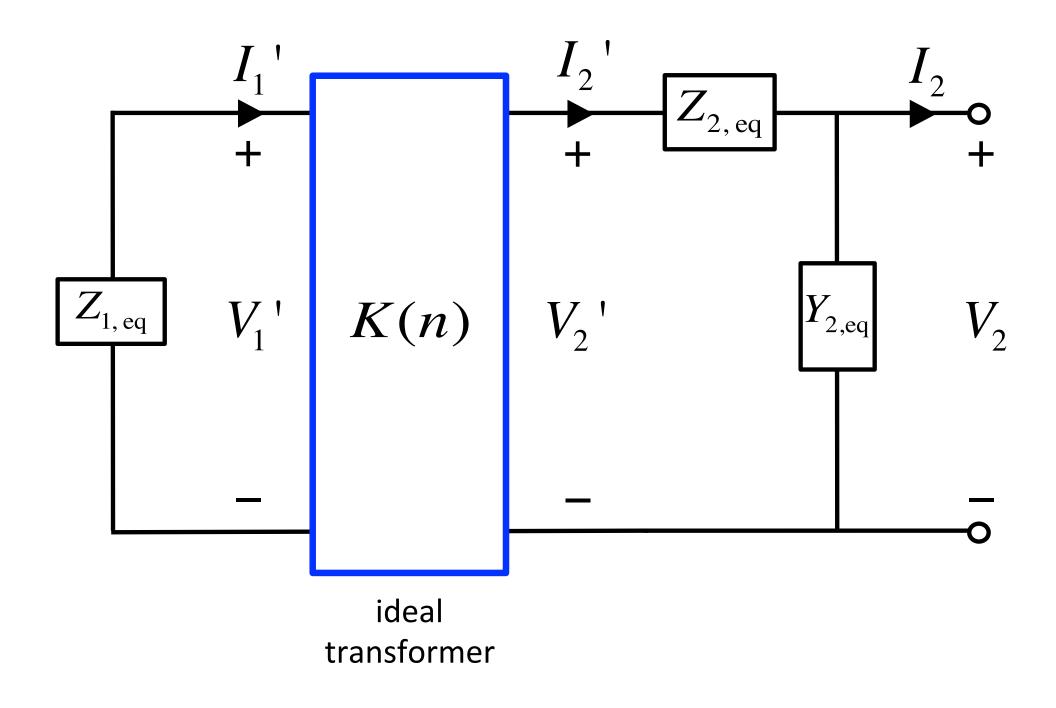

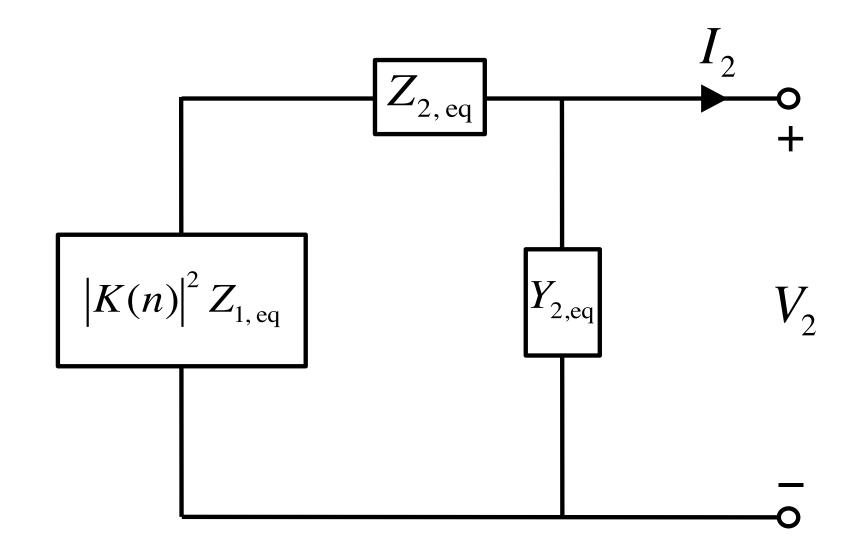

$$\frac{V_2}{I_2} = \left(Y_{2,eq} + \frac{1}{Z_{2,eq} + |K(n)|^2 \cdot Z_{1,eq}}\right)^{-1}$$

Reference from one circuit to the other is not always applicable

- Example: circuits containing parallel paths (see example later)
- Generally applicable in a radial network without parallel paths
- Can always analyze original circuit using Kirchhoff's and Ohm's laws

## Outline


- 1. Single-phase transformer
- 2. Balanced three-phase transformers
- 3. Equivalent impedance
- 4. Per-phase analysis
  - Example
  - Normal system
- 5. Per-unit normalization

# Per-phase analysis

#### **Procedure**

- 1. Convert all sources and loads in  $\Delta$  configurations into their Y equivalents
- 2. Convert all ideal transformers in  $\Delta$  configurations into their Y equivalents
- 3. Obtain phase a equivalent circuit by connecting all neutrals
- 4. Solve for desired phase-a variables
  - Use Thevenin equivalent of series impedances and shunt admittances in networks containing transformers whenever applicable, e.g., for a radial network
- 5. Obtain variables for phases b and c by subtracting  $120^{\circ}$  and  $240^{\circ}$  from phase a variables (positive sequence sources)
  - If variables in the internal of  $\Delta$  configurations are desired, derive them from original circuits


# Per-phase analysis Example

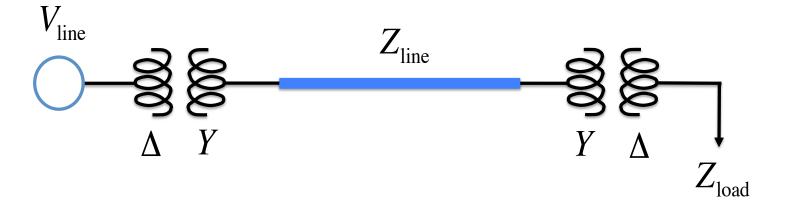


#### Balanced 3 $\phi$ system

- Generator with line voltage  $V_{\mathsf{line}}$
- Step-up  $\Delta Y$  transformer
- Transmission line with series impedance  $Z_{\mathrm{line}}$
- Step-down  $\Delta Y$  transformer (primary on right)
- Load with impedance  $Z_{\text{load}}$
- Single-phase transformer with voltage gain n and series impedance  $3Z_l$  on primary side

# Per-phase analysis Example

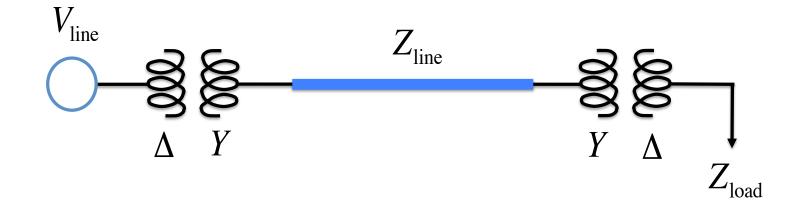

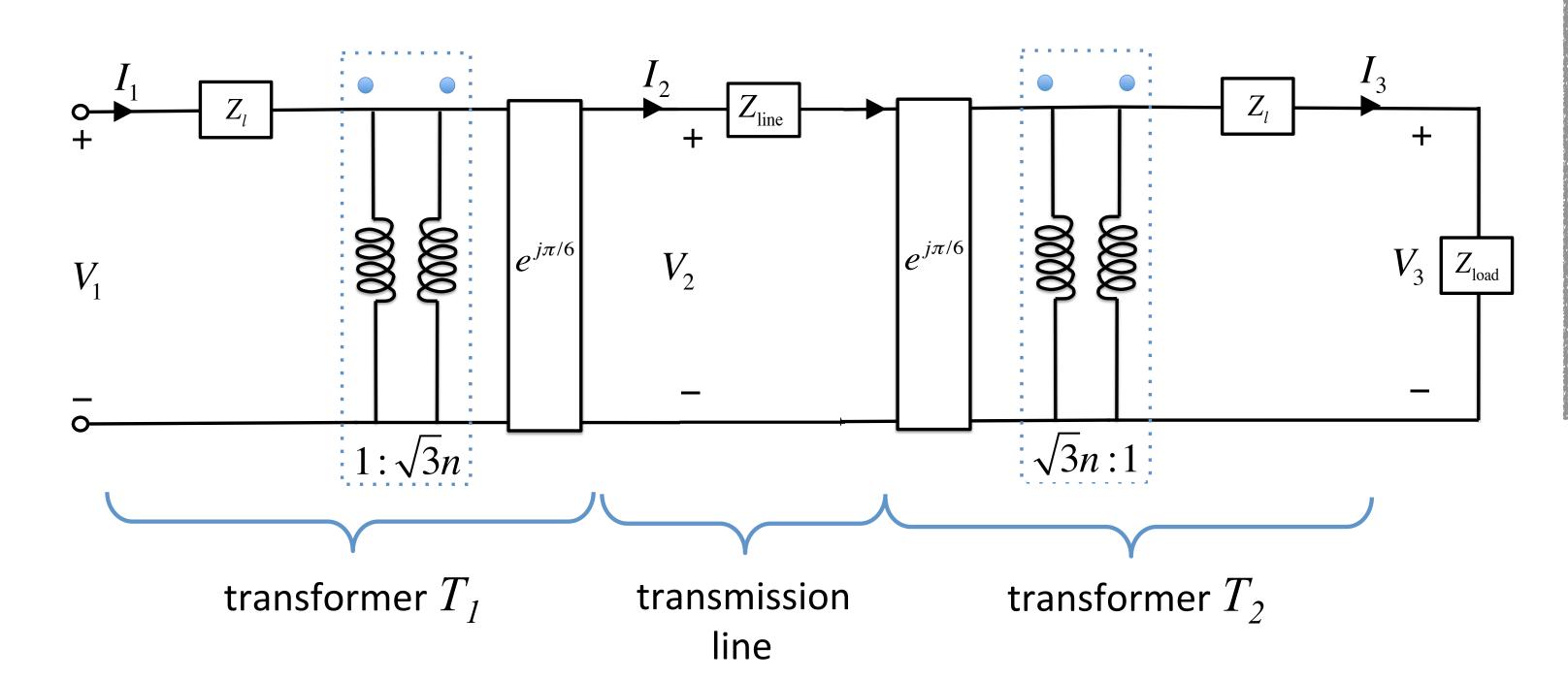


#### Balanced $3\phi$ system


- Generator with line voltage  $V_{\mathsf{line}}$
- Step-up  $\Delta Y$  transformer
- Transmission line with series impedance  $Z_{\mathrm{line}}$
- Step-down  $\Delta Y$  transformer (primary on right)
- Load with impedance  $Z_{\text{load}}$
- Single-phase transformer with turns ratio n and series impedance  $3Z_l$  on primary side

$$V_1 = \frac{V_{\text{line}}}{\sqrt{3} e^{i\pi/6}} \qquad Z^Y = Z$$

# Per-phase analysis

#### Example

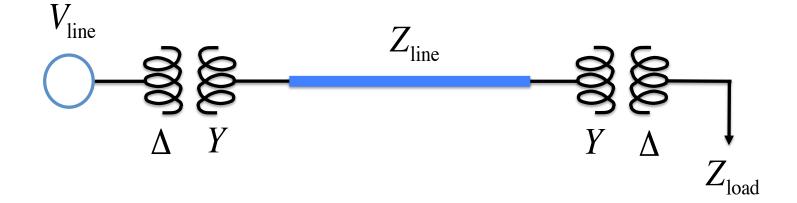

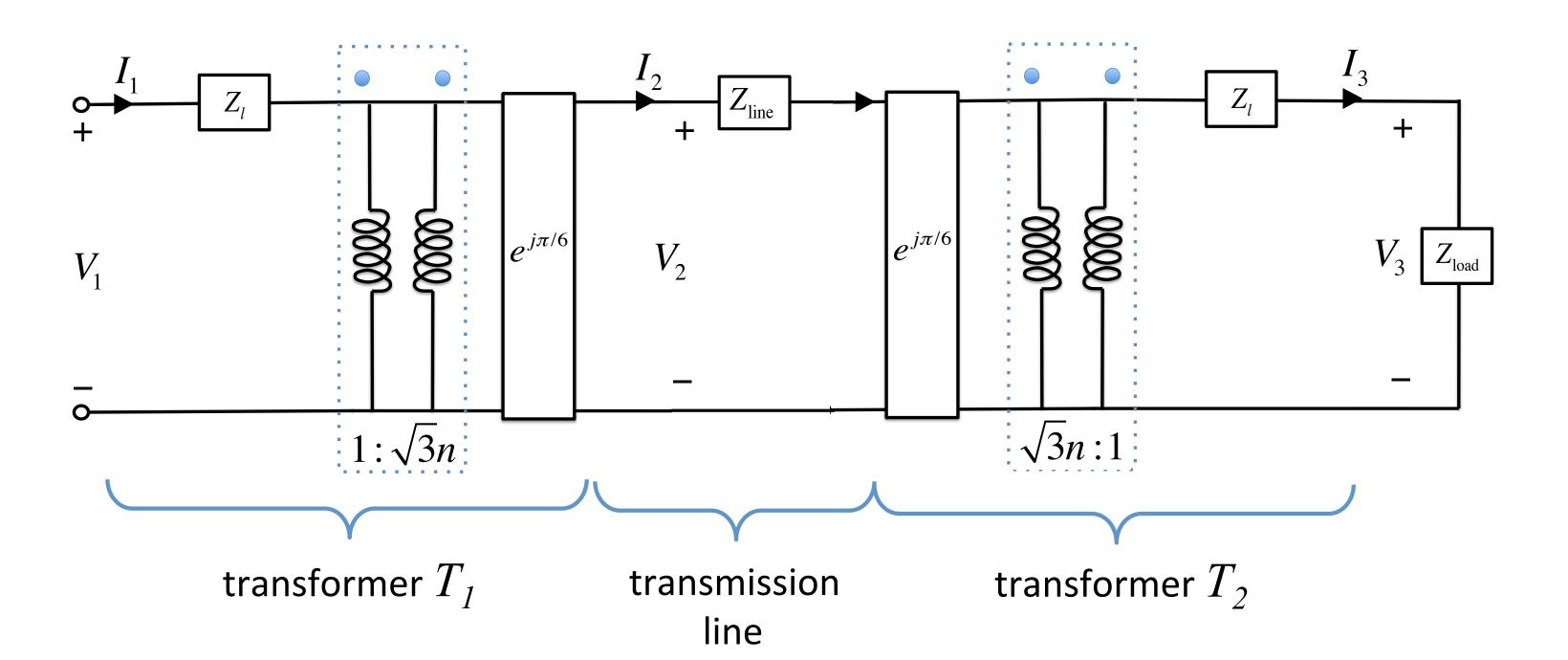



#### **Calculate**

- Generator current  $I_1$
- Transmission line current  $I_2$
- Load current  $I_3$
- Load voltage  $V_3$
- Power delivered to load:  $V_3I_3^*$

$$V_1 = \frac{V_{\text{line}}}{\sqrt{3} e^{i\pi/6}} \qquad Z^Y = Z_l$$

# Per-phase analysis Example

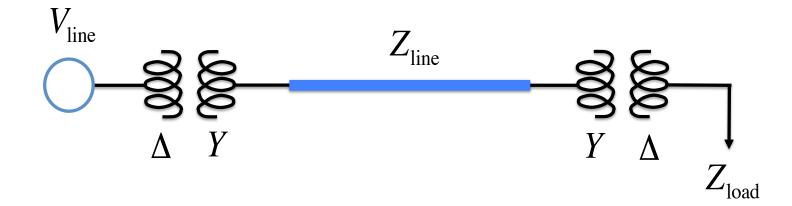

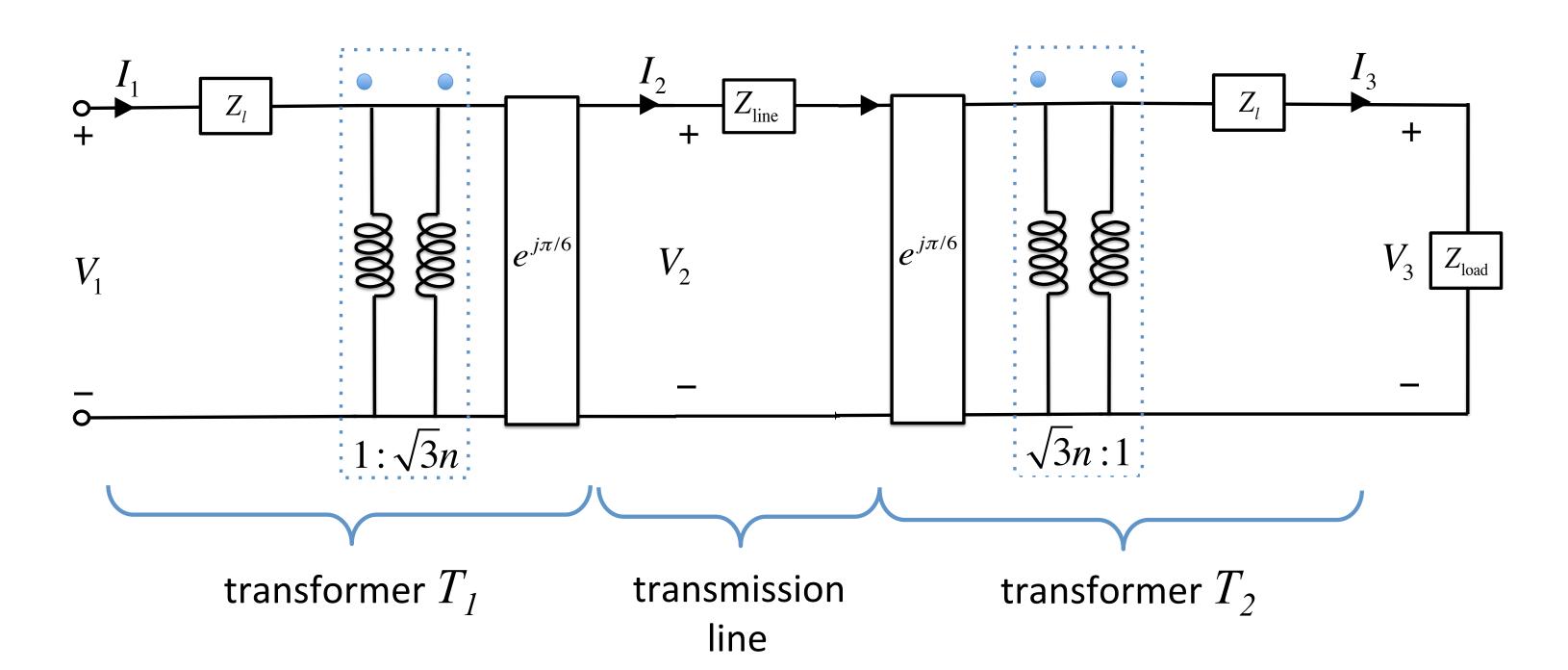


#### **Solution strategy**

- Refer all impedances to primary side of step-up transformer
- Derive driving-point impedance  $V_1/I_1$
- Derive generator current  $I_1$
- Propagate calculation towards load

$$V_1 = \frac{V_{\text{line}}}{\sqrt{3} e^{i\pi/6}} \qquad Z^Y = Z_0^Y$$


# Per-phase analysis

#### Example

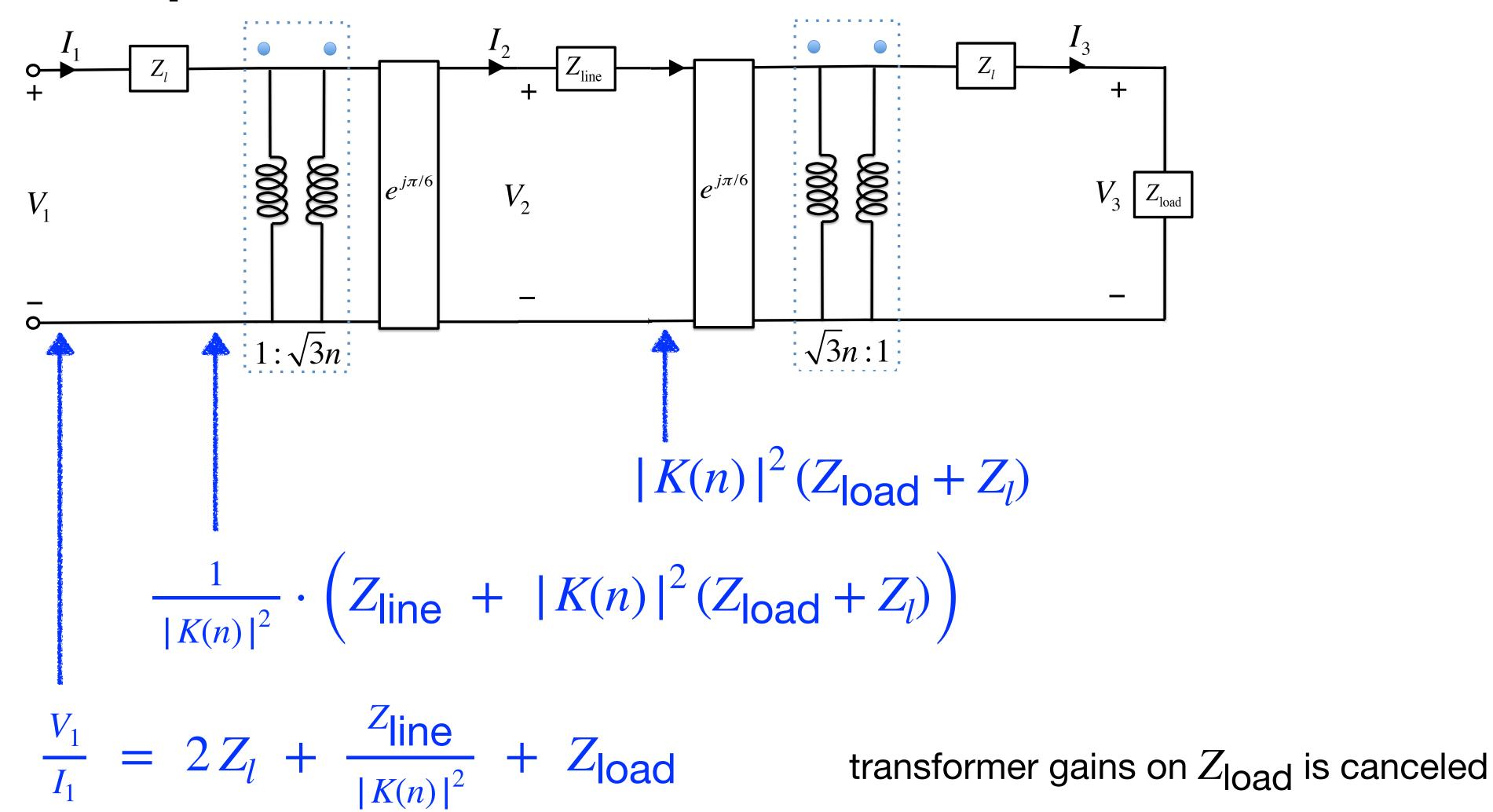

# Per-phase analysis

#### Example

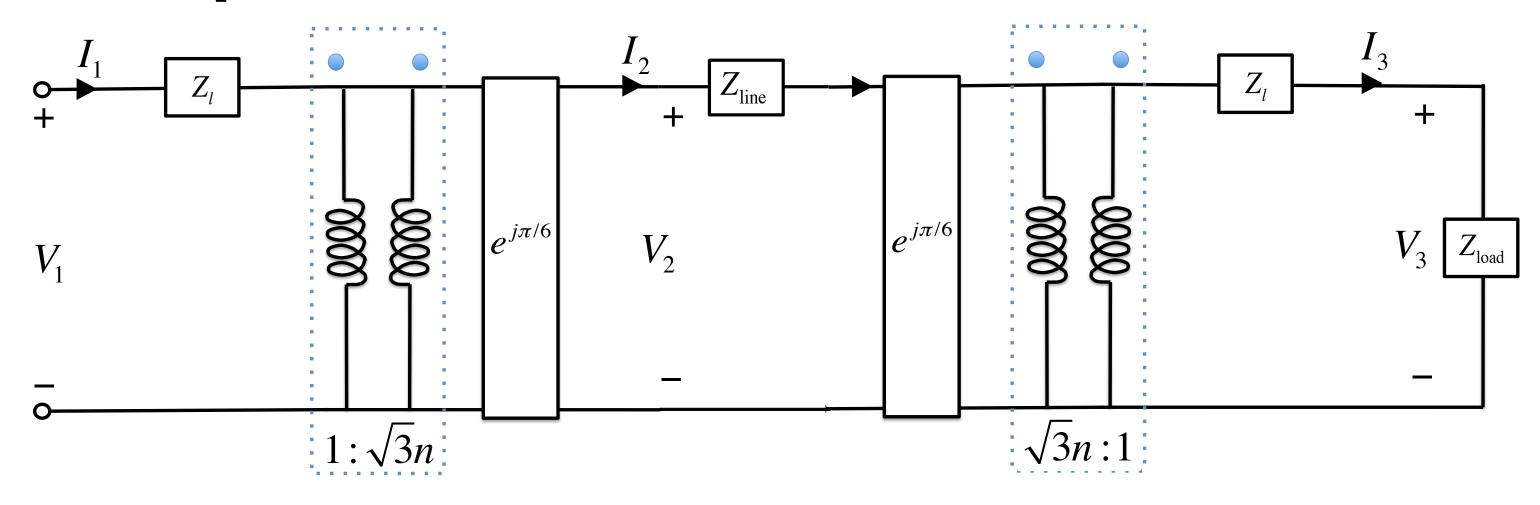


$$I_{1} = \frac{V_{\text{line}} / (\sqrt{3}e^{i\pi/6})}{2Z_{l} + \frac{Z_{\text{line}}}{|K(n)|^{2}} + Z_{\text{load}}}$$

$$I_3 = \bar{K}(n) I_2 = I_1$$
 $V_3 = Z_{load} I_3 = Z_{load} I_1$ 

$$I_2 = \frac{I_1}{\bar{K}(n)}$$

# Per-phase analysis

#### Example

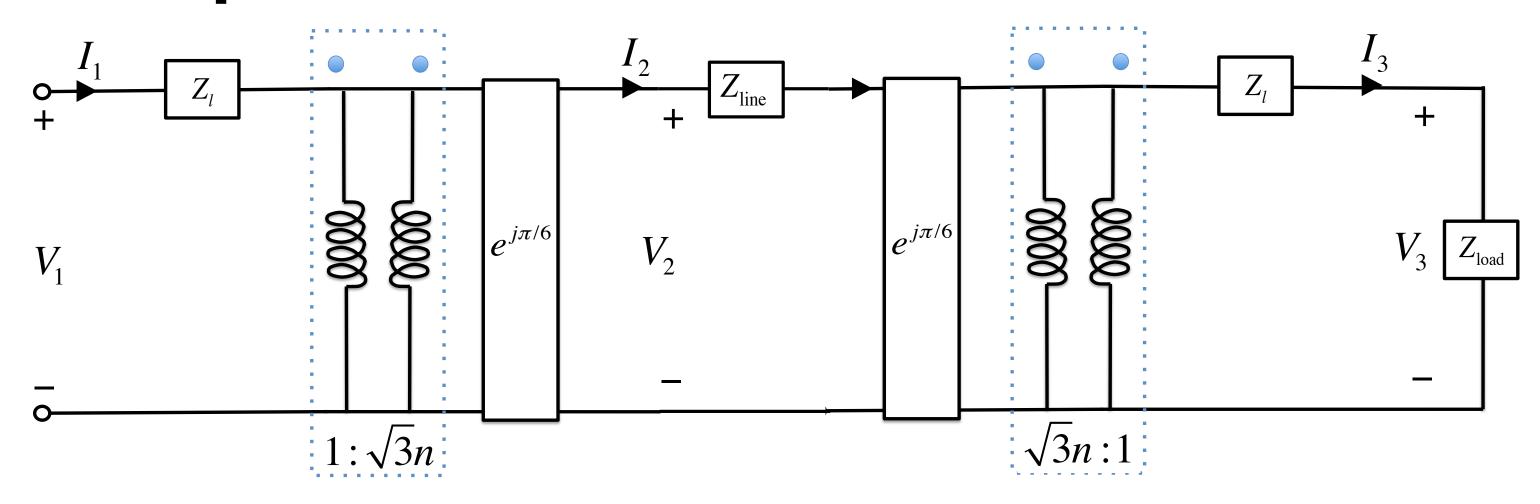


$$I_{1} = \frac{V_{\text{line}} / (\sqrt{3}e^{i\pi/6})}{2Z_{l} + \frac{Z_{\text{line}}}{|K(n)|^{2}} + Z_{\text{load}}}$$

$$I_{3} = I_{1}$$

$$V_{3} = Z_{\text{load}} I_{1}$$

- External behavior does not depend on connection-induced phase shift  $e^{i\pi/6}$
- Only internal variables  $I_{\mathrm{line}}$  does

# Simplified model for terminal behavior

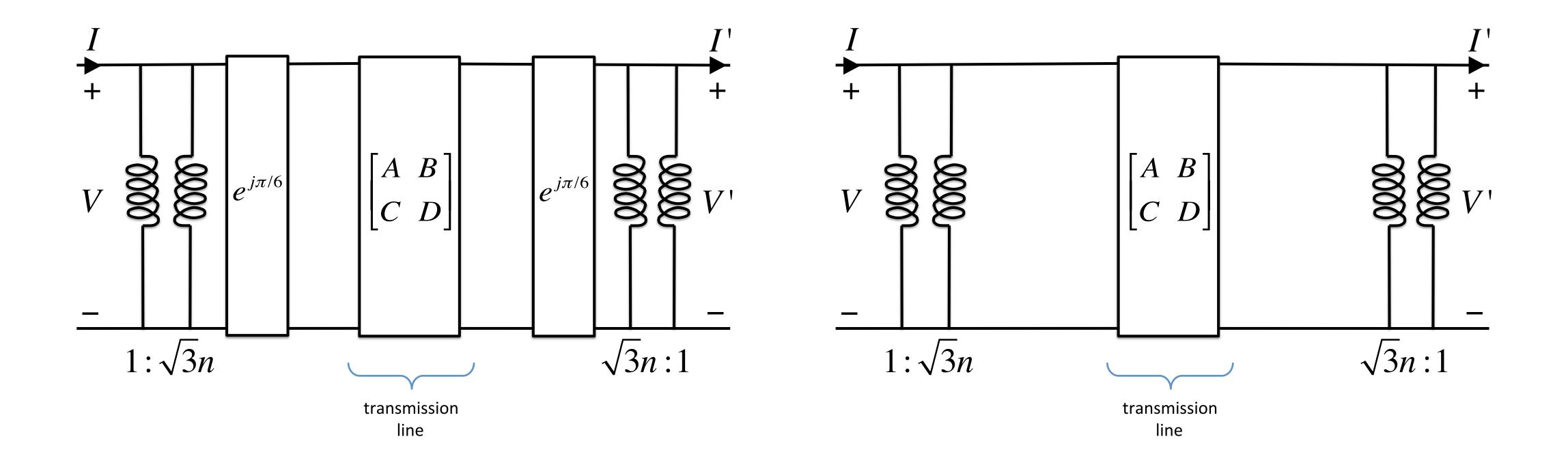

Terminal behavior does not depend on  $e^{i\pi/6}$ 


The simplified model has the same transmission matrix

A system is normal if, in its per-phase circuit, the product of complex ideal transformer gains around every loop is 1


Equivalently, on each parallel path,

- 1. Product of ideal transformer gain magnitudes is the same, and
- 2. Sum of ideal transformer phase shifts is the same

#### Example

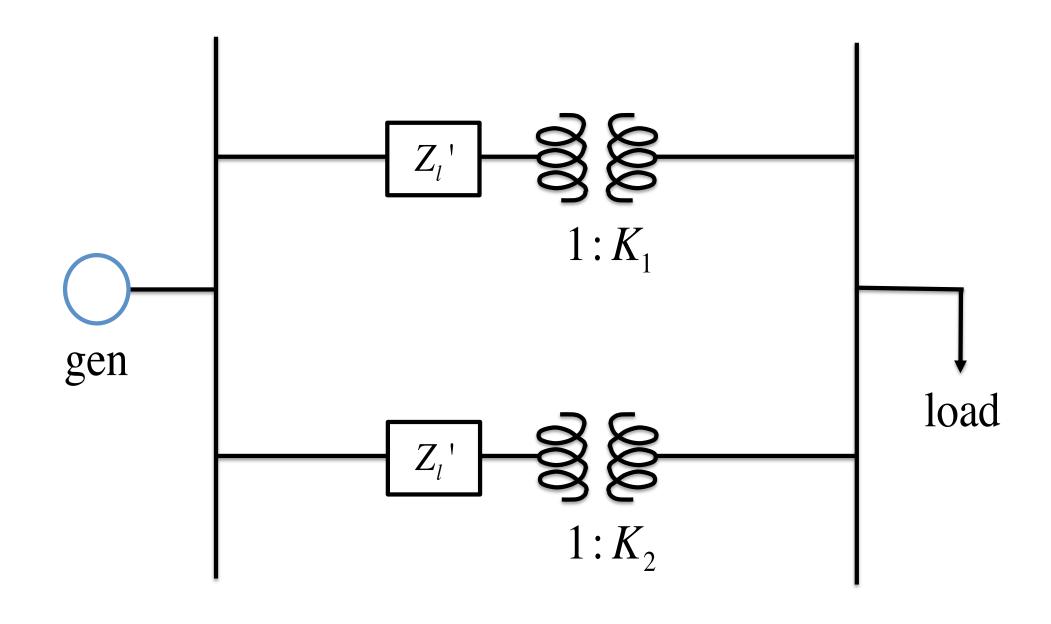

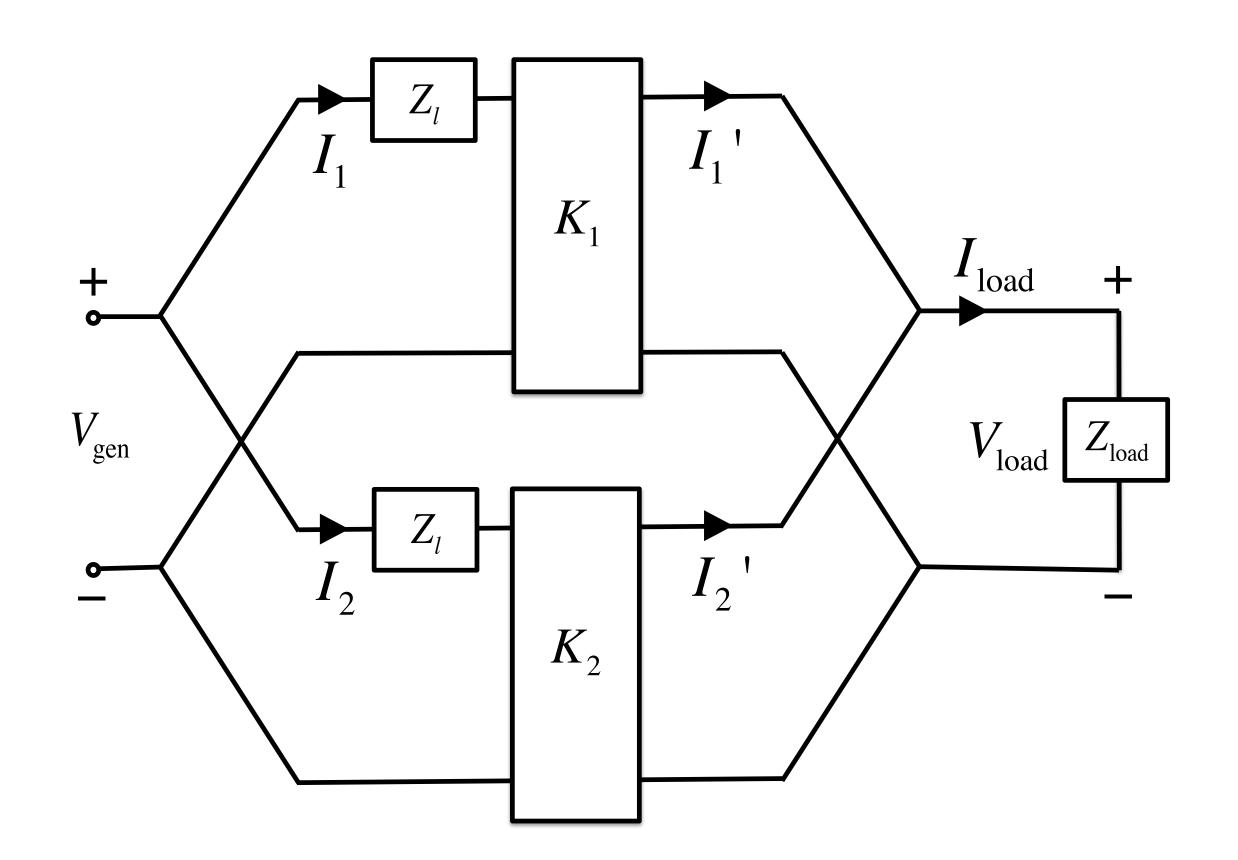Generator & load connected by two  $3\phi$  transformers in parallel (forming a loop)



#### Example


#### **Calculate**

- Load current  $I_{load}$
- Line currents  $I_1'$ ,  $I_2'$

in terms of  $V_{\rm gen},\,Z_{\it l},\,Z_{\rm load}$ 
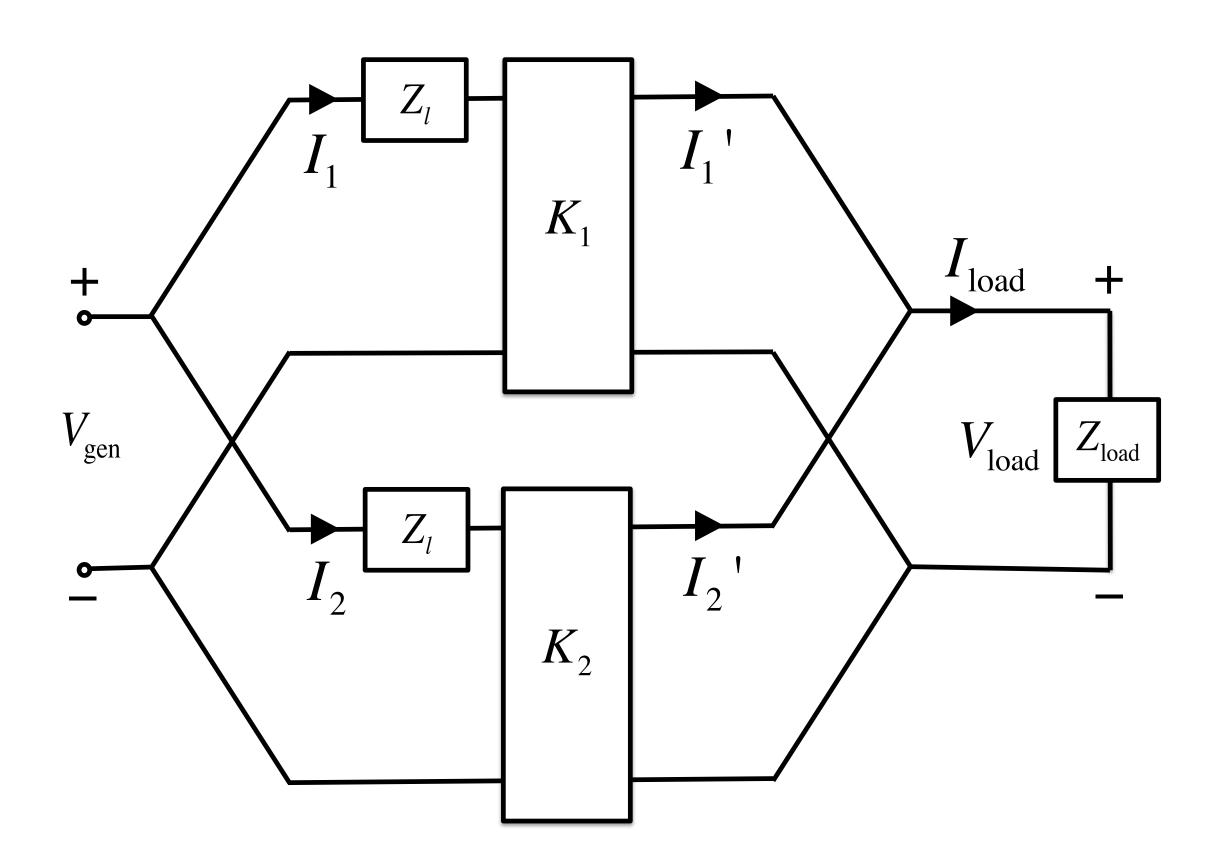
#### Implications when

- $K_2 = K_1$  (normal system)
- $K_2 = K_1 e^{i\theta}$
- $K_2 = k \cdot K_1$




# Normal system Example

$$K_2 = K_1$$
 (normal system):

• 
$$I'_1 = I'_2$$
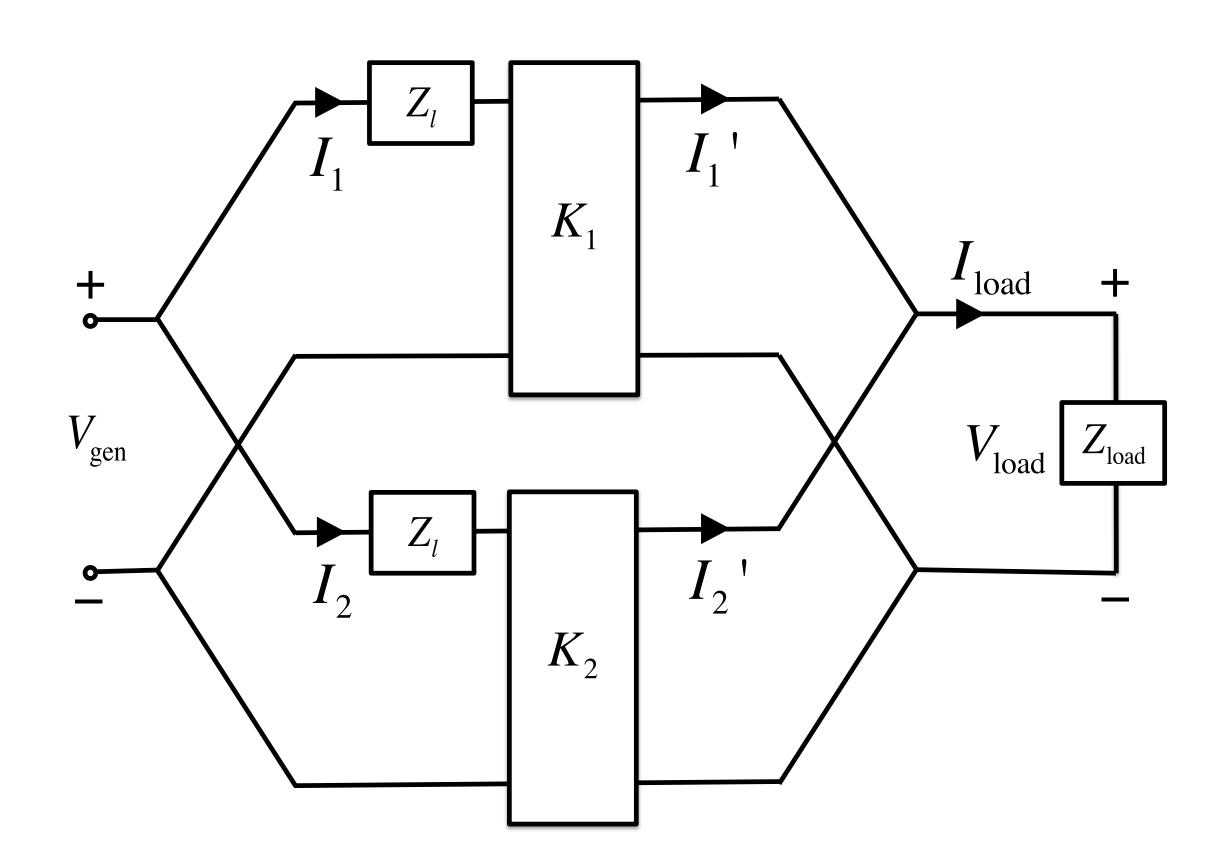
$$\frac{I_{\text{load}}}{I_1'} = \frac{I_{\text{load}}}{I_2'} = 2$$



#### Example

$$K_2 = K_1 e^{i\theta}:$$


$$I'_1 \neq I'_2$$

$$\left|\frac{I_{\text{load}}}{|I'_1|} = \frac{\left|1 + e^{i\theta}\right|}{|\alpha_1|}, \quad \frac{\left|I_{\text{load}}\right|}{|I'_2|} = \frac{\left|1 + e^{i\theta}\right|}{|\alpha_2|}$$

Example:  $K_2 = K_1 e^{i\pi/6}$ :

$$\frac{\left|I_{\text{load}}\right|}{|I'_{1}|} = 20.6\%, \quad \frac{\left|I_{\text{load}}\right|}{|I'_{2}|} = 17.1\%$$

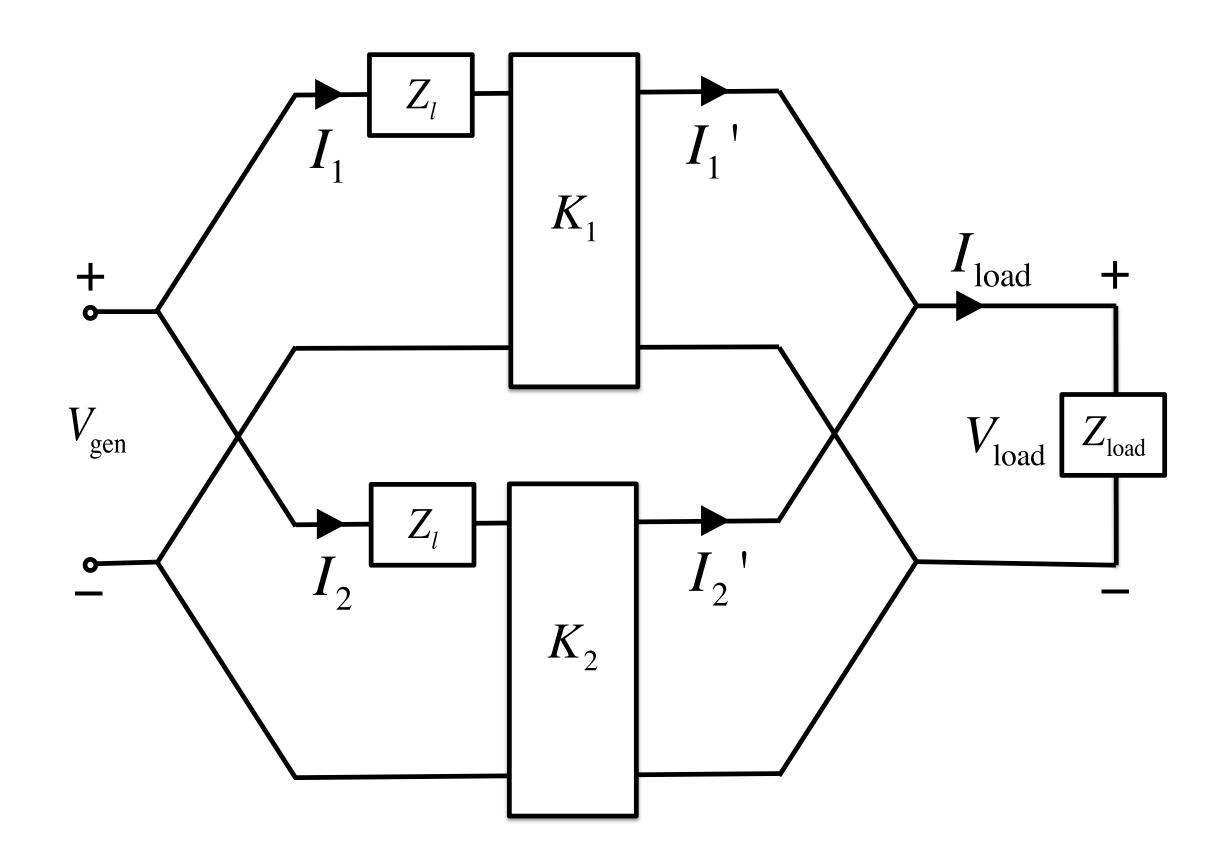Most current loops between transformers without entering load




#### Example

$$K_2 = K_1 e^{i\theta}$$
:
•  $I_1' \neq I_2'$ 

$$|I_1 = e^{i\theta}| \quad |I_1 = e^{i\theta}|$$

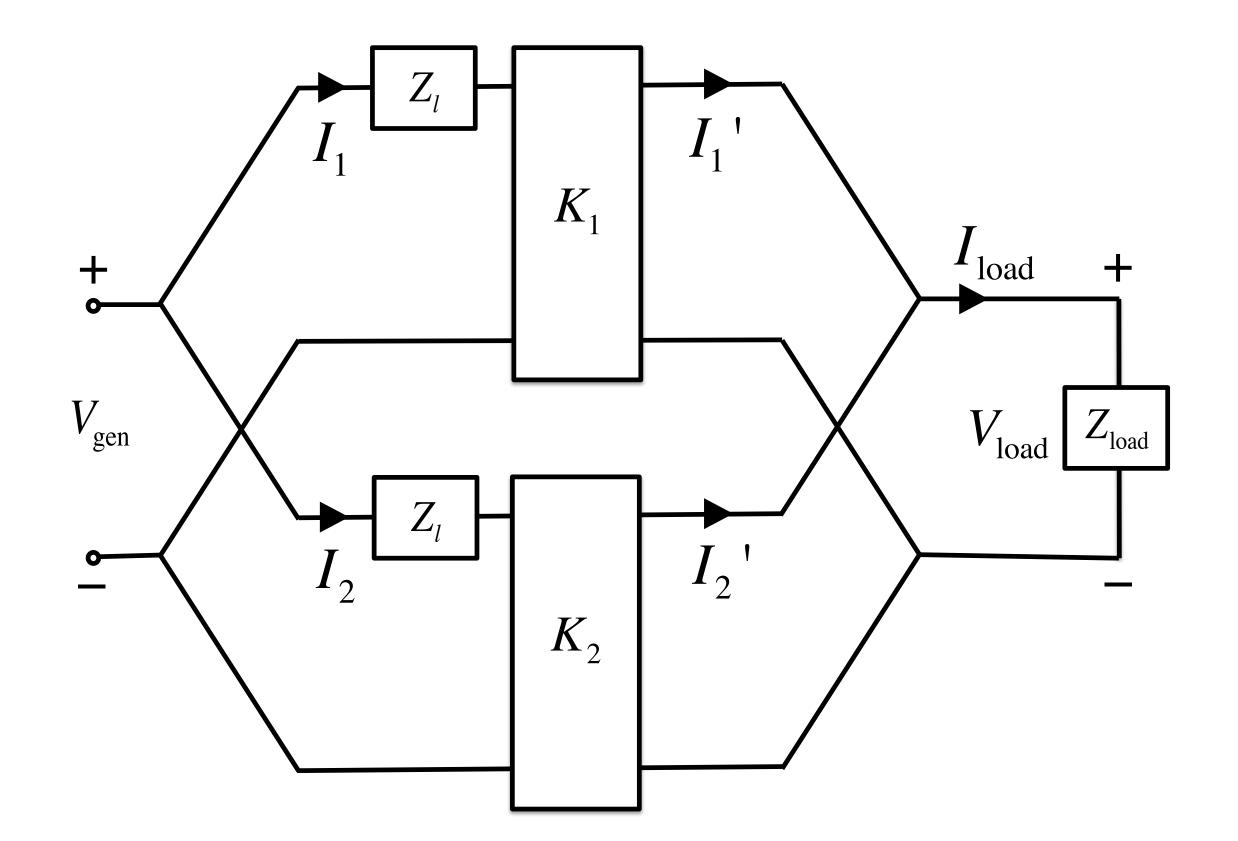Example:  $K_2 = K_1 e^{i\pi/6}$ :

• 
$$S_{\text{gen}} = 183 \angle 71^{\circ}$$
,  $S_{\text{load}} = 60 \angle 0^{\circ}$  MVA



Per-phase circuit

Most current loops between transformers without entering load

#### Example

$$K_2 = k \cdot K_1:$$


$$\cdot I'_1 \neq I'_2$$

$$\cdot \frac{\left|I_{\text{load}}\right|}{\left|I'_1\right|} = \frac{1+k^{-1}}{\left|\alpha_1\right|}, \quad \frac{\left|I_{\text{load}}\right|}{\left|I'_2\right|} = \frac{1+k}{\left|\alpha_2\right|}$$

Example:  $K_2 = 2K_1$ :

$$\frac{\left|I_{\text{load}}\right|}{|I_1'|} = 29.4\%, \quad \frac{\left|I_{\text{load}}\right|}{|I_2'|} = 29.9\%$$

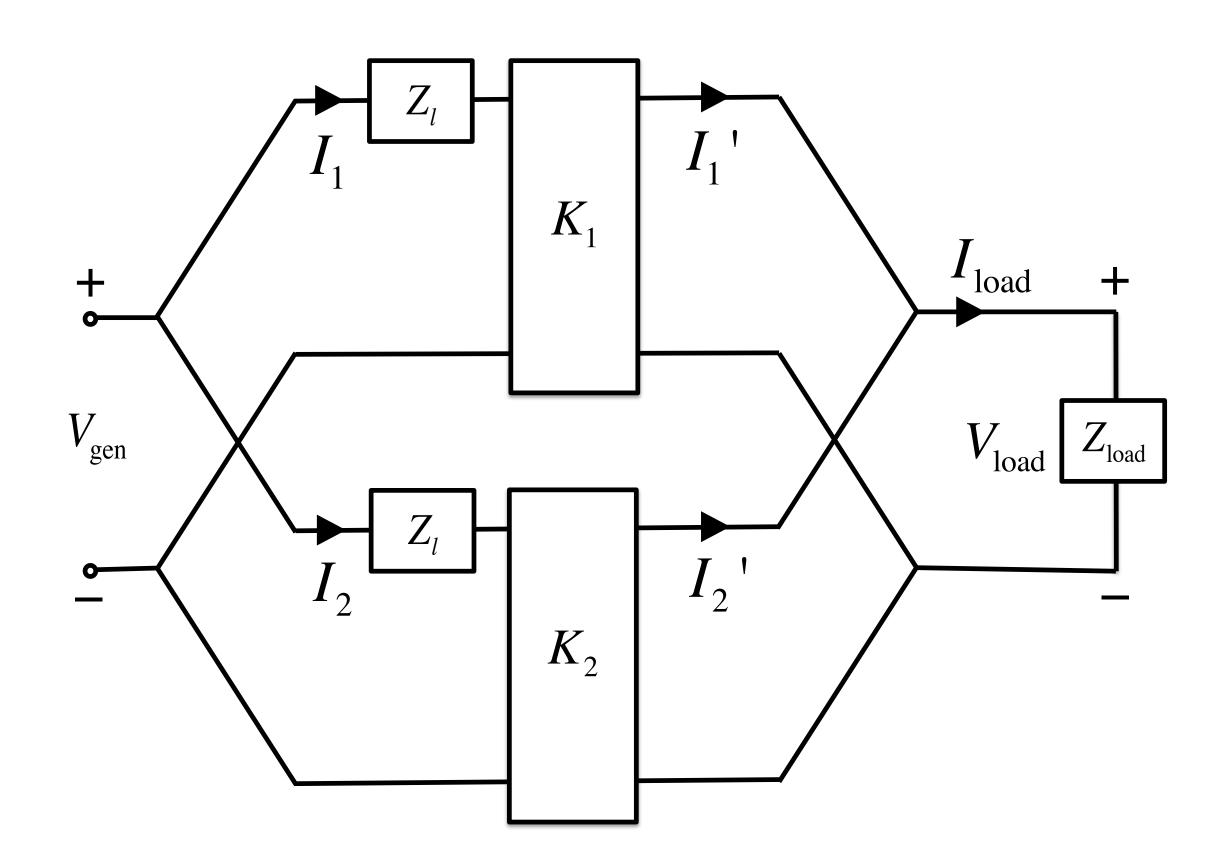Most current loops between transformers without entering load



### Outline

- 1. Single-phase transformer
- 2. Balanced three-phase transformers
- 3. Equivalent impedance
- 4. Per-phase analysis
- 5. Per-unit normalization
  - Kirchhoff's and Ohm's laws
  - Across ideal transformer
  - Three-phase quantities
  - Per-unit per-phase analysis

### Per-unit normalization

• Quantities of interest: voltages V, currents I, power S, impedances Z

quantity in p.u. = 
$$\frac{\text{actual quantity}}{\text{base value of quantity}}$$

- Base values
  - Real positive values
  - Same units as actual quantities
- Choose base values to satisfy same physical laws
  - Kirchhoff's and Ohm's laws
  - Across ideal transformer
  - Relationship between  $3\phi$  and  $1\phi$  quantities

### Per-unit normalization

#### General procedure

- 1. Choose voltage base value  $V_{1B}$  for (say) area 1
- 2. Choose power base value  $S_R$  for entire network
- 3. Calculate all other base values from physical laws

#### Example: Choose

- 1.  $V_{1B}$  = nominal voltage magnitude of area 1
- 2.  $S_B$  = rated apparent power of a transformer in area 1

### How to calculate the other base values $(V_{iB}, I_{iB}, Z_{iB})$ ?

• Consider single-phase or per-phase circuit of balanced  $3\phi$  system

### Kirchhoff's and Ohm's laws

Given base values  $(V_{1B}, S_B)$ , within area 1:

$$I_{1B} := rac{S_B}{V_{1B}} A, \qquad Z_{1B} := rac{V_{1B}^2}{S_B} \Omega$$

Then: physical laws are satisfied by both the base values and p.u. quantities

$$V_{1B} = Z_{1B}I_{1B},$$
  $V_{1pu} = Z_{1pu}I_{1pu}$   
 $S_B = V_{1B}I_{1B},$   $S_{1pu} = V_{1pu}I_{1pu}$ 

Can perform circuit analysis using pu quantities instead of actual quantities

### Kirchhoff's and Ohm's laws

#### Other quantities

These quantities  $(V_{1B}, S_B, I_{1B}, Z_{1B})$  serve as base values for other quantities within area 1, with appropriate units

•  $S_B$  is base value for real power in W, reactive power in var


$$P_{1pu} := \frac{P_1}{S_R}, \qquad Q_{1pu} := \frac{Q_1}{S_R}, \qquad S_{1pu} = P_{1pu} + iQ_{1pu}$$

•  $Z_{1R}$  is base value for resistances & reactances in  $\Omega$ 

$$R_{1\text{pu}} := \frac{R_1}{Z_{1R}}, \qquad X_{1\text{pu}} := \frac{X_1}{Z_{1R}}, \qquad Z_{1\text{pu}} = R_{1\text{pu}} + iX_{1\text{pu}}$$

•  $Y_{1B}:=1/Z_{1B}$  in  $\Omega^{-1}$  is base value for conductances, susceptances, & admittances
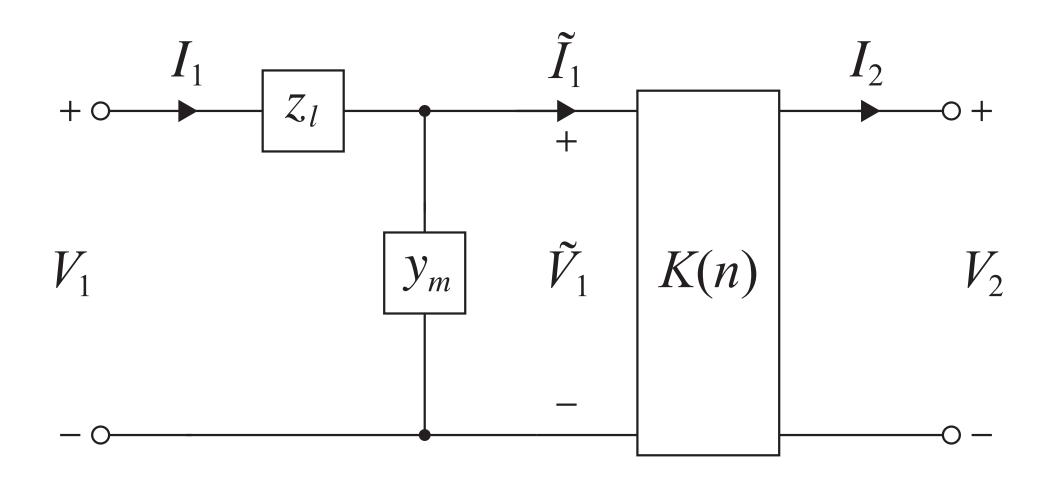
$$G_{1pu} := \frac{G_1}{Y_{1B}}, \qquad B_{1pu} := \frac{B_1}{Y_{1B}}, \qquad Y_{1pu} = G_{1pu} + iB_{1pu} = \frac{1}{Z_{1pu}}$$




Choose 
$$\left(V_{2B},I_{2B},Z_{2B}\right)$$
 according to

$$V_{2B} := |K(n)| V_{1B} \quad V$$

$$I_{2B} := \frac{I_{1B}}{|K(n)|} A$$

$$Z_{2B} := |K(n)|^2 Z_{1B} \Omega$$

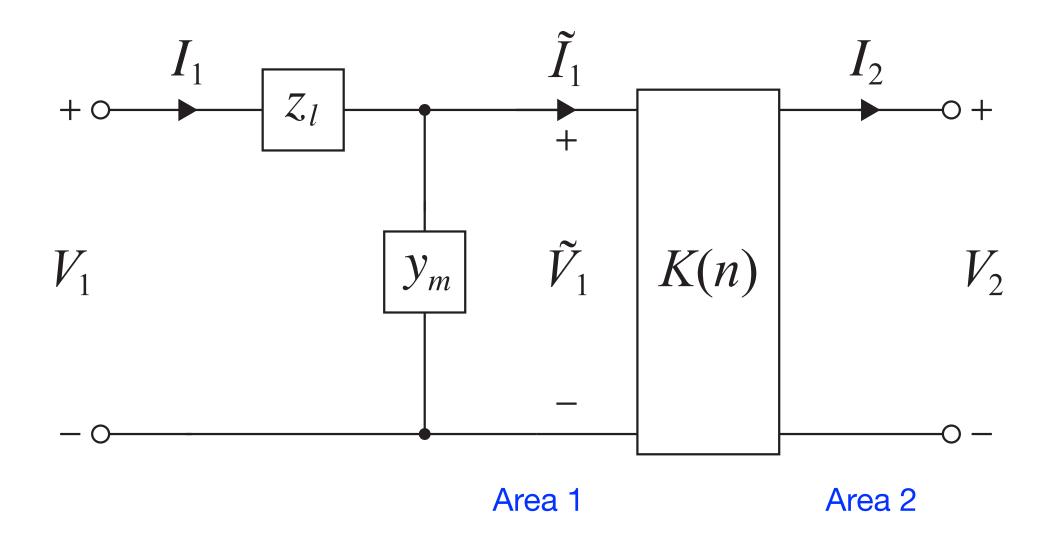Base values remain real positive  $S_B$  remains base value for power




#### External behavior

$$\tilde{V}_{1\text{pu}} = \frac{\tilde{V}_{1}}{V_{1B}} = \frac{V_{2}}{K(n)} \frac{|K(n)|}{V_{2B}} = V_{2\text{pu}} e^{-j \angle K(n)} \qquad \text{If } \angle K(n) = 0 \text{ then}$$

$$\tilde{I}_{1\text{pu}} = \frac{\tilde{I}_{1}}{\tilde{I}_{1B}} = \frac{K^{*}(n)I_{2}}{|K(n)|I_{2B}} = I_{2\text{pu}} e^{-j \angle K(n)}$$
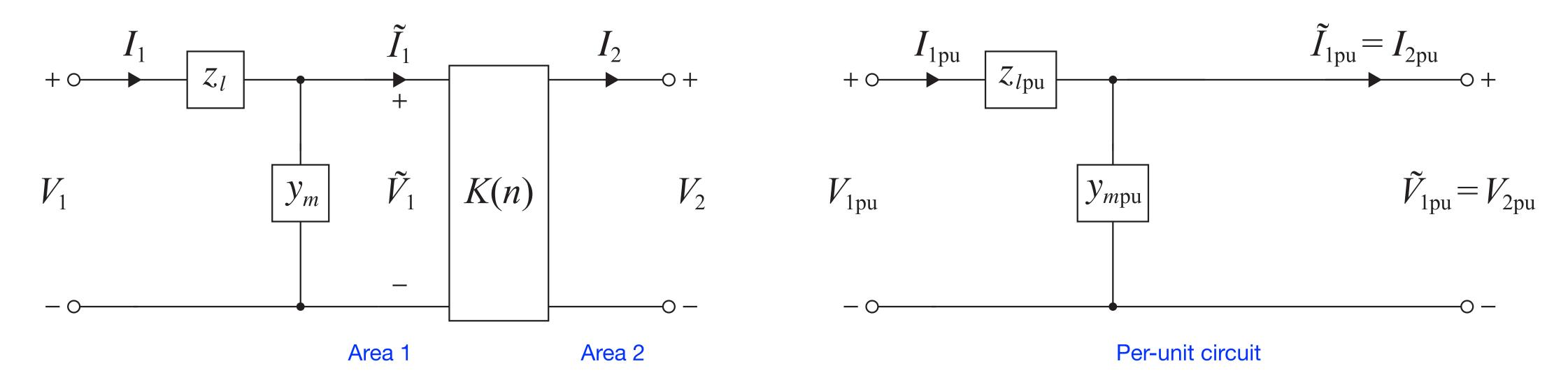
$$\tilde{V}_{1\text{pu}} = V_{2\text{pu}}, \quad \tilde{I}_{1\text{pu}} = I_{2\text{pu}}$$




#### External behavior

$$\tilde{V}_{1pu} = \frac{\tilde{V}_{1}}{V_{1B}} = \frac{V_{2}}{K(n)} \frac{|K(n)|}{V_{2B}} = V_{2pu} e^{-j \angle K(n)}$$

$$\tilde{I}_{1pu} = \frac{\tilde{I}_{1}}{\tilde{I}_{1B}} = \frac{K^{*}(n)I_{2}}{|K(n)|I_{2B}} = I_{2pu} e^{-j \angle K(n)}$$

If 
$$\angle K(n) = 0$$
 then 
$$\tilde{V}_{1\text{pu}} = V_{2\text{pu}}, \quad \tilde{I}_{1\text{pu}} = I_{2\text{pu}}$$

Ideal transformer has disappeared!

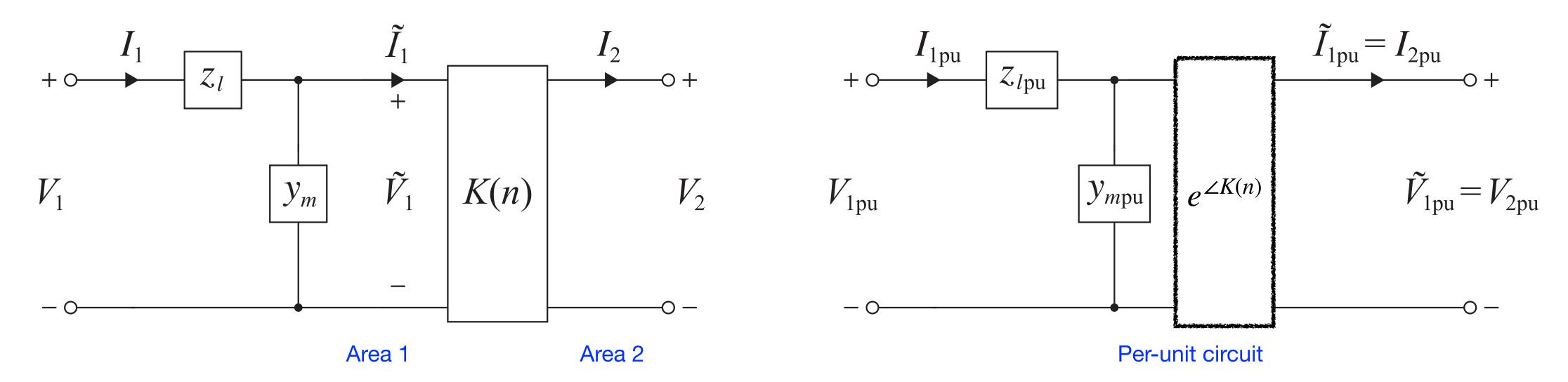

#### External behavior

$$\tilde{V}_{1pu} = \frac{\tilde{V}_{1}}{V_{1B}} = \frac{V_{2}}{K(n)} \frac{|K(n)|}{V_{2B}} = V_{2pu} e^{-j \angle K(n)}$$

$$\tilde{I}_{1pu} = \frac{\tilde{I}_{1}}{\tilde{I}_{1B}} = \frac{K^{*}(n)I_{2}}{|K(n)|I_{2B}} = I_{2pu} e^{-j \angle K(n)}$$

#### Otherwise


 pu circuit contains an off-nominal phase-shifting transformer

Example

Given nameplate rating of generator

- Voltage v V
- Apparent power s VA

Calculate base values

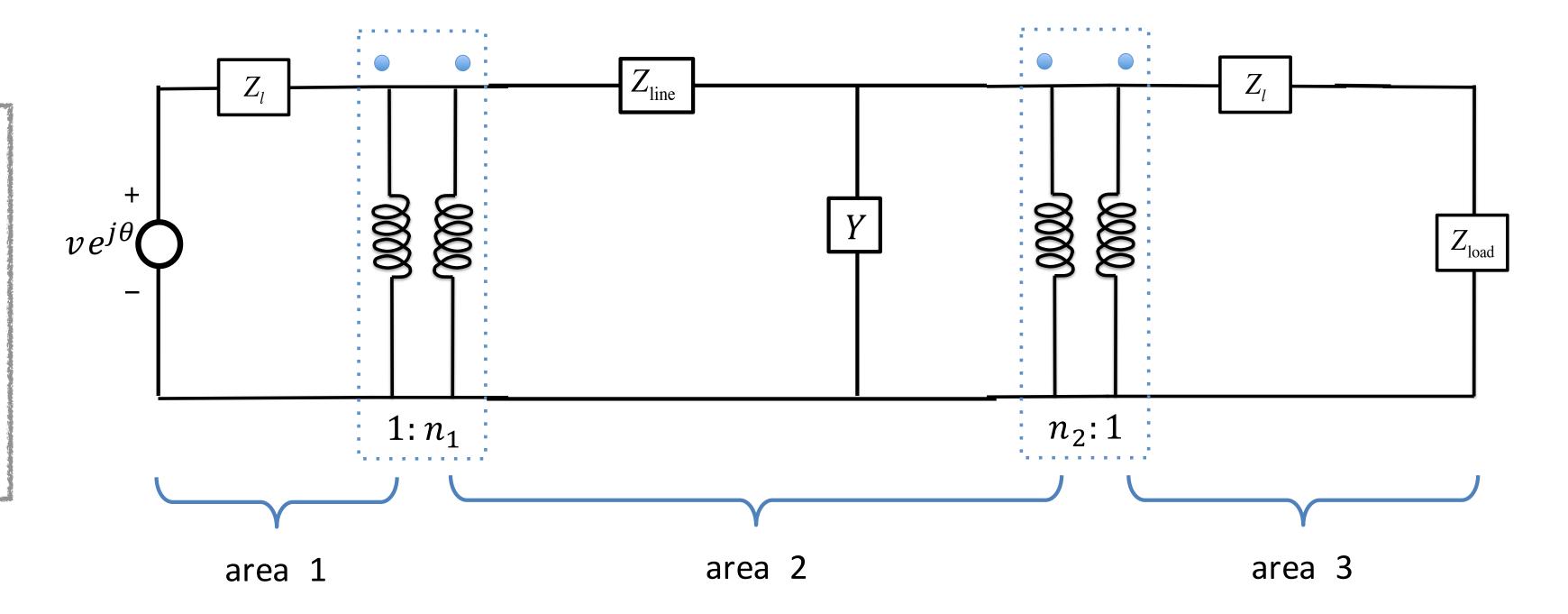

Voltage base  $V_{1B} := v$ , power base  $S_B := s$ 

- Area 1:  $I_{1B} := s/v$ ,  $Z_{1B} := v^2/s$
- Area 2:  $V_{2B} := n_1 v$ ,  $I_{2B} := s/(n_1 v)$ ,  $Z_{2B} := (n_1 v)^2/s$ ,  $Y_{2B} := s/(v_1 v)^2$
- Area 3:  $V_{3B} := n_1 v/n_2$ ,  $I_{3B} := n_2 s/(n_1 v)$ ,  $Z_{3B} := (n_1 v)^2/(n_2^2 s)$ ,  $Y_{3B} := (n_2^2 s)/(v_1 v)^2$

# 3\$\phi\$ quantities

Given  $1\phi$  devices (generators, lines, loads) with

- with 1 $\phi$  quantities  $\left(S^{1\phi},V^{1\phi},I^{1\phi},Z^{1\phi}\right)$
- and their base values

Construct balanced  $3\phi$  devices from these  $1\phi$  devices

- What are  $3\phi$  quantities of interest?
- What are base values so that  $3\phi$  quantities equal to  $1\phi$  quantities in p.u.?

Base values should satisfy the same  $3\phi$  relationships as actual quantities Values depend on the configuration, Y or  $\Delta$ 

# $3\phi$ quantities

#### Y configuration

In terms of  $(S^{1\phi}, V^{1\phi}, I^{1\phi}, Z^{1\phi})$  and their base values

•  $3\phi$  power (total power to/from 3  $1\phi$  devices):

$$S^{3\phi} = 3S^{1\phi},$$

Line-to-line voltage

$$V^{\parallel} = \sqrt{3}e^{i\pi/6}V^{\ln},$$

Line current

$$I^{3\phi} = I_{an} = I^{1\phi},$$

Line-to-neutral voltage

$$V^{\mathsf{ln}} = V^{1\phi}$$
.

Impedance

$$Z^{3\phi} = Z^{1\phi},$$

# $3\phi$ quantities

#### Y configuration

In terms of  $\left( S^{1\phi}, V^{1\phi}, I^{1\phi}, Z^{1\phi} \right)$  and their base values

•  $3\phi$  power (total power to/from 3  $1\phi$  devices):

$$S^{3\phi} = 3S^{1\phi}, \qquad S_B^{3\phi} = 3S_B^{1\phi}$$

Line-to-line voltage

$$V^{\parallel} = \sqrt{3}e^{i\pi/6}V^{\ln}, \qquad V_B^{\parallel} = \sqrt{3}V_B^{\ln}$$

Line current

$$I^{3\phi} = I_{an} = I^{1\phi}, \qquad I_{R}^{3\phi} = I_{R}^{1\phi}$$

Line-to-neutral voltage

$$V_B^{\mathsf{ln}} = V^{1\phi}, \qquad V_B^{\mathsf{ln}} = V_B^{1\phi}$$

Impedance

$$Z_{B}^{\phi} = Z^{1\phi}, \qquad Z_{B}^{3\phi} = Z_{B}^{3\phi}$$

#### Calculation

Base values satisfy the same relationship

# $3\phi$ quantities

#### $\Delta$ configuration

In terms of  $\left(S^{1\phi},V^{1\phi},I^{1\phi},Z^{1\phi}\right)$  and their base values

•  $3\phi$  power (total power to/from 3  $1\phi$  devices):

$$S^{3\phi} = 3S^{1\phi},$$

Line-to-line voltage

$$V^{\parallel} = \sqrt{3}e^{i\pi/6}\,V^{\ln},$$

Line current

$$I^{3\phi} = I_{ab} - I_{ca} = \sqrt{3} e^{-i\pi/6} I^{1\phi},$$

Line-to-neutral voltage

$$V^{\mathsf{ln}} = \left(\sqrt{3} e^{i\pi/6}\right)^{-1} V^{1\phi},$$

Impedance

$$Z^{3\phi} = Z^{1\phi}/3,$$

#### Note:

 $V^{\rm ln},\,Z^{3\phi}$  are voltage and & impedance in Y equivalent circuit

# 3\$\phi\$ quantities

#### $\Delta$ configuration

In terms of  $\left(S^{1\phi},V^{1\phi},I^{1\phi},Z^{1\phi}\right)$  and their base values •  $3\phi$  power (total power to/from 3  $1\phi$  devices):

$$S^{3\phi} = 3S^{1\phi},$$

$$S_B^{3\phi} = 3S_B^{1\phi}$$

Line-to-line voltage

$$V^{\parallel} = \sqrt{3}e^{i\pi/6}\,V^{\ln},$$

$$V_B^{\parallel} = \sqrt{3} V_B^{\ln}$$

Line current

$$I^{3\phi} = I_{ab} - I_{ca} = \sqrt{3} e^{-i\pi/6} I^{1\phi}, \qquad I_{p}^{3\phi} = \sqrt{3} I_{p}^{1\phi}$$

$$I_B^{3\phi} = \sqrt{3} I_B^{1\phi}$$

Line-to-neutral voltage

$$V^{\text{ln}} = \left(\sqrt{3} e^{i\pi/6}\right)^{-1} V^{1\phi},$$

$$V_B^{\text{ln}} = (\sqrt{3})^{-1} V_B^{1\phi}$$

Impedance

$$Z^{3\phi} = Z^{1\phi}/3,$$

$$Z_B^{3\phi} = Z_B^{1\phi}/3$$

#### Note:

and & impedance in Y equivalent circuit

# Per-unit quantities

Per-unit quantities satisfy

$$S_{\text{pu}}^{3\phi} = S_{\text{pu}}^{1\phi},$$
  $V_{\text{pu}}^{\text{II}} = V_{\text{pu}}^{\text{In}},$   $Z_{\text{pu}}^{3\phi} = Z_{\text{pu}}^{1\phi}$   $\left|V_{\text{pu}}^{\text{In}}\right| = \left|V_{\text{pu}}^{1\phi}\right|,$   $\left|I_{\text{pu}}^{3\phi}\right| = \left|I_{\text{pu}}^{1\phi}\right|$ 

- $3\phi$  quantities equal  $1\phi$  quantities in p.u.
- modulo phase shifts in  $\Delta$  configuration:

$$V_{\text{pu}}^{\text{ln}} := \frac{V^{\text{ln}}}{V_{B}^{\text{ln}}} = \frac{\left(\sqrt{3}e^{i\pi/6}\right)^{-1}V^{1\phi}}{\left(\sqrt{3}\right)^{-1}V_{B}^{1\phi}} = e^{-i\pi/6}V_{\text{pu}}^{1\phi}$$

# Per-unit per-phase analysis

- 1. For single-phase system, pick power base  $S_B^{1\phi}$  for entire system and voltage base  $V_{1B}^{1\phi}$  in area 1, e.g., induced by nameplate ratings of transformer
- 2. For balanced  $3\phi$  system, pick  $3\phi$  power base  $S_B^{3\phi}$  and line-to-line voltage base  $V_B^{II}$  induced by nameplate ratings of  $3\phi$  transformer. Then choose power & voltage bases for per-phase equivalent circuit:

$$S_B^{1\phi} := S_B^{3\phi} / 3, \qquad V_{1B}^{1\phi} := V_{1B}^{\parallel} / \sqrt{3}$$

 $S_{1R}^{1\phi}$  will be power base for entire per-phase circuit.

3. Calculate current and impedance bases in that area:

$$I_{1B} := \frac{S_B^{1\phi}}{V_{1B}^{1\phi}}, \qquad Z_{1B} := \frac{\left(V_{1B}^{1\phi}\right)^2}{S_B^{1\phi}}$$

# Per-unit per-phase analysis

4. Calculate base values for voltages, currents, and impedances in areas i connected to area 1 using the magnitude  $n_i$  of transformer gains (assume area 1 is primary):

$$V_{iB}^{1\phi} := n_i V_{1B}^{1\phi}, \qquad V_{iB}^{\parallel} := n_i V_{1B}^{\parallel}, \qquad I_{iB} := \frac{1}{n_i} I_{1B}, \qquad Z_{iB} := n_i^2 Z_{1B}$$

Continue this process to calculate the voltage, current, and impedance base values for all areas

# Per-unit per-phase analysis

- 5. For real, reactive, apparent power in entire system, use  $S_B^{1\phi}$  as base value.
  - For resistances and reactances, use  $Z_{iB}$  as base value in area i.
  - For admittances, conductances, and susceptancesq, use  $Y_{iB} := 1/Z_{iB}$  as base value in area i
- 6. Draw impedance diagram of entire system, and solve for desired per-unit quantities
- 7. Convert back to actual quantities if desired

# Summary

- 1. Single-phase transformer
  - Ideal transformer gain *n*, equivalent circuit
- 2. Three-phase transformer
  - YY,  $\Delta\Delta$ ,  $\Delta Y$ ,  $Y\Delta$ : external behavior, YY equivalent
- 3. Equivalent impedance
  - Short cut for analyzing circuits containing transformers
  - Transmission matrix, driving-point impedance
- 4. Per-phase analysis
- 5. Per-unit normalization
  - Physical laws, across transformer,  $3\phi$  quantities, per-unit per-phase analysis