

The Flow of Power

Steven Low



Caltech

Simons Institute: Real-time Decision Making Bookcamp
Power Systems, Berkeley, January 2018



Bootcamp: Power systems

The flow of power (S Low)

- Basic concepts and models
- Power flow and optimization

The flow of information (S Meyn)

- Distributed control architectures

The flow of money (K Poolla)

- Market structures and services

from steady state to dynamics
from engineering to economics



R. Karp's instruction

"... the level should be sufficiently elementary that an expert on the topic will be bored."



The flow of power I

Basic concepts and models

Why smart grid? (15 mins)

Three-phase AC transmission: 3 key ideas (30 mins)

- Phasor representation
- Balanced operation
- Per-phase analysis

Device models (30 mins)

- Transmission line
- Transformer
- Generator



The flow of power II

Power flow and optimization

Network models (10mins)

- Admittance matrix
- Power flow models

Optimal power flow problems (35mins)

- Formulation and example
- Convex relaxations
- Real-time OPF




Why smart grid?



Watershed moment

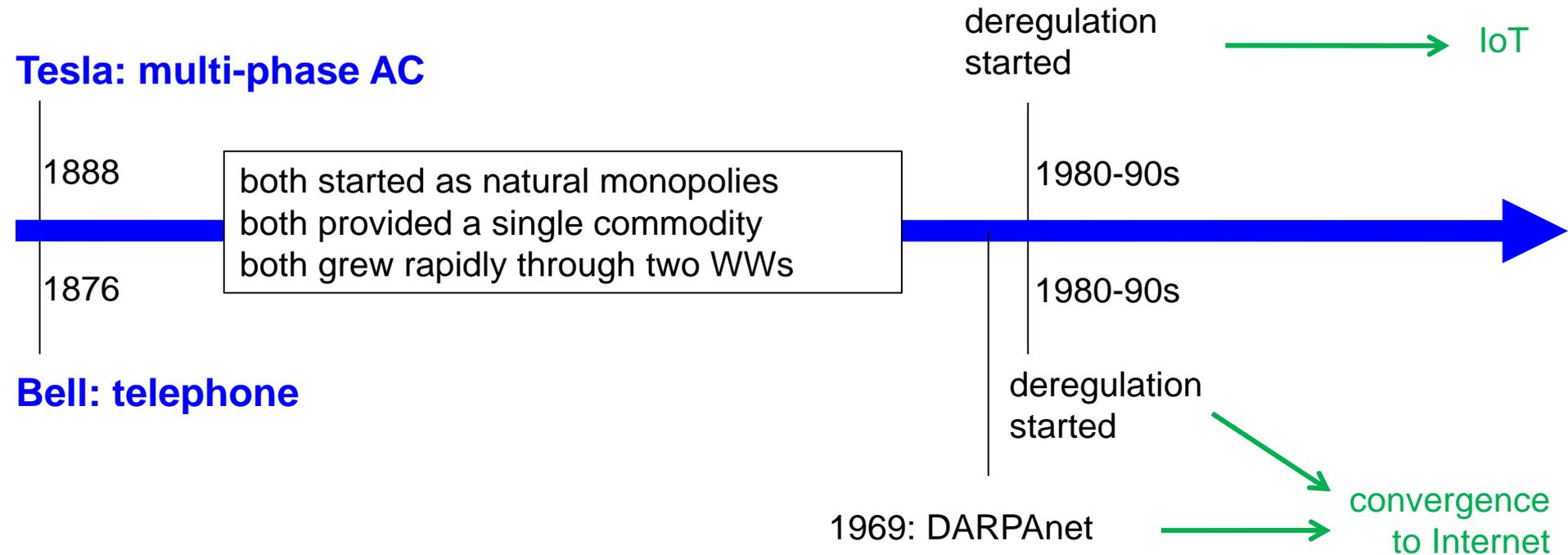Energy network will undergo similar **architectural transformation** that phone network went through in the last two decades to become the world's largest and most complex IoT





Watershed moment

Industries will be restructured

AT&T, MCI, McCaw Cellular, **Qualcom**

Google, Facebook, Twitter, Amazon, eBay, Netflix

Infrastructure will be reshaped

Centralized intelligence, vertically optimized

Distributed intelligence, layered architecture



Watershed moment

The five largest companies in 2006 ...

1 Exxon Mobil	\$540 BILLION MARKET CAP
2 General Electric	463
3 Microsoft	355
4 Citigroup	331
5 Bank of America	290



Watershed moment

The five largest companies in 2006 ...

1 Exxon Mobil	\$540 BILLION MARKET CAP
2 General Electric	463
3 Microsoft	355
4 Citigroup	331
5 Bank of America	290



... and now (April 20, 2017)

1 Apple	\$794
2 Alphabet (Google)	593
3 Microsoft	506
4 Amazon	429
5 Facebook	414

What will drive power network transformation ?



Electricity gen & transportation

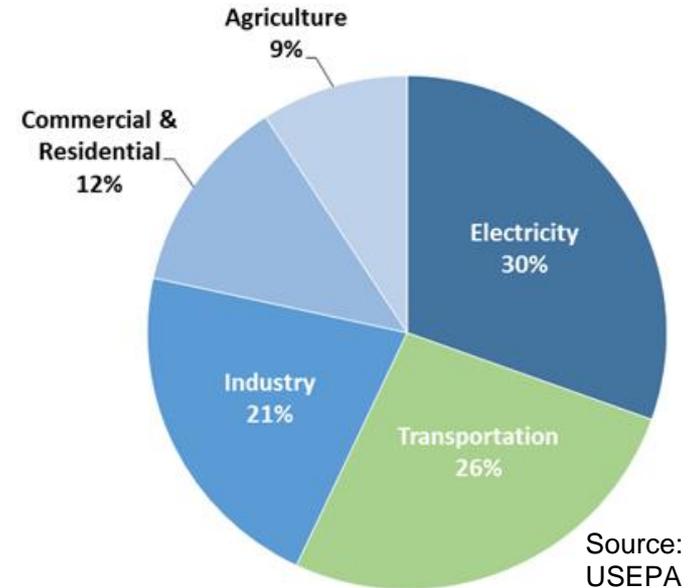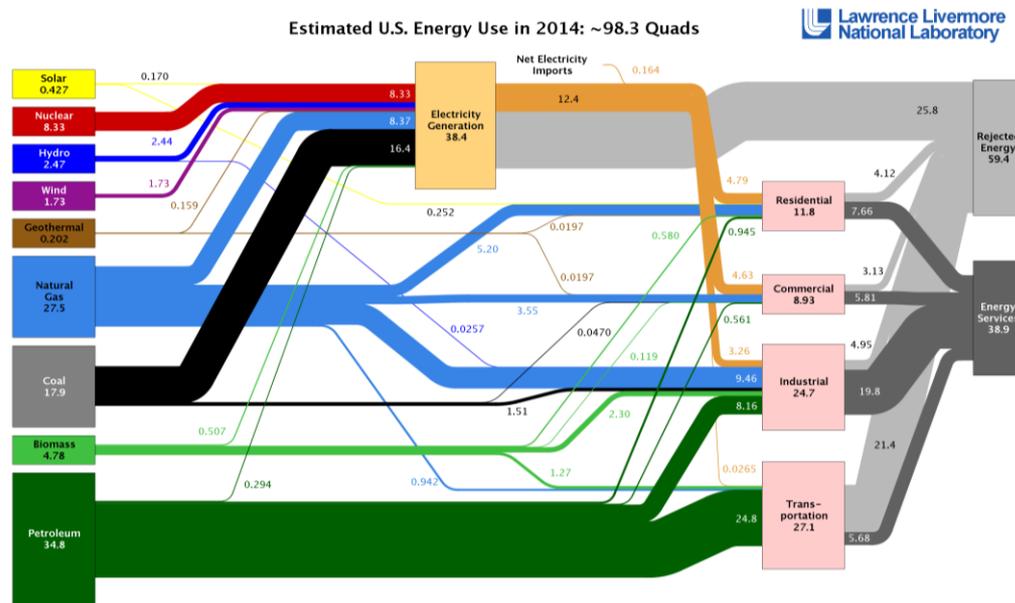

They consume the most energy

- Consume 2/3 of all energy in US (2014)

They emit the most greenhouse gases

- Emit >1/2 of all greenhouse gases in US (2014)

To drastically reduce greenhouse gases

- Generate electricity from renewable sources
- Electrify transportation



World energy stats (2011)

Consumption	519 quad BTU
petroleum	34%
coal	29%
gas	23%
renewable (elec)	8%
nuclear	5%

top 5
countries

Consumption	519 (quad BTU)	per capita (mil BTU)
China	20%	78
US	19%	313
Russia	6%	209
India	5%	20
Japan	4%	164
total	54%	



World energy stats (2011)


Consumption	519 quad BTU
petroleum	34%
coal	29%
gas	23%
renewable (elec)	8%
nuclear	5%

top 5 countries

Consumption	519 (quad BTU)	CO2 emission
China	20%	27%
US	19%	17%
Russia	6%	5%
India	5%	5%
Japan	4%	4%
total	54%	58%



US greenhouse gas emission 2014

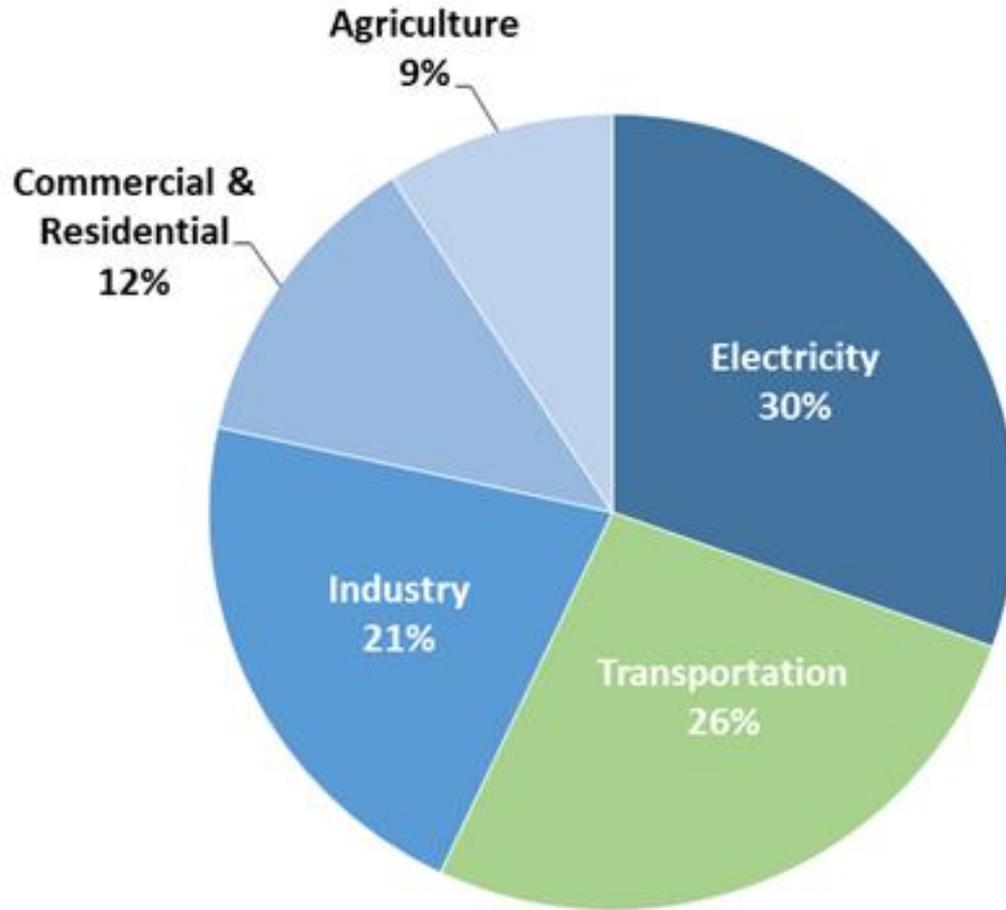


Electricity generation and transportation are top-two GHG emitters (56% total)

... and they consume the most energy (66% total)

Total (2014) = 6,870 Million Metric Tons of CO₂ equivalent




US energy flow 2014

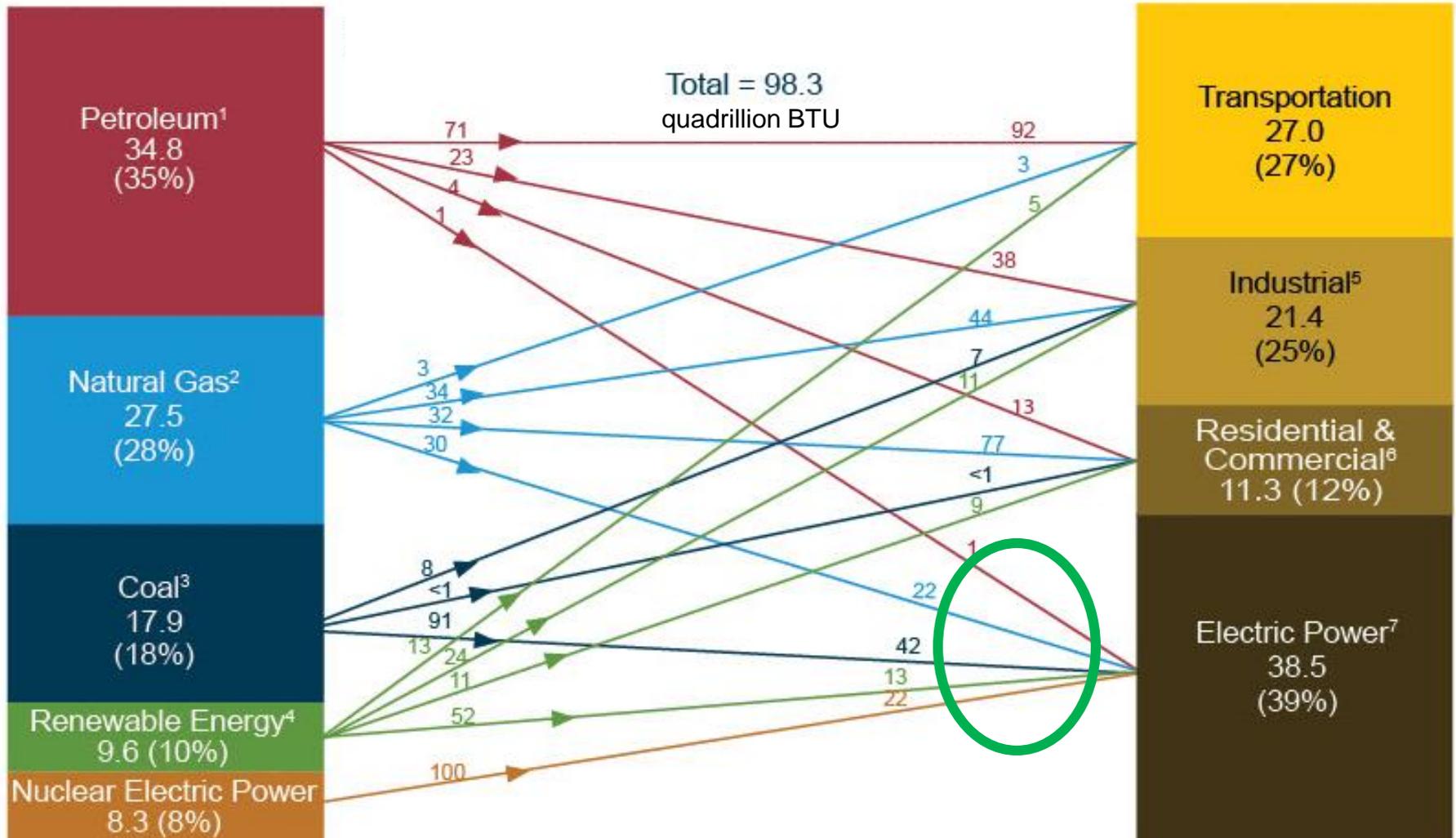






US electricity flow 2014



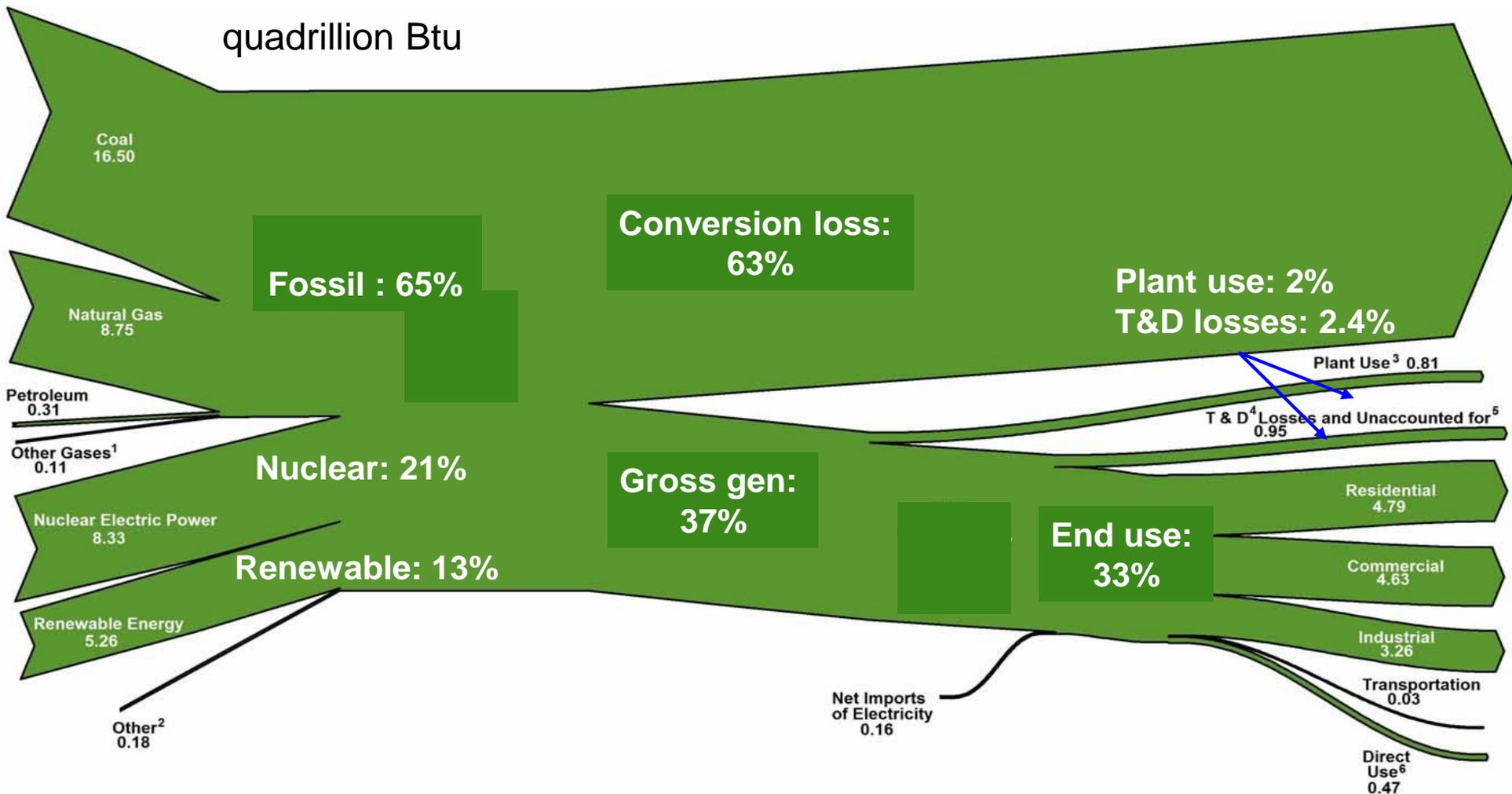


US total energy use: 98.3 quads
For electricity gen: 39%

US dirty supply

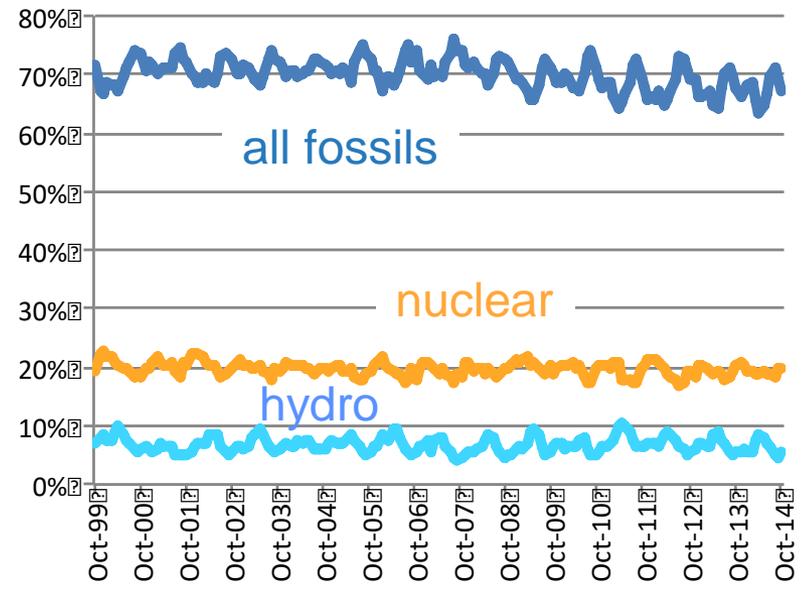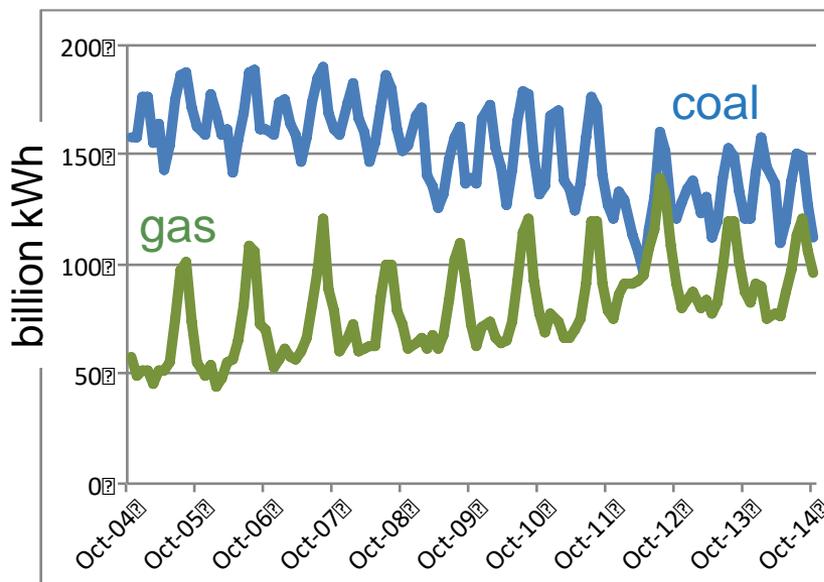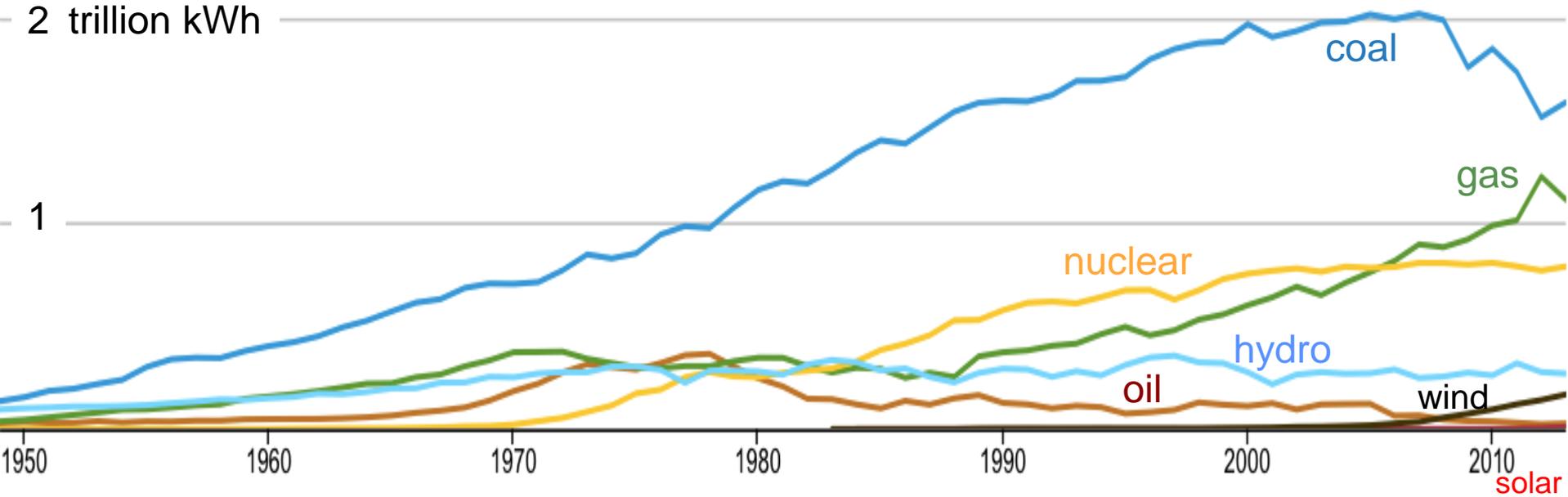


US renewable generations

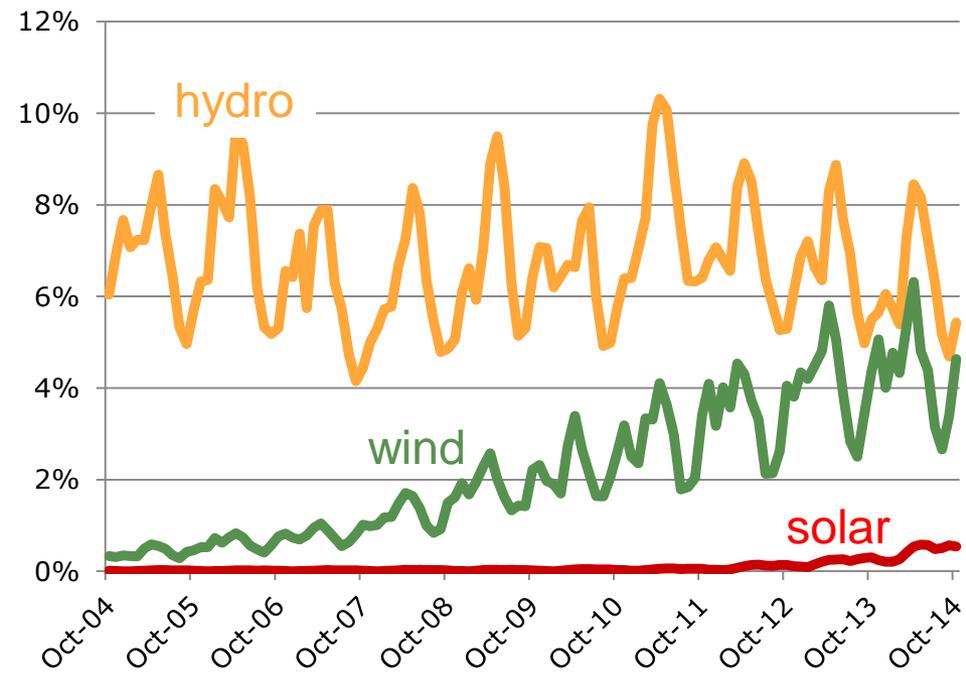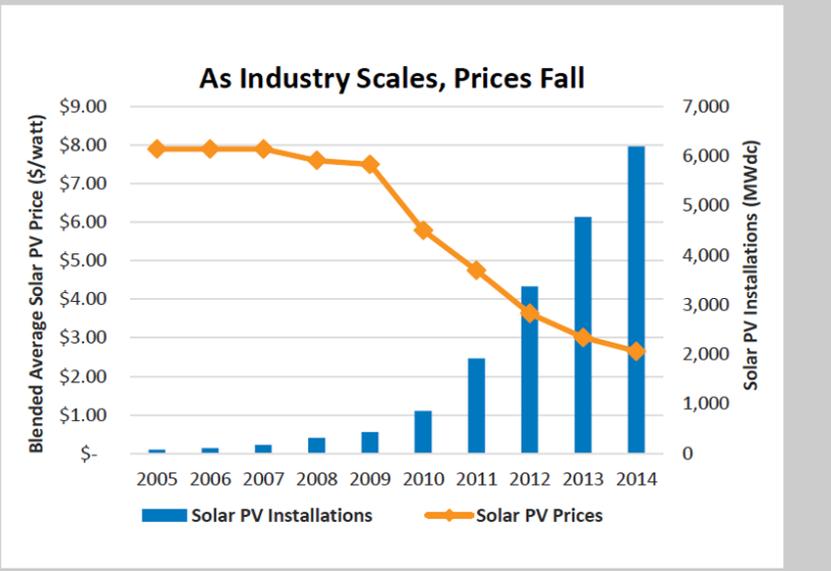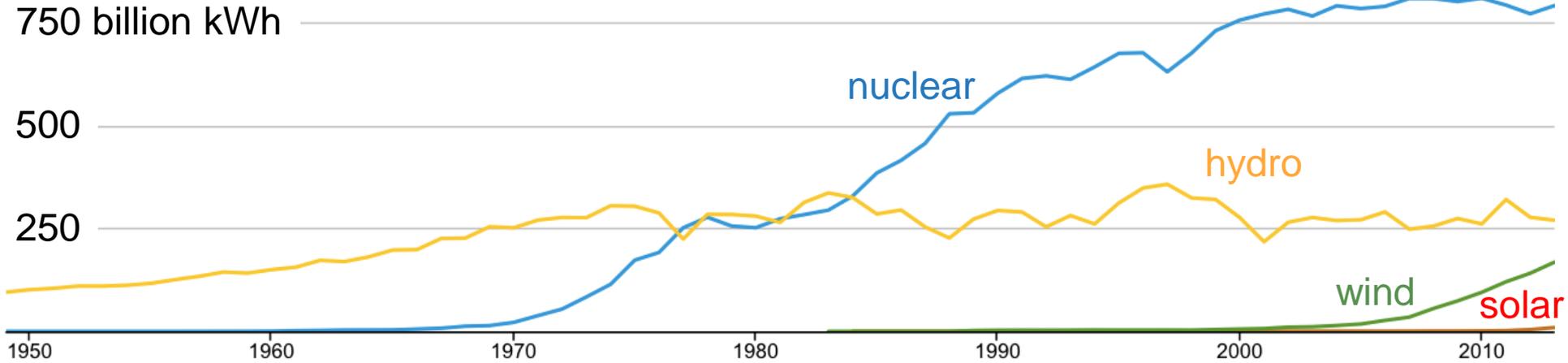

US wind capacity

A Growing Source

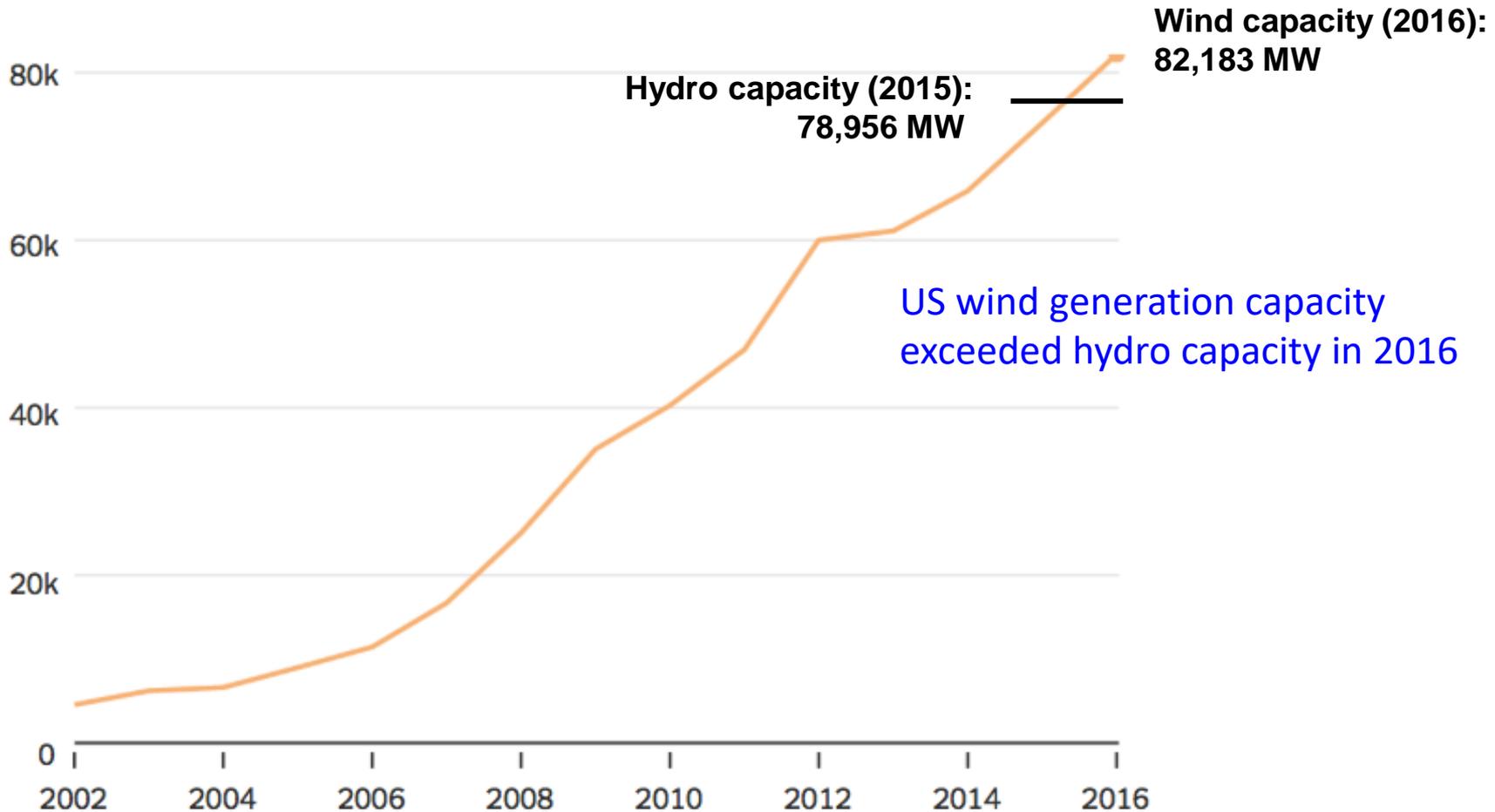
Cumulative wind power capacity in the United States, in megawatts.




Source: American Wind Energy Association

US solar capacity

Yearly U.S. Solar Installations

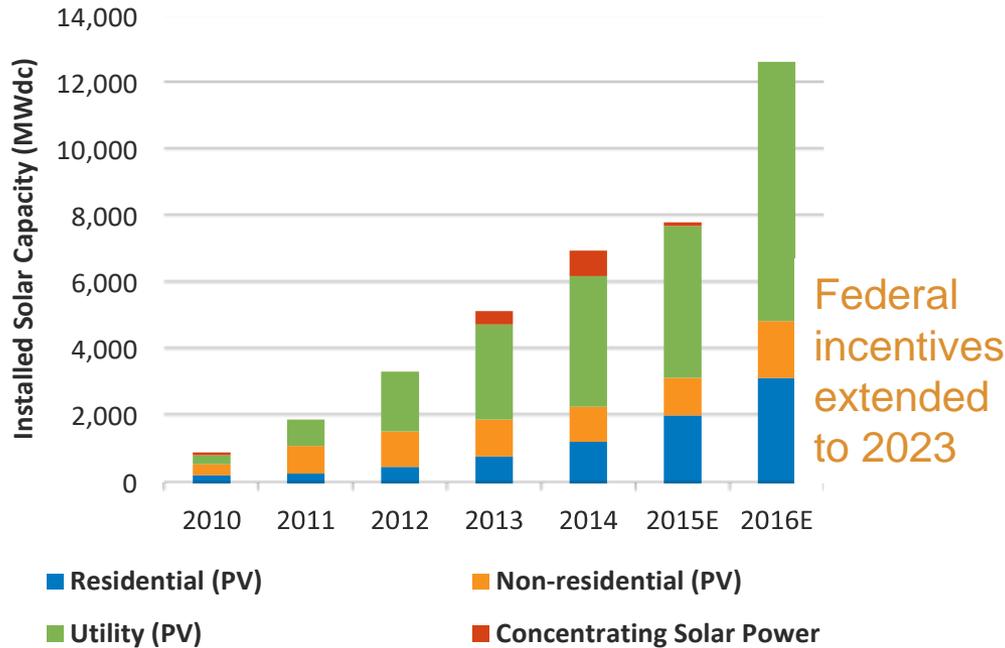

2014 New Electric Capacity Installed

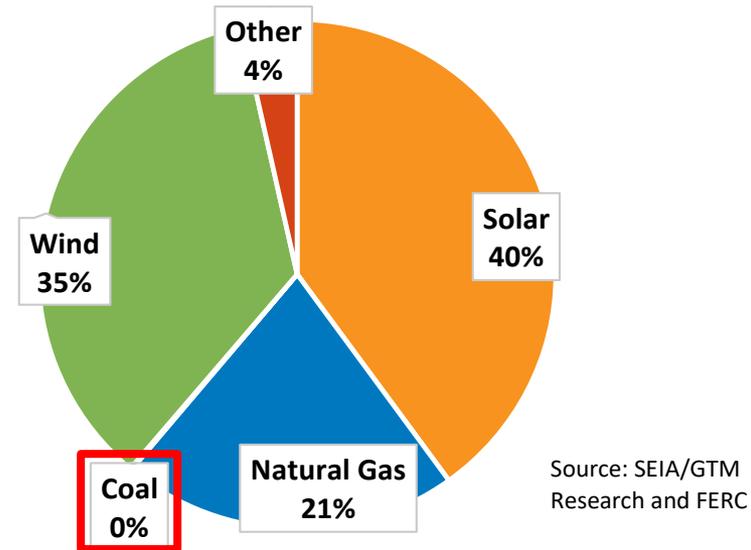


US solar industry snapshot

- US installed solar capacity by mid 2015: ~23 GW
 - 784K homes and businesses
- Q2 2015 solar installation: 1.4 GW
 - Utility: 729 MW
 - Residential: 473 MW (70% growth yr-on-yr)
- H1 2015: a new solar installation / 2 mins

Annual PV additions: historic data vs IEA WEO predictions

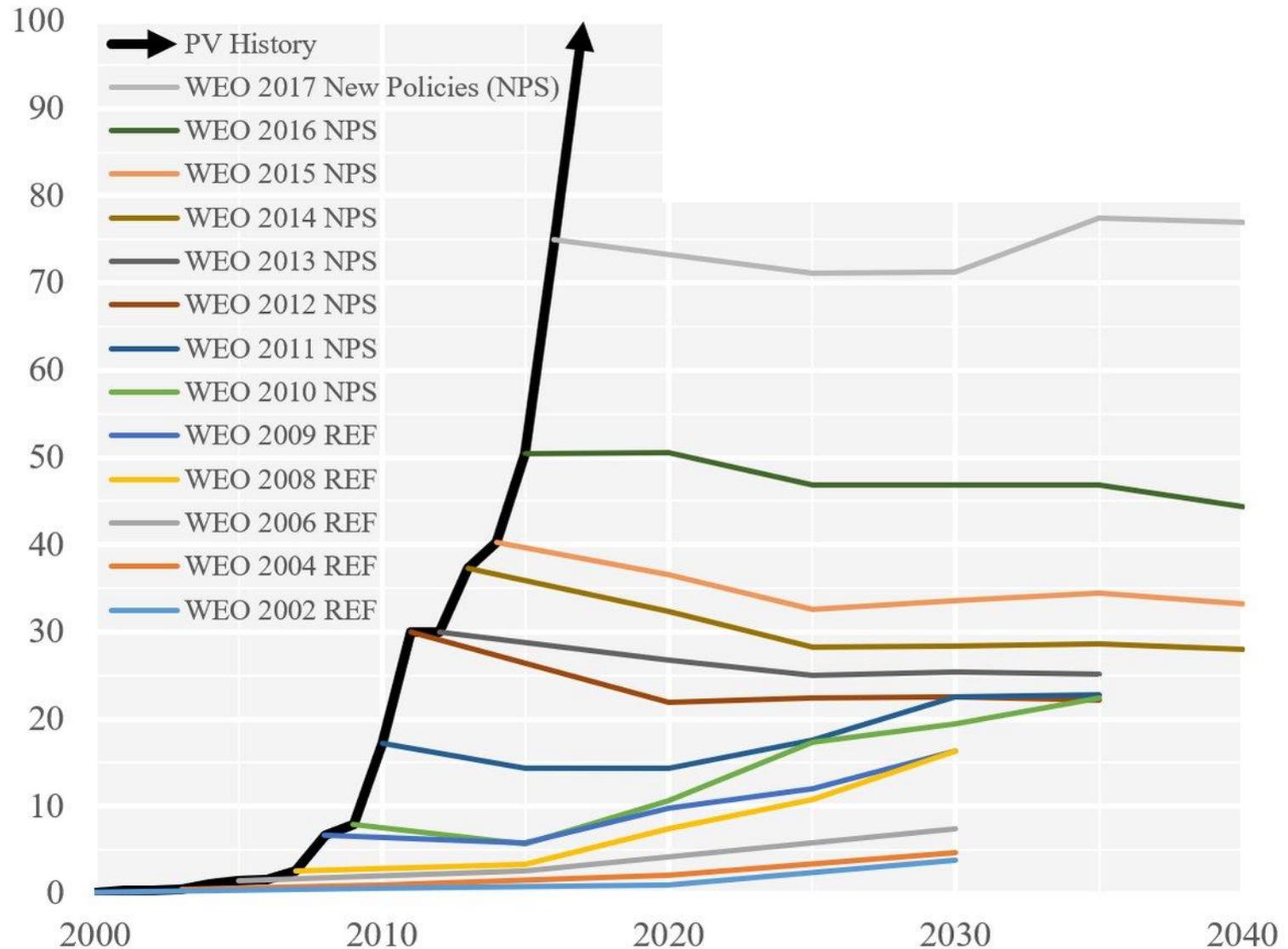In GW of added capacity per year - source International Energy Agency - World Energy Outlook



Power the world by solar



■ 1980 (based on actual use)
207,368 SQUARE KILOMETERS

■ 2008 (based on actual use)
366,375 SQUARE KILOMETERS

■ 2030 (projection)
496,805 SQUARE KILOMETERS

- Areas are calculated based on an assumption of 20% operating efficiency of collection devices and a 2000 hour per year natural solar input of 1000 watts per square meter striking the surface.
- These 19 areas distributed on the map show roughly what would be a reasonable responsibility for various parts of the world based on 2009 usage. They would be further divided many times, the more the better to reach a diversified infrastructure that localizes use as much as possible.
- The large square in the Saharan Desert (1/4 of the overall 2030 required area) would power all of Europe and North Africa. Though very large, it is 18 times less than the total area of that desert.
- The definition of "power" covers the fuel required to run all electrical consumption, all machinery, and all forms of transportation. It is based on the US Department of Energy statistics of worldwide Btu consumption and estimates the 2030 usage (678 quadrillion Btu) to be 44% greater than that of 2008.
- Area calculations do not include magenta border lines.





Uncertainty



Tehach


700

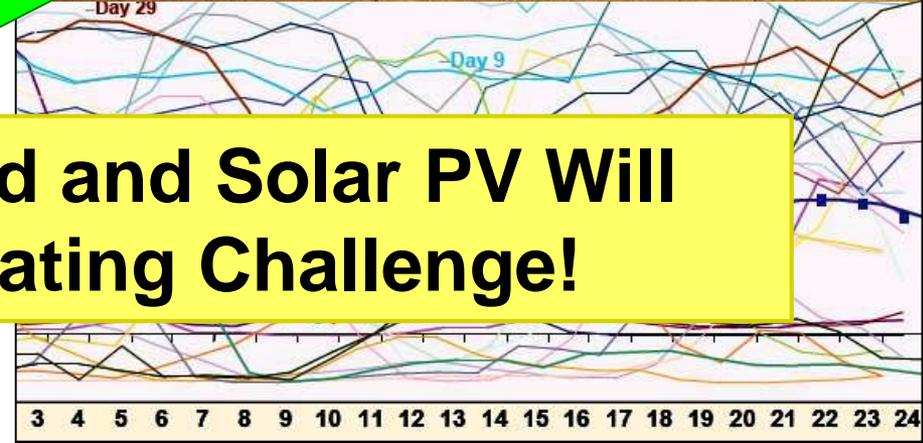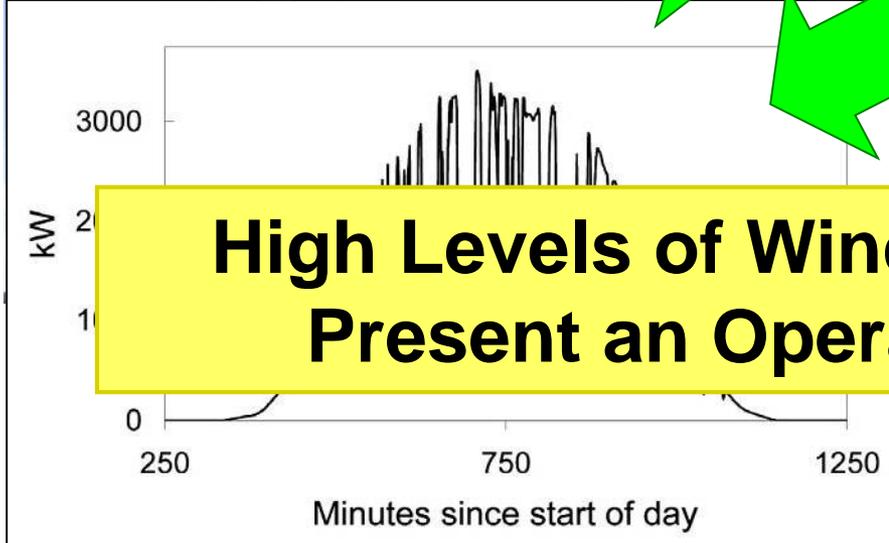

High Levels of Wind and Solar PV Will Present an Operating Challenge!

Source: Rosa Yang, EPRI

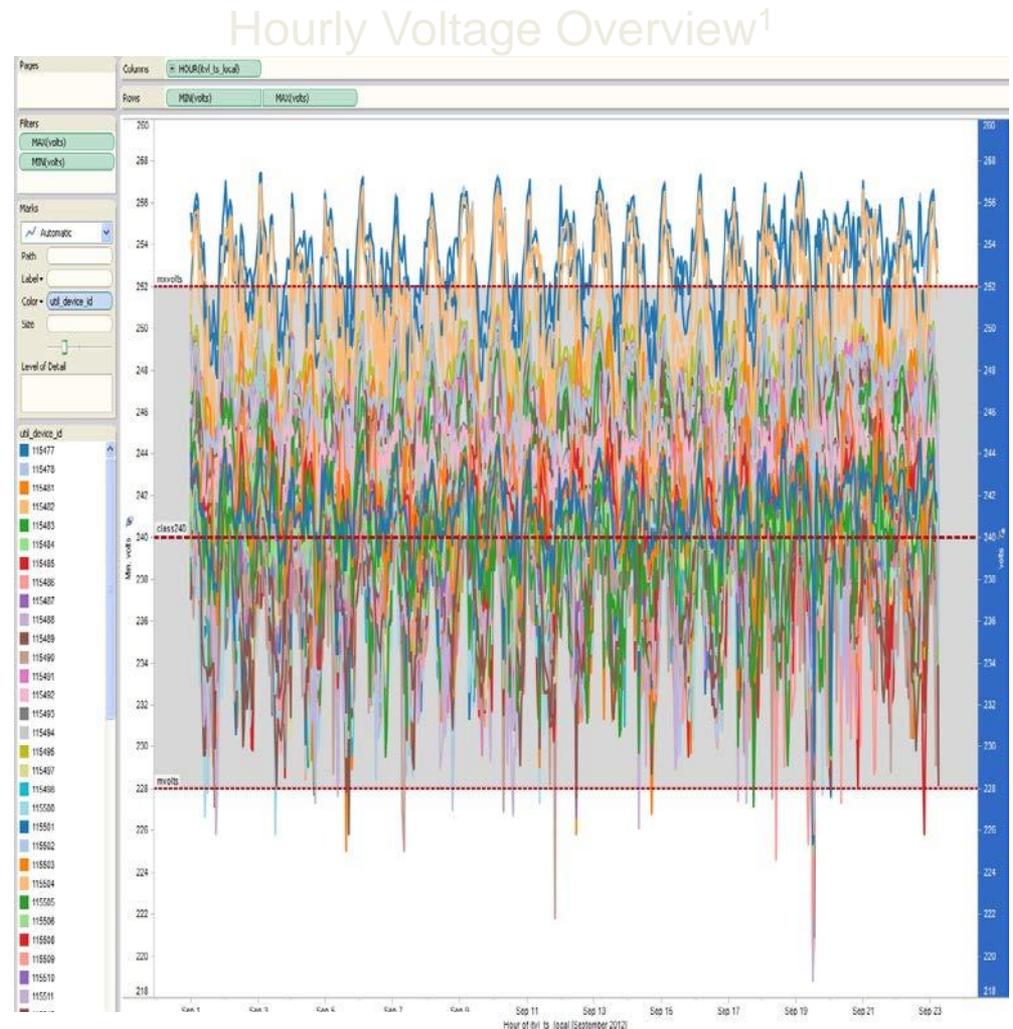- 68 meters (residential)
- Sept 2012 (23 days)
- 240 volts
- +/-5% min-228/max-252
- Hourly by meter #
- A few “high” meters
- Larger # of low meters



Voltage violations are quite frequent



High Penetration

2013

Feb 13-14, San Diego, CA


Source: Leon Roose, University of Hawaii
 Development & demo of smart grid inverters for high-penetration PV applications

Hourly Voltage Overview¹

Hawaii's solar power flare-up: Too much of a good thing?

So many private solar panels are returning power to the grid that utilities systems can't handle it all.

November 17, 2013

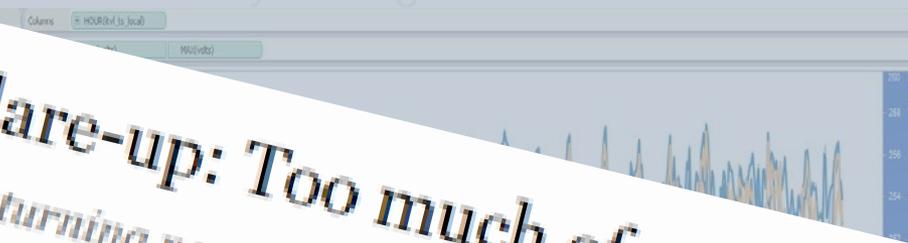

Germany's Green Energy Destabilizing Electric Grids

“Energiewende”

JANUARY 23, 2013

Power struggle: Green energy versus a grid that's not ready

Minders of a fragile national power grid say the rush to renewable energy might actually make it harder to keep the lights on.

December 02, 2013 | By Evan Halper

Renewable Energy Revolution Hiccups: Grid Instability

By Catalina Schröder

Sudden fluctuations in Germany's power grid are causing major damage to power companies. While many of them have responded by getting their own backup generators, they warn that companies might be forced to shut down with the issues fast.


WALL

Power customers opt to go off grid

Power customers are opting to go off grid as a result of a September surge in energy prices, according to a survey by the utility. The survey also found that many customers have opted to go off grid as a result of a September surge in energy prices, according to a survey by the utility. The survey also found that many customers have opted to go off grid as a result of a September surge in energy prices, according to a survey by the utility.



Today's grid

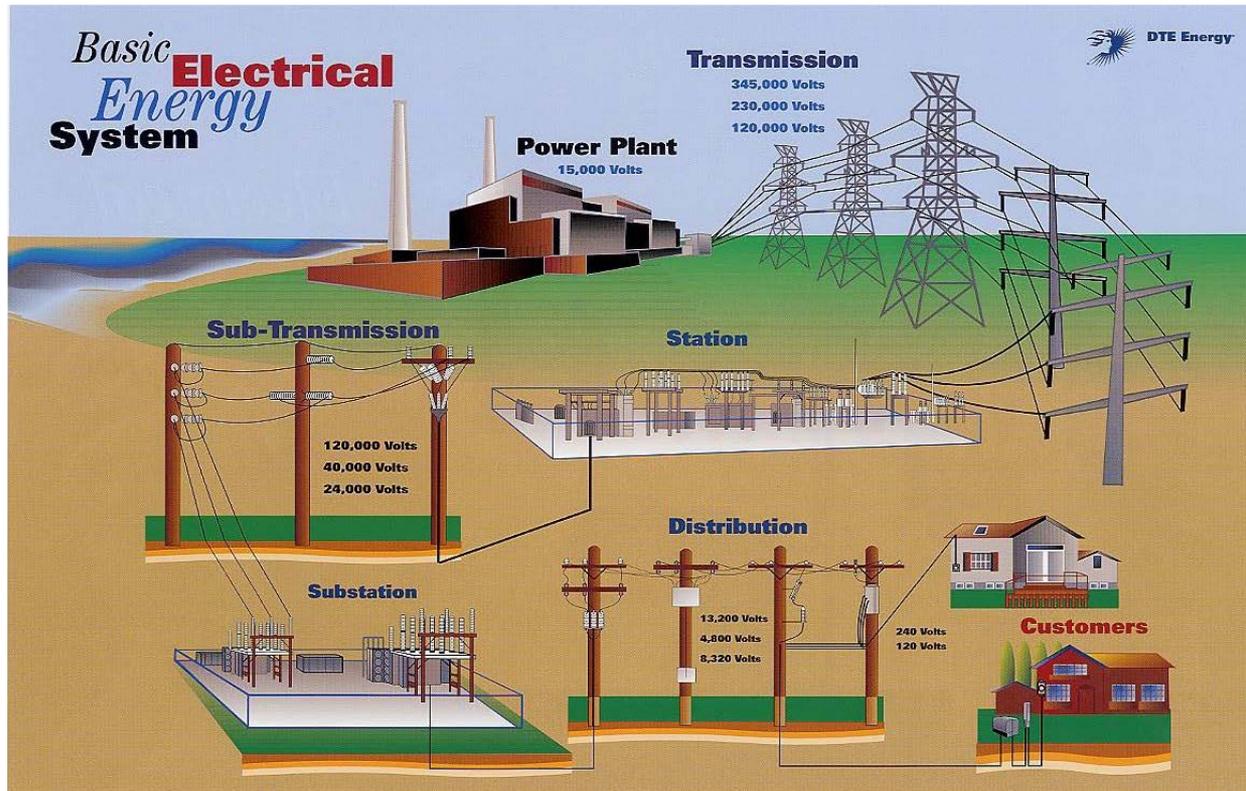

Few large generators

- ~10K bulk generators (>90% capacity), actively controlled

Many dump loads


- 131M customers, 3,100 utilities, ~billion passive loads

Control paradigm: schedule supply to match demand

- Centralized, human-in-the-loop, worst case, deterministic



Future grid

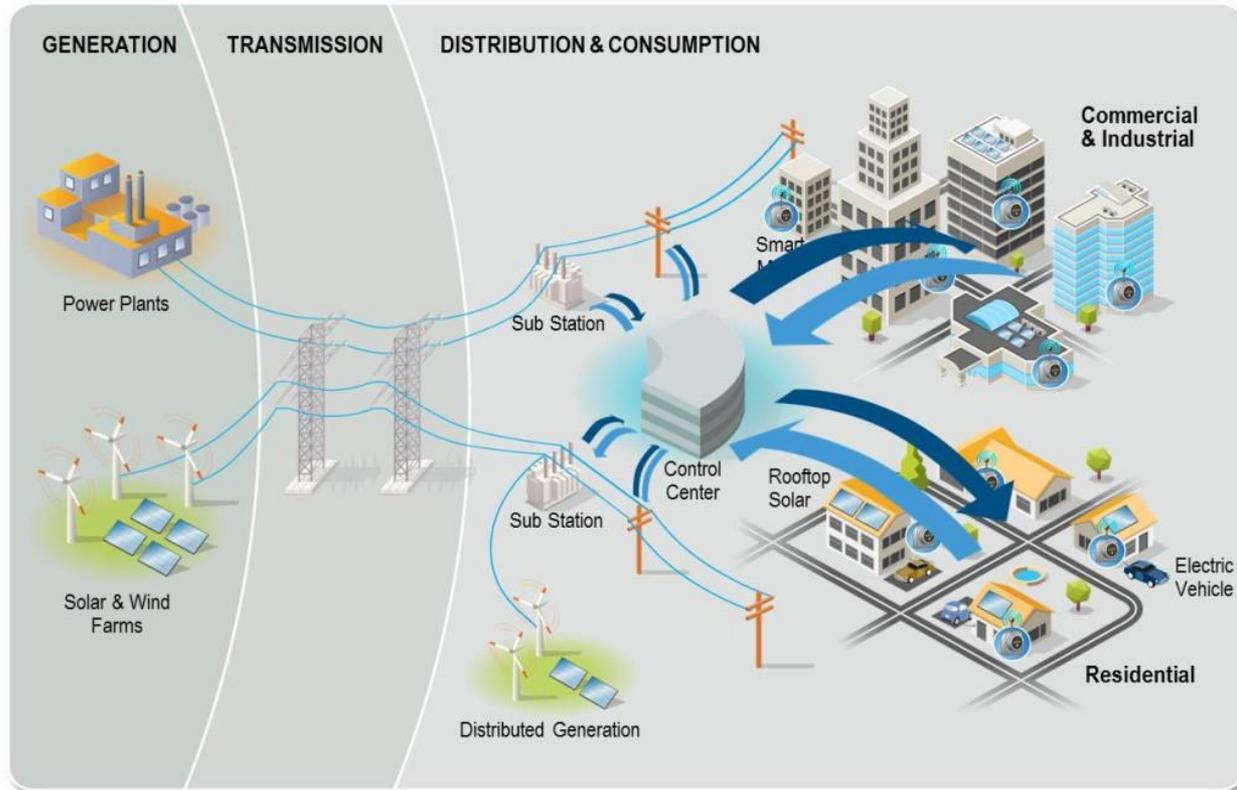

Wind and solar farms are not dispatchable


- Many small distributed generations

Network of distributed energy resources (DERs)

- EVs, smart buildings/appliances/inverters, wind turbines, storage

Control paradigm: match demand to volatile supply

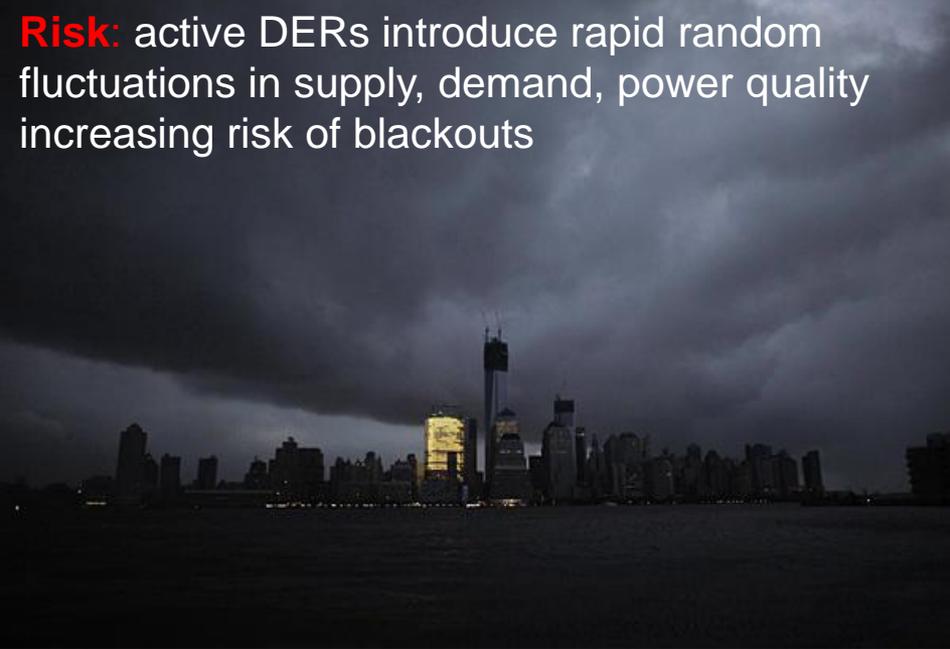- Distributed, real-time feedback, risk limiting, robust




Risk: active DERs introduce rapid random fluctuations in supply, demand, power quality increasing risk of blackouts


Opportunity: active DERs enables realtime dynamic network-wide feedback control, improving robustness, security, efficiency

SMART GRID

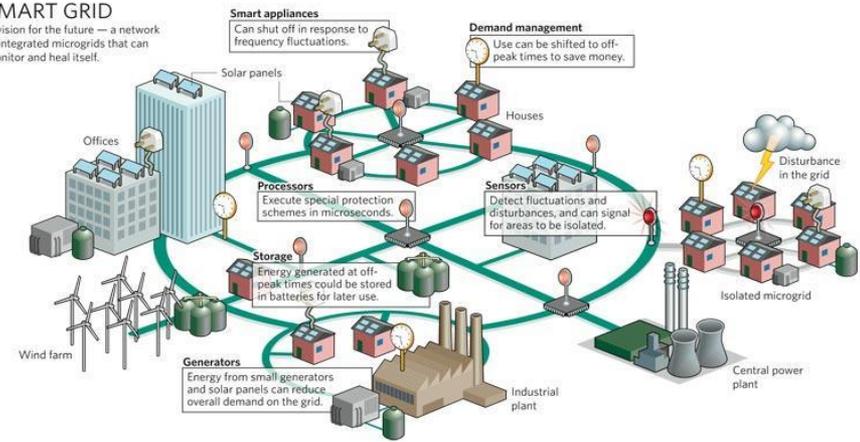
A vision for the future — a network of integrated microgrids that can monitor and heal itself.



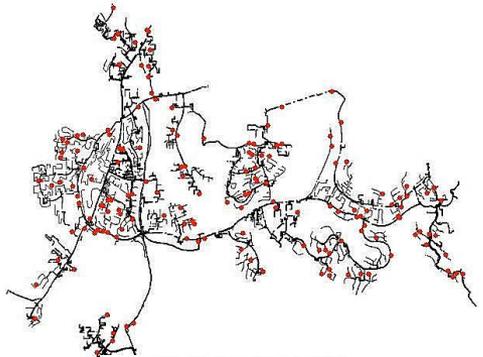Caltech research: distributed control of networked DERs



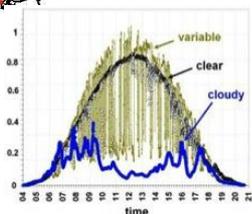- Foundational theory, practical algorithms, concrete applications
- Integrate engineering and economics
- Active collaboration with industry





Recap

Global energy demand will continue to grow

There is more renewable energy than the world ever needs

- Someone will figure out how to capture and store it

There will be connected intelligence everywhere

- Cost of computing, storage, communication and manufacturing will continue to drop

→ Power system will transform into the largest and most complex Internet of Things

- Generation, transmission, distribution, consumption, storage



Recap

To develop technologies that will enable and guide the historic transformation of our power system

- Materials, devices, systems, theory, algorithms
- Control, optimization, stochastics, data, economics



Motivation: Optimal power flow

min	$\text{tr} (CVV^H)$	gen cost, power loss
over	(V, s, l)	
subject to	$s_j = \text{tr} (Y_j^H VV^H)$	power flow equation
	$l_{jk} = \text{tr} (B_{jk}^H VV^H)$	line flow
	$\underline{s}_j \leq s_j \leq \bar{s}_j$	injection limits
	$\underline{l}_{jk} \leq l_{jk} \leq \bar{l}_{jk}$	line limits
	$\underline{V}_j \leq V_j \leq \bar{V}_j$	voltage limits

- Y_j^H describes network topology and impedances
- s_j is net power injection (generation) at node j



The flow of power I

Basic concepts and models

Why smart grid? (15 mins)

Three-phase AC transmission: 3 key ideas (30 mins)

- Phasor representation
- Balanced operation
- Per-phase analysis

Device models (30 mins)

- Transmission line
- Transformer
- Generator



Visualizing the grid

adapted from

Electric Power Delivery Systems (


Tutorial at U.C. Berkeley (

September 11, 2009 (

(


Dr. Alexandra "Sascha" von Meier (

003/45/7844

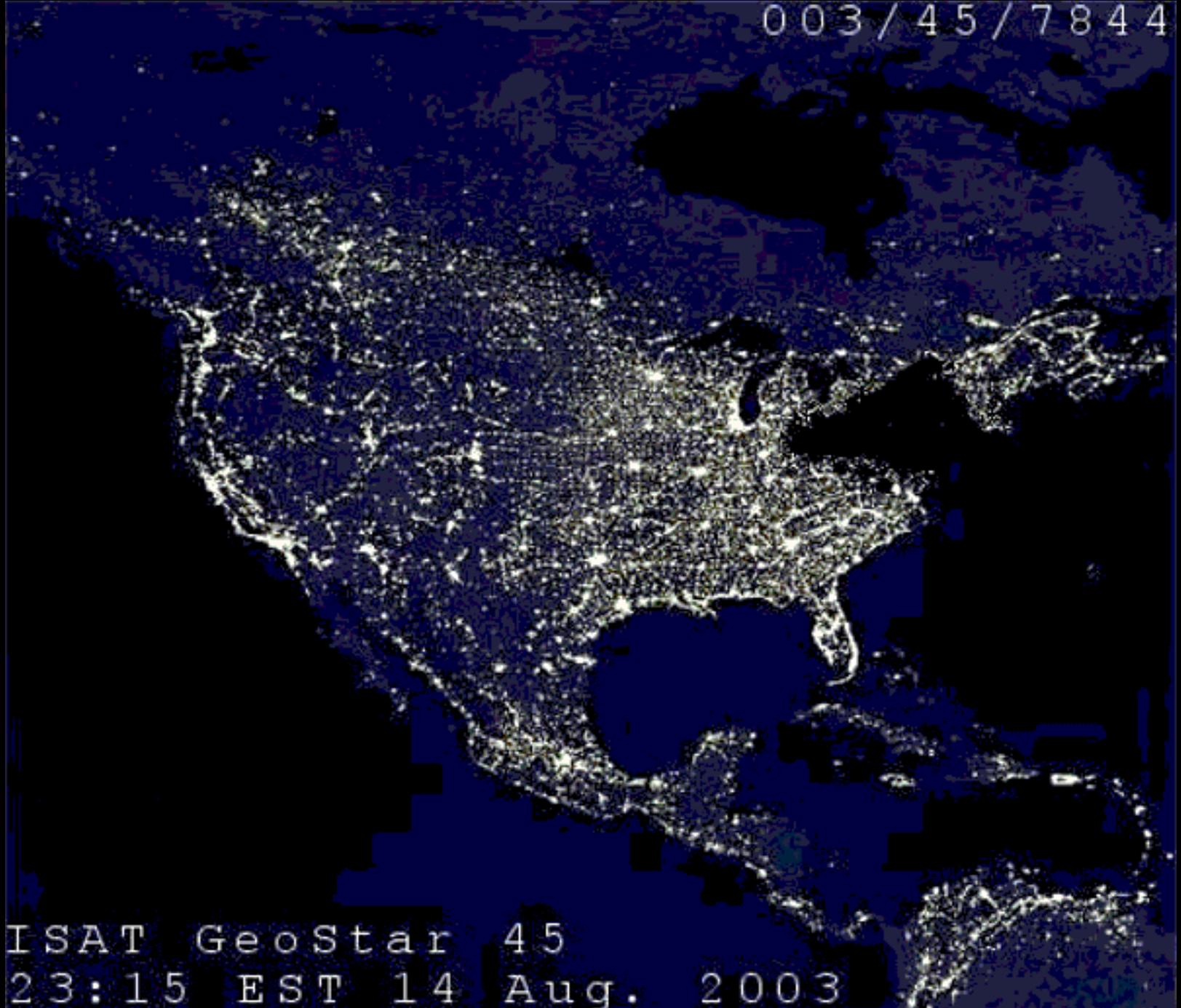

ISAT GeoStar 45
23:15 EST 14 Aug. 2003

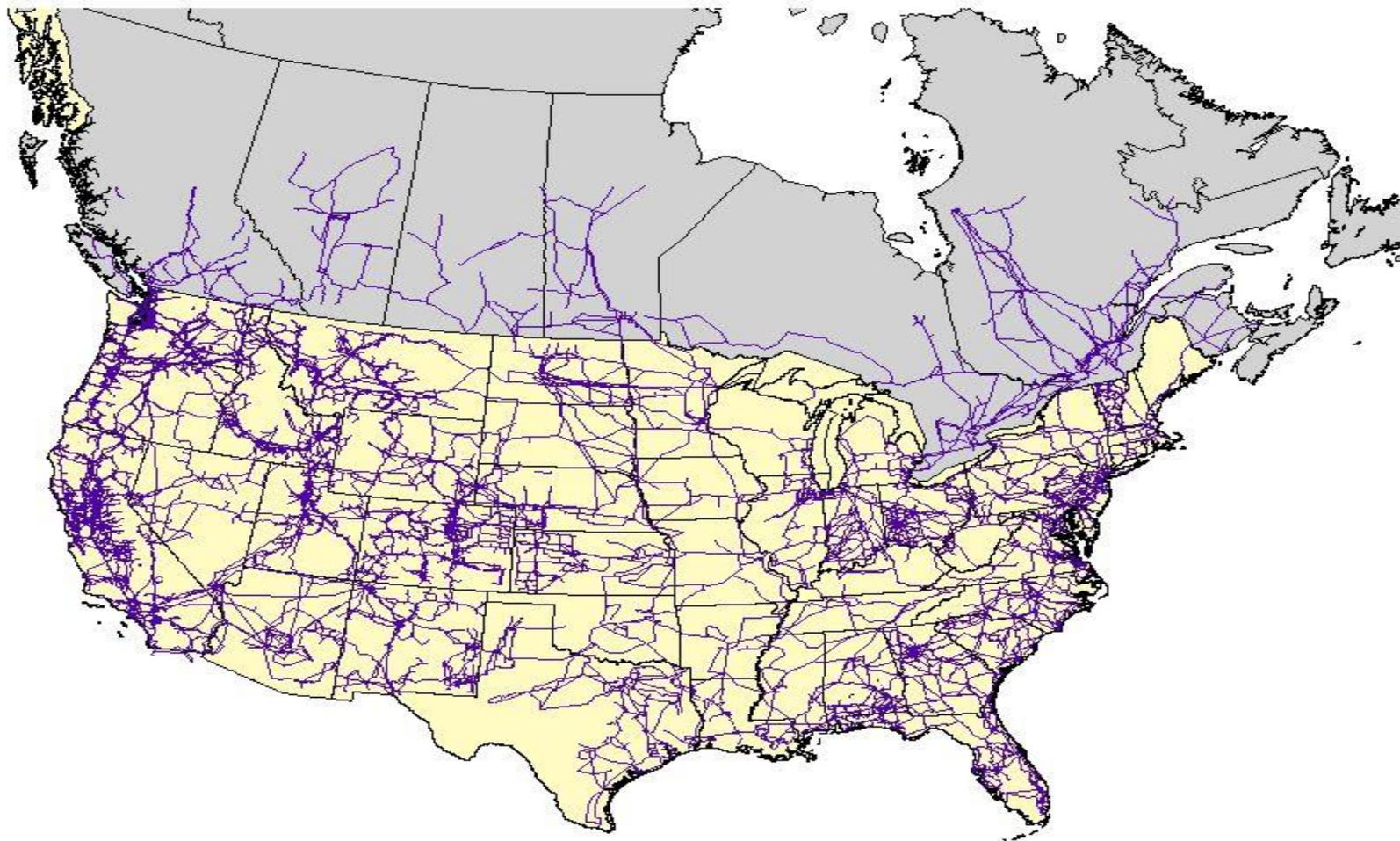
PennWell MAPSearch Electric Transmission & Distribution Systems



Transmission lines: 190K miles
Distribution lines: 73K miles
(2002)



Today's grid

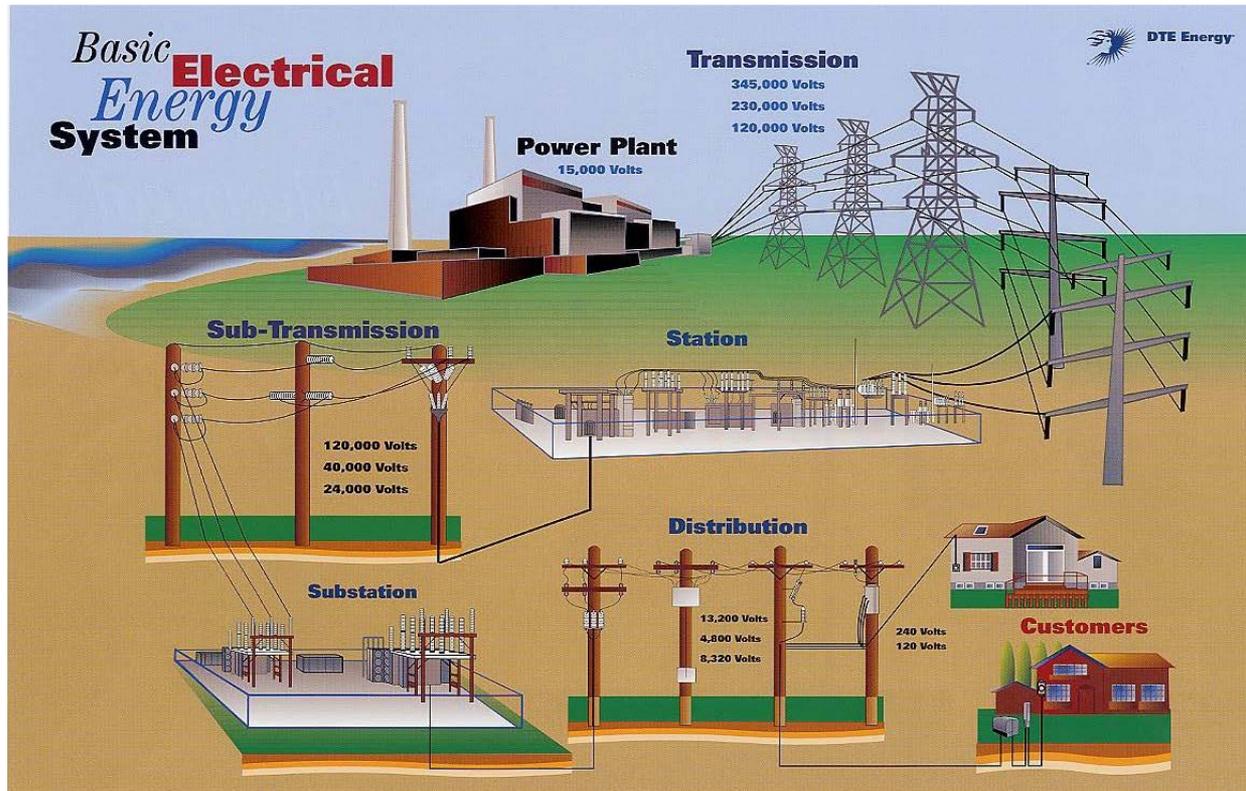

Few large generators

- ~10K bulk generators (>90% capacity), actively controlled


Many dump loads

- 131M customers, 3,100 utilities, ~billion passive loads

Control paradigm: schedule supply to match demand


- Centralized, human-in-the-loop, worst case, deterministic

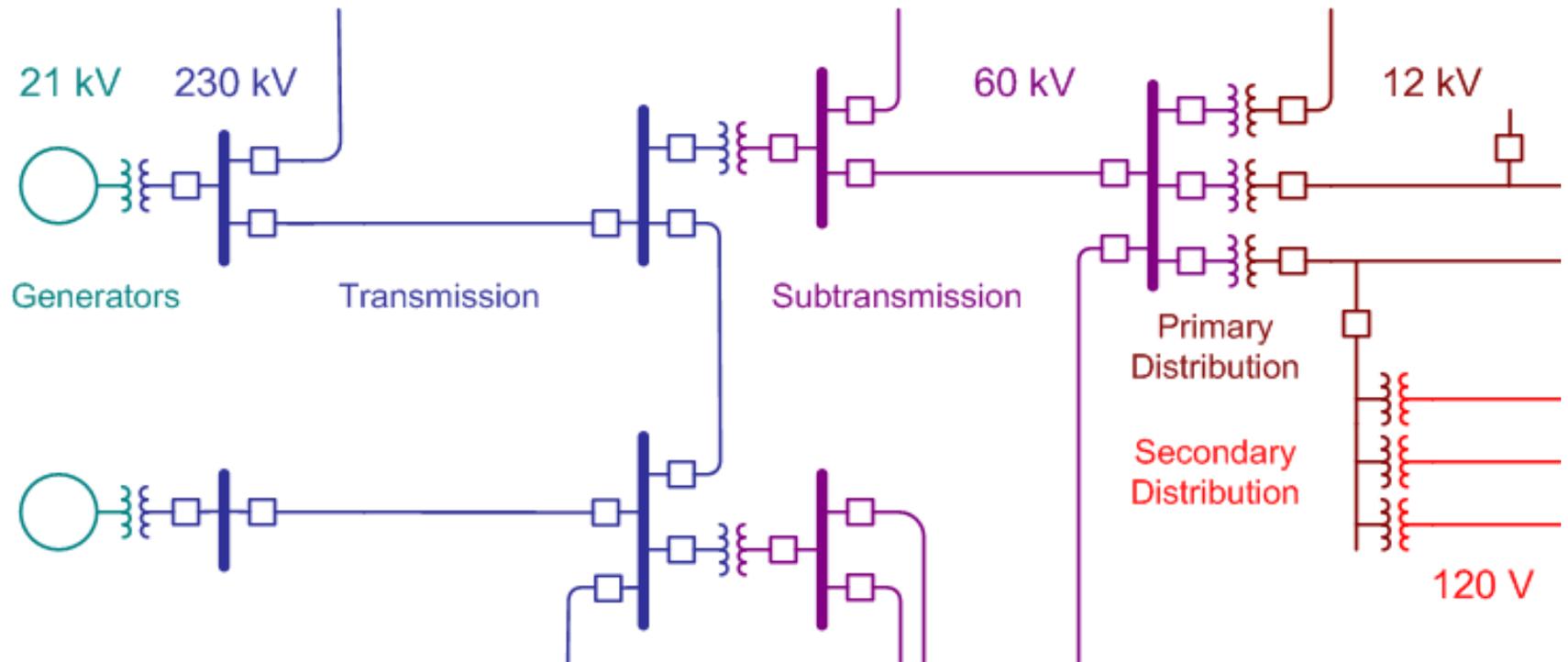Power System Structure with typical voltage levels





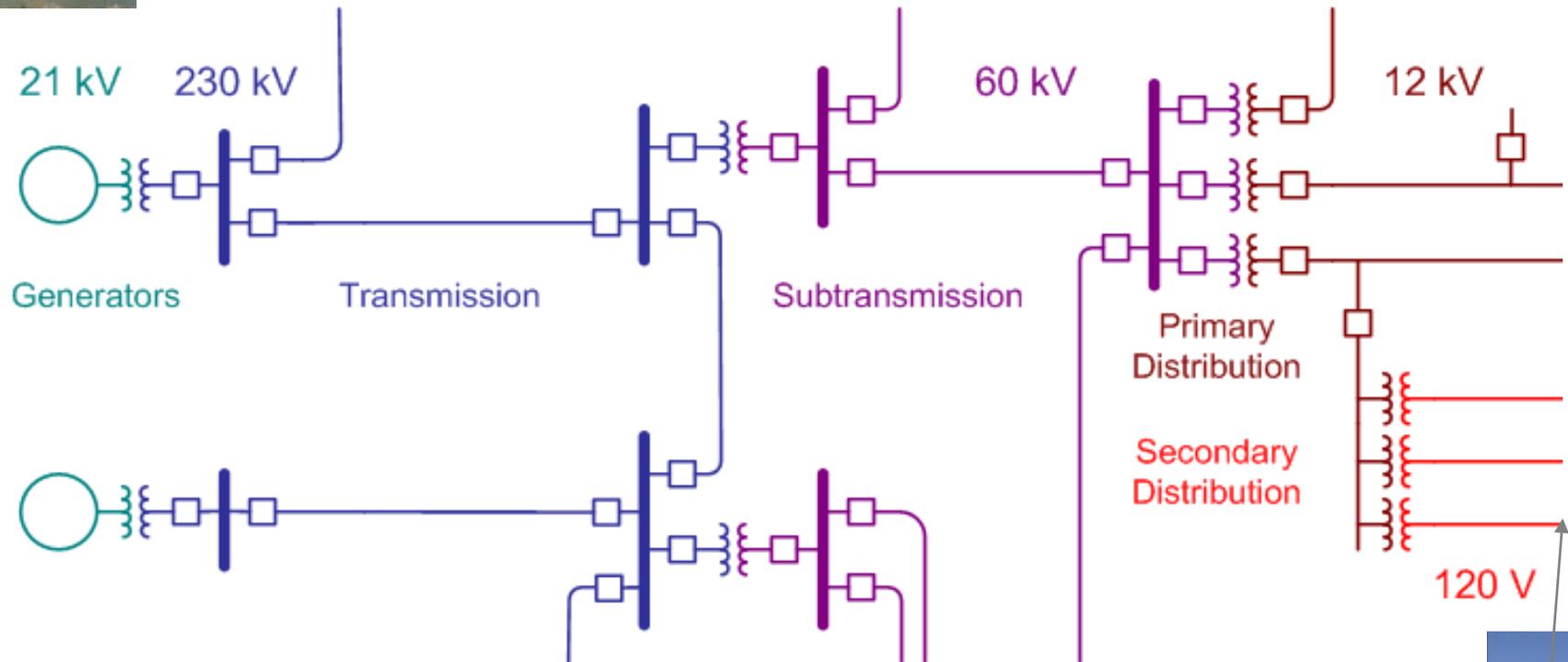Power System Structure with typical voltage levels




service drop



transmission line

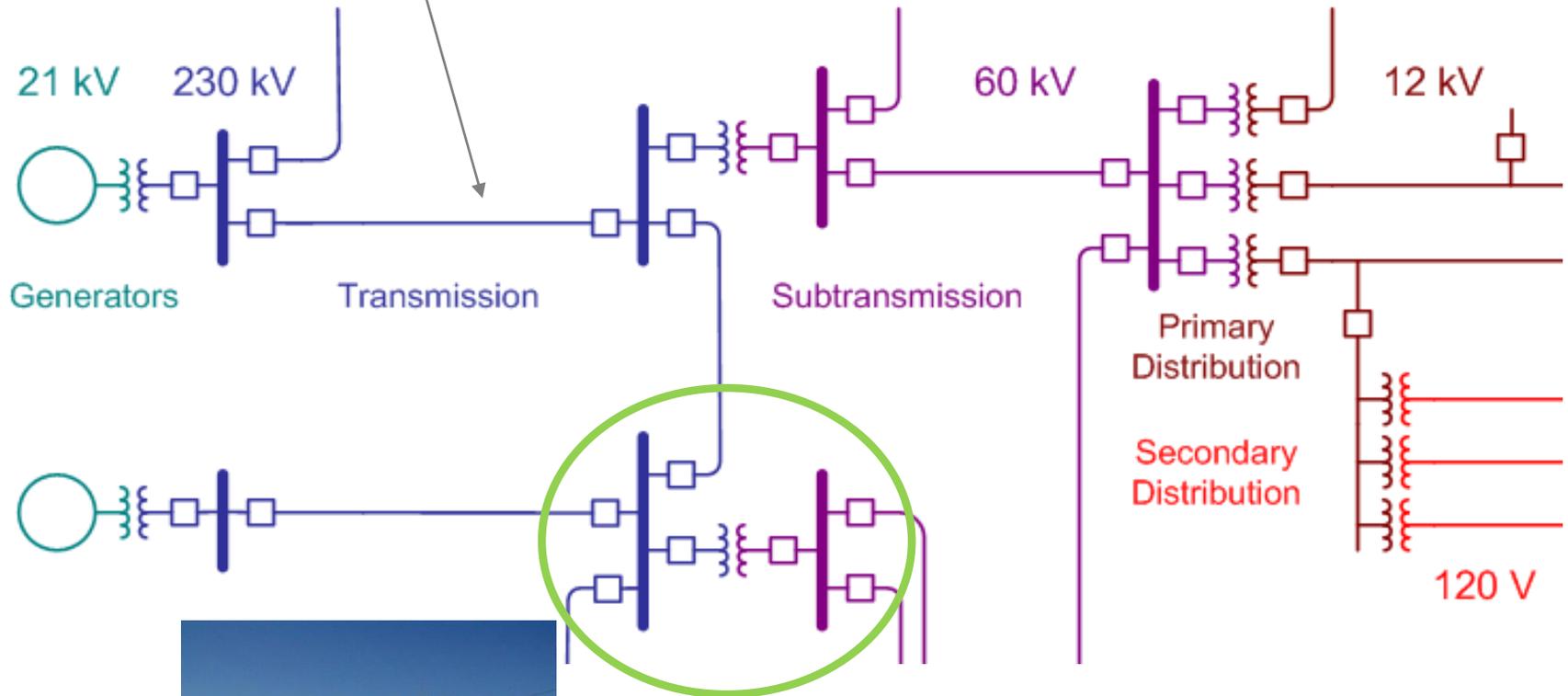Power System Structure with typical voltage levels




transmission substation


distribution
substation



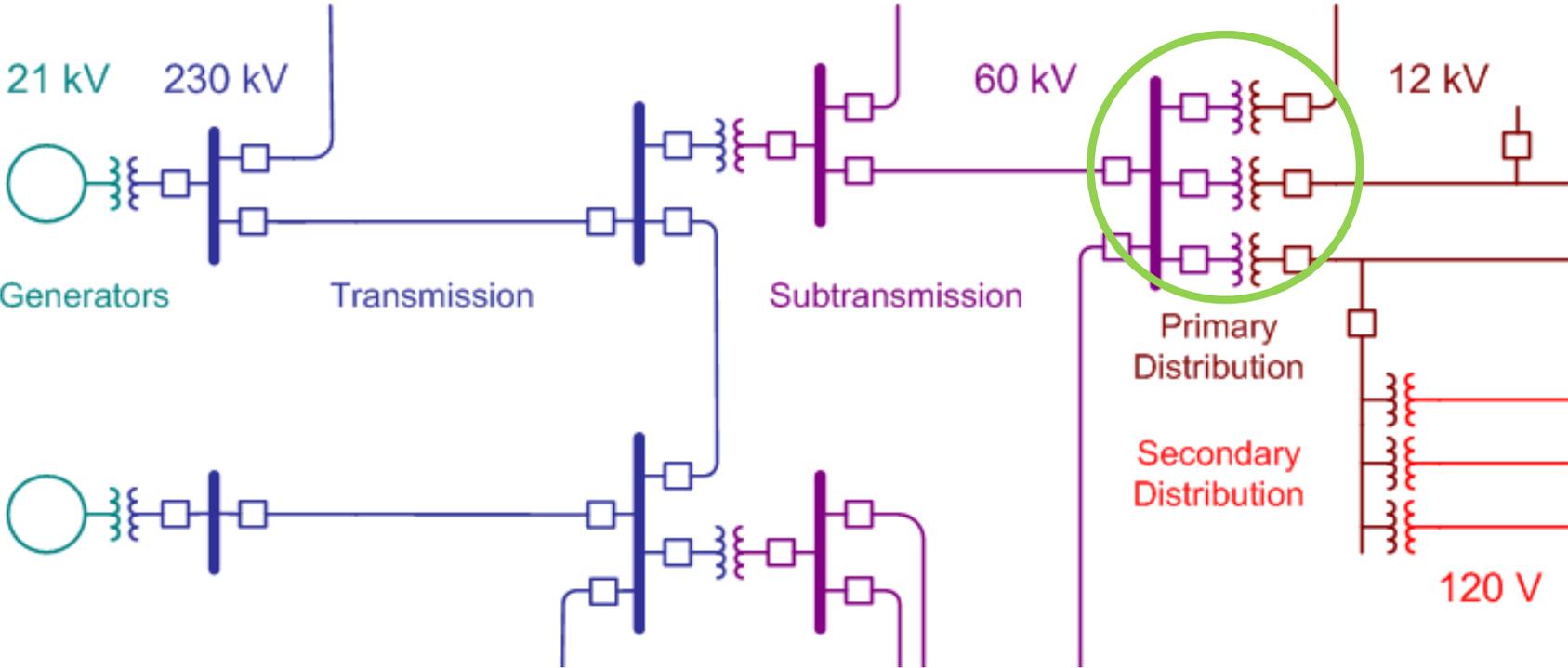Power System Structure with typical voltage levels



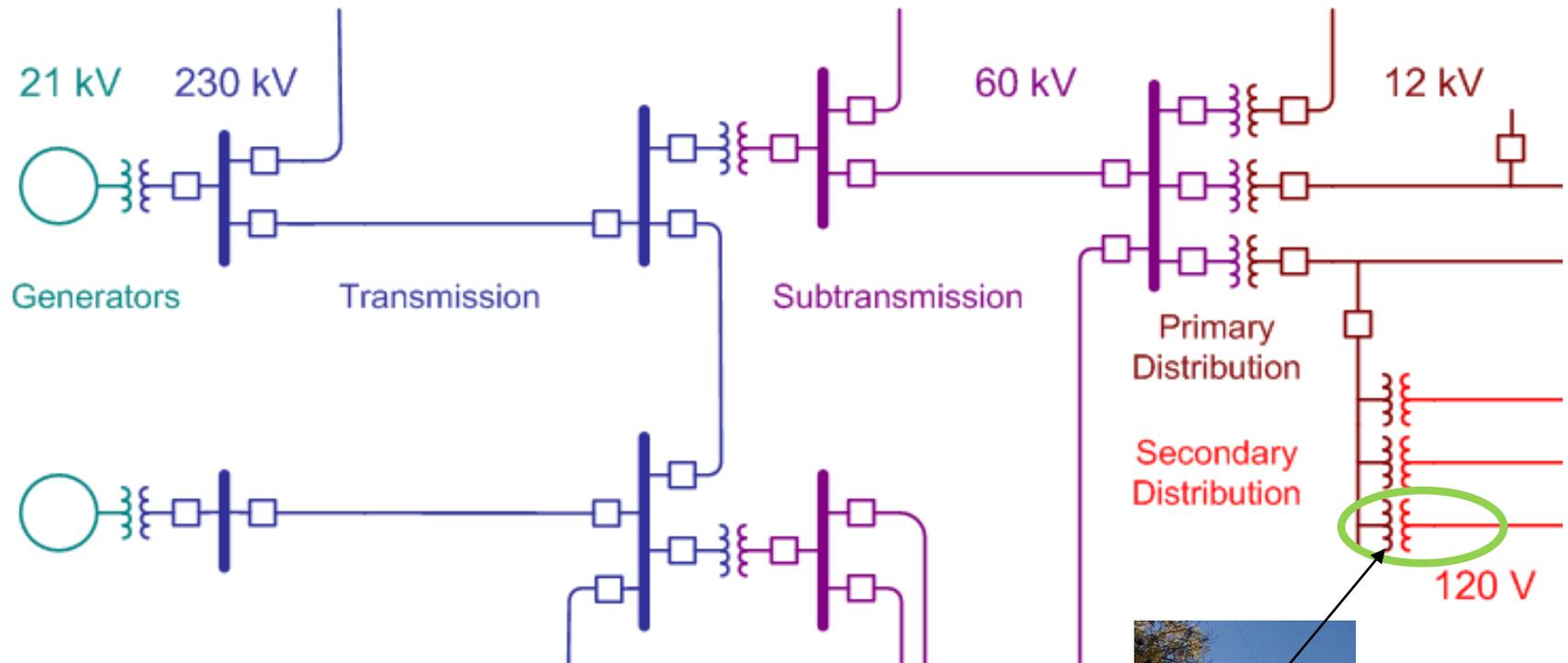
Power System Structure with typical voltage levels



transformer &
distribution line



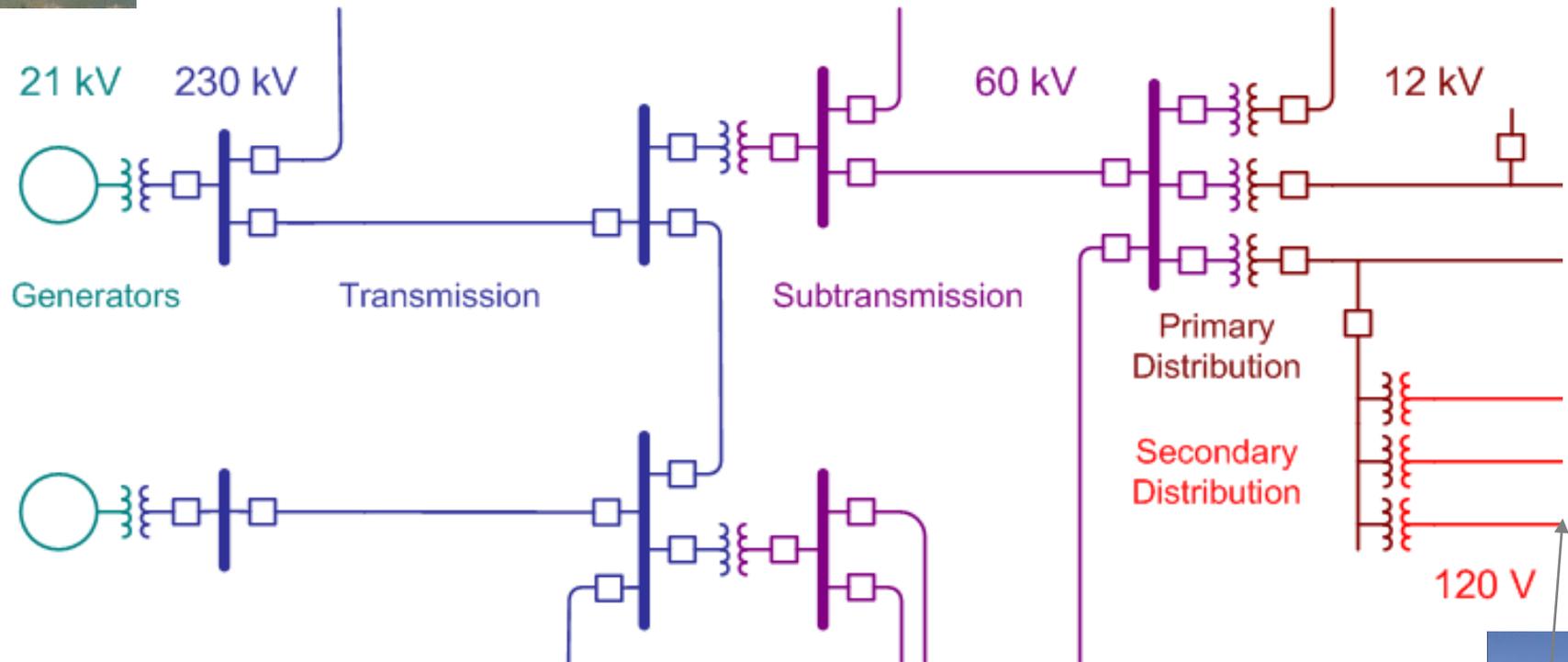Power System Structure with typical voltage levels



service drop



Mathematical model

Quantities of interest

- Voltage, current, power, energy
- All are sinusoidal functions of time



Mathematical model

Quantities of interest

- Voltage, current, power, energy
- All are sinusoidal functions of time

Voltage

$$v(t) = V_{\max} \cos(\omega t + \phi_V)$$

↑
nominal frequency

North/Central Americas: 60 Hz

Most other major countries: 50 Hz

- Steady state: frequencies at all points are nominal
- Reasonable model at timescales of minute and up
- Dynamic models at sec-min timescale: S Meyn's tutorial

this part of tutorial is all about steady state



Phasor representation

Quantities of interest

- Voltage, current, power, energy
- All are sinusoidal functions of time

Voltage

$$v(t) = V_{\max} \cos(\omega t + q_V)$$

↑
amplitude

↑
phase

voltage
phasor

$$V = \frac{V_{\max}}{\sqrt{2}} e^{jq_V}$$



Phasor representation

Quantities of interest

- Voltage, current, power, energy
- All are sinusoidal functions of time

Voltage

$$v(t) = V_{\max} \cos(\omega t + q_V)$$

voltage
phasor

$$V = \frac{V_{\max}}{\sqrt{2}} e^{jq_V}$$

$$v(t) = \operatorname{Re} \left\{ \sqrt{2} V e^{j\omega t} \right\} = \operatorname{Re} \left\{ V_{\max} e^{j(\omega t + q_V)} \right\}$$



Phasor representation

Quantities of interest

- Voltage, current, power, energy
- All are sinusoidal functions of time

Voltage

$$v(t) = V_{\max} \cos(\omega t + q_V)$$

voltage
phasor

$$V = \frac{V_{\max}}{\sqrt{2}} e^{jq_V}$$

$$|V| = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \quad \text{RMS}$$



Phasor representation

Voltage

$$v(t) = V_{\max} \cos(\omega t + q_V)$$

$$V = \frac{V_{\max}}{\sqrt{2}} e^{jq_V}$$

Current

$$i(t) = I_{\max} \cos(\omega t + q_I)$$

$$I = \frac{I_{\max}}{\sqrt{2}} e^{jq_I}$$




Linear circuit elements

Resistor R $v(t) = R \times i(t)$



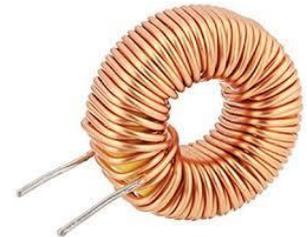Inductor L $v(t) = L \times \frac{di}{dt}(t)$



Capacitor C $i(t) = C \times \frac{dv}{dt}(t)$



these are main circuit elements to model the grid



Linear circuit elements


Resistor R $v(t) = R \times i(t)$

$$V = R \times I$$



Inductor L $v(t) = L \times \frac{di}{dt}(t)$

$$V = j\omega L \times I$$

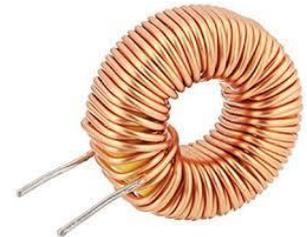

Capacitor C $i(t) = C \times \frac{dv}{dt}(t)$



$$V = (j\omega C)^{-1} \cdot I$$






Linear circuit elements

time domain

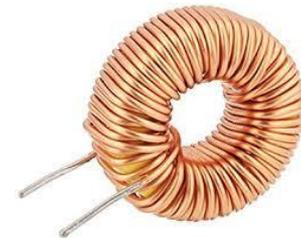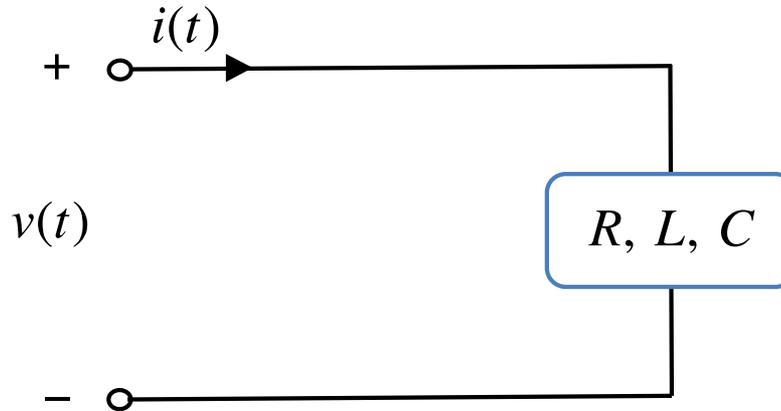

phasor domain

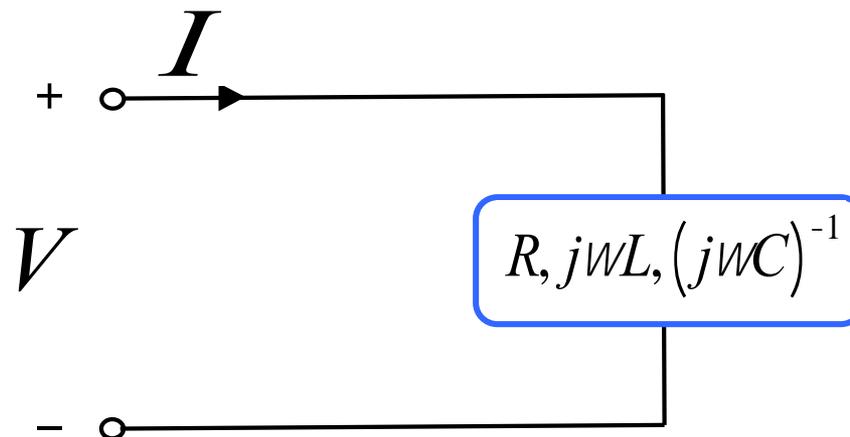



Complex power

Quantities of interest

- Voltage, current, power, energy
- All are sinusoidal functions of time

Instantaneous power

$$\begin{aligned} p(t) &= v(t)i(t) \\ &= \frac{V_{m \text{ ax}} I_{m \text{ ax}}}{2} (\underbrace{\cos(q_V - q_I)}_{\text{average power}} + \cos(2\omega t + q_V + q_I)) \end{aligned}$$



Complex power

Quantities of interest

- Voltage, current, power, energy
- All are sinusoidal functions of time

Instantaneous power

$$p(t) = v(t)i(t)$$
$$= \frac{V_{m \text{ ax}} I_{m \text{ ax}}}{2} (\underbrace{\cos(\varphi_V - \varphi_I)}_{\text{average power}} + \cos(2\omega t + \varphi_V + \varphi_I))$$

average power

Complex power

$$S := VI^* = P + jQ$$

real (active) power

reactive power



Phasor analysis

Steady state behavior described by algebraic equations

- Instead of dynamic equations

Circuit analysis

- Voltages and currents are linear

Power flow analysis

- Power flow equations are nonlinear

$$p(t) = v(t)i(t)$$

$$S := VI^*$$

We will describe device and network models, and analyze them, in phasor domain




3-phase AC : 3 key ideas

- Phasor representation
- Balanced operation
- Per-phase analysis




3-phase AC system

3 single-phase system:

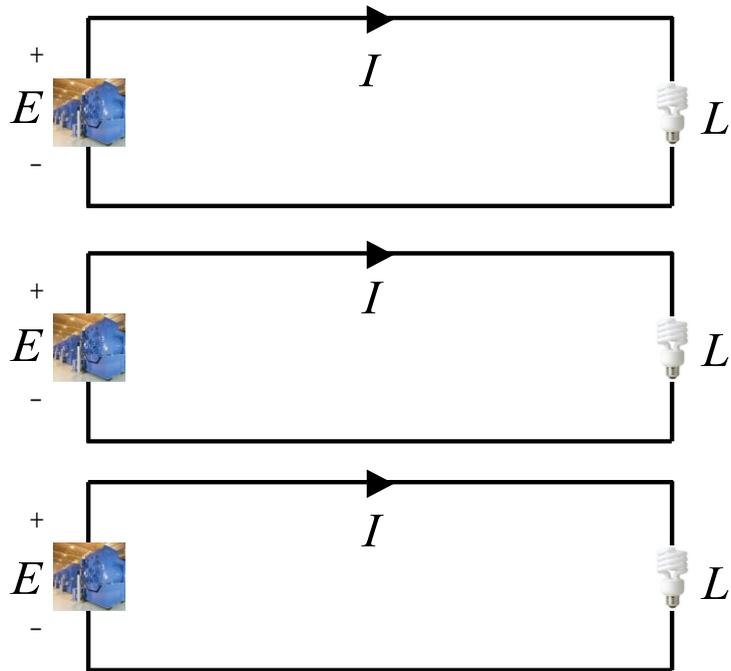


single 3-phase system:

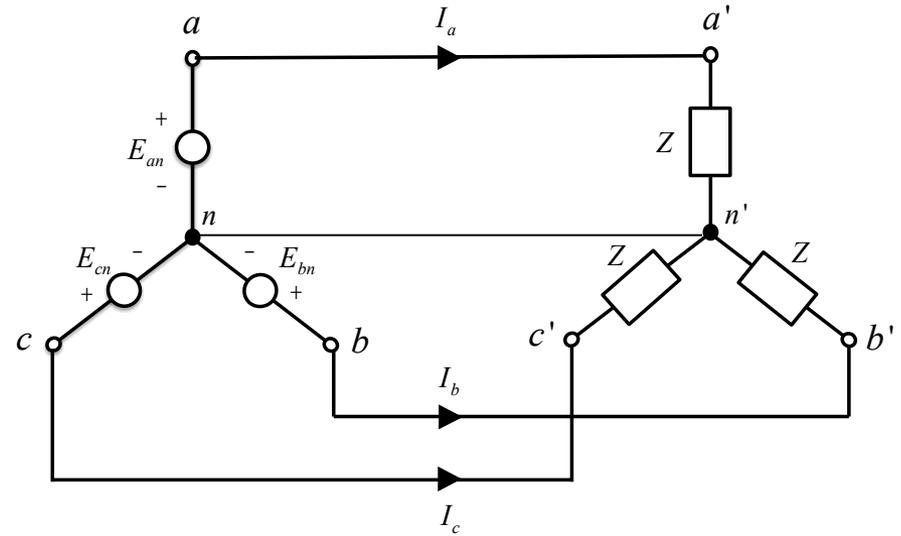




3-phase AC system

Y-configuration:


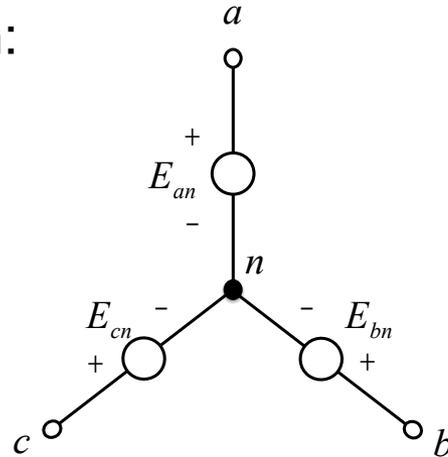


voltage source

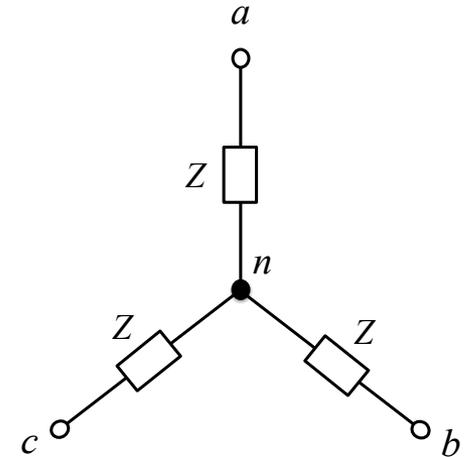

impedance load


Delta-configuration:

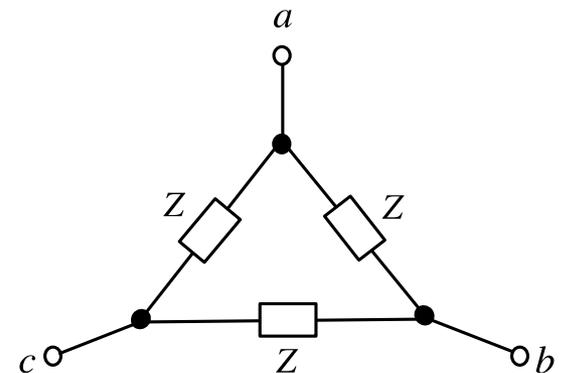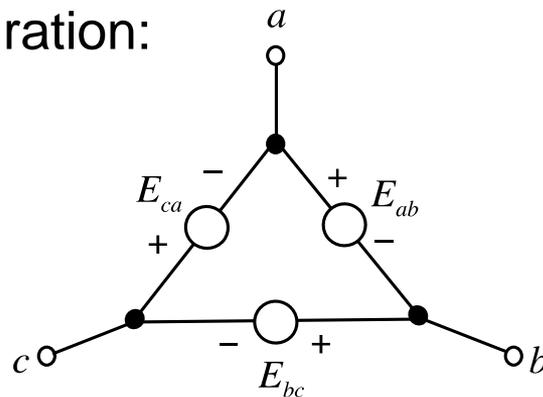




3-phase AC system

Y-configuration:

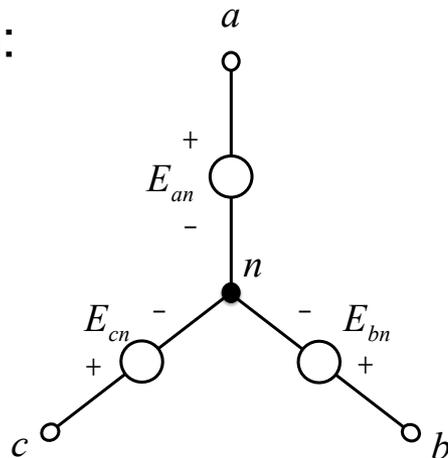

voltage source

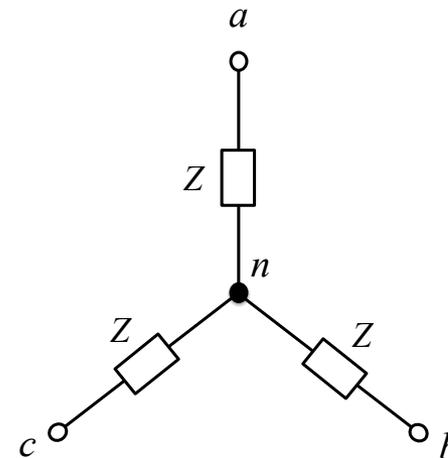


impedance load

Balanced 3p source

- Equal in magnitude, 120 deg difference in phase
- $E_{an} = 1 \angle \phi$, $E_{bn} = 1 \angle \phi - 120^\circ$, $E_{cn} = 1 \angle \phi + 120^\circ$

Balanced 3p impedance load

- Identical impedances

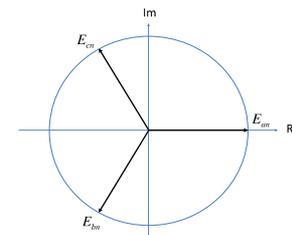




3-phase AC system

Balanced 3p source

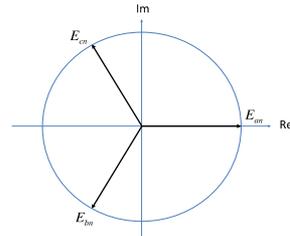- Equal in magnitude, 120 deg difference in phase
- $E_{ab} = 1\angle\theta$, $E_{bc} = 1\angle\theta - 120^\circ$, $E_{ca} = 1\angle\theta + 120^\circ$





Balanced 3p impedance load

- Identical impedances

voltage source


impedance load

Delta-configuration:

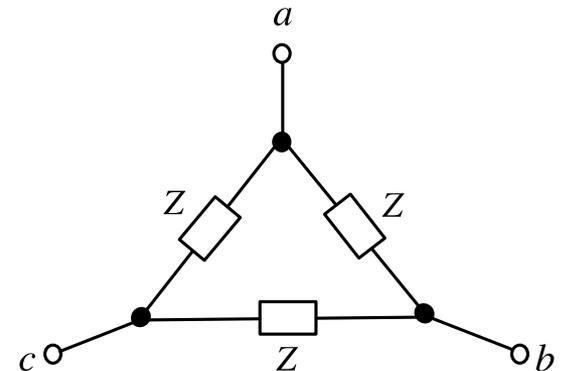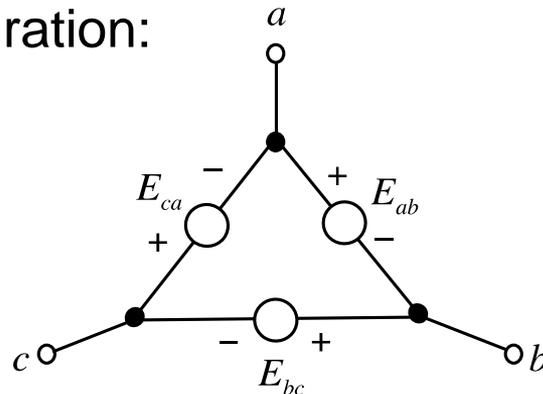



Balanced 3-phase system

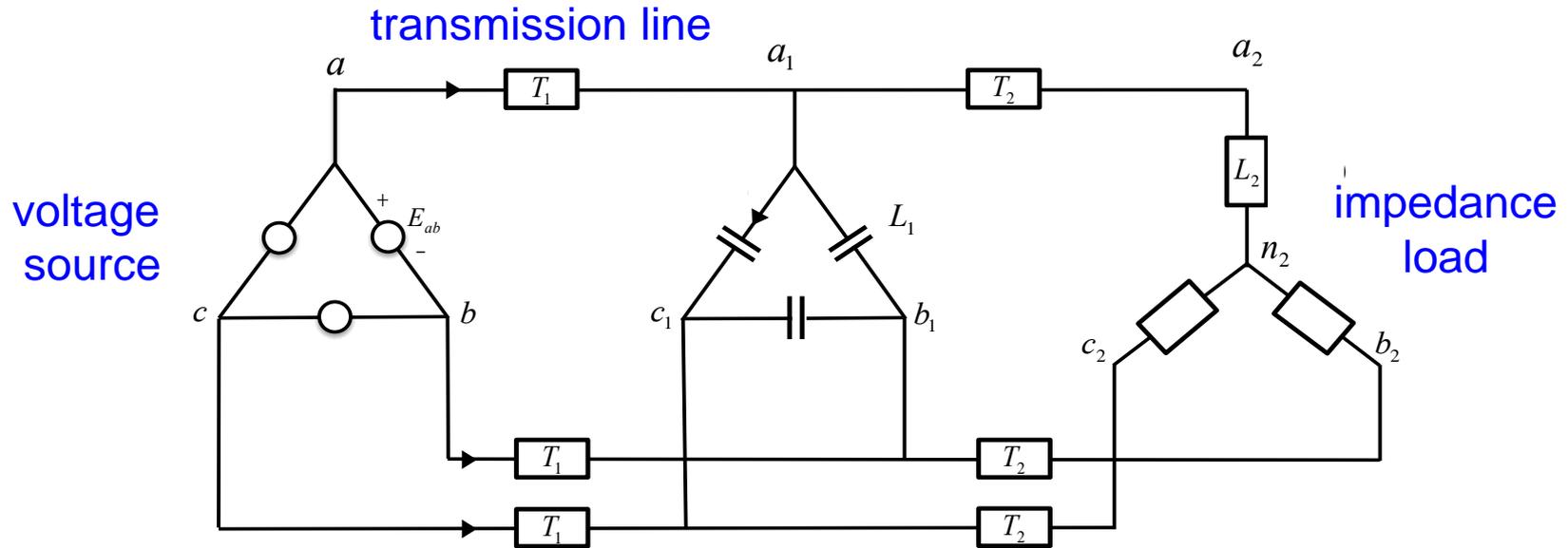

Balanced 3p operation

- Balanced 3p sources
- Balanced 3p loads
- Balanced (identical) transmission lines



Advantages

1-phase $p(t) = v(t)i(t), \quad S := VI^*$

3-phase $S_{3f} := V_a I_a^* + V_b I_b^* + V_c I_c^*$



Advantages

1-phase $p(t) = v(t)i(t), \quad S := VI^*$

3-phase $S_{3f} := V_a I_a^* + V_b I_b^* + V_c I_c^* = 3S$

$$p_{3f}(t) := v_a(t)i_a(t) + v_b(t)i_b(t) + v_c(t)i_c(t)$$



Advantages

1-phase $p(t) = v(t)i(t), \quad S := VI^*$

3-phase $S_{3f} := V_a I_a^* + V_b I_b^* + V_c I_c^* = 3S$

$$\begin{aligned} p_{3\phi}(t) &:= v_a(t)i_a(t) + v_b(t)i_b(t) + v_c(t)i_c(t) \\ &= 3|V_a||I_a|\cos(\phi_V - \phi_I) = 3P \end{aligned}$$

Advantages of balanced 3p operation

- Instantaneous power is constant in t !
- Uses $\sim 1/2$ as much materials (wires) as three 1p system
- Incurs $\sim 1/2$ as much active power loss as three 1p system




3-phase AC : 3 key ideas

- Phasor representation
- Balanced operation
- Per-phase analysis



Per-phase analysis: Wye

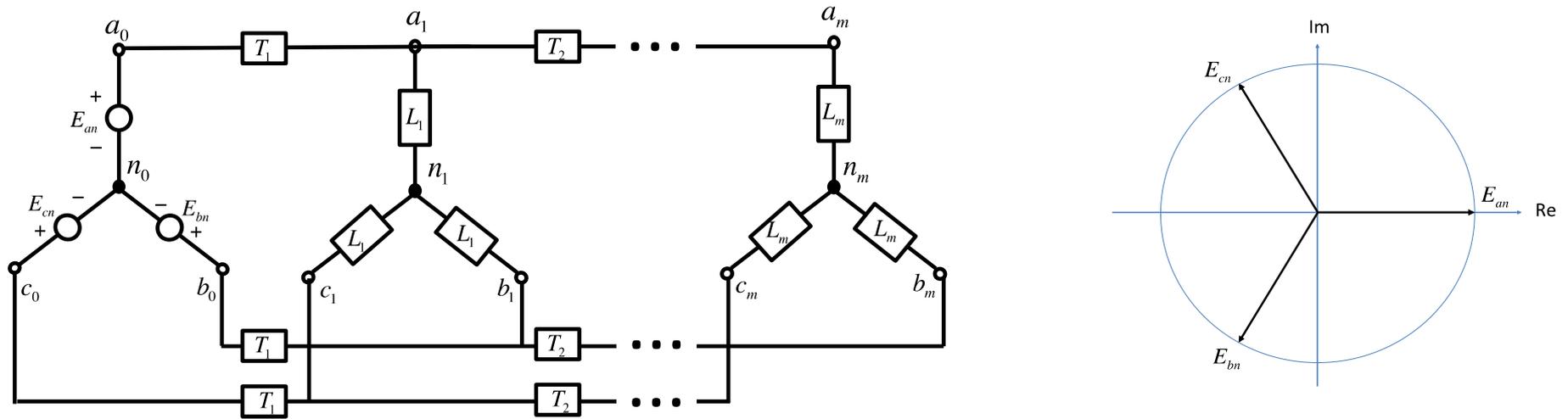


Important properties of balanced 3p system

- All $V_{\text{neutral-neutral}} = 0$



Per-phase analysis: Wye

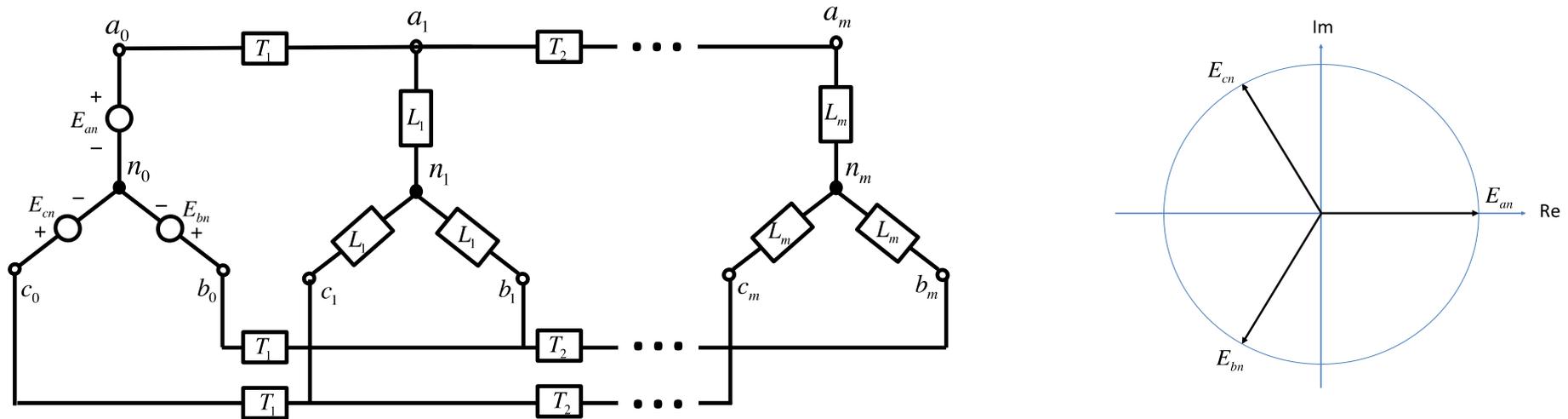


Important properties of balanced 3p system

- All $V_{\text{neutral-neutral}} = 0$
- All voltages and currents are 3-phase balanced
- Phases are decoupled, i.e., variables in each phase depend **only** on quantities in that phase




Per-phase analysis: Wye

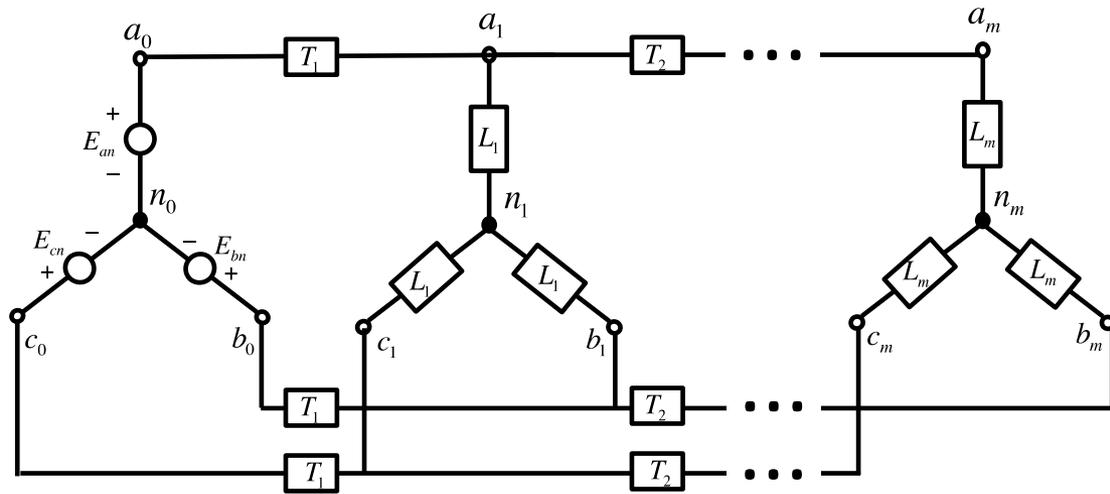

Properties:

- All $V_{\text{neutral-neutral}} = 0$
- All voltages and currents are 3-phased balanced
- Phases are decoupled

per-phase equivalent circuit

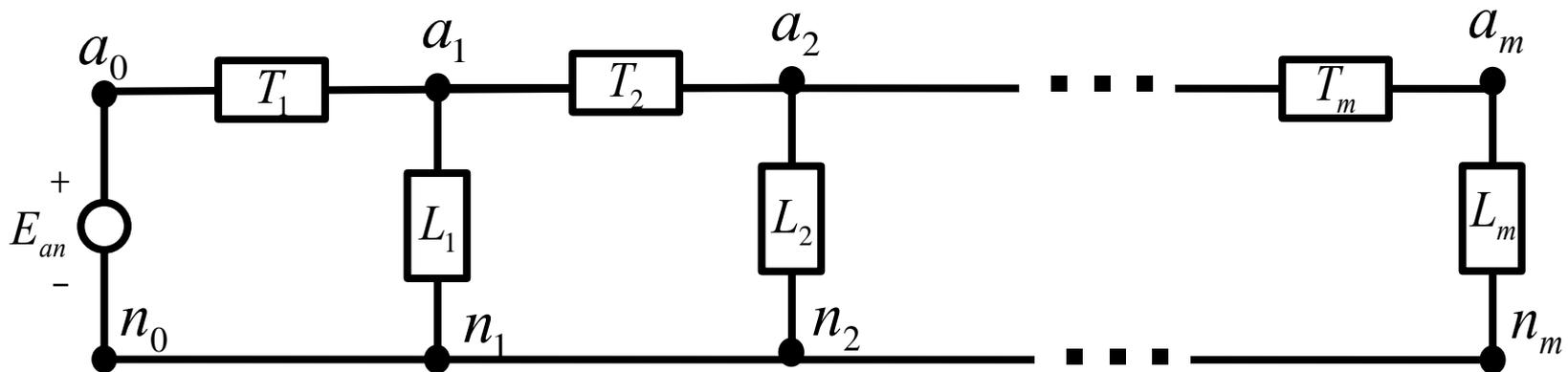






Delta-Wye transformation

Equivalent 3p sources: same external behavior

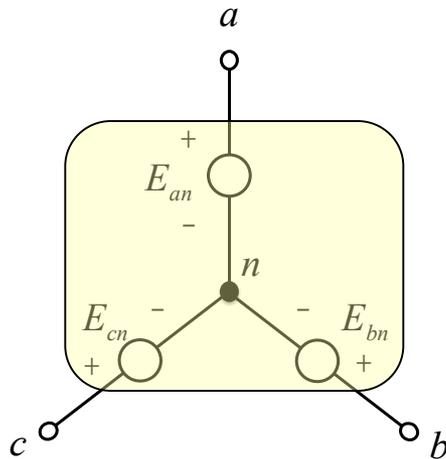line-to-line voltages: $E_{ab}^Y = E_{ab}^\Delta$, $E_{bc}^Y = E_{bc}^\Delta$, $E_{ca}^Y = E_{ca}^\Delta$


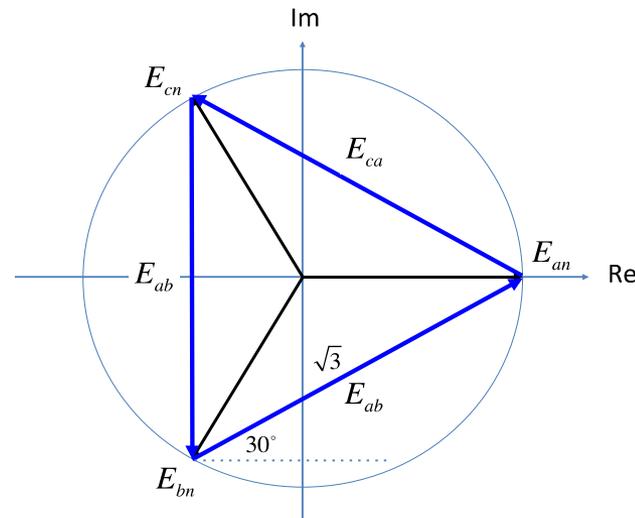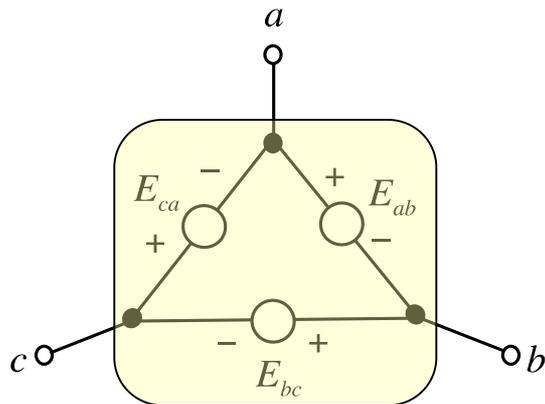
$$E_{an}^Y = \frac{E_{ab}^\Delta}{\sqrt{3} e^{j\pi/6}}$$






Delta-Wye transformation

Equivalent 3p sources: same external behavior

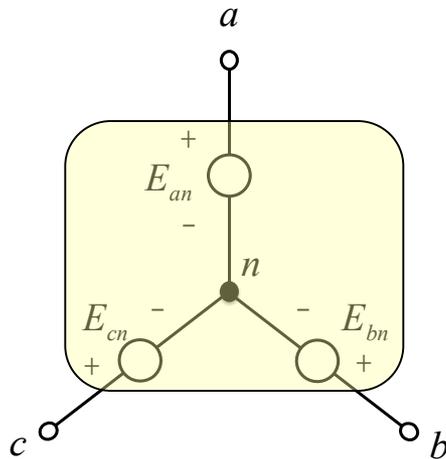
line-to-line voltages: $E_{ab}^Y = E_{ab}^\Delta$, $E_{bc}^Y = E_{bc}^\Delta$, $E_{ca}^Y = E_{ca}^\Delta$



$$E_{an}^Y = \frac{E_{ab}^\Delta}{\sqrt{3} e^{j\pi/6}}$$

$$E_{bn}^Y = \frac{E_{bc}^\Delta}{\sqrt{3} e^{j\pi/6}}$$

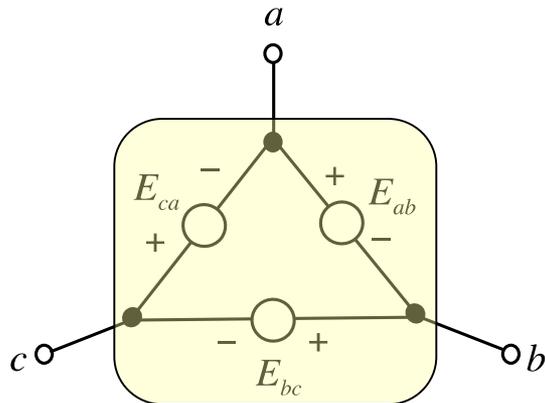
$$E_{cn}^Y = \frac{E_{ca}^\Delta}{\sqrt{3} e^{j\pi/6}}$$






Delta-Wye transformation

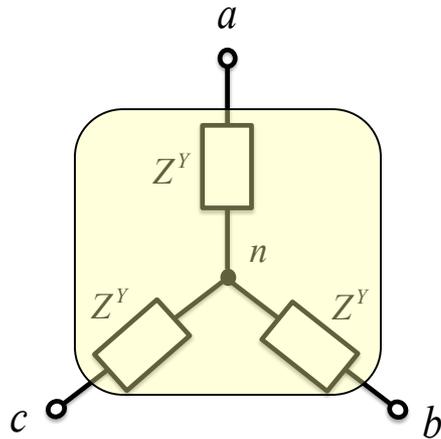Equivalent 3p sources: same external behavior
same terminal currents on same line-to-line voltages




$$Z^Y = \frac{Z^D}{3}$$

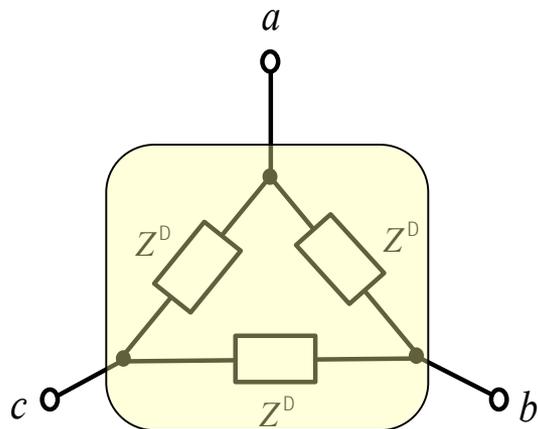





Per-phase analysis

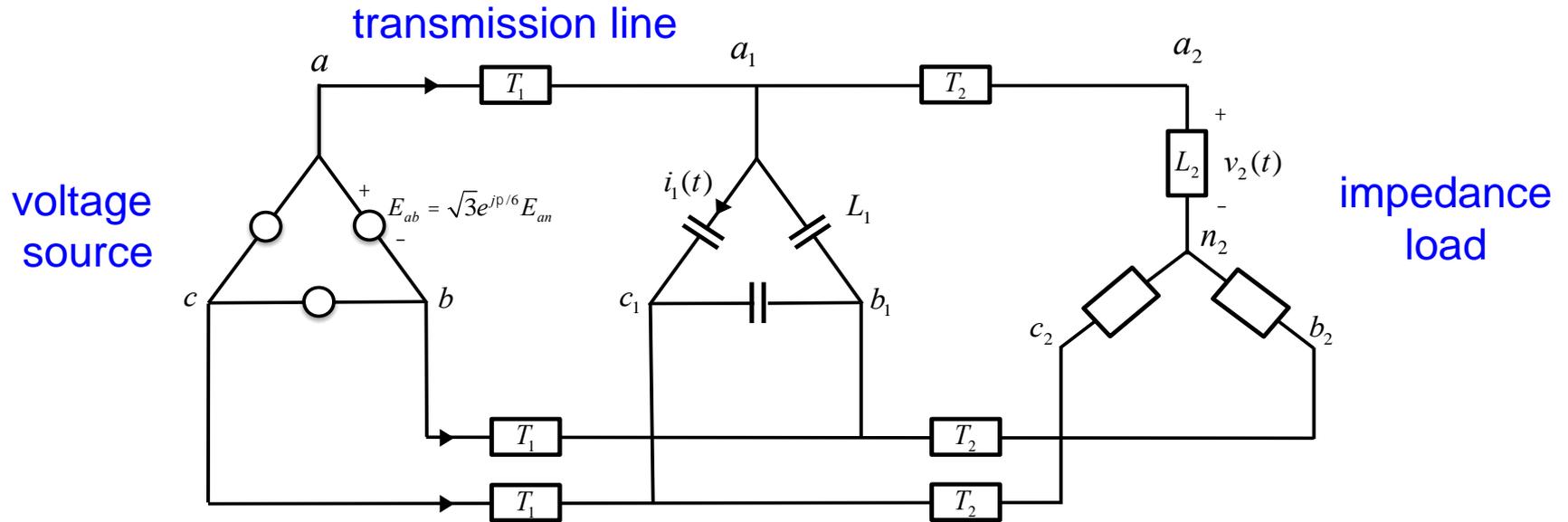

- Convert all Delta sources and loads into Wye
- Solve phase a circuit with **all** neutrals connected for desired variables
- Phase b / c variables: subtract / add 120deg to phase a variables
- If variables internal to Delta configurations are desired, solve them from original circuit



Per-phase analysis

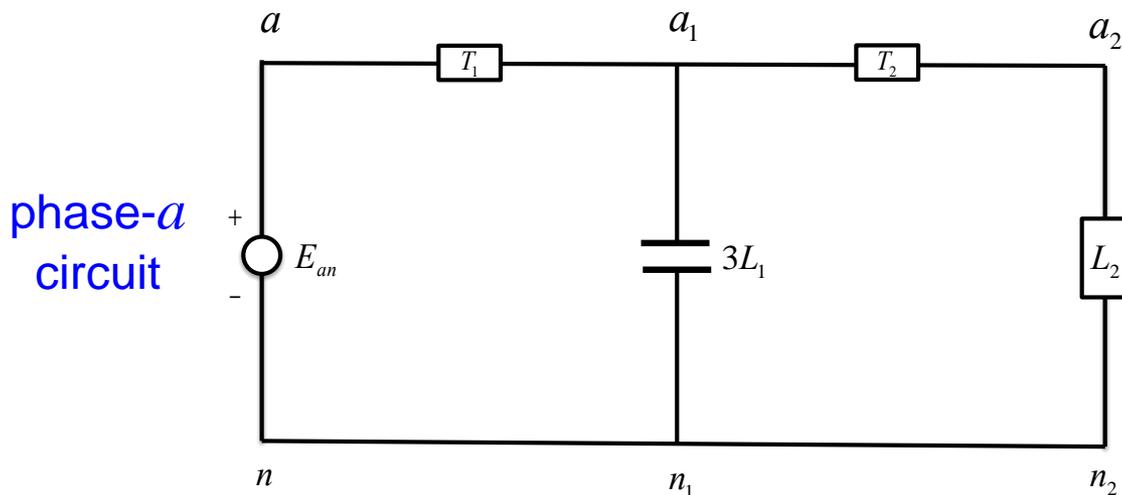
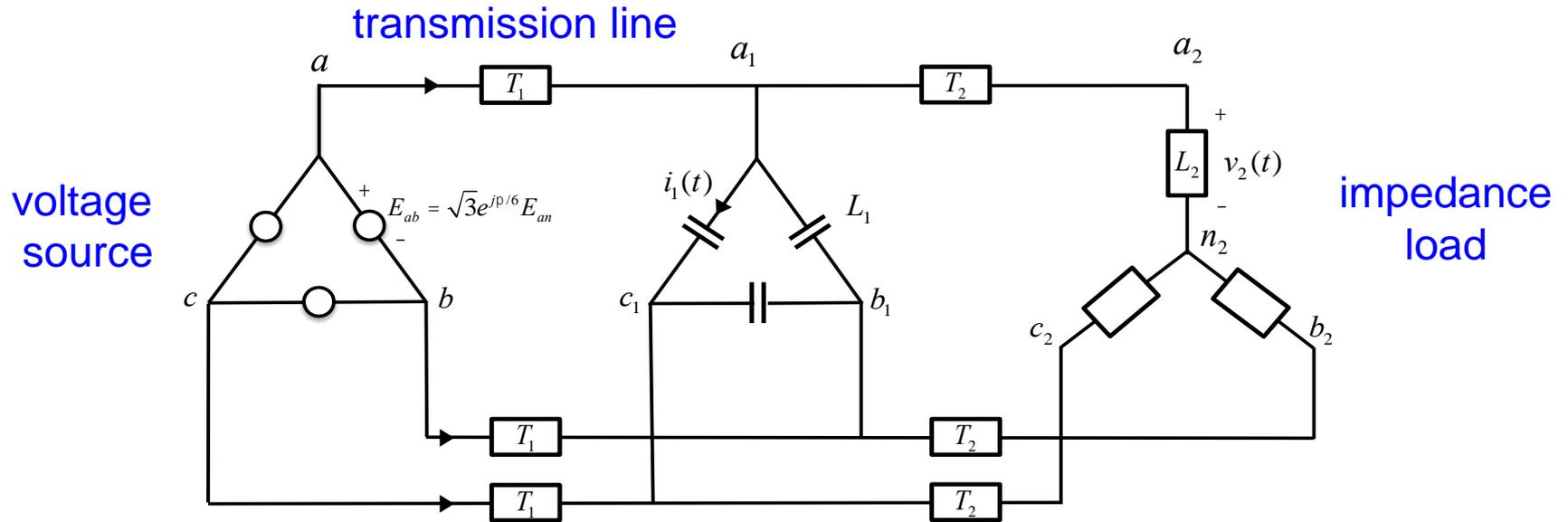


Solve for V_2

$$\text{P } v_2(t) = \text{Re}(\sqrt{2}V_2 e^{j\omega t})$$



Per-phase analysis

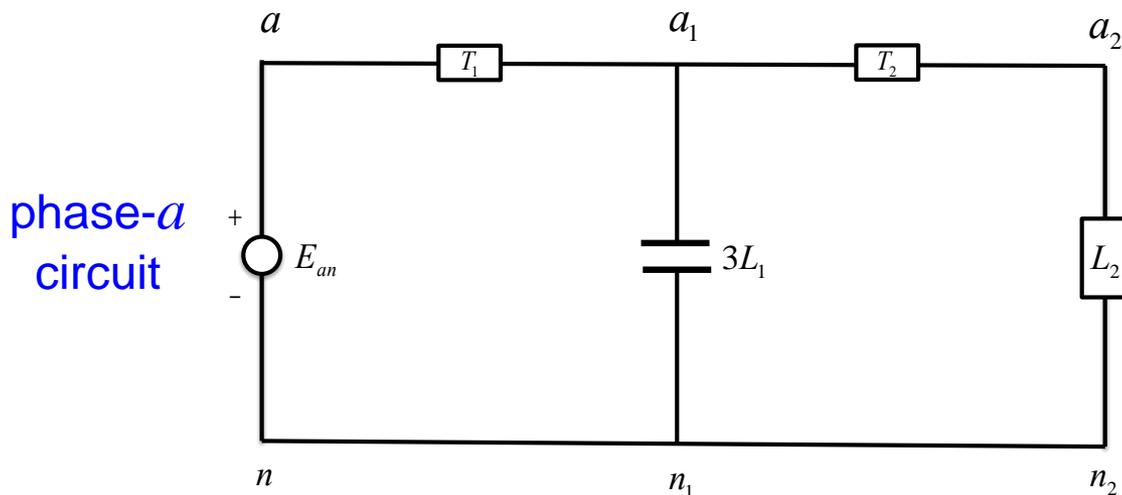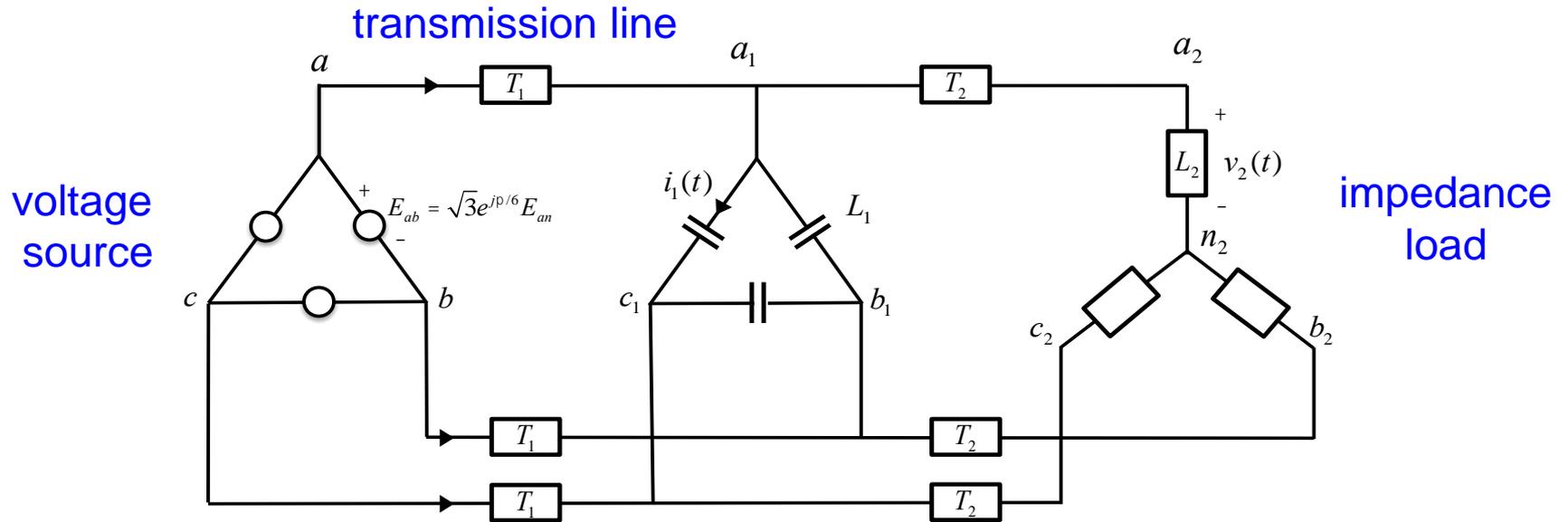

Solve for V_1

$$\supset V_{ca} = \sqrt{3}e^{j\pi/6} V_1 \times e^{j2\pi/3}$$

$$\supset I_{ca} = L_1 V_{ca}$$

$$\supset i_1(t) = -\text{Re}\left(\sqrt{2}I_{ca}e^{j\omega t}\right)$$



Recap: basic concepts

3-phase AC transmission system

- Phasor representation
- Balanced operation
- Per-phase analysis

We will describe device and network models, and analyze them, in phasor domain, using per-phase analysis



The flow of power I

Basic concepts and models

Why smart grid? (15 mins)

Three-phase AC transmission: 3 key ideas (30 mins)

- Phasor representation
- Balanced operation
- Per-phase analysis


Device models (30 mins)

- Transmission line
- Transformer
- Generator



Transmission line model

Π model of transmission line

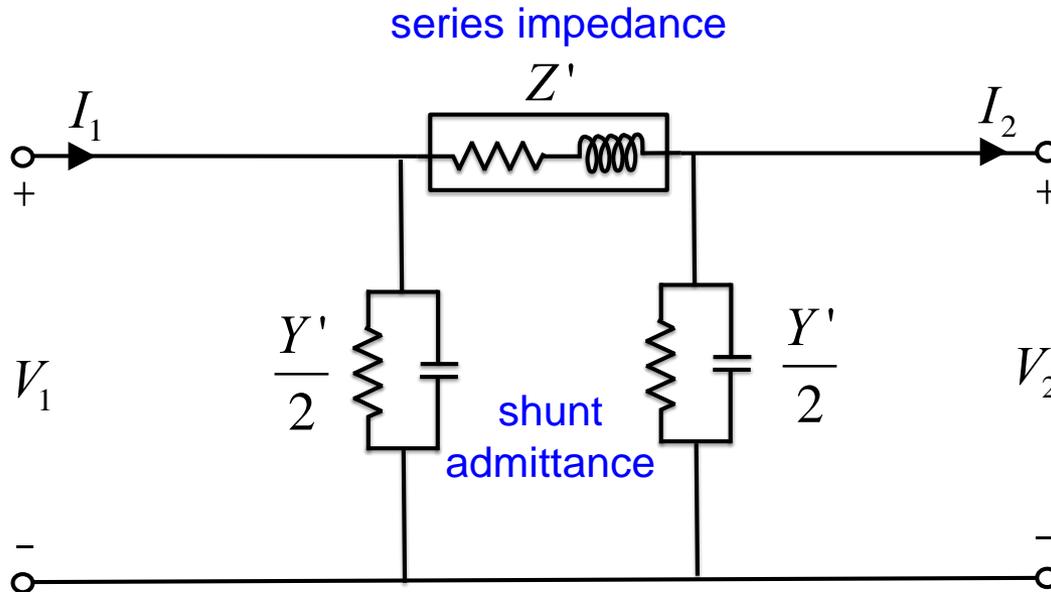

- Terminal behavior $(V_2, I_2) \mapsto (V_1, I_1)$
- What do line parameters (Z', Y') depend on ?
- What about a 3-phase line ?
- What are some implications ?



Transmission line model


Line inductance l

total flux linkages $\lambda(t) = l \times i(t)$

Multiple conductors

$$\lambda_k = i_k \underbrace{\frac{\mu_0}{2\pi} \ln \frac{1}{r'_k}}_{l_k} + \sum_{k' \neq k} i_{k'} \underbrace{\frac{\mu_0}{2\pi} \ln \frac{1}{d_{kk'}}}_{l_{kk'}}$$

self inductance mutual inductance

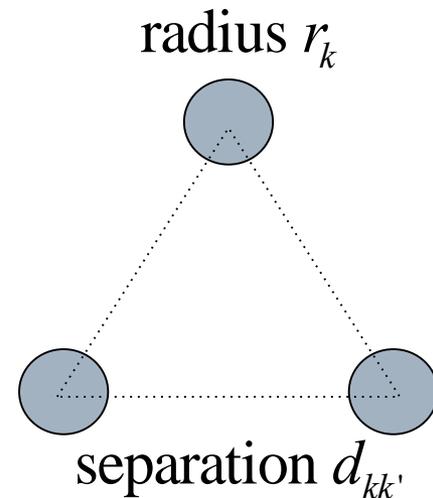



Transmission line model


Conditions

- Symmetric 3-phase line
- $i_a(t) + i_b(t) + i_c(t) = 0$

Multiple conductors

$$l_a(t) = \frac{\mu_0}{2\pi} \ln \frac{D}{r'} \times i_a(t)$$

“self-inductance” l H/m

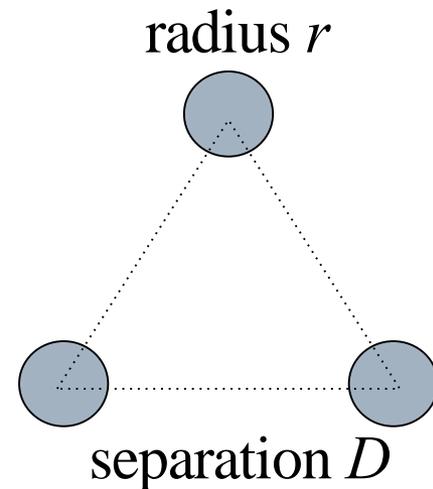

The phases are decoupled !



Transmission line model


Line capacitance c

total charge / m $q(t) = c \times v(t)$

Multiple conductors

$$v_k = q_k \underbrace{\frac{1}{2\pi\epsilon} \ln \frac{1}{r_k}}_{1/c_k} + \sum_{k' \neq k} q_{k'} \underbrace{\frac{1}{2\pi\epsilon} \ln \frac{1}{d_{kk'}}}_{1/c_{kk'}}$$

self inductance mutual inductance

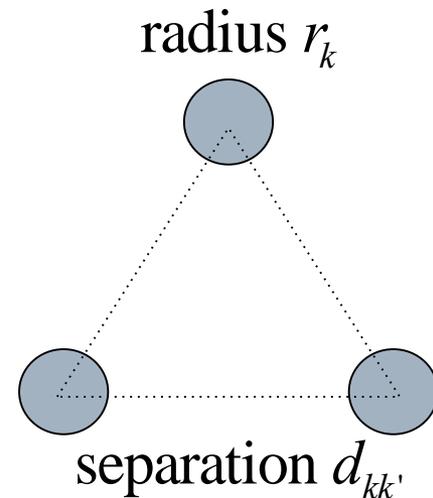




Transmission line model

Conditions

- Symmetric 3-phase line
- $q_a(t) + q_b(t) + q_c(t) = 0$

Multiple conductors
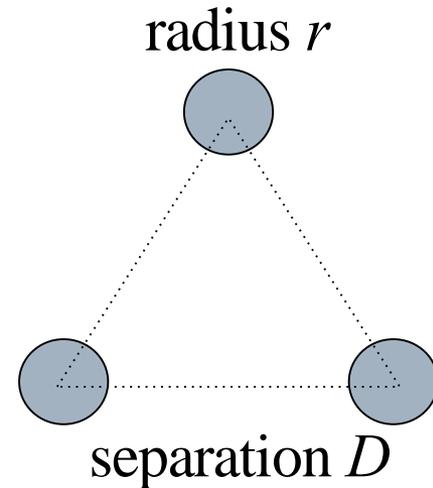
$$v_k(t) = \underbrace{\frac{1}{2pe} \ln \frac{D}{r}}_{\text{"self-capacitance"} \ 1/c \ \text{F/m}} \times q_k(t)$$



The phases are decoupled !



Transmission line model

Line parameters (balanced 3p line)

- Phases are decoupled


- series impedance $z = r + j\omega l \quad \text{W/m}$

shunt admittance (to neutral) $y = g + j\omega c \quad \text{W}^{-1} / \text{m}$

- Line inductance and capacitance

$$l = \frac{\mu_0}{2\pi} \ln \frac{D}{r'} \quad \text{H/m}$$
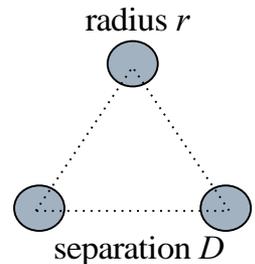
$$c = \frac{2\pi\epsilon}{\ln(D/r)} \quad \text{F/m}$$




- Line resistance r / conductance g depend on wire material & size



Transmission line model


per-phase model of phase voltage:

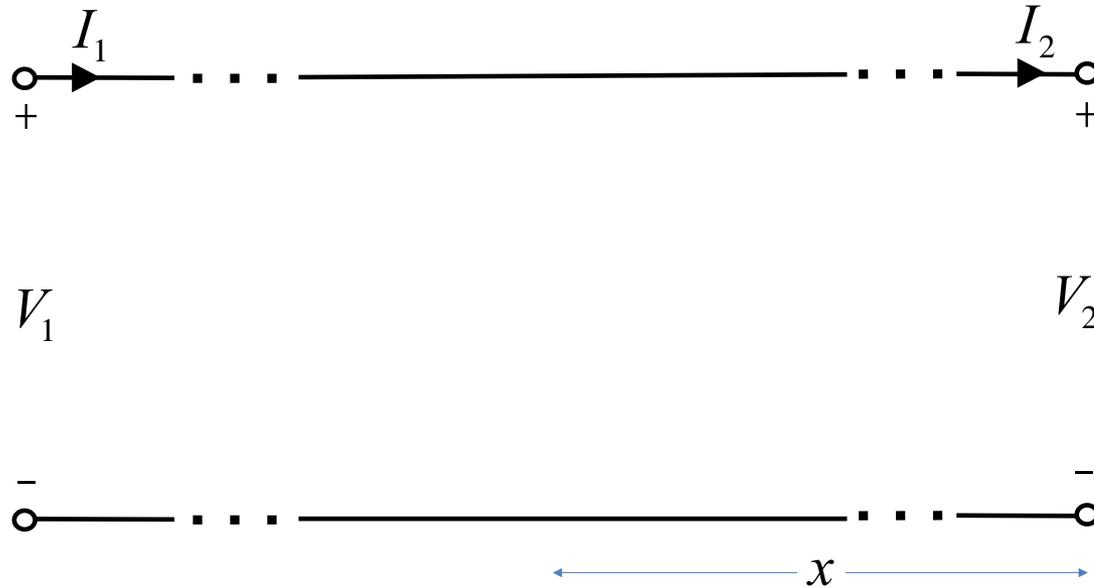



Transmission line model

per-phase model of phase voltage:

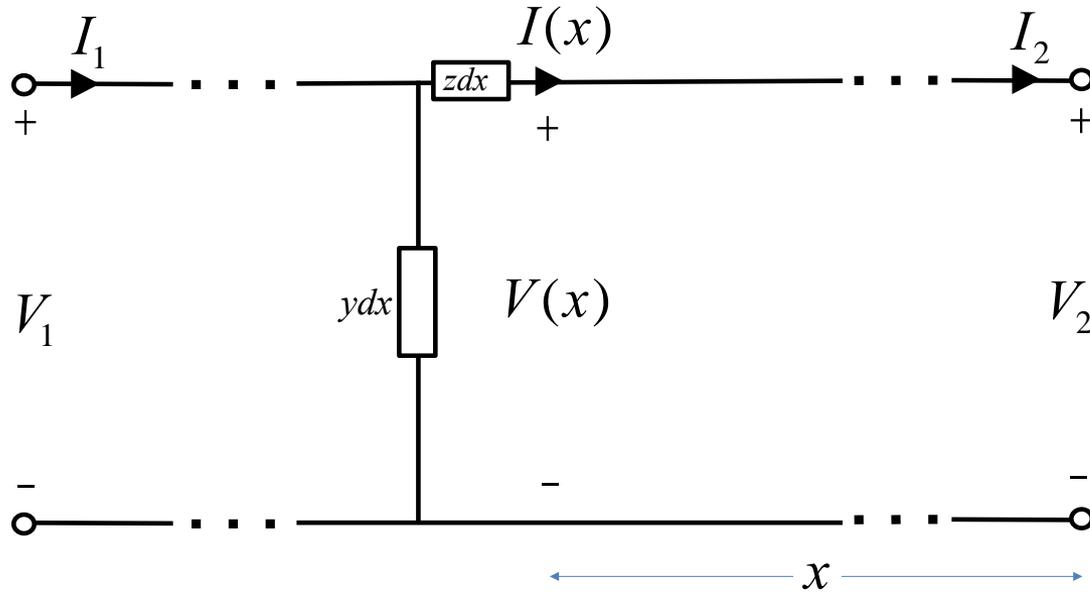

$$\begin{aligned} \frac{dV}{dx} &= -z I(x) \\ \frac{dI}{dx} &= -y V(x) \end{aligned}$$

$$(V_2, I_2) \mapsto (V_1, I_1)$$


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \cosh(\gamma l) & Z_c \sinh(\gamma l) \\ Z_c^{-1} \sinh(\gamma l) & \cosh(\gamma l) \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$Z_c := \sqrt{\frac{z}{y}} \quad \text{and} \quad \gamma := \sqrt{zy}$$



Transmission line model

Π model of transmission line

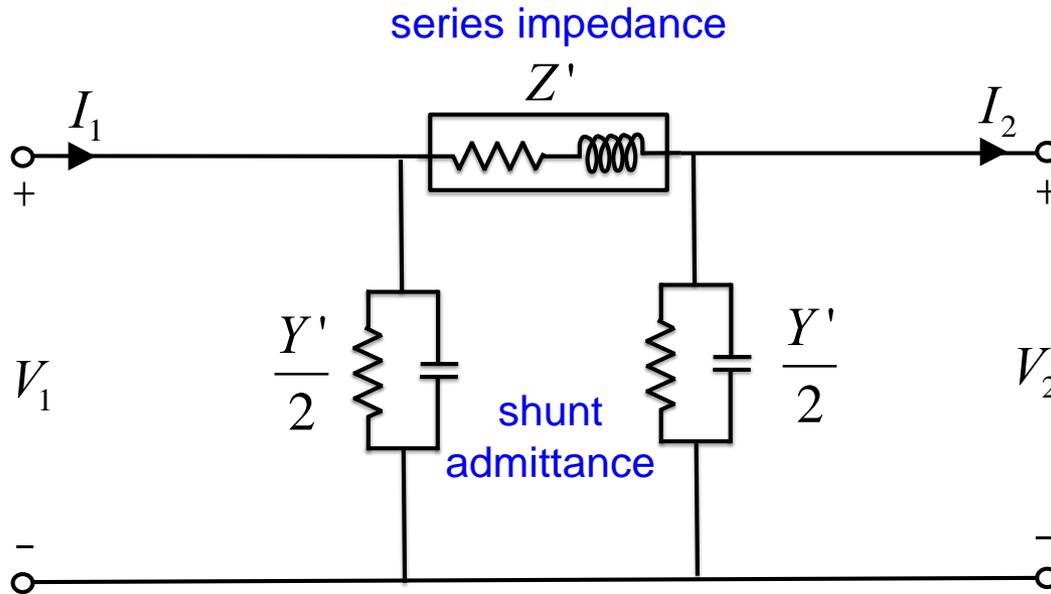

$$Z' = Z \times \frac{\sinh(gl)}{gl}$$

$$Y' = Y \times \frac{\tanh(gl/2)}{gl/2}$$

$$Z := z\ell$$

$$Y := y\ell$$




Transmission line model


Long line ($l > 150\text{mi}$): $Z' = Z \times \frac{\sinh(gl)}{gl}$

$$Y' = Y \times \frac{\tanh(gl / 2)}{gl / 2}$$

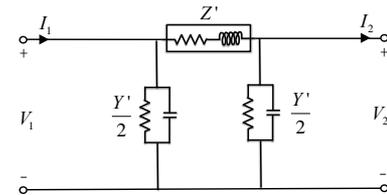Long line ($50 < l < 150\text{mi}$): $Z' = Z$
 $Y' = Y$



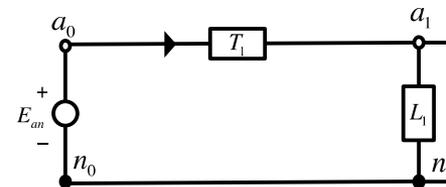Long line ($l < 50\text{mi}$): $Z' = Z$
 $Y' = 0$




$$Z := z\ell$$
$$Y := y\ell$$



Transmission line model

High voltage min transmission line loss

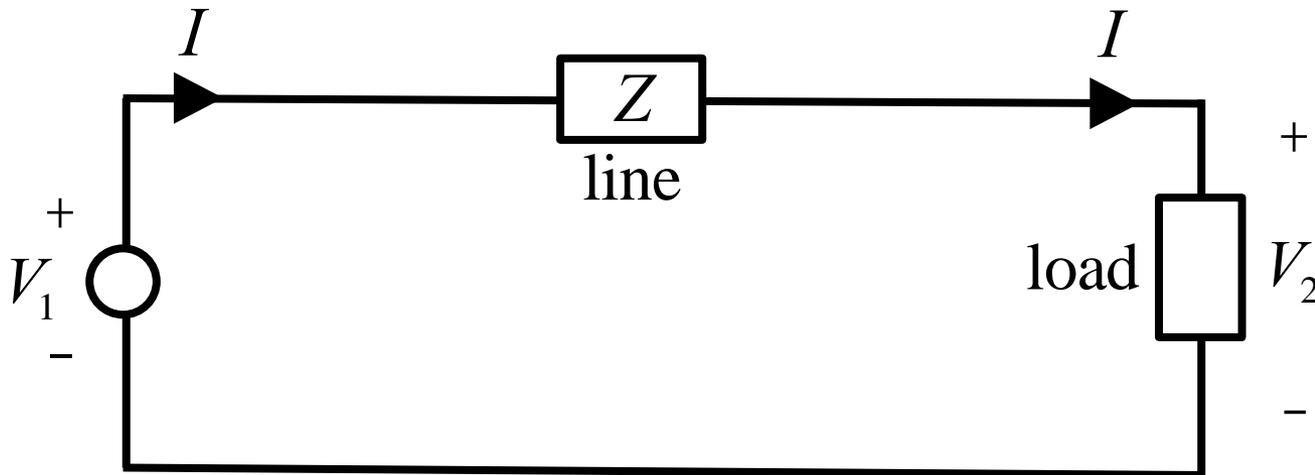

Specified: required load power $|S_2|$ and voltage $|V_2|$



$$P \quad |I| = \frac{|S_2|}{|V_2|} \quad \text{line loss} = R|I|^2$$



Transmission line model

Recap

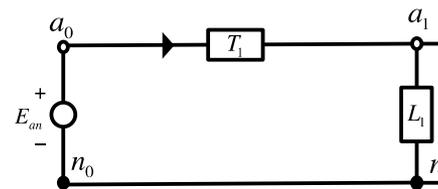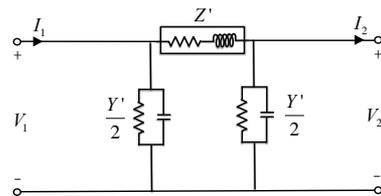- Line characteristics depend on materials, size, and geometry of 3-phase line
- Linear per-phase circuit model $(V_2, I_2) \mapsto (V_1, I_1)$
- \mathcal{P} circuit model: series impedance + shunt admittance





The flow of power I

Basic concepts and models

Why smart grid? (15 mins)

Three-phase AC transmission: 3 key ideas (30 mins)

- Phasor representation
- Balanced operation
- Per-phase analysis


Device models (30 mins)

- Transmission line
- Transformer
- Generator



Transformer model

Single-phase **ideal** transformer n

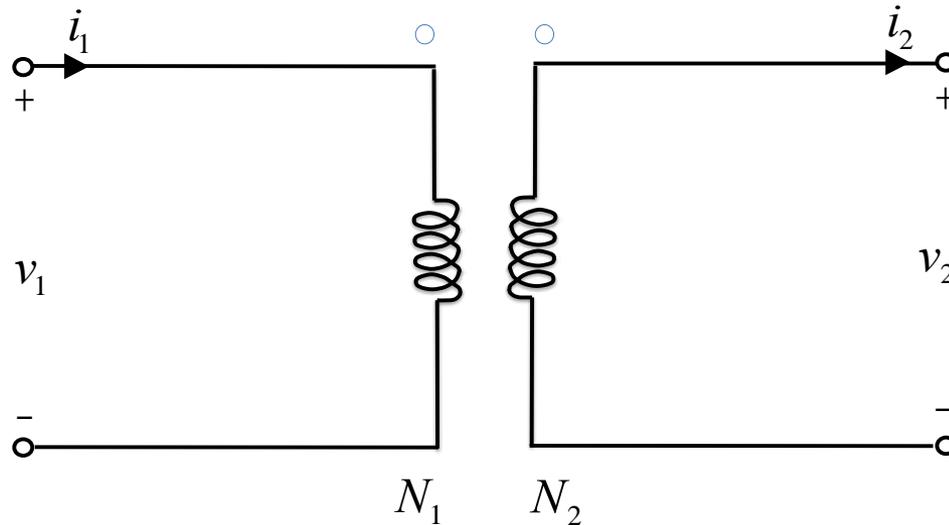


$$n := \frac{N_2}{N_1} \qquad a := \frac{N_1}{N_2}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \underbrace{\begin{bmatrix} a & 0 \\ 0 & n \end{bmatrix}}_{T_{\text{ideal}}} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \qquad \frac{-S_{21}}{S_{12}} := \frac{V_2 I_2^{\leftarrow}}{V_1 I_1^{\leftarrow}} = n \cdot a = 1$$



Transformer model

Single-phase (non-ideal) transformer

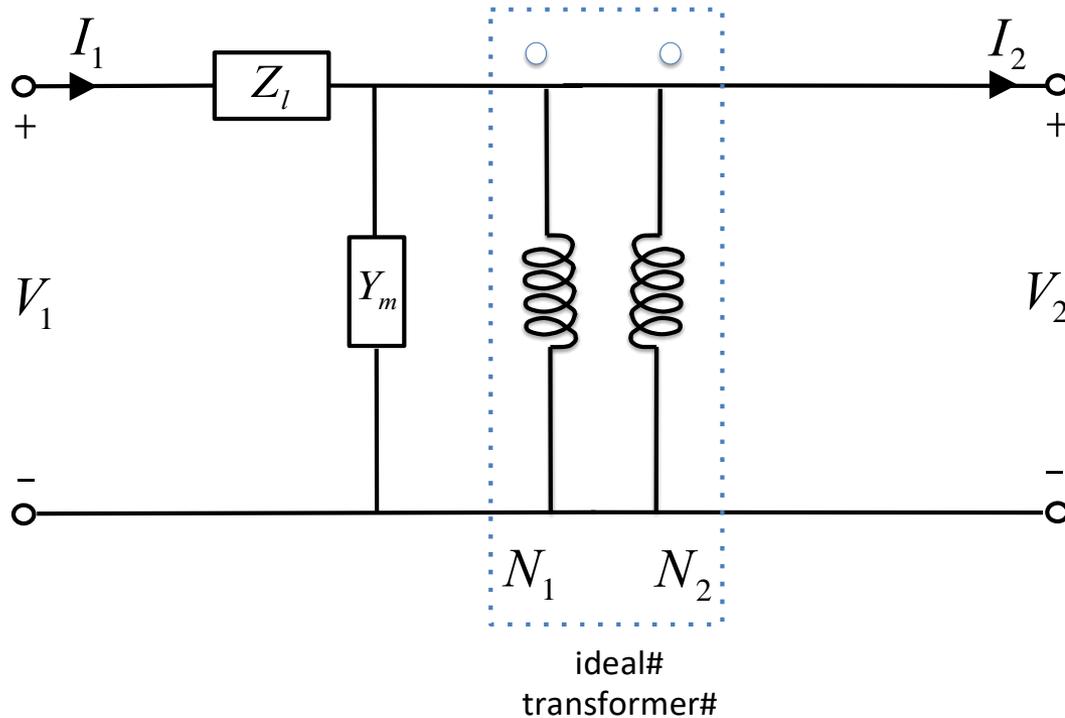


parameters (n, Z_l, Y_m)

(Z_l, Y_m) can be easily measured



Transformer model

Single-phase (non-ideal) transformer






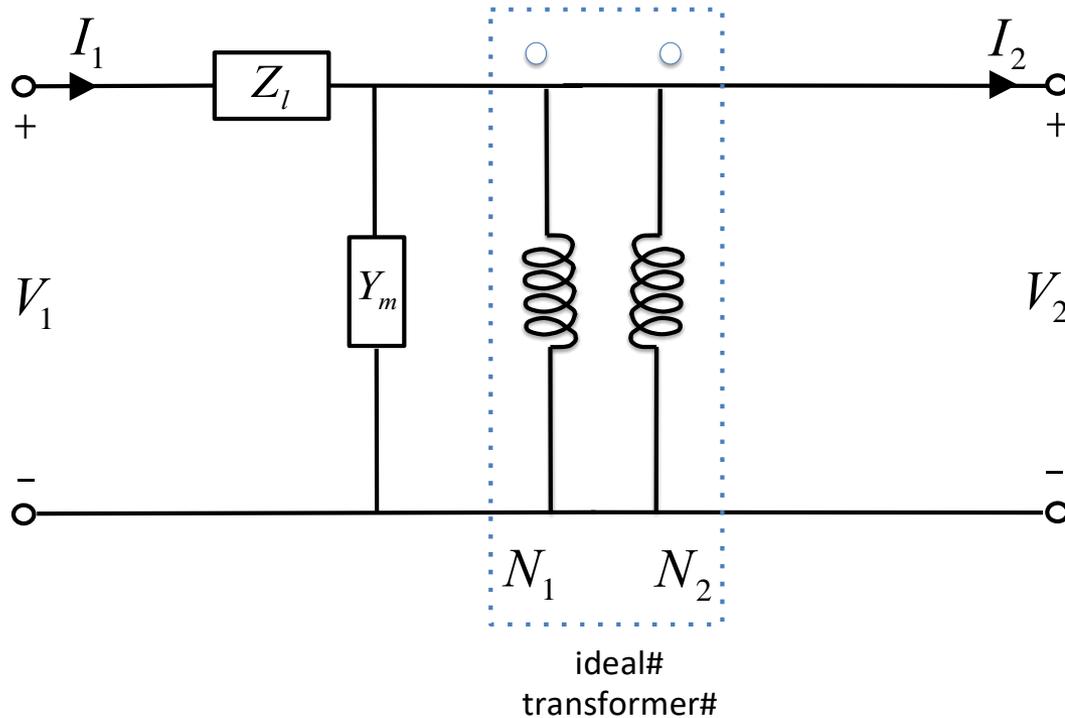


$$\begin{aligned} \hat{V}_1 &= a(1 + Z_l Y_m) \hat{V}_2 \\ \hat{I}_1 &= a Y_m \hat{V}_2 + n \hat{I}_2 \end{aligned}$$



Transformer model

3-phase ideal transformer

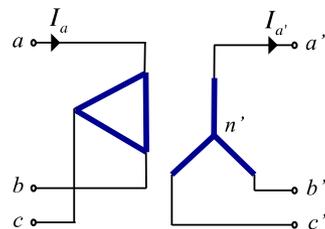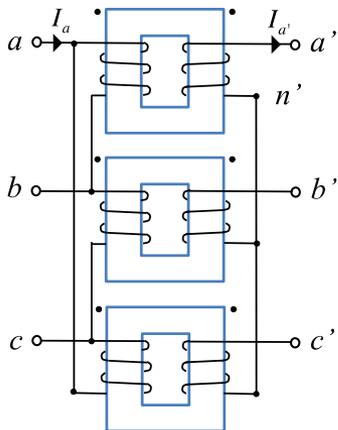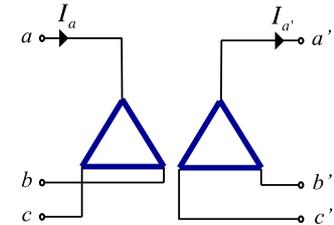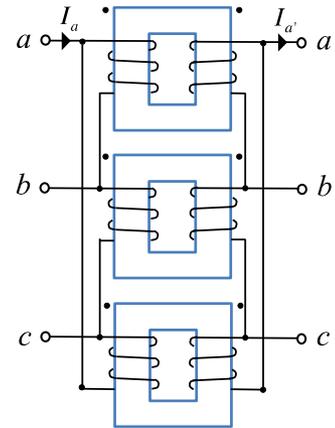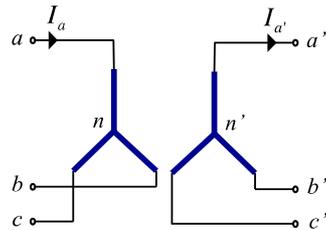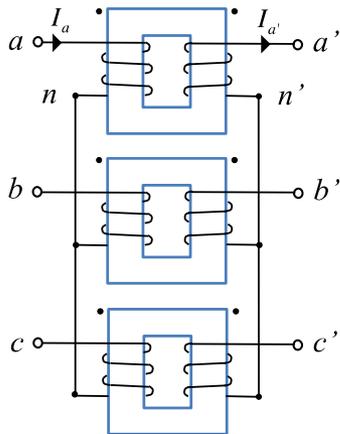



Transformer model

3-phase *ideal* transformer

Property	Gain
Voltage gain	$K(n)$
Current gain	$\frac{1}{K^*(n)}$
Power gain	1

Configuration	Gain
YY	$K_{YY}(n) := n$

per-phase properties



Transformer model

3-phase *ideal* transformer

Property	Gain
Voltage gain	$K(n)$
Current gain	$\frac{1}{K^*(n)}$
Power gain	1

Configuration	Gain
YY	$K_{YY}(n) := n$
$\Delta\Delta$	$K_{\Delta\Delta}(n) := n$

per-phase properties



Transformer model

3-phase *ideal* transformer

Property	Gain
Voltage gain	$K(n)$
Current gain	$\frac{1}{K^*(n)}$
Power gain	1

Configuration	Gain
YY	$K_{YY}(n) := n$
$\Delta\Delta$	$K_{\Delta\Delta}(n) := n$
ΔY	$K_{\Delta Y}(n) := \sqrt{3}n e^{j\pi/6}$

per-phase properties



Transformer model

3-phase *ideal* transformer

Property	Gain
Voltage gain	$K(n)$
Current gain	$\frac{1}{K^*(n)}$
Power gain	1


Configuration	Gain
YY	$K_{YY}(n) := n$
$\Delta\Delta$	$K_{\Delta\Delta}(n) := n$
ΔY	$K_{\Delta Y}(n) := \sqrt{3}n e^{j\pi/6}$
$Y\Delta$	$K_{Y\Delta}(n) := \frac{n}{\sqrt{3}} e^{j\pi/6}$

per-phase properties



Transformer model

Per-phase equivalent circuit

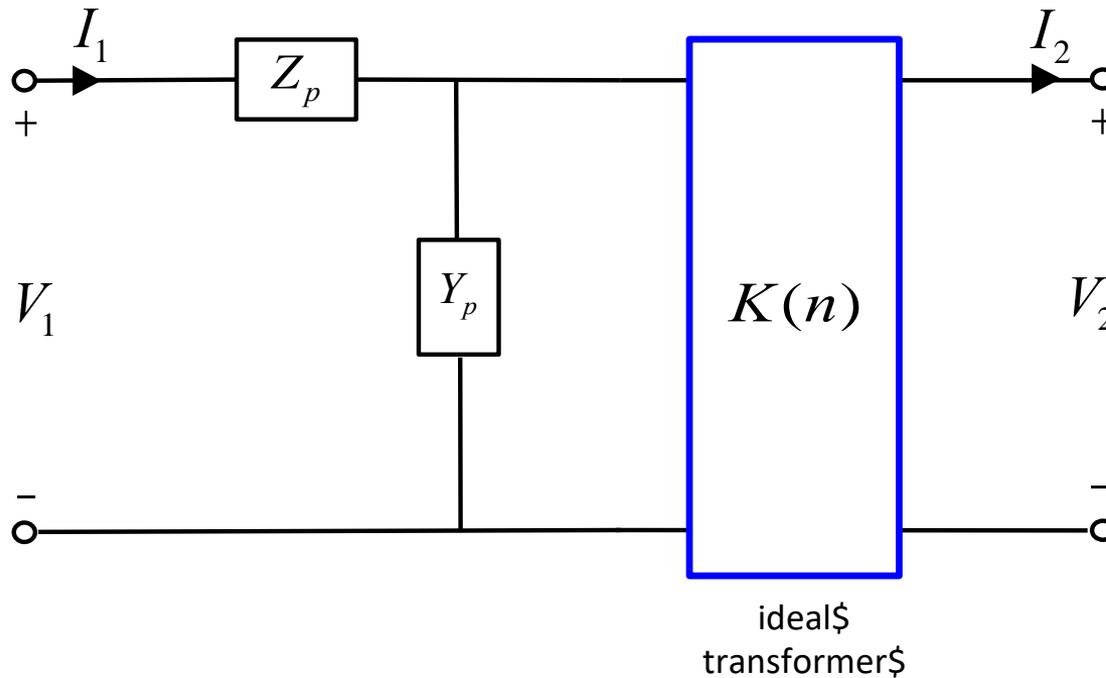


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 + Z_p Y_p & Z_p \\ Y_p & 1 \end{bmatrix} \begin{bmatrix} K^{-1}(n) & 0 \\ 0 & K^*(n) \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$



Transformer model


Recap

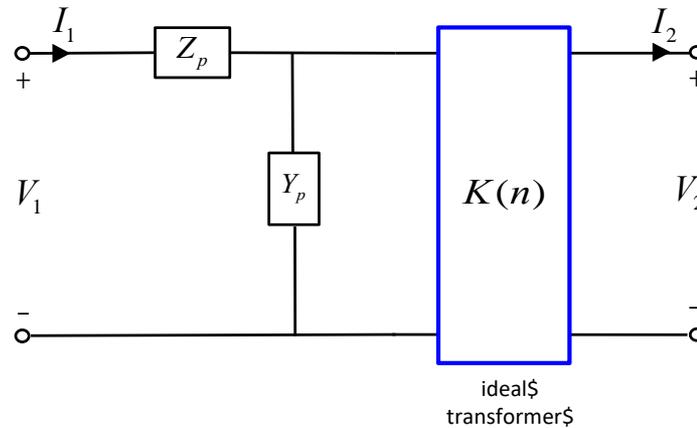- Four configurations: YY, DD, DY, YD
- Linear per-phase circuit model $(V_2, I_2) \mapsto (V_1, I_1)$





Generator model

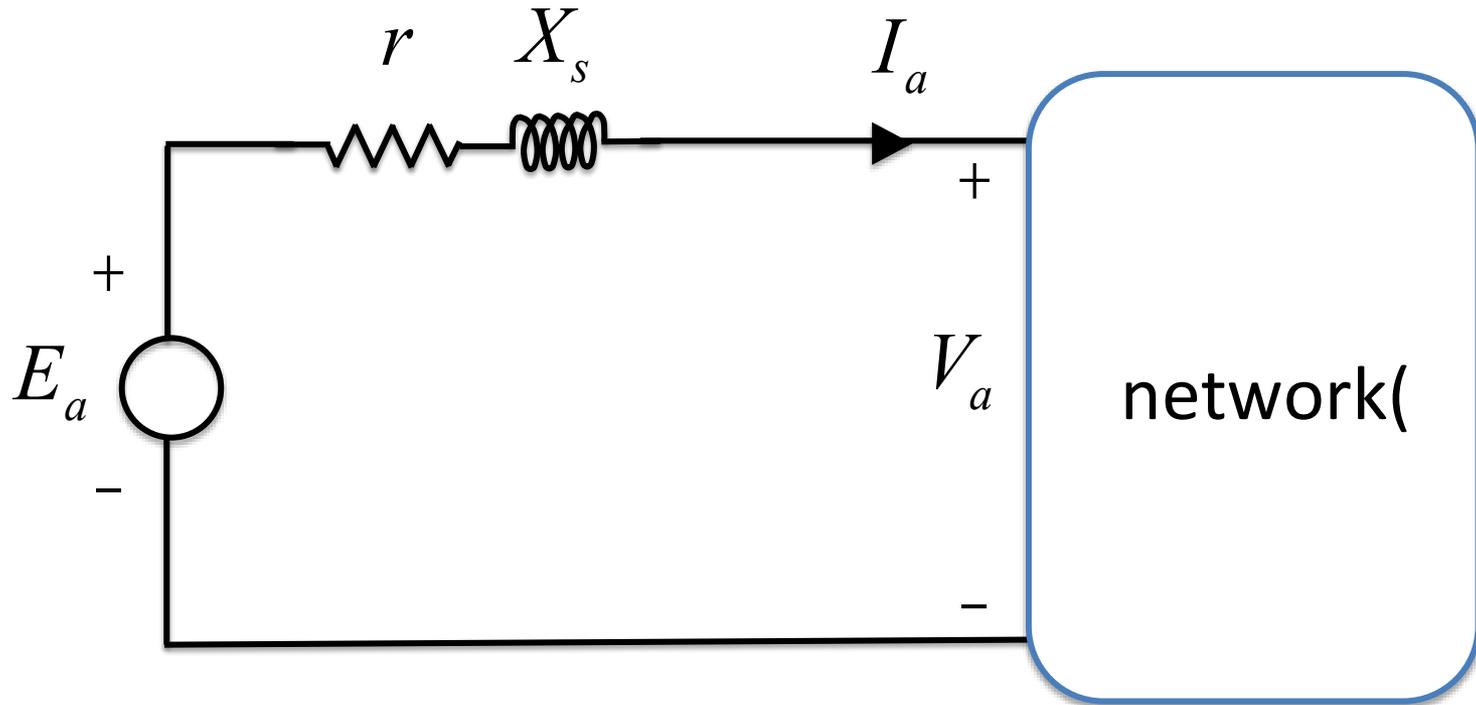


V_a : terminal voltage

E_a : open-circuit (internal) voltage



Putting everything together

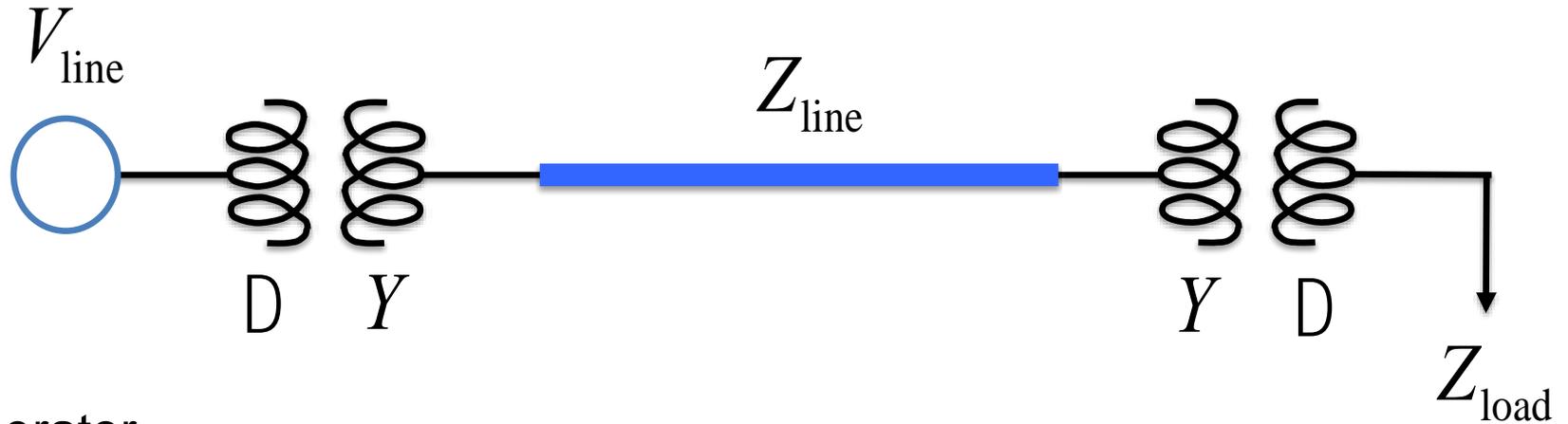

3p generator
(terminal
voltage)


3p transformer
(stepup)

3p transmission
line


3p transformer
(stepdown)



Putting everything together

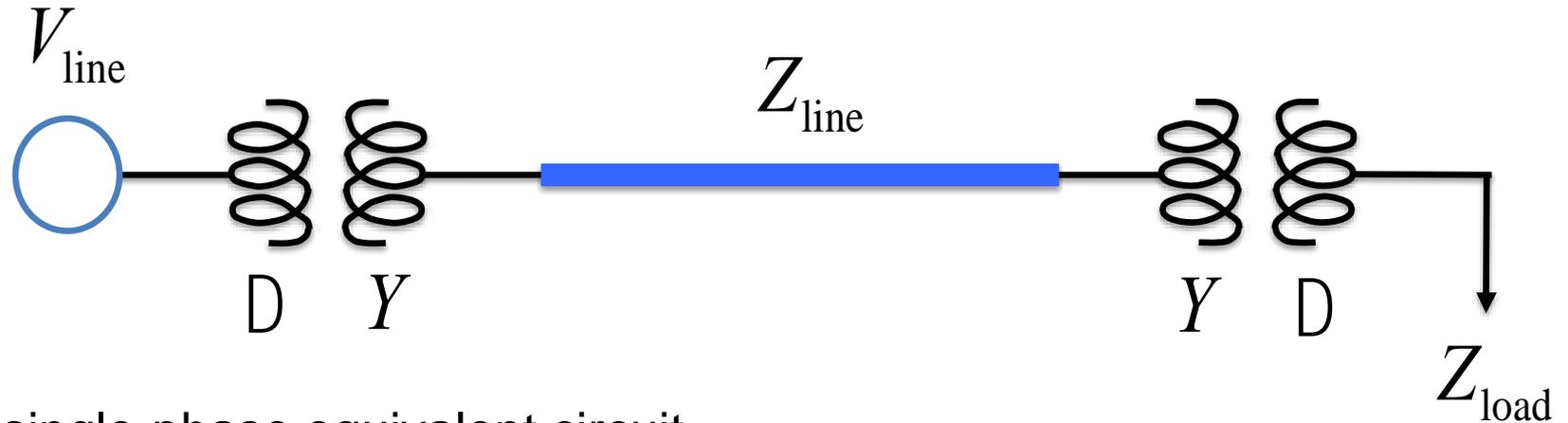

single-phase equivalent circuit

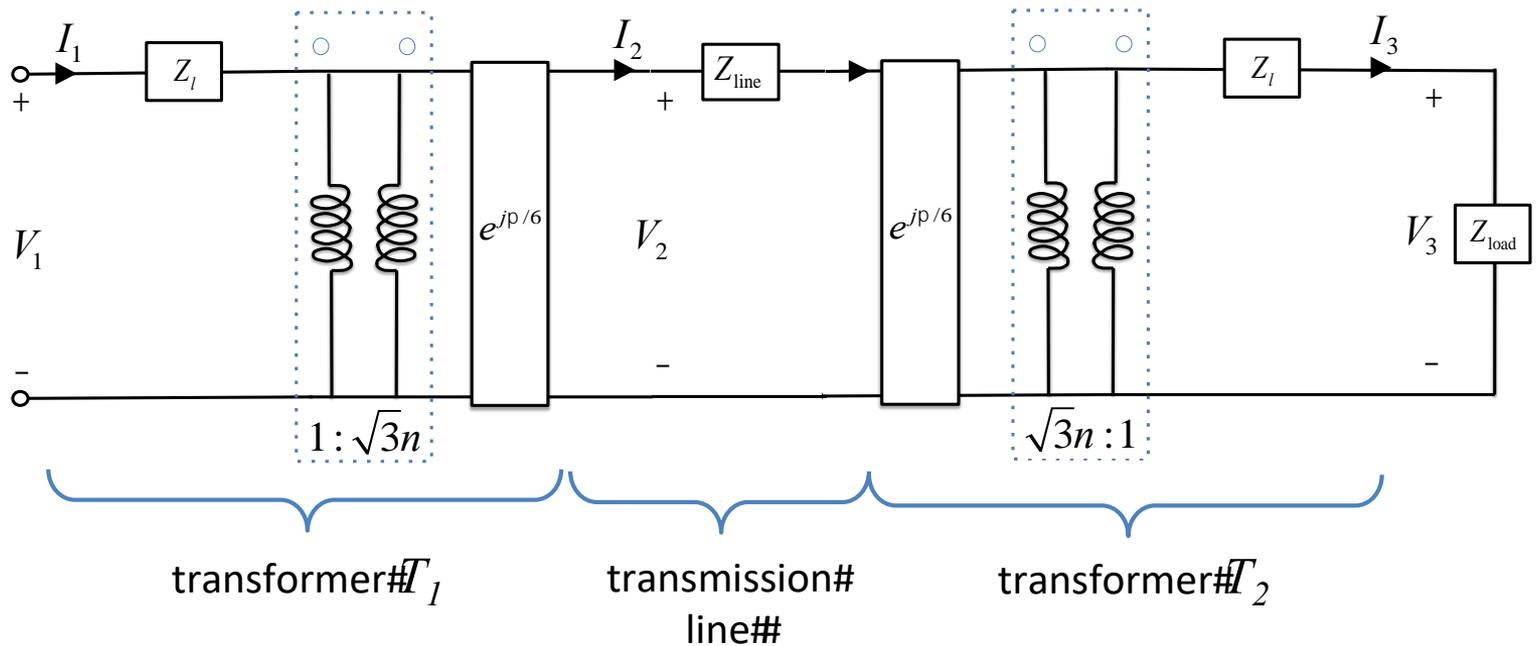



The flow of power II

Power flow and optimization

Network models (10mins)



- Admittance matrix
- Power flow models

Optimal power flow problems (35mins)

- Formulation and example
- Convex relaxations
- Real-time OPF




Example circuit model

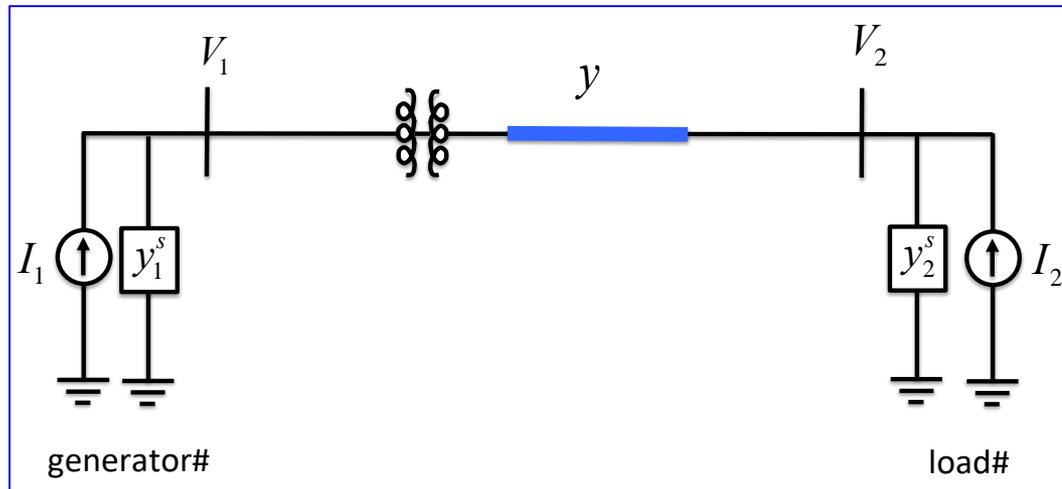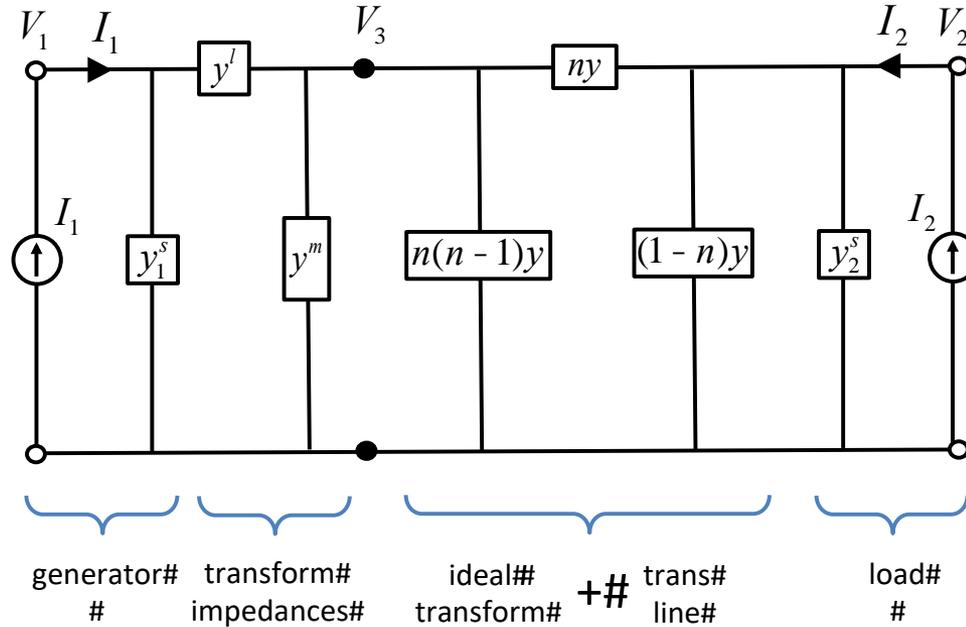




Network model

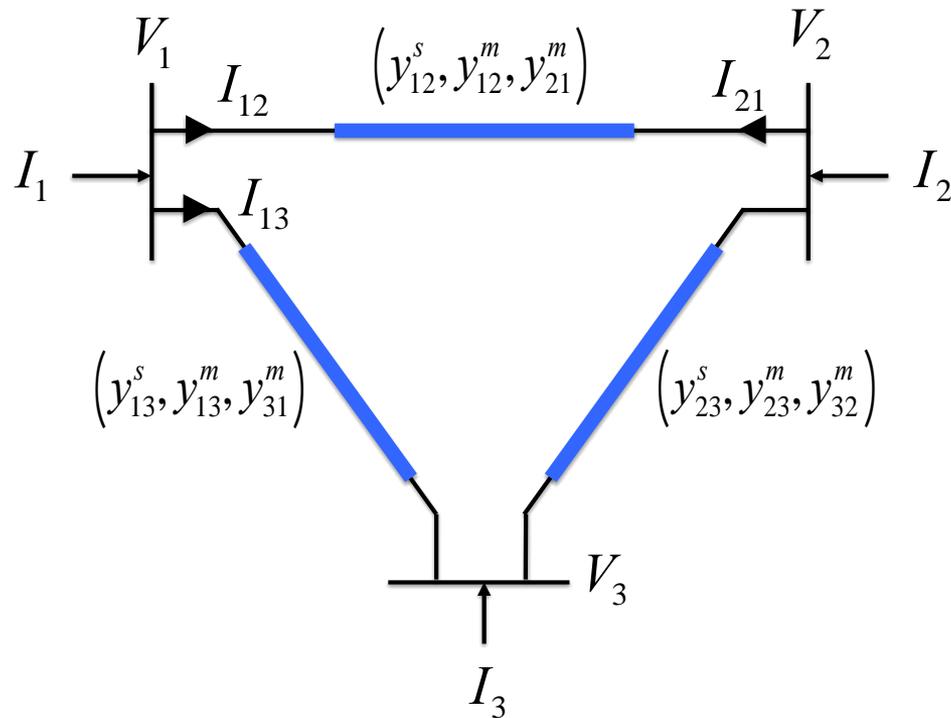

- Each line modeled as Π model
- Series impedence
 - Shunt admittance at each end
 - They may **not** be equal



Network admittance matrix

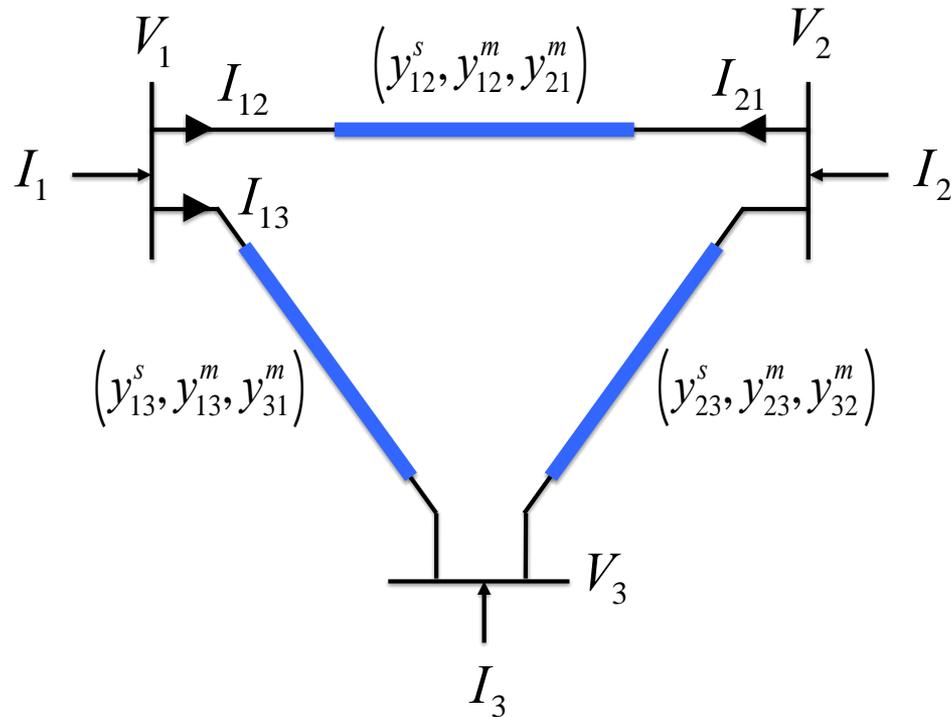


$$I = YV$$

Y : network graph + admittances



Network admittance matrix

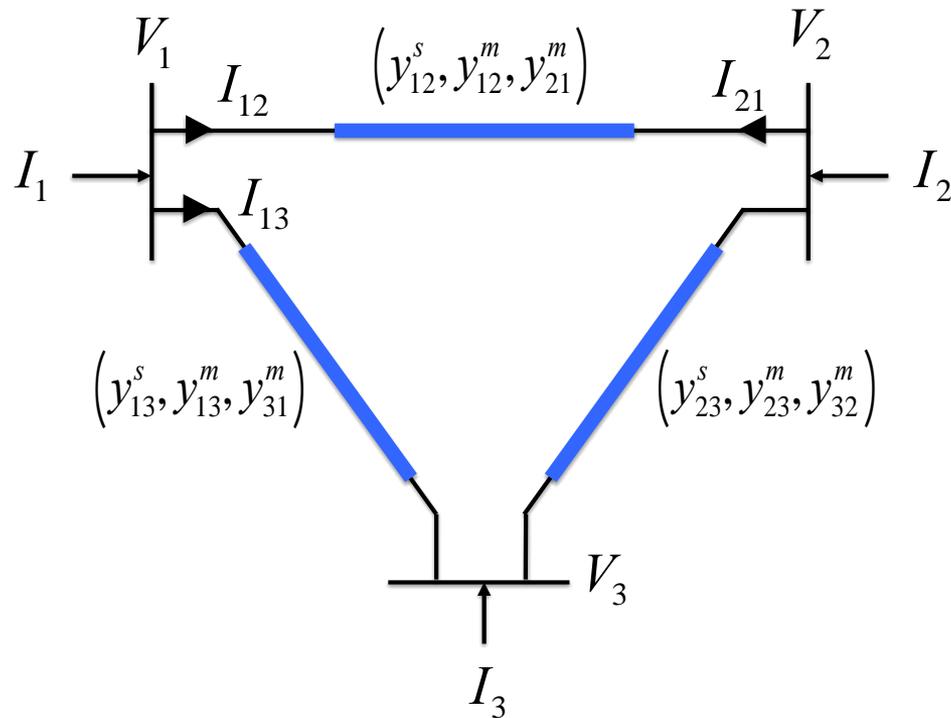

$$Y_{jk} = \begin{cases} -y_{jk}^s, & j \sim k \ (j \neq k) \\ \sum_{k: j \sim k} y_{jk}^s + y_{jj}^m, & j = k \\ 0 & \text{otherwise} \end{cases}$$

$$y_{jj}^m := \sum_{k: j \sim k} y_{jk}^m$$



The flow of power II

Power flow and optimization

Network models (10mins)


- Admittance matrix
- Power flow models

Optimal power flow problems (35mins)

- Formulation and example
- Convex relaxations
- Real-time OPF



Bus injection model

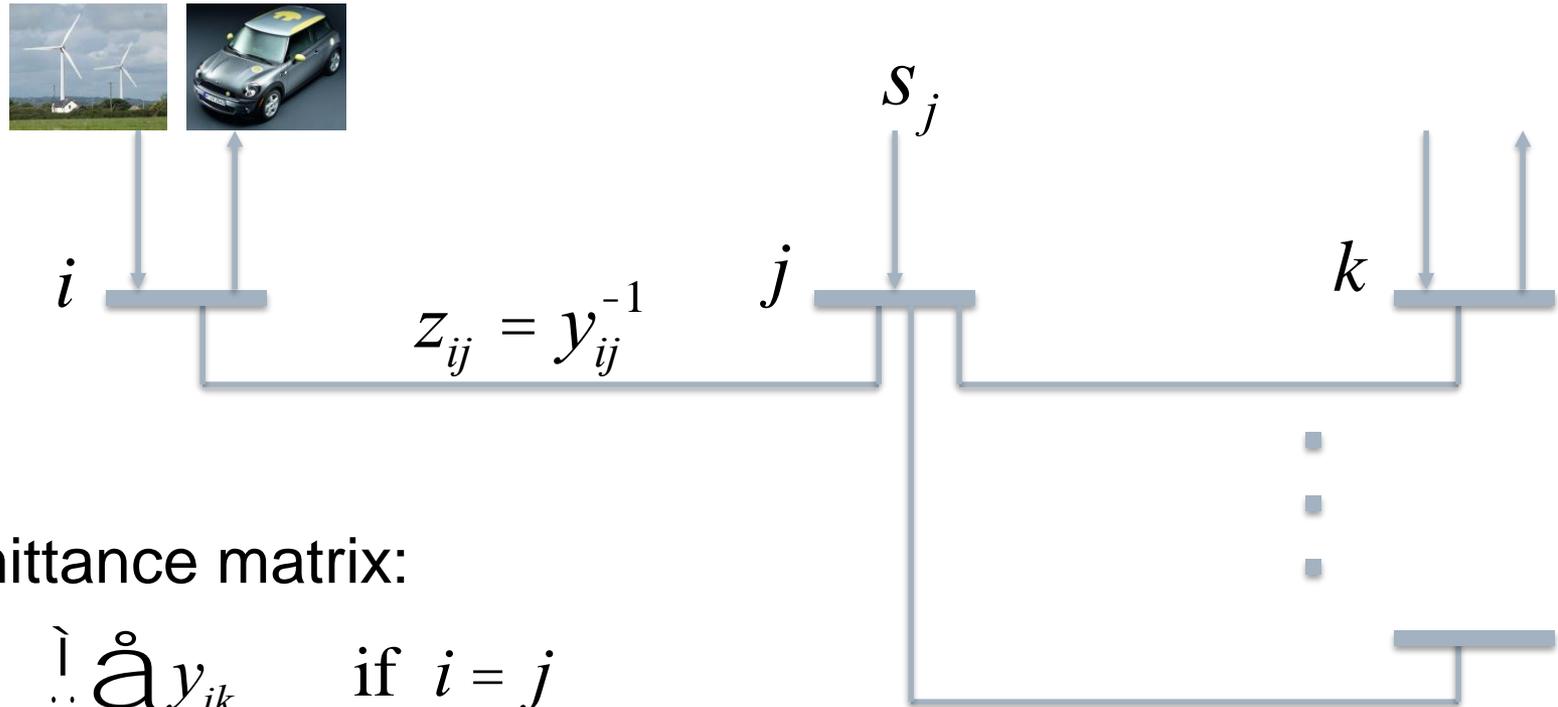

admittance matrix:

$$Y_{ij} := \begin{cases} \hat{a} y_{ik} & \text{if } i = j \\ -y_{ij} & \text{if } i \sim j \\ 0 & \text{else} \end{cases}$$

graph G : undirected

Y specifies topology of G and impedances z on lines



Bus injection model

$$I = YV$$


Kirchhoff law

$$s_j = V_j I_j^* \quad \text{for all } j$$

power balance

admittance matrix:
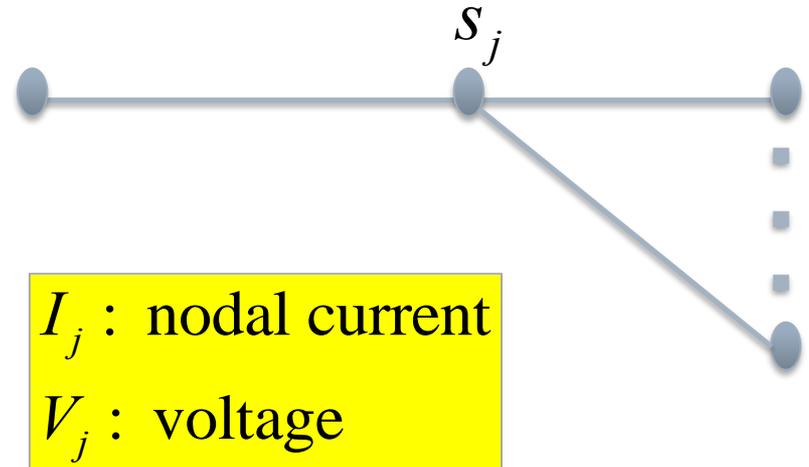
$$Y_{ij} := \begin{cases} \sum_{k \sim i} y_{ik} & \text{if } i = j \\ -y_{ij} & \text{if } i \sim j \\ 0 & \text{else} \end{cases}$$





Bus injection model

$$I = YV$$

Kirchhoff law

$$s_j = V_j I_j^* \quad \text{for all } j$$

power balance

Eliminate I :

$$s_j = \mathring{a} \sum_{k:k \sim j} y_{jk}^* \left(|V_j|^2 - V_j V_k^* \right) \quad \text{for all } j$$



Bus injection model

Complex form:

$$s_j = \sum_{k:k \sim j} \hat{a}_{jk} y_{jk}^* \left(|V_j|^2 - V_j V_k^* \right) \quad \text{for all } j$$

Polar form:

$$p_j = \left(\sum_{k=0}^n g_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| (g_{jk} \cos \theta_{jk} - b_{jk} \sin \theta_{jk})$$

$$q_j = \left(\sum_{k=0}^n b_{jk} \right) |V_j|^2 - \sum_{k \neq j} |V_j| |V_k| (b_{jk} \cos \theta_{jk} + g_{jk} \sin \theta_{jk})$$

Cartesian form:

$$p_j = \sum_{k=0}^n (g_{jk} (e_j^2 + f_j^2) - g_{jk} (e_j e_k + f_j f_k) + b_{jk} (f_j e_k - e_j f_k))$$

$$q_j = \sum_{k=0}^n (b_{jk} (e_j^2 + f_j^2) - b_{jk} (e_j e_k + f_j f_k) - g_{jk} (f_j e_k - e_j f_k))$$



Bus injection model

DC power flow

$$p_j = \sum_{k=0}^n b_{jk} |V_j| |V_k| (\theta_j - \theta_k)$$

Assumptions:

- Lossless short line
- Small angle difference
- Fixed voltage magnitude
- Ignore reactive power



The flow of power II

Power flow and optimization

Network models (10mins)

- Admittance matrix
- Power flow models

Optimal power flow problems (35mins)

- Formulation and example
- Convex relaxations
- Real-time OPF



Optimal power flow (OPF)

OPF is solved routinely for

- network control & optimization decisions
- market operations & pricing
- at timescales of mins, hours, days, ...

Non-convex and hard to solve

- Huge literature since 1962
- Common practice: DC power flow (LP)
- Also: Newton-Raphson, interior point, ...

$$\min c(x) \quad \text{s. t.} \quad F(x) = 0, \quad x \in \bar{x}$$



Optimal power flow

min	$\text{tr} (CVV^H)$	gen cost, power loss
over	(V, s, l)	
subject to	$s_j = \text{tr} (Y_j^H VV^H)$	power flow equation
	$l_{jk} = \text{tr} (B_{jk}^H VV^H)$	line flow
	$\underline{s}_j \leq s_j \leq \bar{s}_j$	injection limits
	$\underline{l}_{jk} \leq l_{jk} \leq \bar{l}_{jk}$	line limits
	$\underline{V}_j \leq V_j \leq \bar{V}_j$	voltage limits

- Y_j^H describes network topology and impedances
- s_j is net power injection (generation) at node j



Optimal power flow

min	$\text{tr} (CVV^H)$	gen cost, power loss
over	(V, s, l)	
subject to	$s_j = \text{tr} (Y_j^H VV^H)$	power flow equation
	$l_{jk} = \text{tr} (B_{jk}^H VV^H)$	line flow
	$\underline{s}_j \preceq s_j \preceq \bar{s}_j$	injection limits
	$\underline{l}_{jk} \preceq l_{jk} \preceq \bar{l}_{jk}$	line limits
	$\underline{V}_j \preceq V_j \preceq \bar{V}_j$	voltage limits

nonconvex feasible set (nonconvex QCQP)



- Y_j^H not Hermitian (nor positive semidefinite)
- C is positive semidefinite (and Hermitian)



Optimal power flow

OPF problem underlies numerous applications

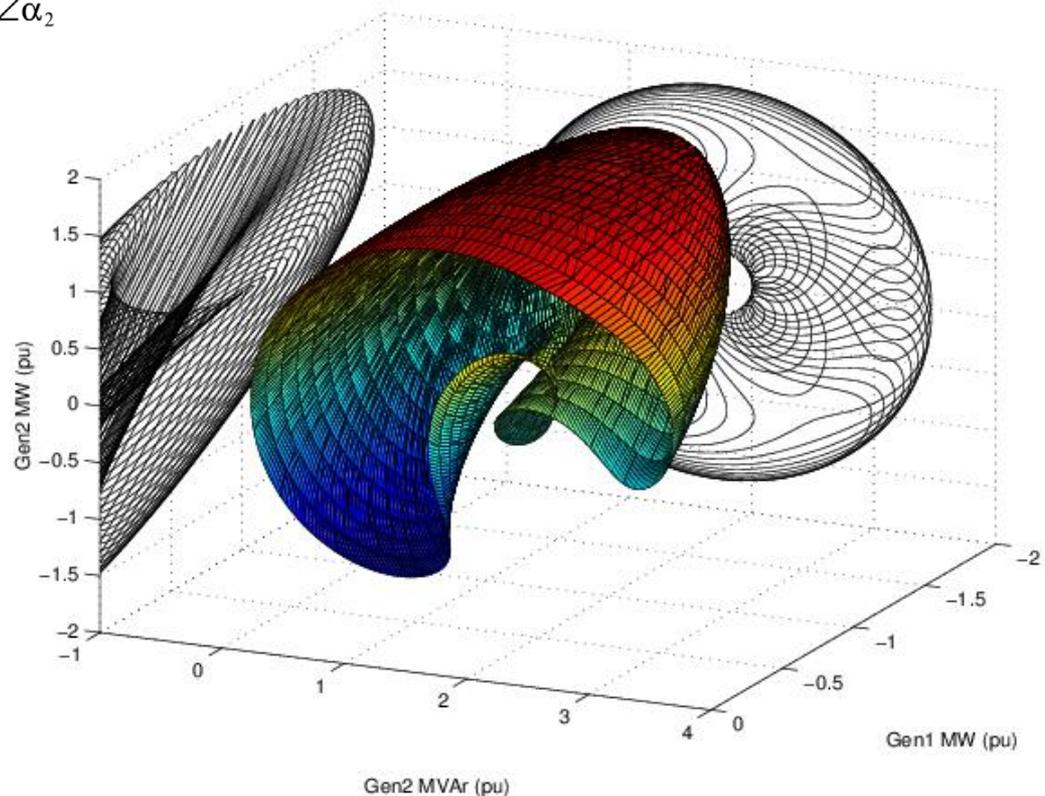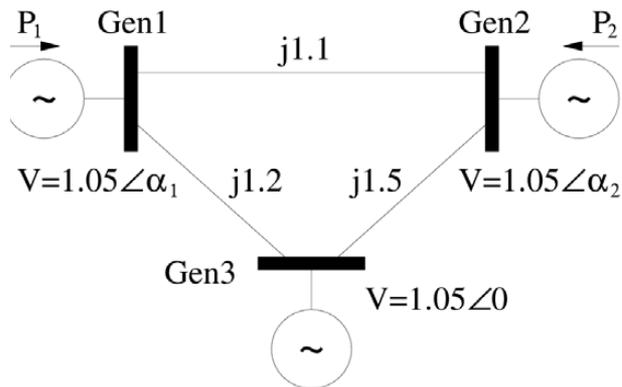- nonlinearity of power flow equations \rightarrow nonconvexity





Dealing with nonconvexity

Linearization

- DC approximation

Convex relaxations

- Semidefinite relaxation (Lasserre hierarchy)
- QC relaxation (van Hentenryck)
- Strong SOCP (Sun)



Dealing with nonconvexity

Linearization

- DC approximation

Convex relaxations

- Semidefinite relaxation (Lasserre hierarchy)
- QC relaxation (van Hentenryck)
- Strong SOCP (Sun)

Realtime OPF

- Online algorithm, as opposed to offline
- Also tracks time-varying OPF



Relaxations of AC OPF

dealing with nonconvexity



Bose (UIUC)



Chandy



Farivar (Google)



Gan (FB)



Lavaei (UCB)




Li (Harvard)

many others at & **outside** Caltech ...



Equivalent feasible sets

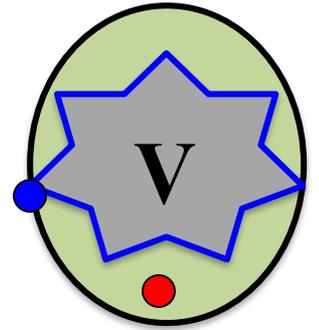

$$\min \quad \text{tr } CVV^H$$

$$\text{subject to } \underline{s}_j \in \boxed{\text{tr} \left(Y_j^H VV^H \right)} \in \bar{s}_j \quad \underline{v}_j \in |V_j|^2 \in \bar{v}_j$$

quadratic in V
linear in W

Equivalent problem:

$$\min \quad \text{tr } CW$$

$$\text{subject to } \boxed{\underline{s}_j \in \text{tr} \left(Y_j^H W \right) \in \bar{s}_j \quad \underline{v}_j \in W_{jj} \in \bar{v}_j}$$

$$W \succeq 0, \text{ rank } W = 1$$

convex in W
except this constraint



Solution strategy


$$\text{OPF:} \quad \min_{x \in \mathbf{X}} f(x)$$

$$\text{relaxation:} \quad \min_{\hat{x} \in \mathbf{X}^+} f(\hat{x})$$

If optimal solution \hat{x}^* satisfies easily checkable conditions, then optimal solution x^* of OPF can be recovered



Equivalent relaxations

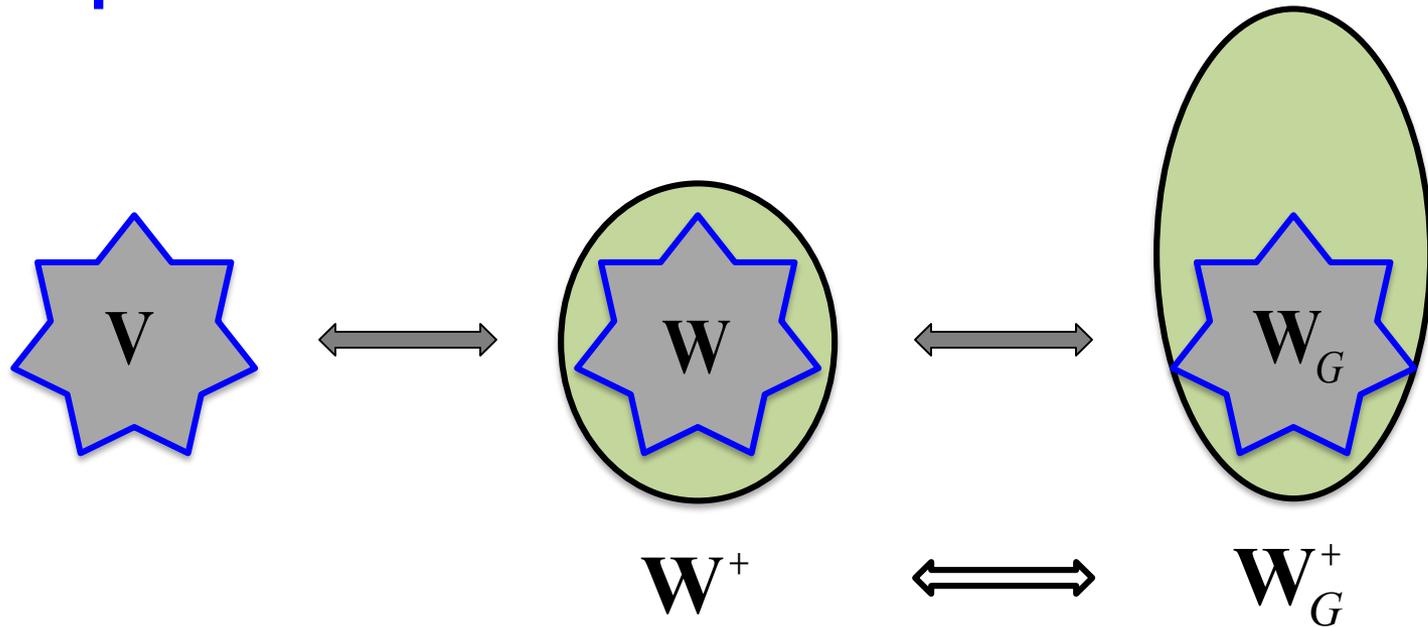

Theorem

- Radial G : SOCP is equivalent to SDP ($v \subseteq w^+ @ w_G^+$)
- Mesh G : SOCP is strictly coarser than SDP

For radial networks: always solve SOCP !



Exact relaxation

For **radial** networks, **sufficient** conditions on

- power injections bounds, or
- voltage upper bounds, or
- phase angle bounds



Exact relaxation

For radial networks, sufficient conditions on

- power injections bounds, or
- voltage upper bounds, or
- phase angle bounds



Exact relaxation

QCQP (C, C_k)

$$\min \quad \text{tr}(Cxx^H)$$

$$\text{over } x \in \mathbf{C}^n$$

$$\text{s.t.} \quad \text{tr}(C_k xx^H) \leq b_k \quad k \in K$$

graph of QCQP

$$G(C, C_k) \text{ has edge } (i, j) \iff$$

$$C_{ij} \neq 0 \text{ or } [C_k]_{ij} \neq 0 \text{ for some } k$$

QCQP over tree

$$G(C, C_k) \text{ is a tree}$$




Exact relaxation

QCQP (C, C_k)

$$\min \quad \text{tr}(Cxx^H)$$

$$\text{over } x \in \mathbf{C}^n$$
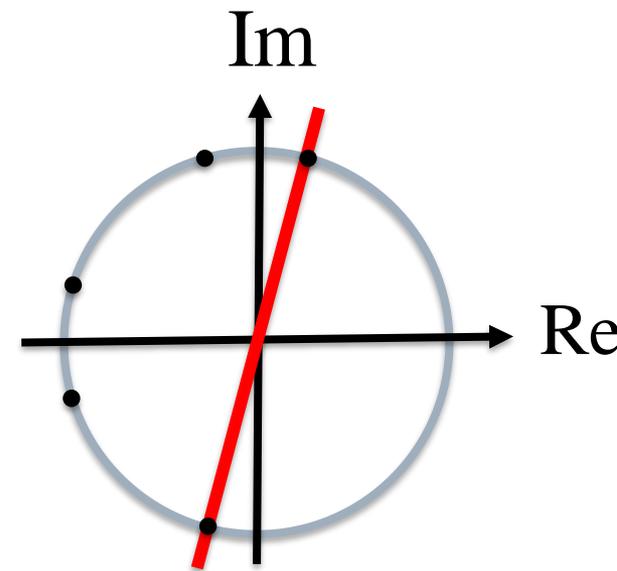
$$\text{s.t.} \quad \text{tr}(C_k xx^H) \leq b_k \quad k \in K$$



Key condition


$i \sim j$: $(C_{ij}, [C_k]_{ij}, \dots, k)$ lie on half-plane through 0

Theorem

SOCP relaxation is exact for
QCQP over tree



Implication on OPF

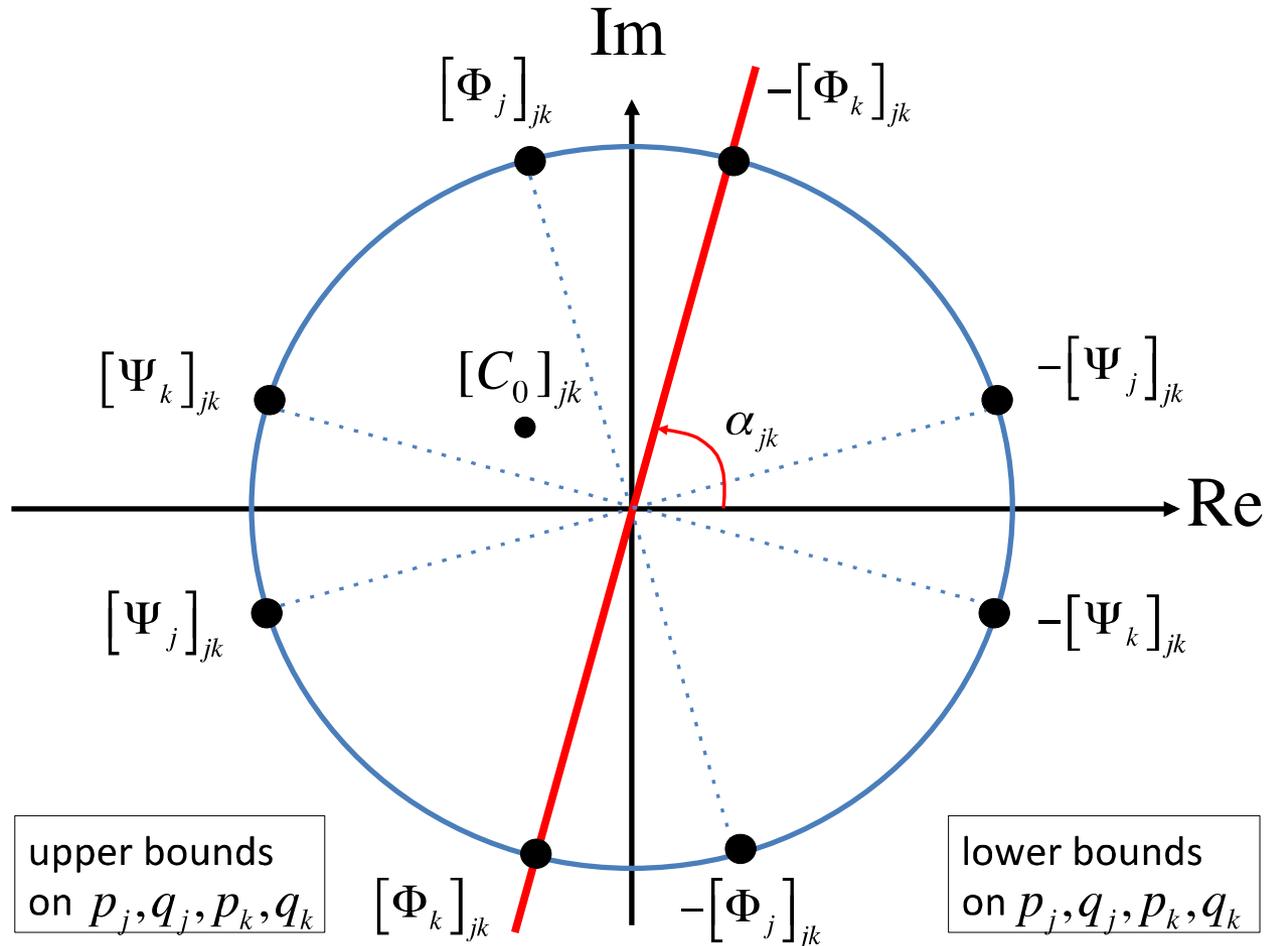


Not both lower & upper bounds on real & reactive powers at both ends of a line can be finite




Example

Real Power

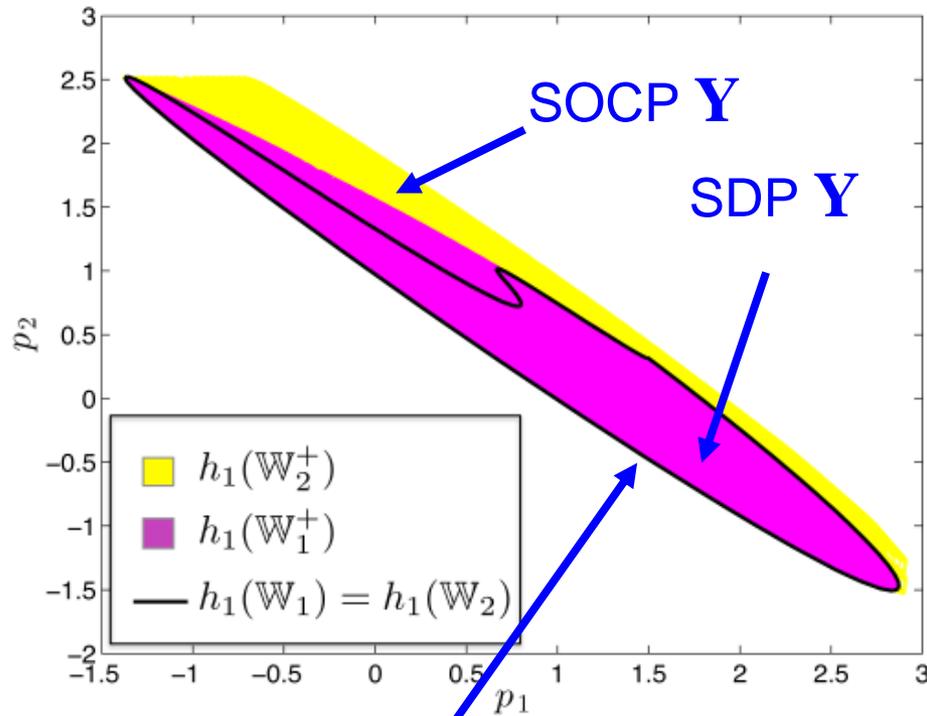

Reactive Power

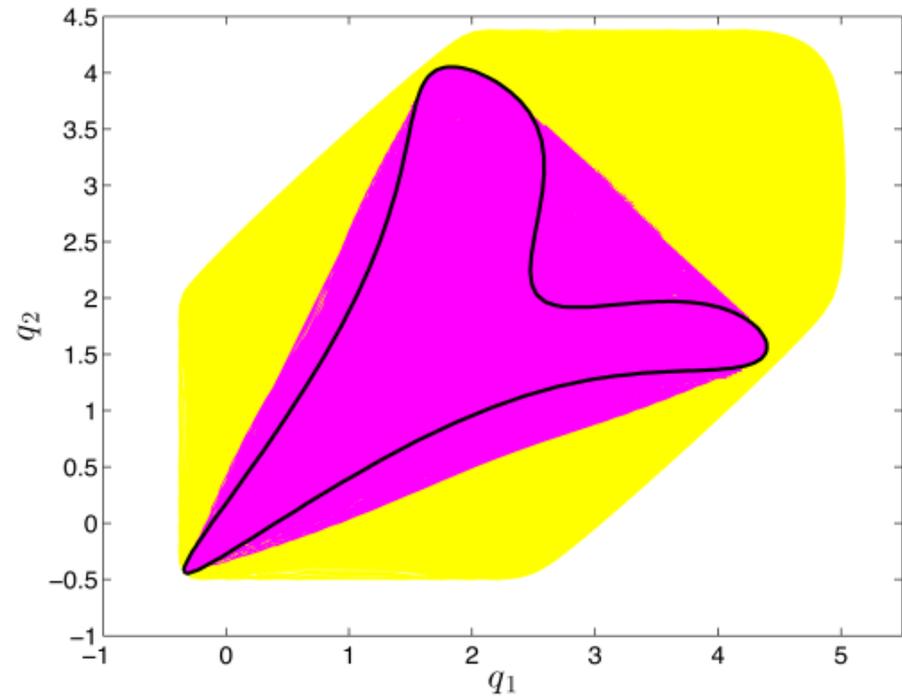

power flow solution \mathbf{X}

- Relaxation is exact if \mathbf{X} and \mathbf{Y} have same Pareto front
- SOCP is faster but coarser than SDP



Potential benefits

IEEE test systems

SDP cost

MATPOWER cost

Syst	rank (\bar{X}_0)	J°	\bar{J}
9	1	5296.7	5296.7
30	1	576.9	576.9
118	1	129661	129661
14A	1	8092.8	9093.8

12.4% lower cost than solution from nonlinear solver MATPOWER




Potential benefits

Case study on an SCE feeder


- Southern California
- 1,400 residential houses, ~200 commercial buildings
- Controllable loads: EV, pool pumps, HVAC, PV inverters
- Formulated as an OPF problem, multiphase unbalanced radial network

baseline

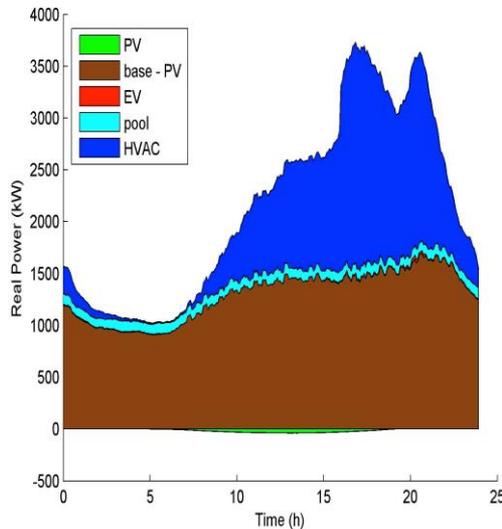

peak load reduction: 8%
energy cost reduction: 4%

optimized

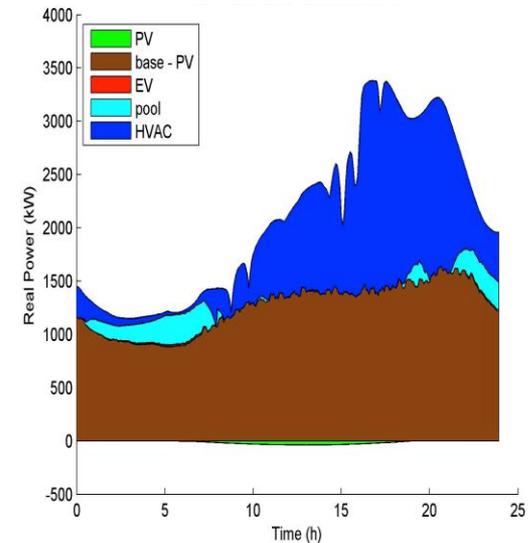




Realtime AC OPF for tracking



Gan (FB)

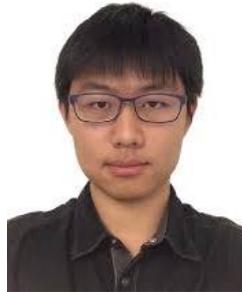

Tang (Caltech)



Dvijotham (DeepMind)

See also: Dall'Anese et al, Bernstein et al,
Hug & Dorfler et al, Callaway et al

Gan & L, JSAC 2016
Tang et al, TSG 2017



Motivations

Simplify OPF simulation/solution

- Solving static OPF with simulator in the loop
- Avoid modifying GridLab-D during ARPA-E GENI (2012-15)

Deal with nonconvexity

- Network computes power flow solutions in real time at scale for free
- Exploit it for our optimization/control

Track optimal solution of time-varying OPF

- Uncertainty will continue to increase
- Real-time measurements increasingly become available on seconds timescale
- Must, and can, close the loop in the future



Dealing with nonconvexity

Linearization

- DC approximation

Convex relaxations

- Semidefinite relaxation (Lasserre hierarchy)
- QC relaxation (van Hentenryck)
- Strong SOCP (Sun)

Realtime OPF

- Online algorithm, as opposed to offline
- Also tracks time-varying OPF



Literature

Static OPF:

- ❑ Gan and Low, JSAC 2016
- ❑ Dall'Anese, Dhople and Giannakis, TPS 2016
- ❑ Arnold et al, TPS 2016
- ❑ A. Hauswirth, et al, Allerton 2016

Time-varying OPF:

- ❑ Dall'Anese and Simonetto, TSG 2016
- ❑ Wang et al, TPS 2016
- ❑ Tang, Dvijotham and Low, TSG 2017
- ❑ Tang and Low, CDC 2017

Earlier relevant work on voltage control

- ❑ Survey: Molzahn et al, TSG 2017



OPF


$$\min c_0(y) + c(x)$$

over x, y

s. t.

controllable
devices

uncontrollable
state

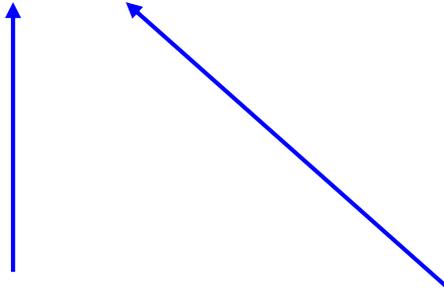



OPF

$$\min \quad c_0(y) + c(x)$$

$$\text{over } x, y$$

$$\text{s. t. } F(x, y) = 0$$

power flow equations



OPF

$$\min c_0(y) + c(x)$$

$$\text{over } x, y$$

$$\text{s. t. } F(x, y) = 0$$

power flow equations

$$y \in \bar{y}$$

operational constraints

$$x \in X := \{\underline{x} \leq x \leq \bar{x}\}$$

capacity limits

$$\text{Assume: } \frac{\partial F}{\partial y} \neq 0 \quad \Rightarrow \quad y(x) \text{ over } X$$



OPF: eliminate y

$$\min_x c_0(y(x)) + c(x)$$

$$\text{s. t. } y(x) \in \bar{y}$$

$$x \in X := \{\underline{x} \leq x \leq \bar{x}\}$$

Theorem [Huang, Wu, Wang, & Zhao. TPS 2016]

For DistFlow model, controllable (feasible) region

$$\{x \mid y(x) \in \bar{y}, x \in X\}$$

is convex (despite nonlinearity of $y(x)$)



OPF: add barrier or penalty

$$\min_x c_0(y(x)) + c(x)$$

$$\text{s. t. } y(x) \in \bar{y}$$

$$x \hat{\in} X := \{\underline{x} \leq x \leq \bar{x}\}$$



add barrier or penalty function
to remove operational constraints

$$\min f(x, y(x); m)$$

$$\text{over } x \hat{\in} X$$

f : nonconvex



Online (feedback) perspective

DER : gradient update

$$x(t+1) = G(x(t), y(t))$$

cyber
network

control
 $x(t)$

measurement,
communication
 $y(t)$

Network: power flow solver

$$y(t) : F(x(t), y(t)) = 0$$

physical
network

- Explicitly exploits network as power flow solver
- Naturally tracks changing network conditions



Outline: realtime OPF

Motivation

Problem formulation

Static OPF

[Gan & Low, JSAC 2016]

- 1st order algorithm
- Optimality properties

Time-varying OPF

[Tang, Dj, & Low, TSG 2017]

- 2nd order algorithm
- Tracking performance
- Distributed implementation

[Tang & Low, CDC 2017]





Static OPF

$$\begin{array}{ll} \min & f(x, y(x); m) \\ \text{over} & x \in X \end{array}$$

gradient projection algorithm:

$$x(t+1) = \hat{P}_X \left(x(t) - h \frac{\nabla_x f}{\|\nabla_x f\|} (t) \right)$$

active control

$$y(t) = y(x(t))$$

law of physics



Local optimality

Under appropriate assumptions

- $x(t)$ converges to set of local optima
- if #local optima is finite, $x(t)$ converges



Global optimality

Assume: $p_0(x)$ convex over X

$v_k(x)$ concave over X

$$A := \{x \in X : v(x) \in a\bar{v} + (1-a)\underline{v}\}$$

Theorem

If $\text{co}\{\text{local optima}\}$ are in A then

- $x(t)$ converges to the set of global optima
- $x(t)$ itself converges a global optimum if
#local optima is finite



Global optimality

Assume: $p_0(x)$ convex over X

$v_k(x)$ concave over X

$$A := \{x \in X : v(x) \in a\bar{v} + (1-a)\underline{v}\}$$

Theorem

- Can choose a s.t.

$A \rightarrow$ original feasible set

- If SOCP is exact over X , then assumption holds




Suboptimality gap

any local
optimum

any original
feasible pt
slightly away
from X boundary

$$f(x^*) - f(\hat{x}) \leq r \gg 0$$

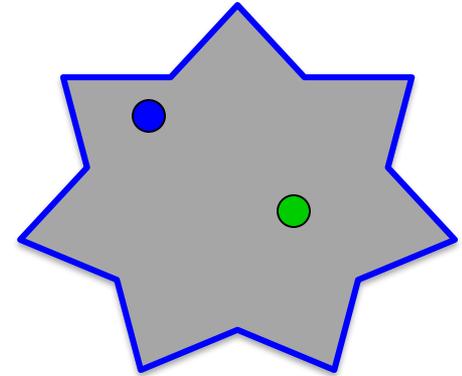

- Informally, a local minimum is almost as good as any strictly interior feasible point



Simulations

# bus	CVX		IPM		error	speedup
	obj	time(s)	obj	time(s)		
42	10.4585	6.5267	10.4585	0.2679	-0.0e-7	24.36
56	34.8989	7.1077	34.8989	0.3924	+0.2e-7	18.11
111	0.0751	11.3793	0.0751	0.8529	+5.4e-6	13.34
190	0.1394	20.2745	0.1394	1.9968	+3.3e-6	10.15
290	0.2817	23.8817	0.2817	4.3564	+1.1e-7	5.48
390	0.4292	29.8620	0.4292	2.9405	+5.4e-7	10.16
490	0.5526	36.3591	0.5526	3.0072	+2.9e-7	12.09
590	0.7035	43.6932	0.7035	4.4655	+2.4e-7	9.78
690	0.8546	51.9830	0.8546	3.2247	+0.7e-7	16.12
790	0.9975	62.3654	0.9975	2.6228	+0.7e-7	23.78
890	1.1685	67.7256	1.1685	2.0507	+0.8e-7	33.03
990	1.3930	74.8522	1.3930	2.7747	+1.0e-7	26.98
1091	1.5869	83.2236	1.5869	1.0869	+1.2e-7	76.57
1190	1.8123	92.4484	1.8123	1.2121	+1.4e-7	76.27
1290	2.0134	101.0380	2.0134	1.3525	+1.6e-7	74.70
1390	2.2007	111.0839	2.2007	1.4883	+1.7e-7	74.64
1490	2.4523	122.1819	2.4523	1.6372	+1.9e-7	74.83
1590	2.6477	157.8238	2.6477	1.8021	+2.0e-7	87.58
1690	2.8441	147.6862	2.8441	1.9166	+2.1e-7	77.06
1790	3.0495	152.6081	3.0495	2.0603	+2.1e-7	74.07
1890	3.8555	160.4689	3.8555	2.1963	+1.9e-7	73.06
1990	4.1424	171.8137	4.1424	2.3586	+1.9e-7	72.84



Outline: realtime OPF

Motivation

Problem formulation

Static OPF

[Gan & Low, JSAC 2016]

Dynamic OPF

[Tang, Dj, & Low, TSG 2017]

- 2nd order algorithm
- Tracking performance
- Distributed implementation


[Tang & Low, CDC 2017]

See also: Dall'Anese and Simonetto, TSG 2016
Wang et al, TPS 2016







Tracking performance

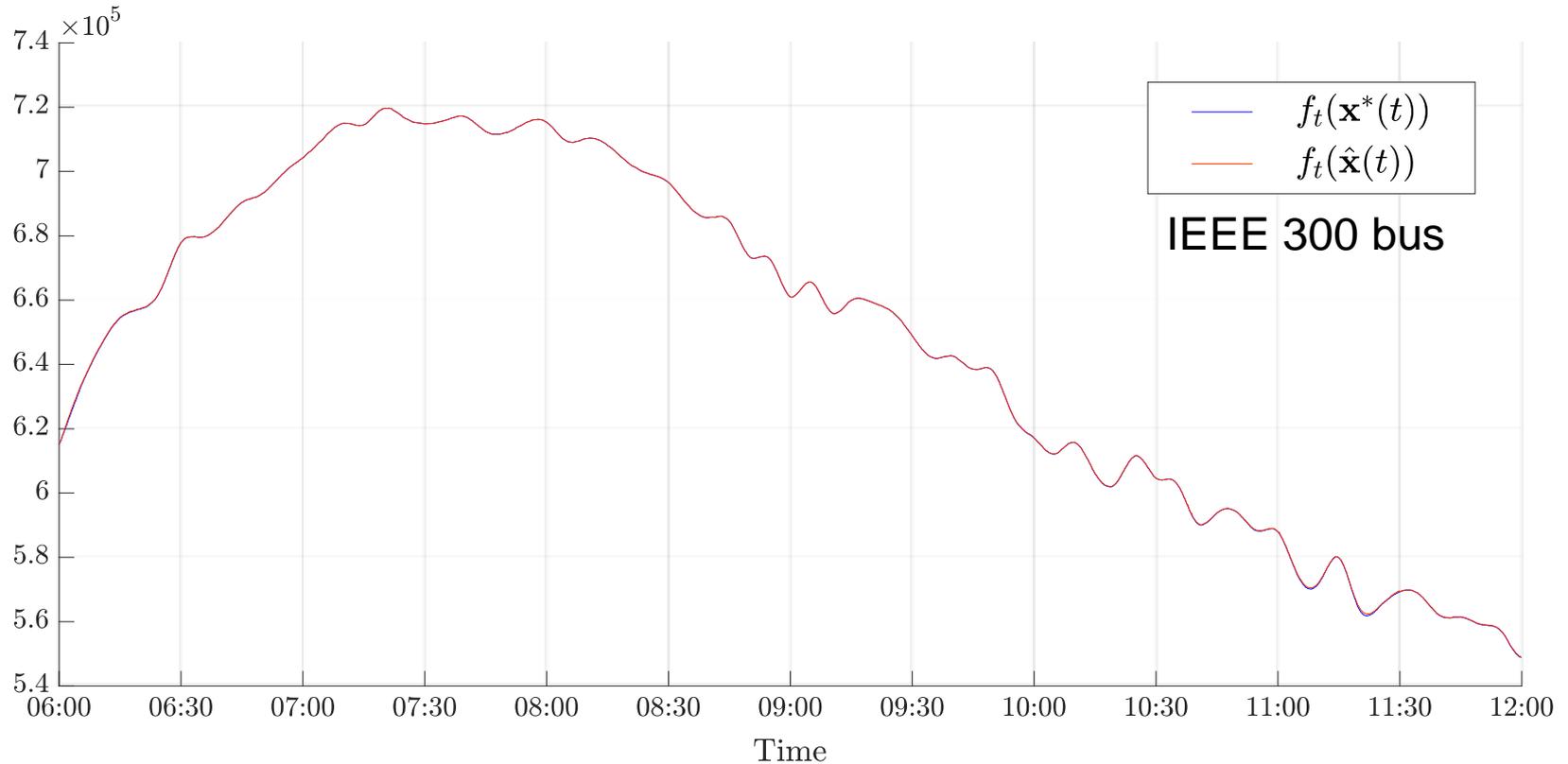

realtime OPF algorithms can track time-varying OPF well



Tracking performance

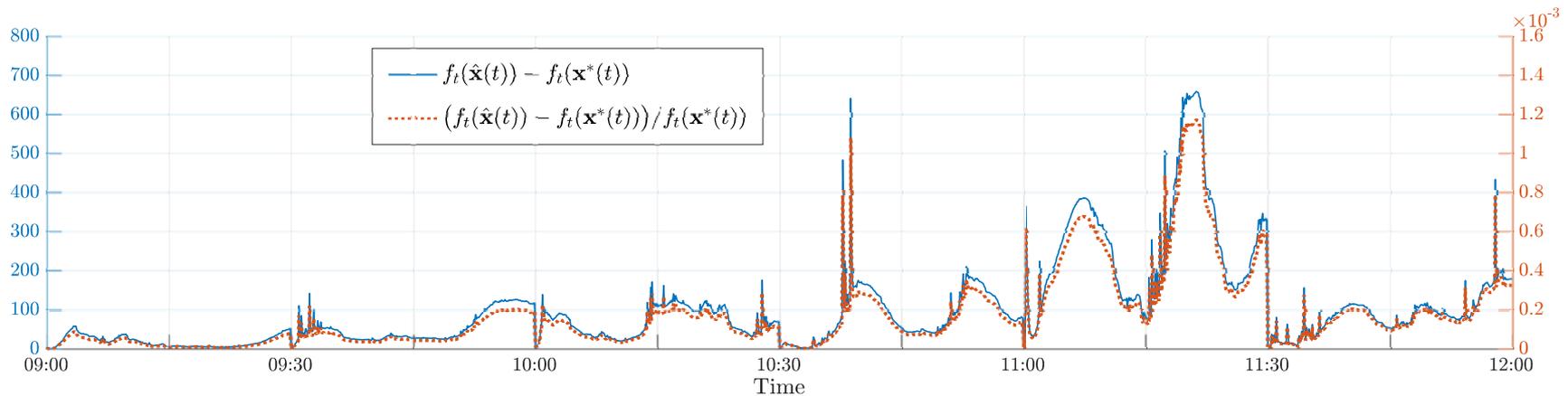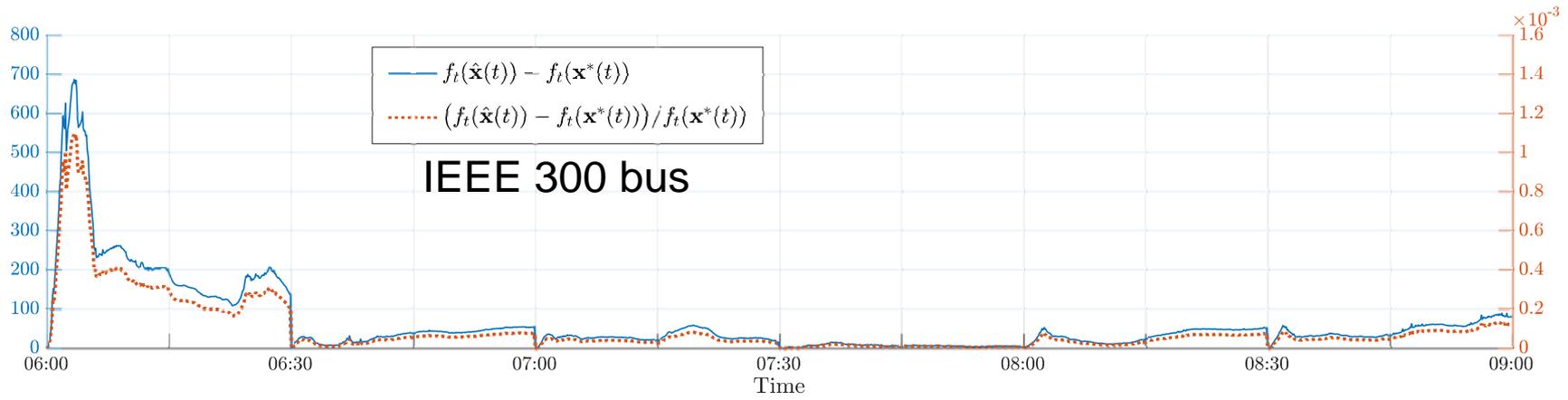

realtime OPF algorithms can track time-varying OPF well



Drifting OPF

$$\min_x c_0(y(x)) + c(x)$$

$$\text{s. t. } y(x) \in \bar{y}$$

$$x \in X$$



static
OPF

$$\min_x c_0(y(x), g_t) + c(x, g_t)$$

$$\text{s. t. } y(x, g_t) \in \bar{y}$$

$$x \in X$$



drifting
OPF



Drifting OPF

$$\begin{array}{ll} \min & f_t(x, y(x); m_t) \\ \text{over} & x \in X_t \end{array}$$

Quasi-Newton algorithm:

$$x(t+1) = \hat{x}(t) - h(H(t))^{-1} \frac{\nabla f_t}{\nabla x}(x(t)) \Big|_{x_t} \quad \text{active control}$$

$$y(t) = y(x(t)) \quad \text{law of physics}$$



Drifting OPF

$$\begin{array}{ll} \min & f_t(x, y(x); m_t) \\ \text{over} & x \hat{\mid} X_t \end{array}$$

Computing $x(t+1)$ by solving convex QP:

$$\begin{array}{ll} \min_x & \left(\nabla f_t(x(t)) \right)^T (x - x(t)) \\ & + \frac{1}{2} (x - x(t))^T B_t(x(t)) (x - x(t)) \\ \text{s. t.} & x \in X_t \end{array}$$

e.g. approx Hessian



Tracking performance

$$\text{error} := \frac{1}{T} \mathring{a} \int_{t=1}^T \|x^{\text{online}}(t) - x^*(t)\|$$

control error

(assuming $x^{\text{online}}(0) = x^*(0)$)



Tracking performance

$$\text{error} := \frac{1}{T} \mathring{a} \left\| x^{\text{online}}(t) - x^*(t) \right\|$$

Theorem

$$\text{error} \leq \frac{e}{\sqrt{l_m / l_M} - e} \cdot \frac{1}{T} \sum_{t=1}^T \left(\left\| x^*(t) - x^*(t-1) \right\| + D_t \right)$$

- avg rate of drifting
- of optimal solution
 - of feasible set



Tracking performance

$$\text{error} := \frac{1}{T} \mathring{a} \left\| x^{\text{online}}(t) - x^*(t) \right\|$$

Theorem

$$\text{error} \leq \frac{e}{\sqrt{l_m / l_M} - e} \cdot \frac{1}{T} \sum_{t=1}^T \left(\left\| x^*(t) - x^*(t-1) \right\| + D_t \right)$$



error in Hessian approx




Tracking performance

$$\text{error} := \frac{1}{T} \mathring{a} \left\| x^{\text{online}}(t) - x^*(t) \right\|$$

Theorem

$$\text{error} \leq \frac{e}{\sqrt{l_m / l_M} - e} \cdot \frac{1}{T} \sum_{t=1}^T \left(\left\| x^*(t) - x^*(t-1) \right\| + D_t \right)$$

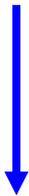

“condition number”
of Hessian



Implementation

Implement L-BFGS-B


- More scalable
- Handles (box) constraints X

Simulations

- IEEE 300 bus





Tracking performance

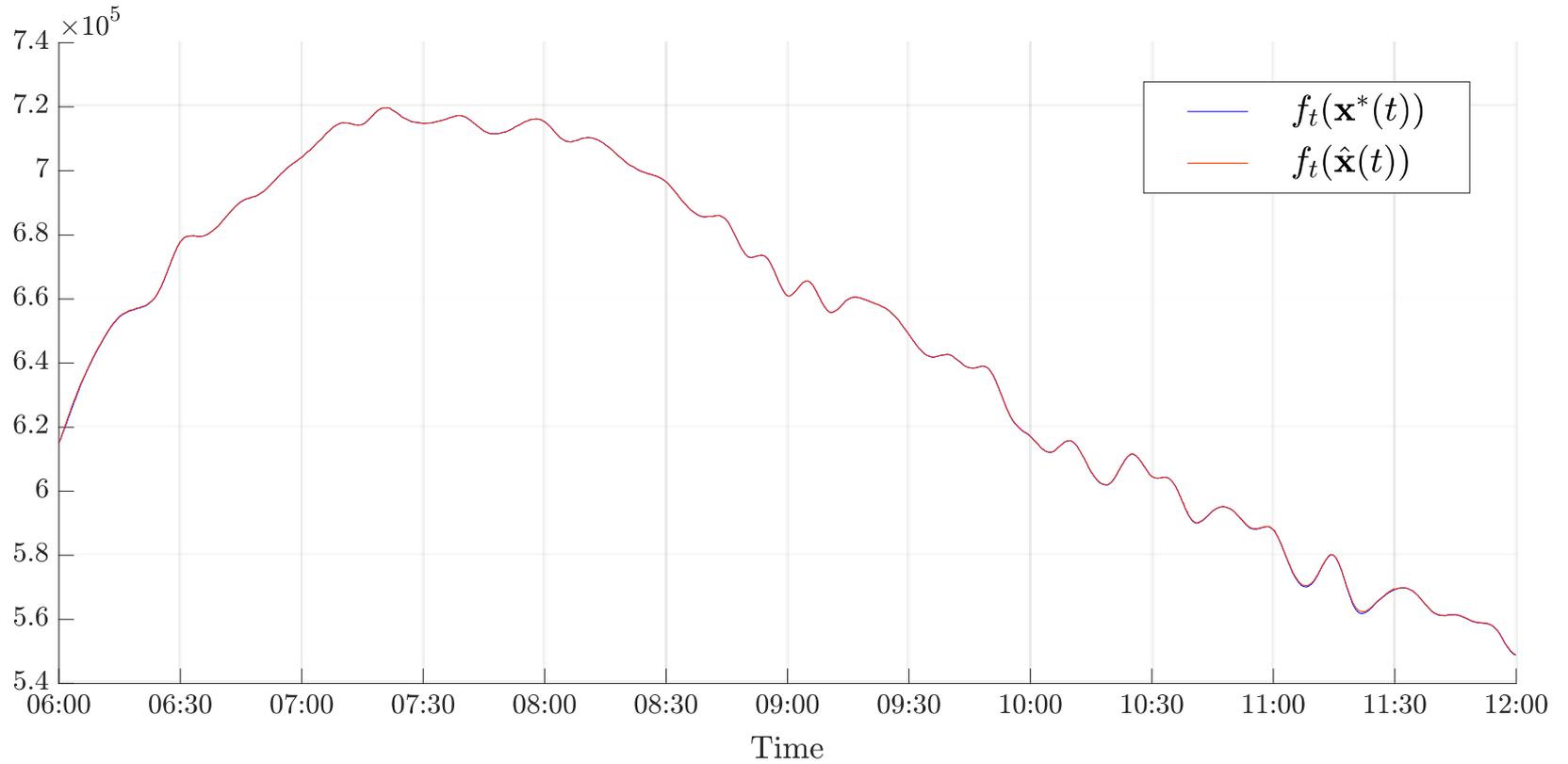

IEEE 300 bus



Tracking performance

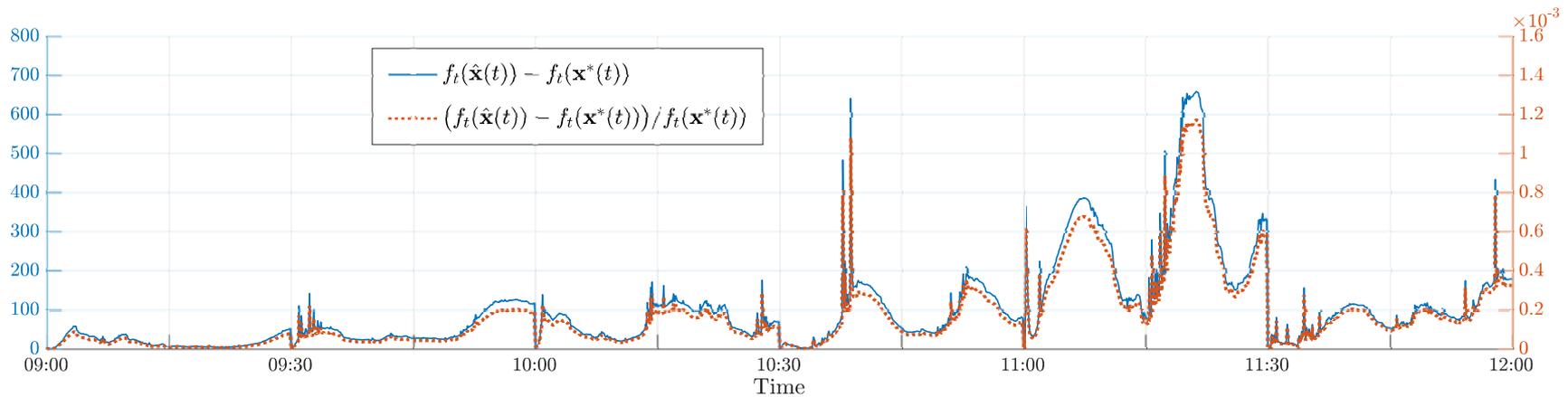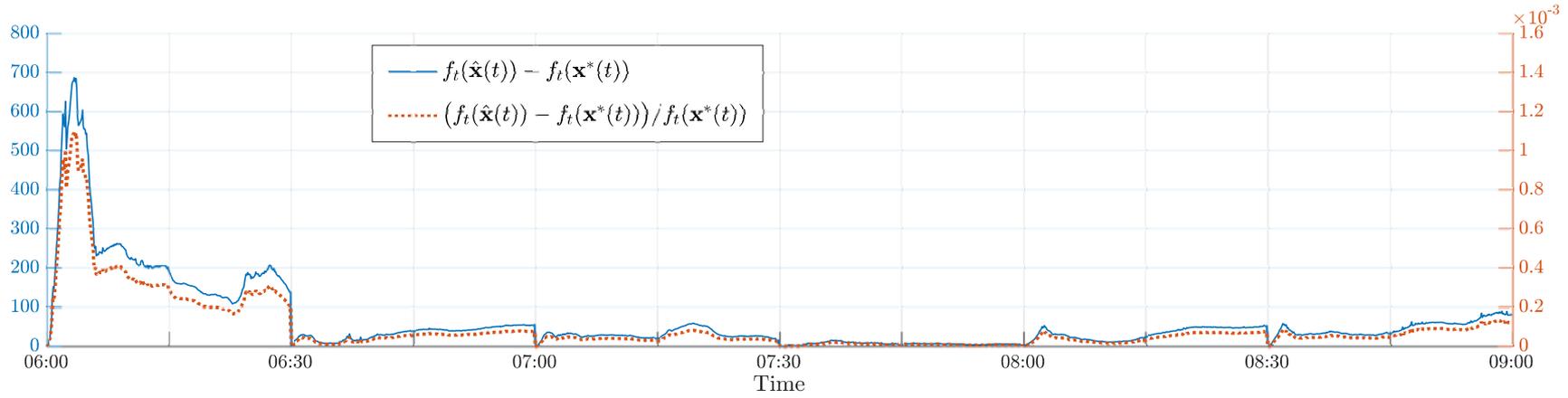

IEEE 300 bus



Key message

Large network of DERs

- Real-time optimization at scale
- Computational challenge: power flow solution

Online optimization [feedback control]

- Network computes power flow solutions in real time at scale for free
- Exploit it for our optimization/control
- Naturally adapts to evolving network conditions

Examples

- Slow timescale: OPF
- Fast timescale: frequency control